

List of Asides

CHAPTER 1 Electronic Circuit Design 1

- A1.1** Source Models: Thévenin and Norton 4
- A1.2** Controlled, or Dependent, Sources 5
- A1.3** Nodal versus Loop Analysis 6
- A1.4** Attenuation Factors 8
- A1.5** Maximum Power and Signal Transfer 9
- A1.6** Single-Pole Transfer Functions 15
- A1.7** Signal Classification 22

CHAPTER 2 Semiconductor Physics and Electronic Devices 43

- A2.1** Band Diagrams, the Fermi Level, and Carrier Concentrations 53
- A2.2** Quantum Mechanical Tunneling 61
- A2.3** Ideal Diode 66
- A2.4** Direct Bandgap and Indirect Bandgap Semiconductors 85

CHAPTER 5 Operational Amplifiers 211

- A5.1** Differential-Mode and Common-Mode Signals 219
- A5.2** Grounding, Differential-mode Signals and Interference Rejection 220

CHAPTER 6 Small-Signal Linearity and Amplification 85

- A6.1** Load Lines 275
- A6.2** Notation for Small- and Large-Signal Analysis 281
- A6.3** The Generic Transistor—Part I 283
- A6.4** Unilateral Two-Port Models 284

CHAPTER 7 DC Analysis Biasing 301

- A7.1** DC Impedance Reflection 331
- A7.2** The Generic Transistor—Part II 352
- A7.3** Worst-Case and Monte-Carlo Analysis 353
- A7.4** Variations in Discrete Passive Component Values 355
- A7.5** Standard Component Values 356

CHAPTER 8 Low-Frequency Small-Signal AC Analysis and Amplifiers 371

- A8.1** The Split-Source Transformation and Source Absorption Theorem 378

- A8.2** Impedance Reflection Revisited, the Small-Signal Midband AC Case 404

CHAPTER 9 Amplifier Frequency Response 513

- A9.1** Broadband Decoupling 518
- A9.2** The Transition Frequency of a BJT 522
- A9.3** Miller's Theorem 529
- A9.4** The Relationship Between Gain and Bandwidth in Amplifiers 537

CHAPTER 10 Feedback 659

- A10.1** History: The Invention of Negative Feedback 661
- A10.2** Normalized Gain Sensitivity 663
- A10.3** The Four Feedback Topologies 666
- A10.4** Notation Used in Practical Feedback Analysis 685
- A10.5** Output Resistance of Series–Series Triple 707

CHAPTER 11 Filters and Tuned Amplifiers 801

- A11.1** Amplitude Modulation 815

CHAPTER 12 Low-Frequency Large-Signal AC Analysis 863

- A12.1** Distortionless Transmission 898
- A12.2** Maximum Theoretical Efficiency of a Class A Amplifier 910
- A12.3** Maximum Efficiency of Class B Output Stages and Transistor Power Dissipation 915

CHAPTER 13 Data Converters 939

- A13.1** Sample Rate and Aliasing 944

CHAPTER 15 Transistor-Level Digital Circuits 991

- A15.1** Diode Switching—Detailed View 996
- A15.2** Bipolar Transistor Switching Times 1002
- A15.3** Optimum Scaling of CMOS Inverters 1025
- A15.4** The CMOS Transmission Gate 1033

Appendix D Review of Linear Time-Invariant Network Analysis (on the CD)

- AD.1** Complex Exponentials D5
- AD.2** Bode Plots D14