

Table of Contents

Preface xv

Part I The Foundations of Electronic Circuit Design

Chapter 1 Electronic Circuit Design 1

- 1.1 The Process of Design 2
- 1.2 Analysis for Design 3
 - 1.2.1 Frequency-Independent Analysis for Design 3
 - 1.2.2 Frequency-Dependent Analysis for Design 12
- 1.3 Electronic Systems 19
 - 1.3.1 Electronic versus Electric Circuits 19
 - 1.3.2 Analog and Digital Electronic Circuits 21
 - 1.3.3 Modeling Electronic Systems 25
 - 1.3.4 Discrete, Integrated, and Hybrid Circuits 30
- 1.4 Notation 31
 - Solutions to Exercises 32
 - Chapter Summary 34
 - References 35
 - Problems 35

Chapter 2 Semiconductor Physics and Electronic Devices 43

- 2.1 Material Properties 44
 - 2.1.1 Crystal Structure 44
 - 2.1.2 Conductors, Insulators, and Semiconductors 45
 - 2.1.3 Generation and Recombination 47
- 2.2 Conduction Mechanisms 48
 - 2.2.1 Diffusion 48
 - 2.2.2 Drift 49
- 2.3 Conductor-to-Semiconductor Contacts 52
 - 2.3.1 Rectifying Contacts 55
 - 2.3.2 Ohmic Contacts 59
- 2.4 pn-junction Diodes 61
 - 2.4.1 Intuitive Treatment 62
 - 2.4.2 Detailed Analysis of Current Flow 66
 - 2.4.3 Minority-Carrier Profiles 73
 - 2.4.4 Summary of Current Flow 75

	2.4.5	Charge Storage and Varactor Diodes	77
	2.4.6	Breakdown and Zener Diodes	80
	2.4.7	Other Types of Diodes	84
2.5		Bipolar Junction Transistors (BJTs)	85
	2.5.1	Intuitive Treatment	87
	2.5.2	Detailed Analysis of Current Flow	87
	2.5.3	Base Current	92
	2.5.4	Base-Width Modulation (The Early Effect)	98
	2.5.5	Charge Storage	116
	2.5.6	Breakdown Voltages	96
	2.5.7	Other Types of Junction Transistors	98
2.6		Metal-Oxide Semiconductor Field-Effect Transistors (MOSFETs)	98
	2.6.1	Intuitive Treatment	99
	2.6.2	Detailed Analysis of Current Flow	103
	2.6.3	Channel-Length Modulation	115
	2.6.4	Charge Storage	116
	2.6.5	The Effect of Bulk Bias	118
	2.6.6	Breakdown	119
	2.6.7	Short- and Narrow-Channel Effects	120
2.7		Junction Field-Effect Transistors (JFETs)	122
	2.7.1	Intuitive Treatment	122
	2.7.2	Detailed Analysis of Current Flow	124
	2.7.3	Second-Order Effects	127
2.8		Metal-Semiconductor FETs (MOSFETs)	129
2.9		Silicon Controlled Rectifier and Power Handling Devices	130
2.10		Comparison of Devices	133
		Solutions to Exercises	134
		Chapter Summary	136
		References	137
		Problems	137
Chapter 3		Solid-State Device Fabrication	145
3.1		CMOS Technology	146
	3.1.1	The Beginning: Choosing a Substrate	146
	3.1.2	Active Region Formation	147
	3.1.3	<i>N</i> and <i>P</i> Well Formation	150
	3.1.4	Gate Formation	152
	3.1.5	Tip or Extension (LDD) Formation	156
	3.1.6	Source/Drain Formation	158
	3.1.7	Contact and Local Interconnect Formation	160
	3.1.8	Multilevel Metal Formation	162
	3.1.9	Electrical Model Related to Physical Structure	166
3.2		Bipolar Technology	167
	3.2.1	Device Fabrication	167
	3.2.2	Electrical Model Related to Physical Structure	168
		Chapter Summary	168
		References	169
		Problems	169

Chapter 4	Computer-Aided Design: Tools and Techniques	171
4.1	Overview of Simulation Techniques	172
4.1.1	Analog Systems	172
4.1.1	Digital Systems	173
4.1.1	Mixed Analog and Digital Systems	174
4.2	Circuit Simulation Using SPICE	175
4.2.1	SPICE Input and Output	175
4.2.2	Simulation Modes and Types of Analysis	177
4.3	Circuit Elements and Models for SPICE	183
4.3.1	Sources	183
4.3.2	Passive Devices	184
4.3.3	Diodes	184
4.3.4	Bipolar Junction Transistors	186
4.3.5	MOS Field-Effect Transistors	193
4.3.6	Junction Field-effect Transistors and MOSFETs	198
4.4	Macro Models in SPICE	198
	Solutions to Exercises	200
	Chapter Summary	204
	References	204
	Problems	205

Part 2 Analog Electronic Circuit Design

Chapter 5	Operational Amplifiers	211
5.1	Basic Op Amp Circuits	212
5.1.1	The Noninverting Amplifier	212
5.1.2	The Inverting Amplifier	215
5.1.3	The Unity-Gain Amplifier, or Voltage Follower	217
5.1.4	The Differential Amplifier	217
5.1.5	The Instrumentation Amplifier	225
5.1.6	Current Sources	226
5.1.7	Voltage Regulators	227
5.2	Frequency-Dependent Op Amp Circuits	228
5.2.1	The Integrator and First-Order Low-Pass Filter	228
5.2.2	The Differentiator and First-Order High-Pass Filter	231
5.2.3	Second-Order Filters	232
5.3	Nonlinear Op Amp Circuits	235
5.3.1	Comparators	235
5.3.2	Precision Rectification and Clipping	237
5.3.3	Logarithmic Amplifiers	238
5.4	Nonideal Characteristics of Op Amps	239
5.4.1	Finite Gain	240
5.4.2	Input Bias and Offset Currents	241
5.4.3	Input Offset Voltage	243
5.4.4	Finite Input and Output Impedances	244
5.4.5	Finite Bandwidth	246
5.4.6	Common-Mode Rejection Ratio and Power-Supply Rejection Ratio	249
5.4.7	Output Swing Revisited	253

	5.4.8	Slew Rate and Full-Power Bandwidth	253
	5.4.9	Noise	255
	5.4.10	Op Amp Parameter Measurement	255
		Solutions to Exercises	257
		Chapter Summary	258
		References	259
		Problems	259
Chapter 6		Small-Signal Linearity and Amplification	271
6.1		Linear Time-Invariant Networks	272
6.2		Nonlinear Circuit Analysis	273
	6.2.1	Analytical Solution	273
	6.2.2	Graphical Solution	274
	6.2.3	Solving with Models	274
6.3		Small-Signal Analysis	276
	6.3.1	An Alternate View of the Small-Signal Approximation	281
	6.3.2	Accuracy of the Small-Signal Approximation	282
6.4		Small-Signal Amplifiers	282
	6.4.1	Small-signal Models for Transistors	282
	6.4.2	Example Application	286
6.5		Types of Amplifiers	288
	6.5.1	Two-Port Models for Amplifiers	288
	6.5.2	AC- and DC-coupled Transfer Functions	292
		Solutions to Exercises	294
		Chapter Summary	296
		References	296
		Problems	296
Chapter 7		DC Biasing	301
7.1		DC and Large-Signal Low-Frequency Models for Design	302
	7.1.1	Independent Sources	302
	7.1.2	Linear Passive Devices (R_s , L_s , & C_s)	303
	7.1.3	Diodes	304
	7.1.4	Bipolar Junction Transistors	309
	7.1.5	MOS Field-Effect Transistors	315
	7.1.6	Junction Field-Effect Transistors	323
	7.1.7	Comparison of Bipolar and Field-Effect Transistor Biasing	324
7.2		Biasing of Single-Stage Amplifiers	325
	7.2.1	BJT Amplifiers	325
	7.2.2	FET Amplifiers	332
7.3		Biasing of Multistage Amplifiers	341
	7.3.1	Cascaded Bipolar Amplifiers	341
	7.3.2	Cascaded FET Amplifiers	342
7.4		Biasing for Integrated Circuits	342
	7.4.1	Simple Bipolar Current Mirrors	345
	7.4.2	More Advanced Bipolar Current Mirrors	346
	7.4.3	FET Current Mirrors	348
7.5		Biasing of Differential Amplifiers	350

- 7.6 Worst-Case Analysis and Parameter Variation 353
 - Solutions to Exercises 356
 - Chapter Summary 358
 - References 359
 - Problems 359

- Chapter 8 Low-Frequency Small-Signal AC Analysis and Amplifiers 371**
- 8.1 Low-Frequency Small-Signal Models for Design 372
 - 8.1.1 Independent Sources 372
 - 8.1.2 Linear Passive Devices (Rs, Ls, & Cs) 373
 - 8.1.3 Diodes 376
 - 8.1.4 The Generic Transistor 377
 - 8.1.5 Bipolar Junction Transistors 379
 - 8.1.6 MOS Field-Effect Transistors 386
 - 8.1.7 Junction Field-Effect Transistors 389
 - 8.1.8 Comparison of Bipolar and Field-Effect Transistors 390
- 8.2 Stages with Voltage and Current Gain 391
 - 8.2.1 A Generic Implementation: The Common-Merge Amplifier 391
 - 8.2.2 A Bipolar Implementation: The Common-Emitter Amplifier 398
 - 8.2.3 A MOS Implementation: The Common-Source Amplifier 409
- 8.3 Voltage Buffers 416
 - 8.3.1 A Generic Implementation: The Merge Follower 418
 - 8.3.2 A Bipolar Implementation: The Emitter Follower 419
 - 8.3.3 A FET Implementation: The Source Follower 424
- 8.4 Current Buffers 429
 - 8.4.1 A Generic Implementation: The Common-Control Amplifier 429
 - 8.4.2 A Bipolar Implementation: The Common-Base Amplifier 430
 - 8.4.3 A FET Implementation: The Common-Gate Amplifier 432
- 8.5 Integrated Amplifiers 434
 - 8.5.1 The Body Effect in FET Amplifiers 435
 - 8.5.2 Current Mirrors 438
- 8.6 Differential Amplifiers 466
 - 8.6.1 The Generic Differential Pair 446
 - 8.6.2 A Bipolar Implementation: The Emitter-Coupled Pair 459
 - 8.6.3 A FET Implementation: The Source-Coupled Pair 464
- 8.7 Multistage Amplifiers 468
 - 8.7.1 Multistage Bipolar Amplifiers 469
 - 8.7.2 Multistage FET Amplifiers 472
 - 8.7.3 Multistage Amplifiers with Bipolar and Field-Effect Transistors 474
 - 8.7.4 Multistage Amplifiers with Differential Pairs: Operational Amplifiers 474

8.8	Comparison of BJT and FET Amplifiers	478
	Solutions to Exercises	479
	Chapter Summary	484
	References	485
	Problems	486
Chapter 9	Amplifier Frequency Response	513
9.1	High-Frequency Small-Signal Models for Design	514
9.1.1	Independent Sources	514
9.1.2	Linear Passive Elements (Rs, Ls, & Cs)	514
9.1.3	Diodes	519
9.1.4	The Generic Transistor	520
9.1.5	Bipolar Junction Transistors	520
9.1.6	MOS Field-Effect Transistors	524
9.1.7	Junction Field-Effect Transistors	527
9.2	Stages with Voltage and Current Gain	528
9.2.1	A Generic Implementation: The Common-Merge Amplifier	530
9.2.2	A Bipolar Implementation: The Common-Emitter Amplifier	546
9.2.3	A FET Implementation: The Common-Source Amplifier	556
9.2.4	Comparison of Bipolar and FET Implementations	563
9.3	Voltage Buffers	564
9.3.1	A Generic Implementation: The Merge Follower	564
9.3.2	A Bipolar Implementation: The Emitter Follower	570
9.3.3	A FET Implementation: The Source Follower	575
9.4	Current Buffers	578
9.4.1	A Generic Implementation: The Common-Control Amplifier	578
9.4.2	A Bipolar Implementation: The Common-Base Amplifier	579
9.4.3	A FET Implementation: The Common-Gate Amplifier	581
9.5	Comparison of Single-Stage Amplifiers	582
9.5.1	Bipolar Amplifiers	583
9.5.2	FET Amplifiers	585
9.6	Multistage Amplifiers	587
9.6.1	The Common-Merge Merge-Follower Cascade	589
9.6.2	A Bipolar Implementation: The Common-Emitter Emitter-Follower Cascade	593
9.6.3	A FET Implementation: The Common-Source Source-Follower Cascade	596
9.6.4	The Cascode Amplifier: A Common-Merge Common-Control Cascade	600
9.6.5	The Bipolar Cascode Amplifier: A Common-Emitter Common-Base Cascade	603
9.6.6	The MOSFET Cascode Amplifier: A Common-Source Common-Gate Cascade	606

9.7	Differential Amplifiers 608
9.7.1	The Generic Differential Pair 608
9.7.2	A Bipolar Implementation: The Emitter-Coupled Pair 616
9.7.3	A FET Implementation: The Source-Coupled Pair 621
	Solutions to Exercises 625
	Chapter Summary 634
	References 634
	Problems 634
Chapter 10	Feedback 659
10.1	Negative Feedback 660
10.1.1	Ideal Block Diagram Analysis 660
10.1.2	Ideal Analysis and the Characteristics of Negative Feedback 662
10.1.3	First-Order Practical Analysis 674
10.1.4	Advanced Analysis 717
10.1.5	Stability of Systems with Feedback 726
10.1.6	Compensation 736
10.2	Positive Feedback and Oscillators 743
10.2.1	Sinusoidal Oscillators 744
10.2.2	Nonsinusoidal Oscillators 754
	Solutions to Exercises 759
	Chapter Summary 770
	References 771
	Problems 772
Chapter 11	Filters and Tuned Amplifiers 801
11.1	Filters 802
11.1.1	Ideal Transfer Functions 802
11.1.2	Practical Transfer Functions 802
11.1.3	Normalization (Frequency and Component Value Scaling) 813
11.1.4	The Narrowband Approximation 814
11.1.5	Integrated Filters and Simulated Inductors 818
11.1.6	Discrete-time Filters 821
11.2	Tuned Amplifiers 830
11.2.1	Single-Tuned Amplifiers 831
11.2.2	Synchronous and Stagger-Tuned Amplifiers 838
11.3	Phase-Locked Loops 844
11.3.1	First-Order PLLs 848
11.3.2	Second-Order PLLs 849
11.3.3	Type-II PLLs 850
	Solutions to Exercises 851
	Chapter Summary 852
	References 853
	Problems 854
Chapter 12	Low-Frequency Large-Signal AC Analysis 863
12.1	Diode Circuits 864

	12.1.1	Diode Rectifiers	864
	12.1.2	Limiting, Clamping, and Multiplying Circuits	871
	12.1.3	Diode Switching	874
12.2		Amplifiers	875
	12.2.1	Signal Swing in Bipolar Amplifiers	877
	12.2.2	Signal Swing in FET Amplifiers	888
	12.2.3	Distortion in Amplifiers	897
12.3		Output Stages	908
	12.3.1	Class A Output Stages: Classification and Efficiency of Output Stages	908
	12.3.2	Class B and AB Output Stages	912
	12.3.3	More Advanced Output Stages	917
	12.3.4	Power Transistors, Thermal Modeling, and Heat Sinks	919
		Solutions to Exercises	923
		Chapter Summary	925
		References	926
		Problems	927
Chapter 13		Data Converters	939
13.1		Overview	939
	13.1.1	Analog and Digital Signal Processing and Applications of Data Converters	940
	13.1.2	Data Converter Transfer Functions and Specifications	946
13.2		Digital-to-Analog Converters	948
	13.2.1	Resistive DACs	948
	13.2.2	Capacitive DACs	953
13.3		Analog-to-Digital Converters	954
	13.3.1	Sample-and-Hold Circuit	954
	13.3.2	The Successive Approximation ADC	955
	13.3.3	The Dual-Slope ADC	956
	13.3.4	The Flash ADC	957
	13.3.5	Other ADC Architectures	958
		Solutions to Exercises	959
		Chapter Summary	960
		References	960
		Problems	960
Part 3		Digital Electronic Circuit Design	
Chapter 14		Gate-Level Digital Circuits	965
14.1		Background and Binary Logic	966
	14.1.1	Fundamental Characteristics of Digital Circuits	966
	14.1.2	Number Systems	967
	14.1.3	Binary Logic Gates	969
14.2		Flip-Flops	972
	14.2.1	The Set-Reset Flip-Flop	973
	14.2.2	The JK Flip-Flop	974
	14.2.3	The D Flip Flop	977

14.3	Shift Registers and Counters	978
14.4	Reflections on Transmission Lines	980
	Solutions to Exercises	984
	Chapter Summary	986
	References	986
	Problems	986
Chapter 15	Transistor-Level Digital Circuits	991
15.1	Device Modeling for Digital Design	992
	15.1.1 Diodes	992
	15.1.2 Bipolar Junction Transistors	998
	15.1.3 MOS Field-Effect Transistors	1007
15.2	Specification of Logic Gates	1008
	15.2.1 Static Specifications	1008
	15.2.2 Dynamic Specifications	1011
15.3	MOS Digital Circuits	1014
	15.3.1 NMOS	1015
	15.3.2 CMOS Inverter (NOT gate)	1018
	15.3.3 CMOS NOR and NAND Gates	1026
	15.3.4 More Complex CMOS Gates	1030
	15.3.5 Other Types of CMOS Logic	1031
	15.3.6 MOS Memory	1034
15.4	Bipolar Digital Circuits	1043
	15.4.1 Transistor-Transistor Logic (TTL)	1043
	15.4.2 Emitter-Coupled Logic	1051
	Solutions to Exercises	1065
	Chapter Summary	1069
	References	1070
	Problems	1071
Appendixes		
Appendix A	Spice Reference	1083
A.1	Running SPICE	1083
A.2	The Input File	1084
	References	1100
Appendix B	Example Device Models	1101
B.1	Device Data	1101
B.2	Model Libraries from the CD	1102
	References	1105
Appendix C	Two-Port Network Properties (on the CD)	
Appendix D	Review of Linear Time-Invariant Network Analysis (on the CD)	
Answers to Selected Problems		1107
INDEX		1117