

Oct. 19

# EEC 18

Implicants - any valid K-map group  
(P.I.)

~~Prime~~ Prime Implicant - max-size implicant  
(E.P.I.)

Essential Prime Implicant - P.I. that is essential for a min solution

## Minimum Solution:

always contains all EPI's


may " some P.I.'s (not EPI)

never " any plain Implicants (not P.I. or EPI's)

To find min soln:

1) Include all EPI's

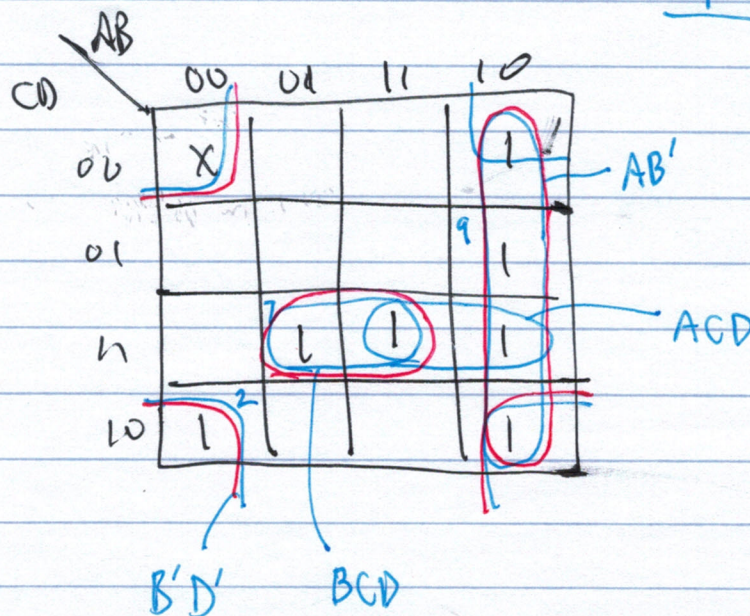2) If necessary, add P.I.'s until all minterms are covered.  
Cover X's only if helpful.



Implicants: all groups

PI's:  $AB'$ ,  $ACD$ ,  $BCD$ ,  $B'D'$

EPI's:  $AB'$ ,  $BCD$ ,  $B'D'$

$m_9 \rightarrow AB'$


$m_7 \rightarrow BCD$

$m_2 \rightarrow B'D'$


To find EPIs:

- 1) Choose a minterm (1 on K-map) and look at all P.I.s that cover it
- 2) If only 1 P.I.,  $\rightarrow$  that one is essential  
If  $> 1$ , P.I.,  $\rightarrow$  learn nothing
- 3) Repeat for all minterms

adders (Unit 4)

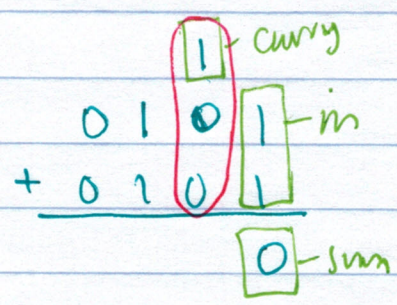


Half Adder

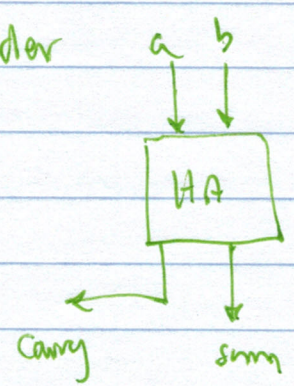

a	b	c	s
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0


Full Adder

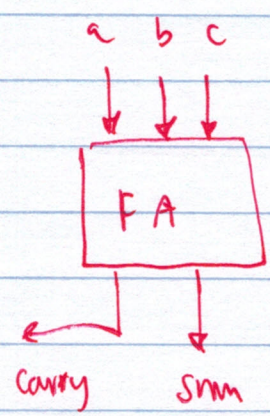

a	b	c	car	sum
0	0	0	0	0
0	0	1	0	1
1	1	1	1	1



$$sum = a \oplus b \oplus c$$

$$car = ab + bc + ac$$

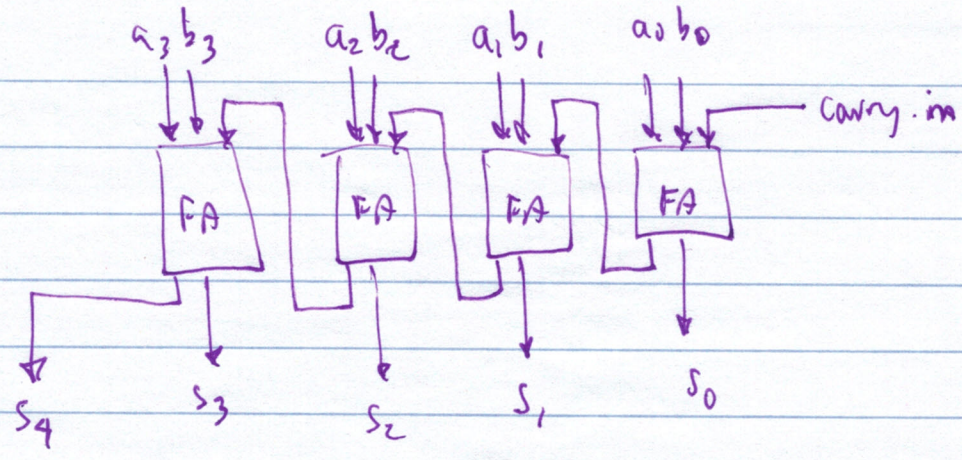

Ripple - Carry Adder  
 - simplest  
 - slowest


Mux

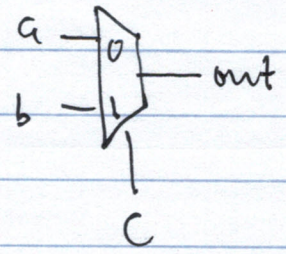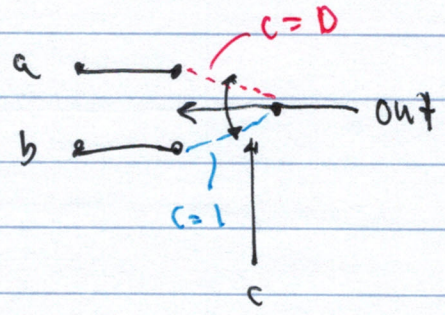


2:1 mux

c	out
0	a
1	b

a	b	c	out
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

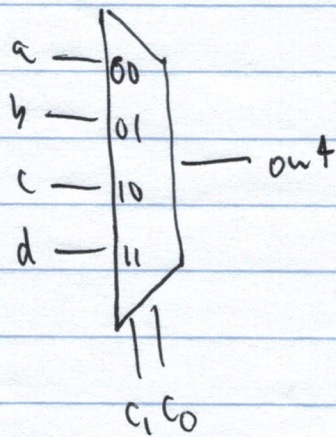

4:1 mux

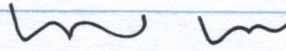  
 $2^N$  inputs     $N$  select bits

### Quine-McCluskey (Unit 6)

- Works with many inputs
- Easy to program

- 1) Find all P.I.s
- 2) ~~Find~~ Find all E.P.I.s
- 3) Build mfn solution

$$\begin{aligned}
 Z &= \sum m(1, 2, 5, 6, 7) \\
 &= A'B'C + A'BC' + AB'C + ABC' + ABC
 \end{aligned}$$

	C	0	1
AB	00		1
	01	1	
	11	1	1
	10		1

	<u>min terms</u>	<u>col 1</u>	<u>col 2</u>
group 0 1's			
group 1 1's	1.	001 ✓	-01
	2	010 ✓	
group 2 1's	5.	101 ✓	-10
	6	110 ✓	1-1
group 3 1's	7	111 ✓	11-

All P.T.s  
 Unchecked terms  
 are P.T.s

List groups by # of 1's in min term

Compare min term pairs in adjacent groups

Copy term pairs that differ in one variable to next column and check "✓" matched terms

Repeat until no more matches

	<u>Prime Implicants</u>	<u>Min terms</u>				
		1	2	5	6	7
EPI	(1,5) B'C	⊗		x		
EPI	(2,6) BC'		⊗		x	
	(5,7) AC			x		x
	(6,7) AB				x	x

Choose

Min solution =  $B'C + BC' + AC$   
 =  $B'C + BC' + AB$


## Multi-level Circuits

Level of a circuit = max. # of gates in series between an input and output

SOP : 2-level : AND - OR

POS : 2-level : OR - AND

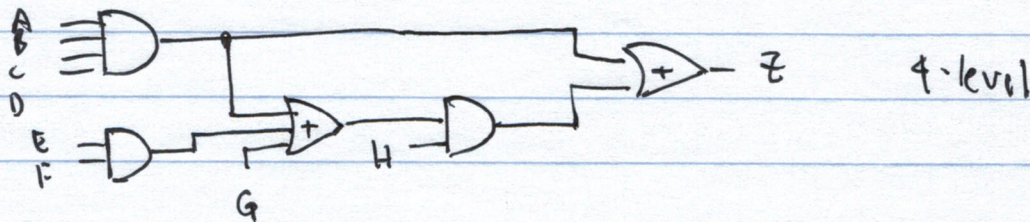Ex.  $Z = (ABCD + EF + G) \cdot H + ABCD$



Why do levels matter?

- # of gates
- fanin ( # of inputs to a gate)
- fanout ( # of outputs of a gate)
- delay

## NANDs and NORs

Min terms and max terms  $\rightarrow$  AND, OR, NOT are "functionally complete"

AND? can't make an inverter  $\rightarrow$  Not functionally complete

$A \cdot A$







OR? can't make an inverter  $\rightarrow$  " " "

$A + A$

INV? 

can't make AND, OR  $\rightarrow$  Not func. complete

$a \& a = a$

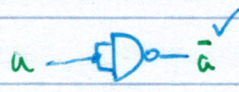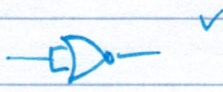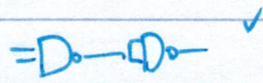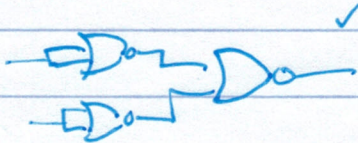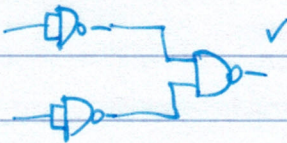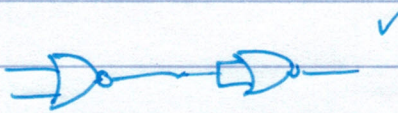	NAND	NOR
NAND?		
NOT		
AND		
OR		

NAND is func. complete!

NOR " " "

