 



12.1 Registers

Def: A register is a set of flip-flops with a common clock signal




Registers are fundamental blocks in any digital system or processor:


Ex: Pipelining to increase throughput

 

 Ex: Storing values from muxes or tri-state buses



 Ex: Implementing feedback -> basis of finite-state machines (FSMs)




 22-141 50 SHEETS
22-142 100 SHEETS
22-144 200 SHEETS



"Enable-able Registers" or "Registers with an Enable Signal"


A signal (in addition to clock) determines when register output can change - analogous to a gated latch



D	Enable	clk	Q+
X	0	↑	Q
0	1	↑	0
1	1	↑	1


(hold, update of register was not enabled)

 Implementation: Use a D flip-flop and a 2-to-1 mux



(Book refers to this as "CE", "clock enable")

 Alternative Implementation: Use a D flip-flop and an AND gate



Why is this bad?

Glitches (e.g., static 0 hazard) on Enable could cause the D flip-flop to sample D by mistake, at some time other than the rising edge of clock!

Registers With Tri-State Outputs


Same as a D flip-flop except output is high impedance when disabled:

D	Enable	clk	Q+
X	0	↑	Hi Z, high impedance, floating, etc.
0	1	↑	0
1	1	↑	1

 22-141 50 SHEETS
22-142 100 SHEETS
22-144 200 SHEETS



Implementation: D flip-flop and tri-state buffer



Many possible variations/combinations, e.g. active low or active high enables, with or without tristate outputs → always check data sheet to understand correct operation.


Accumulators

It is often necessary to keep a running total of a set of numbers in digital applications → store current sum in a register and add next input to it (accumulate the numbers into a total).

Ex: $Z = A + B + C + D + E$

 1.) Implement using intermediate sums and a "tree" of adder circuits:

$W = A + B$
 $X = C + D$
 $Y = X + E$
 $Z = W + Y$



← combinational circuit


2.) Do sum sequentially using accumulator

clear Accumulator	(ACC = 0)		Abbreviate
	$ACC = ACC + A$	⇒	$ACC += A$
	$ACC = ACC + B$		$ACC += B$
	$ACC = ACC + C$		⋮
	$ACC = ACC + D$		⋮
	$ACC = ACC + E$		$ACC += E$

22-141 50 SHEETS
22-142 100 SHEETS
22-144 200 SHEETS





Implementation: register and adder

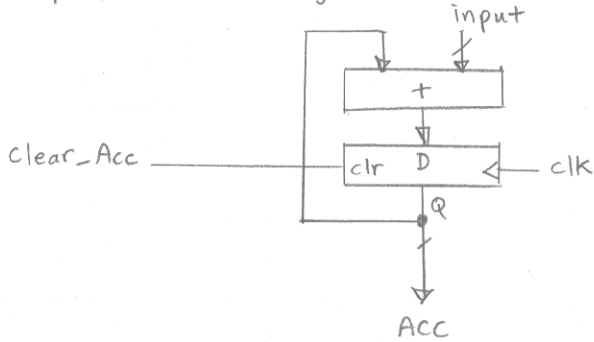


Register allows the use of feedback.

  12.2 Shift Registers


By connecting flip-flops in series, we can shift bits around in a digital word:



original Data 01000111

 


Shift Right 00100011

 


Shift Left 10001110



Rotate Right (Right Circular Shift)

 

Rotate Left (Left Circular Shift)

 

Changes take place on active edge of the clock (either \uparrow or \downarrow)

Multiple combinations of serial/parallel inputs and outputs:


		Inputs	
		Serial	Parallel
Outputs	Serial	X	X
	Parallel	X	X

Accumulator example

50 SHEETS
22-141
100 SHEETS
22-142
200 SHEETS
22-144



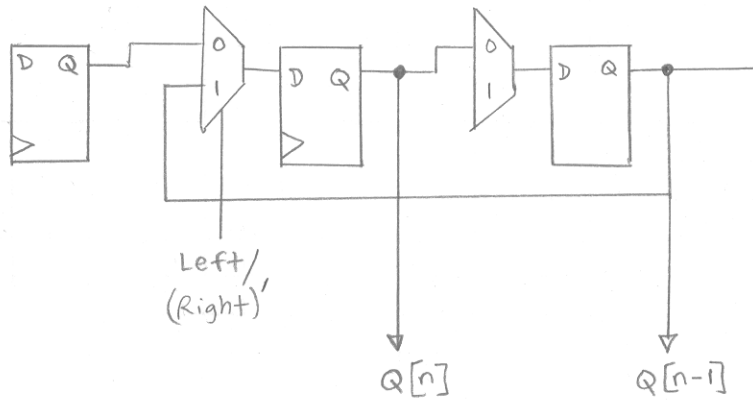Ex: Implement a serial-in parallel-out shift register which can shift left or right



12.3 Binary Counters

State: the set of values (0 or 1) stored in a flip-flop, latch, register, or memory

Counter: a circuit which cycles through a fixed sequence of states

Synchronous counters change state based on a common clock pulse (all flip-flops within the register change values simultaneously).


Ex: Simple 2-bit binary counter

State sequence: 00, 01, 10, 11, 00, 01, ...


Note that the counter "wraps around" or returns to its initial value after reaching its maximum

The LSB switches value every cycle, so we can implement it using a T flip-flop with the input set high.

 The MSB switches whenever the LSB=1, so we use the LSB as the T input to a second T flip-flop:



 We can also describe counter operation using a state graph (or state transition diagram).



General Counter Design

A general approach to designing arbitrary counters is:

- ① Write the desired state sequence/state graph
- ② For each present state, write corresponding next state(s)
- ③ Determine needed FF inputs required to make transitions
- ④ Use combinational logic minimization techniques to find necessary logic for each flip-flop input

Ex: 4 bit counter, increments by 3 each cycle, at 15, it wraps around to \emptyset

Present State	Next State	D Flip-Flop Input				T Flip-Flop Input			
		D ₀	C ₀	B ₀	A ₀	T ₀	T ₁	T ₂	T ₃
0000	0011	0	0	1	1	0	0	1	1
0011	0110	0	1	1	0	0	1	0	1
0110	1001	1	0	0	1	1	1	1	1
1001	1100	1	1	0	0	0	1	0	1
1100	1111	1	1	1	1	0	0	1	1
1111	0000	0	0	0	0	1	1	1	1


If there are additional inputs (e.g. up/down, load, etc.), we can follow one of two approaches to design:

- 1.) List multiple next states (each a function of the extra input(s))
- 2.) Consider all inputs the same: present state and additional inputs

Ex: 2 bit up/down counter using T flip-flops

Up/Down	Present State		Next State		T Flip-Flop Inputs	
	Q1	Q0	Q1 ⁺	Q0 ⁺	T1	T0
0	0	0	0	1	0	1
0	0	1	1	0	1	1
0	1	0	1	1	0	1
0	1	1	0	0	1	1
1	0	0	1	1	1	1
1	1	1	1	0	0	1
1	1	0	0	1	1	1
1	0	1	0	0	0	1

 Input Equations: $T_0 = 1$ $T_1 = Q_0 \oplus \text{Up/Down}$



Alternative approach:

Present State		Next State (up/down = 0)		Next State (up/down = 1)	
Q1	Q0	Q1 ⁺	Q0 ⁺	Q1 ⁺	Q0 ⁺
0	0	0	1	1	1
0	1	1	0	0	0
1	0	1	1	0	1
1	1	0	0	1	0