

Finite State Machine Design


Design Process



- 1) Figure out necessary states from problem specification (e.g., a counter from 0 to 10 needs 11 states)
- 2) Draw state graph
 - Enumerate states
 - capture transitions between states ~~and inputs~~
- 3) Add outputs
 - Moore machine: outputs function of present state only
 - Mealy machine: outputs are function of present state and inputs
- 4) Figure out number of flip-flops required for implementation (minimum # is $\lceil \log_2 (\# \text{ of states}) \rceil$)
- 5) Assign states (assignment may affect the ~~number of flip-flops~~ amount of logic needed)
- 6) Construct a state table
 - Develop equations for next states
- 7) Figure out outputs
 - Develop equations for outputs (different for Moore vs. Mealy)

Ex: Count sequence 0, 9, 15, 2, 7 <repeat>, when $X=0$

If input $X=1$, output 2 and start count from there when $X=0$.
Reset input: go to 9 in the sequence

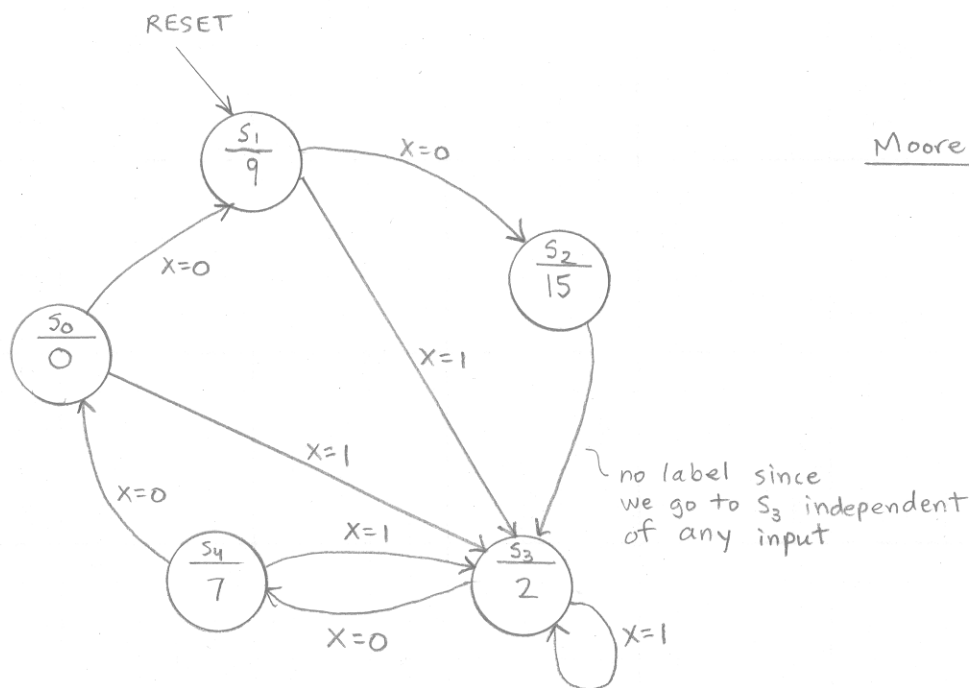5 values in sequence \Rightarrow 5 states ($S_0 - S_4$)



 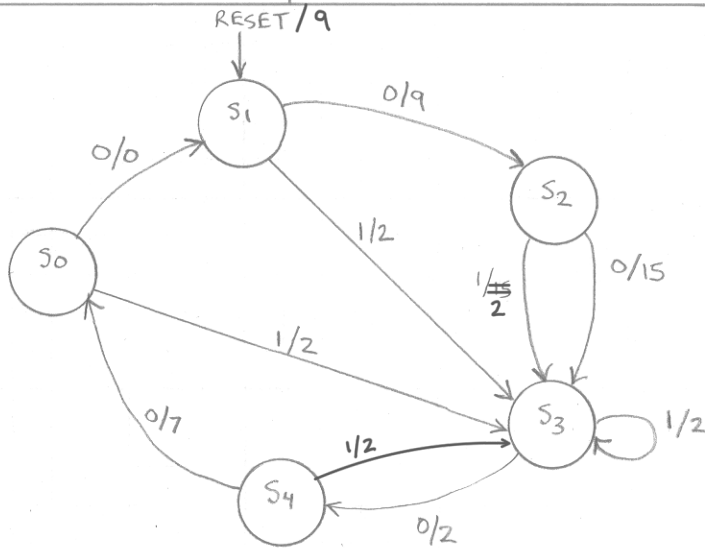

Present State	Next State		Moore Output	Mealy Output	
	X=0	X=1		X=0	X=1
S ₀	S ₁	S ₃	0	0	2
S ₁	S ₂	S ₃	9	9	2
S ₂	S ₃	S ₃	15	15	2
S ₃	S ₄	S ₃	2	2	2
S ₄	S ₀	S ₃	7	7	2

State Assignments

- 1.) Assign in order of normal operating sequence (easy to think about)
- or
- 2.) Assign at random
- or
- 3.) Assign to minimize logic/circuit implementation
- or
- 4.) One-hot encoding
 - Use one flip-flop for each state, so an N-state FSM requires N flip-flops (possibly much larger than log₂ N)
 - Reduces complexity of logic for computing next states and outputs
 - Use when flip-flops are relatively cheap (e.g., FPGAs, CPLDs, etc.)

22-141 50 SHEETS
22-142 100 SHEETS
22-144 200 SHEETS



or
 5.) Gray code (reduces power by reducing number of bit transitions)

Ex: Continue previous example; sequential state assignment

Present State $Q_2 Q_1 Q_0$	Next State		Equations:
	$X=0$ $Q_2^+ Q_1^+ Q_0^+$	$X=1$ $Q_2^+ Q_1^+ Q_0^+$	
S_0 0 0 0	0 0 1	0 1 1	$Q_0^+ = X + X'Q_2'Q_0'$
S_1 0 0 1	0 1 0	0 1 1	$Q_2^+ = X'Q_1Q_0$
S_2 0 1 0	0 1 1	0 1 1	$Q_1^+ = X + X'Q_2'Q_1'Q_0$
S_3 0 1 1	1 0 0	0 1 1	$+ X'Q_2'Q_1Q_0'$
S_4 1 0 0	0 0 0	0 1 1	



Now try one-hot state encoding \rightarrow need 5 flip-flops

Present State $Q_4 Q_3 Q_2 Q_1 Q_0$	Next State		Equations:
	$X=0$	$X=1$	
S_0 0 0 0 0 1	00010	01000	$Q_0^+ = Q_4 \cdot X'$
S_1 0 0 0 1 0	00100	01000	$Q_1^+ = Q_0 \cdot X'$
S_2 0 0 1 0 0	01000	01000	$Q_2^+ = Q_1 \cdot X'$
S_3 0 1 0 0 0	10000	01000	$Q_3^+ = Q_2 \cdot X' + X$
S_4 1 0 0 0 0	00001	01000	$Q_4^+ = Q_3 \cdot X'$



Speed of Moore vs. Speed of Mealy

 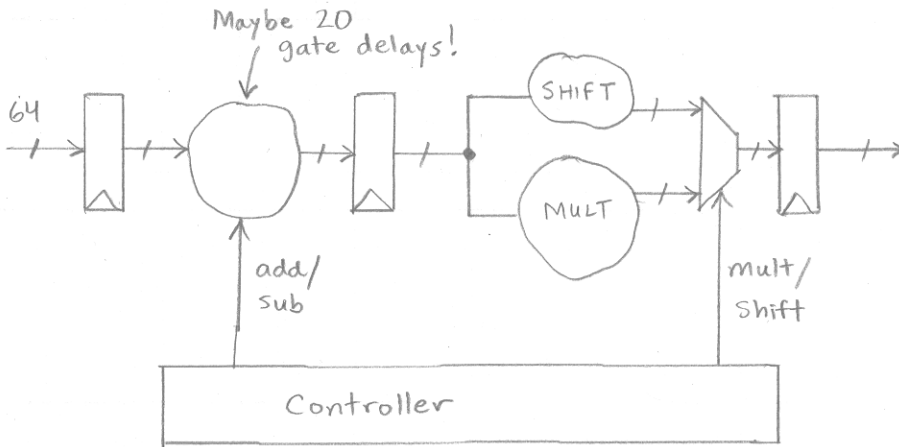Consider a microprocessor data pipeline → the controller can be an FSM



Longest Path

Older computers ~50 gate delays
 fastest current computers ~15

Special purpose processors ~10

- Easier to design a long path with a Mealy machine
- Purely combinational path from input to output yields possibly faster decisions, but potential for hazards

22-141 50 SHEETS
 22-142 100 SHEETS
 22-144 200 SHEETS



Comparing Moore vs. Mealy outputs:

