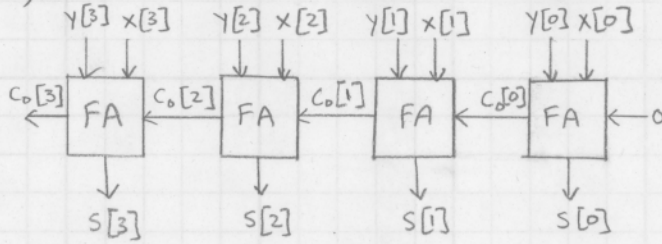


We've looked at fully combinational circuits for addition (the Ripple-Carry Adder):



Let's examine a combinational logic circuit for multiplication:

Array Multiplier

Recall binary (unsigned) multiplication involved creating binary "Partial Products":


Ex: $110_2 = 6_{10}$

$\times 101_2 = 5_{10}$

$$\begin{array}{r} 110 \\ \times 101 \\ \hline 110 \\ 000 \\ \oplus 110 \\ \hline 11110_2 = 30_{10} \checkmark \end{array}$$

Use AND gates to generate partial products ($x \cdot 0 = 0$ and $x \cdot 1 = x$).

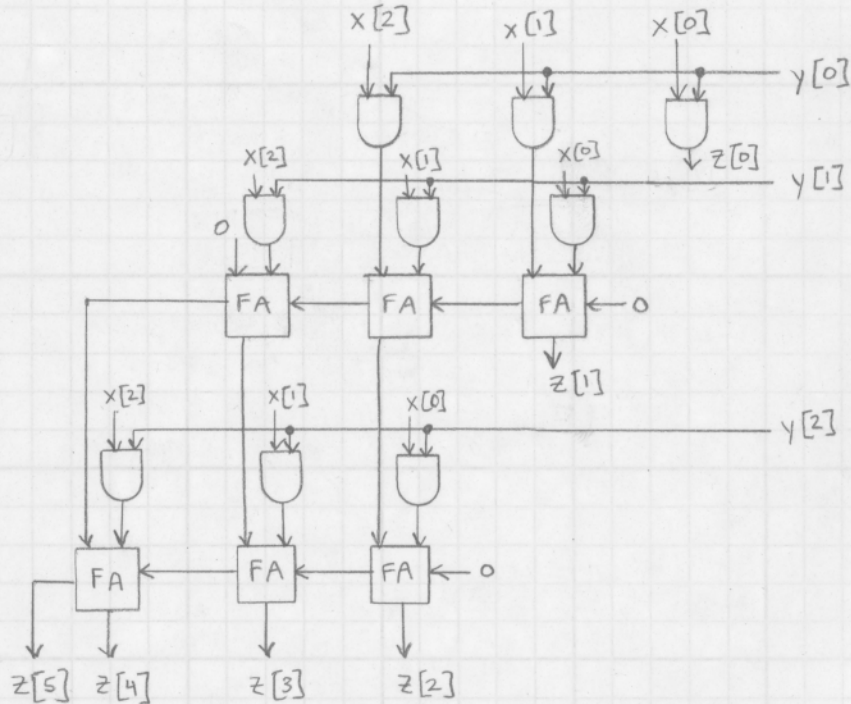Use ripple carry adders to sum partial products.




Note: Two 3-bit operands yield a 6 bit product.
See Rabaey, Digital Integrated Circuits, for more information.

50 SHEETS
100 SHEETS
200 SHEETS



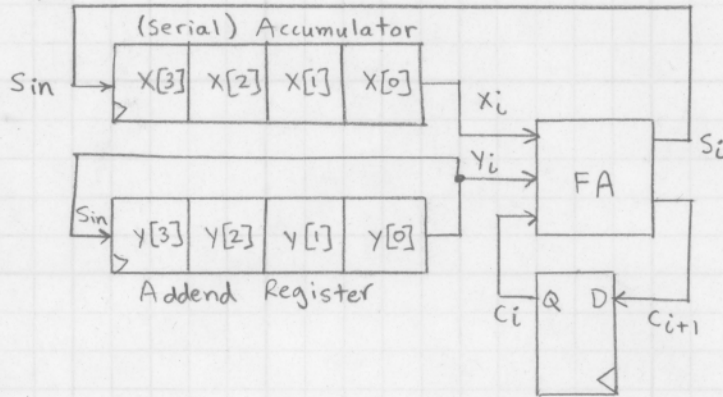
18.1 Serial Adder With Accumulator

One can also exploit sequential circuits to do arithmetic \Rightarrow yields less area, less power (under certain circumstances). The serial adder uses a flip-flop and shift registers to time the carry propagation correctly:



On successive cycles, new addend bits and the carry out from the previous clock cycle are present at the Full Adder inputs.

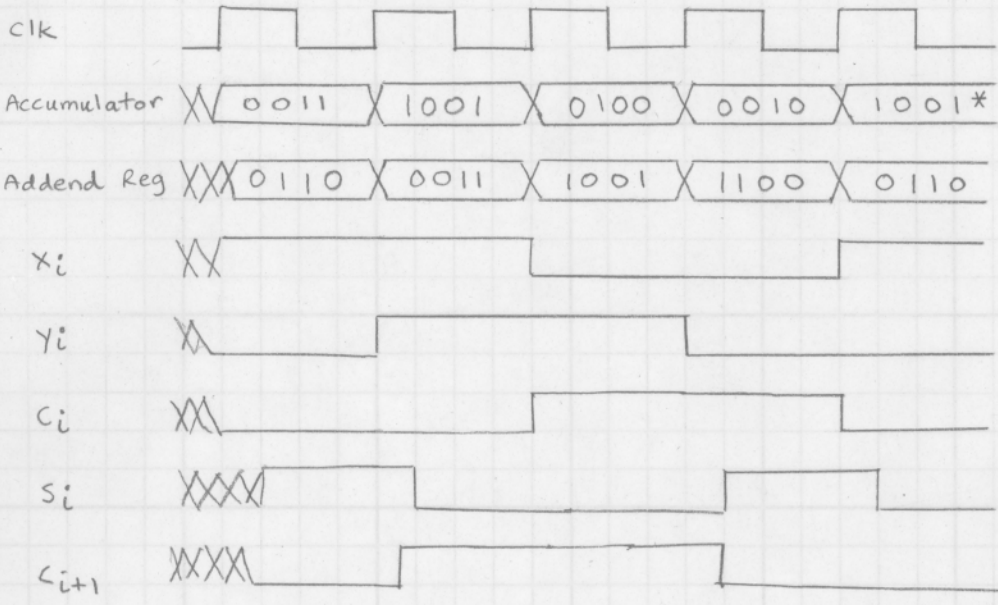Ex: $3_{10} = 0011_2$
 $+ 6_{10} = +0110_2$
 $9_{10} \quad 1001_2$




*final answer

To control shifting, clearing of flip-flops, signaling when result is computed, we need a control FSM.

22-141 50 SHEETS
 22-142 100 SHEETS
 22-144 200 SHEETS
 AMPAD

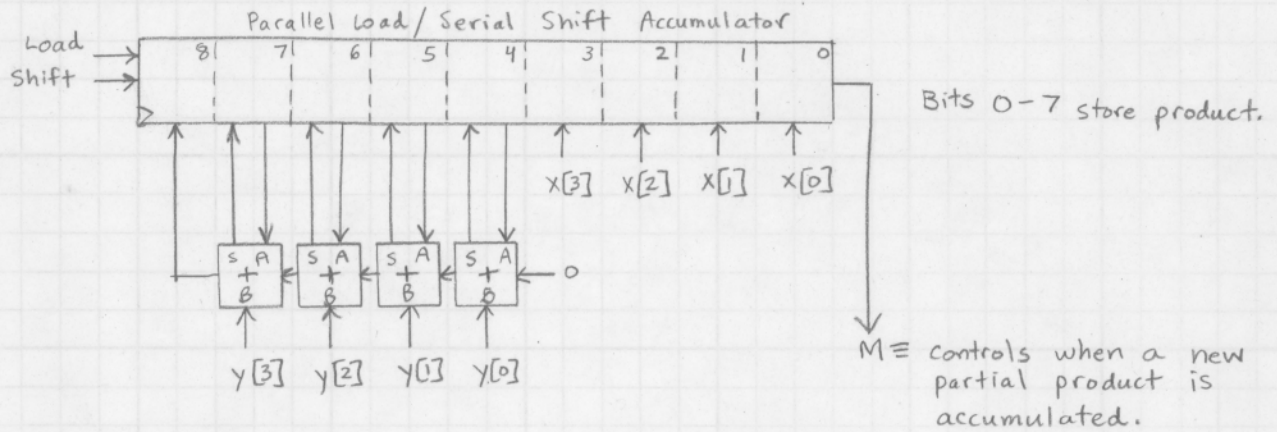18.2 Serial (Shift and Add) Multiplication

A serial multiplier can be made using a shift register and a ripple-carry adder to sum successive partial products into an accumulator:



Ex: $3_{10} \times 4_{10} = 12_{10} \rightarrow$

$$\begin{array}{r} 0011_2 \\ \times 0100_2 \\ \hline 0001100_2 \end{array}$$

Divides product from multiplier

① ACC 0000|0011 } Add and shift (M=1)
 Partial Prod. 0100
 M=1

② ACC 00100|001 } Add and shift (M=1)
 Partial Prod. 0100
 M=1

③ ACC 001100|00 } Shift (M=0)
 Partial Prod. 0100
 M=0

④ ACC 0001100|0 } Shift (M=0)
 Partial Prod. 0100
 M=0

⑤ ACC 00001100 = 12_{10} ✓ Done
 Partial Prod. 0100


50 SHEETS
100 SHEETS
200 SHEETS



Extensions to Adder Circuits

Adding basic logic gates to adders yields multiple functions:

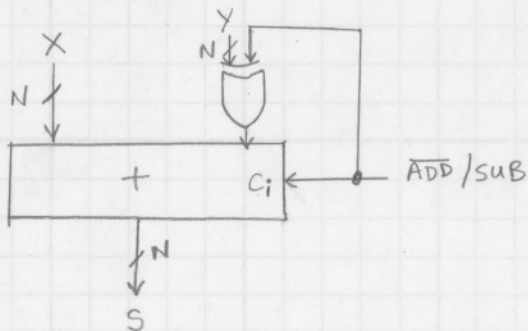Adder/Subtractor ($X, Y \equiv 2$'s complement binary numbers)




$\overline{ADD/SUB} = 0 \rightarrow S = X + Y$

$\overline{ADD/SUB} = 1 \rightarrow S = X - Y = X + (-Y)$

(Note: $Y \oplus 1 = \bar{Y}$)


Comparator

($X, Y \equiv 2$'s complement)

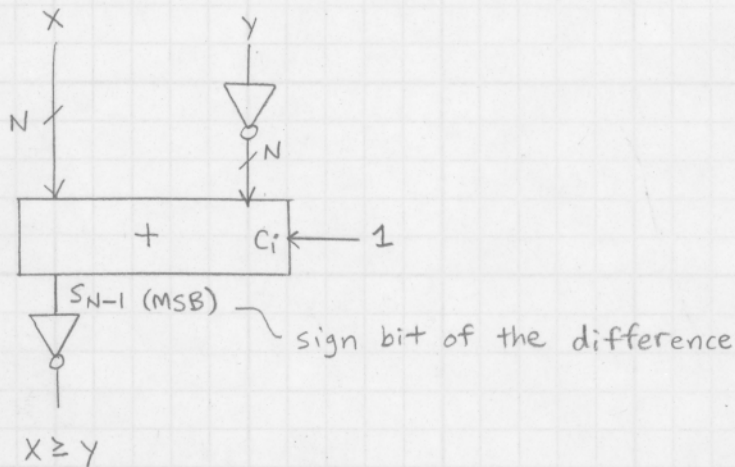

Shifters

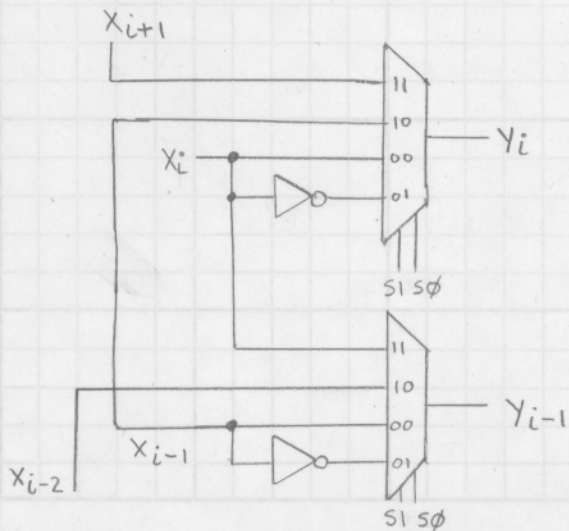Fixed bit shifts (or rotates) can be done with wiring. Programmable shifting requires active circuits (muxes or tri-state buffers).




S1	S0	Yi	
0	0	Xi	buffer
0	1	Xi'	inverter
1	0	Xi-1	left shift
1	1	Xi+1	right shift

50 SHEETS
22-141
100 SHEETS
22-142
200 SHEETS
22-144



Logarithmic Shifter

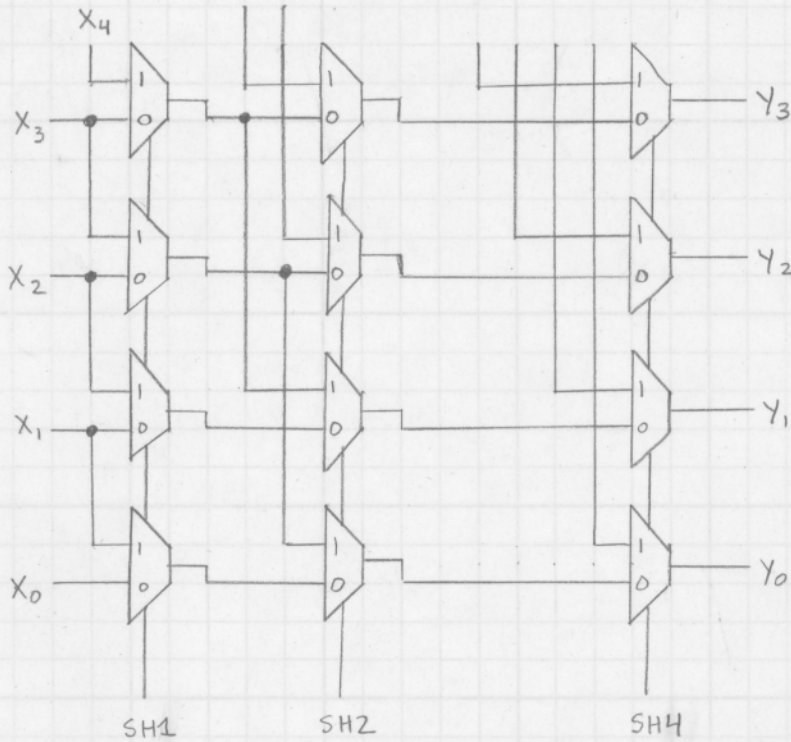A logarithmic shifter uses a tree of muxes to implement a maximum M bit shift in $\log_2 M$ stages.




SH1	SH2	SH4	Y_0
0	0	0	X_0
1	0	0	X_1
0	1	0	X_2
1	1	0	X_3
	⋮		⋮

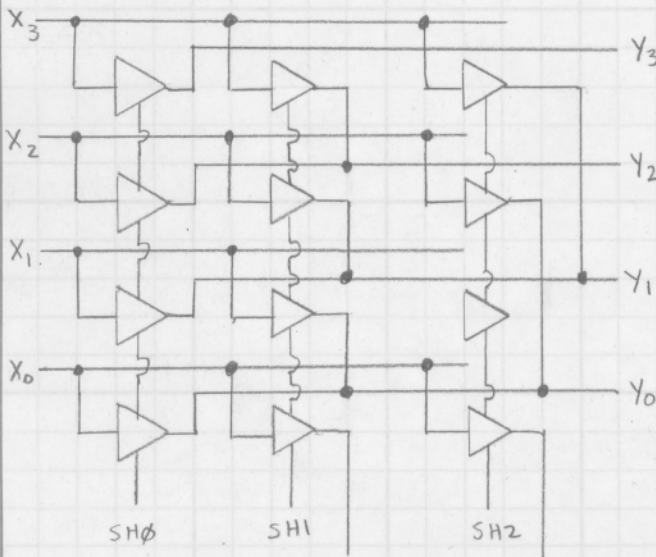22-141 50 SHEETS
22-142 100 SHEETS
22-144 200 SHEETS



Barrel Shifter

A barrel shifter uses an array of switches or tri-state buffers to implement shifting with a constant propagation delay.



SH0	SH1	SH2	Y_0
1	0	0	X_0
0	1	0	X_1
0	0	1	X_2