

## 2.1 Boolean Algebra

Boolean algebra (for our purposes) operates on variables that can take on 1 of 2 values.

EX:  $X = \text{ON}$  or  $\text{OFF}$   
 $= \text{TRUE}$  or  $\text{FALSE}$   
 $= \text{full}$  or  $\text{empty}$   
 $= 1$  or  $0$   
 $= +5\text{V}$  or  $0\text{V}$

It's arbitrary how we assign values as long as we're consistent.



## 2.2 Basic Operations

### Invert/NOT/Complement Operator



Denote inversion/complementation by  $\bar{X}$  or  $X'$  or  $!X$  or  $\sim X$   
 If  $X = \text{ON}$ , then  $\bar{X} = \text{OFF}$   
 If  $Y = 0$ , then  $Y' = 1$

Symbol:  $X \rightarrow \text{Inverter} \rightarrow X'$

Sometimes denoted as just a "bubble"



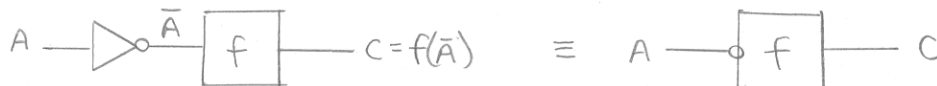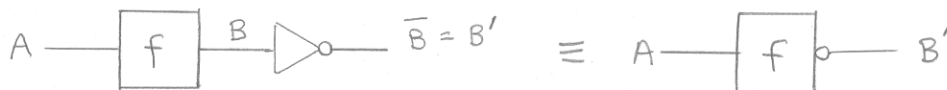If we want to invert B or A, add an inverter or bubble to the output or input, respectively.



Boolean variables have a (very!) limited number of possible values so we can enumerate all possibilities in a truth table.

X	X'
0	1
1	0

Note:  $N$  input Boolean variables have  $2^N$  possible input combinations, so we can build truth tables only for a small number of inputs.

AND Operator

AND must have two or more inputs:

X AND Y AND Z or  $X \cdot Y \cdot Z$  or XYZ or "Product of X, Y, Z"


↑  
By which we mean logical product, not multiplication.

Def: Output is 1 or TRUE only when all inputs are 1 or TRUE.


X	Y	$X \cdot Y$
0	0	0
0	1	0
1	0	0
1	1	1

X	Y	Z	$X \cdot Y \cdot Z$
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

Symbol:   $X \cdot Y$

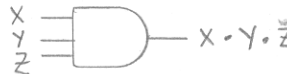  $X \cdot Y \cdot Z$

Ex: Switches in series

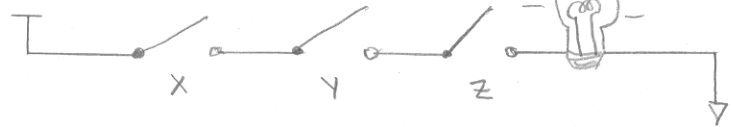OR Operator


Also has two or more inputs: X OR Y OR Z or  $X + Y + Z$  or "Sum of X, Y, Z"


↑ By which we mean logical sum, not addition.

Def: Output is 1 or TRUE if any input is 1 or TRUE.


X	Y	$X + Y$
0	0	0
0	1	1
1	0	1
1	1	1

X	Y	Z	$X + Y + Z$
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1


Symbol:   $X + Y$

  $X + Y + Z$

Ex: Switches in parallel

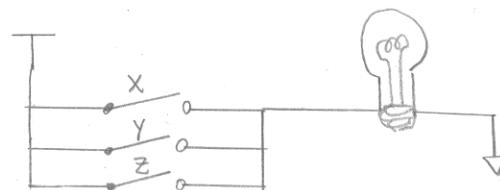


NAND (NOT AND) Operator

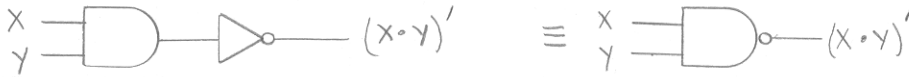

X	Y	$\overline{X \cdot Y}$
0	0	1
0	1	1
1	0	1
1	1	0

NAND is easier to build (much more common) in hardware.

NOR (NOT OR) Operator

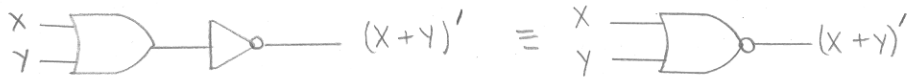

X	Y	$\overline{X + Y}$
0	0	1
0	1	0
1	0	0
1	1	0

XOR (eXclusive OR) Operator

XOR has two or more inputs :  $X$  XOR  $Y$  or  $X \oplus Y$

Def: Output is 1 or TRUE if one or the other inputs (but not both) are 1 or TRUE, i.e.  $X=1$  or  $Y=1$ , exclusively.

X	Y	$X \oplus Y$
0	0	0
0	1	1
1	0	1
1	1	0

Symbol:



Ex:




X



Y




$X \oplus Y$

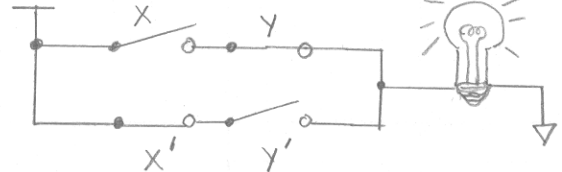

Useful in addition :  $Sum = X \text{ PLUS } Y \equiv Sum = X \oplus Y$

XNOR Operator

Complement of XOR

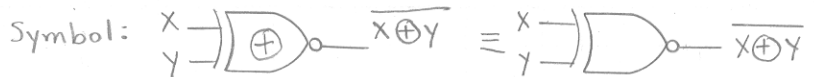


Def: Output is 1 or TRUE if both inputs are the same.

X	Y	$\overline{X \oplus Y}$
0	0	1
0	1	0
1	0	0
1	1	1

XNOR is sometimes called the "equivalence" operator.



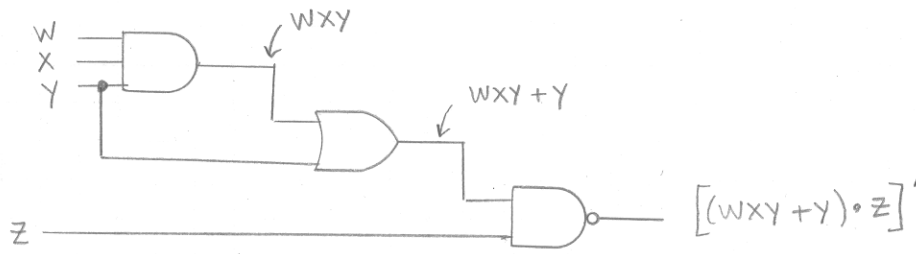More complex expressions are built out of these fundamental blocks:



Literal Def: A variable or its complement in an expression.

Ex:  $[(WXY + Y) \cdot Z]'$  has 5 literals (W, X, Y twice, and Z)

2.4 Basic Theorems

Operations with 0 or 1

$X + 0 = X$   
 $X + 1 = 1$  (set)  
 $X \cdot 0 = 0$  (clear)  
 $X \cdot 1 = X$

We frequently need to set or clear part of a larger binary word (number).

Ex: Set bit 1  $\begin{matrix} XXXX \\ \text{OR } 0001 \\ \hline XXX1 \end{matrix}$

Ex: Clear bits 2 and 3  $\begin{matrix} YYY Y \\ \text{AND } 0011 \\ \hline 00YY \end{matrix}$

Idempotent Laws

OR:  $X + X = X$  Verify using truth table:

X	Y	X + Y
0	0	0 ← Y = X
0	1	1
1	0	1
1	1	1 ← Y = X

Symbolically,  $X \rightarrow \text{AND} \rightarrow X \equiv X \rightarrow \text{OR} \rightarrow X$  (no bubble)

AND:  $X \cdot X = X$  Verify using truth table:

X	Y	X · Y
0	0	0 ← Y = X
0	1	0
1	0	0
1	1	1 ← Y = X

Symbolically,  $X \rightarrow \text{OR} \rightarrow X \equiv X \rightarrow \text{AND} \rightarrow X$

22-141 50 SHEETS  
22-142 100 SHEETS  
22-144 200 SHEETS



