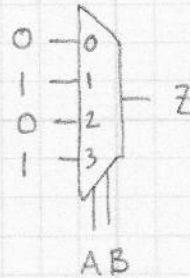


9.2a Using muxes to implement combinational logic

A) Number of mux inputs = $2^{\text{Number of input bits}}$

A	B	Z
0	0	0
0	1	1
1	0	0
1	1	1



B) Number of mux inputs = $\frac{1}{2} \cdot 2^{\text{Num. of input bits}}$


A	B	C	Z
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

$AB=00 \quad Z_{00}=0$

$AB=01 \quad Z_{01}=1$



$AB=10 \quad Z_{10}=C$

$AB=11 \quad Z_{11}=\bar{C}$

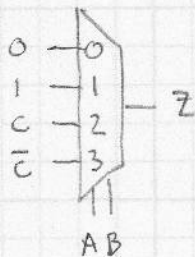

- Assign any input variables to mux control inputs
- For each mux input, there are only four possibilities:
 - 1) 0
 - 2) 1
 - 3) last input variable
 - 4) last input variable inverted
- \therefore Any boolean expression can be implemented

Other solutions:

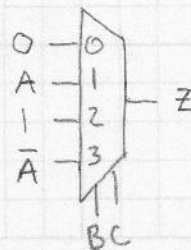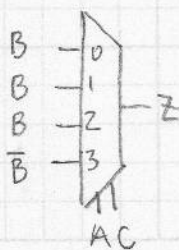

c) Number of mux inputs = $\frac{1}{2^2} \cdot 2^{\text{Number of input bits}}$


1) Approach #1

Look at K-map instead of truth table:

		CD			
		00	01	11	10
AB	00				
	01				
	11				
	10				

There are 6 ways to choose 2 of the 4 input variables:
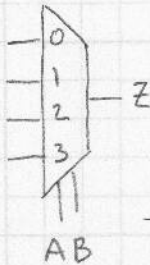
$${}^4C_2 = \frac{4!}{2!(4-2)!} = \frac{24}{2 \cdot 2} = 6$$



Each mux input covers a:
row in K-map

CD column in K-map

AC box

AD split boxes

BC split boxes

BD split boxes

A		0	1	0
0				
1				

B		0	1	0
0				
1				
0				

AB				
00				
01				
11				
10				

		CD			
		00	01	11	10
AB	00				
	01				
	11				
	10				

A	C	0	1
0			
1			

B	C	0	1
0			
1			
0			

There are 16 possible combinations for each box of 4 outputs. 6 are trivial to implement, the other 10 require a gate.

- Designer judgment is required to find the best solution



2) Approach #2

- Find minimum SOP or POS solution
- Use mux to implement a sub-term

Ex: $Z = AC'D + BD$

