

# **7 BASIC DIAGRAMS**


# Basic Diagrams

## 1. Block diagram

- Just like it says; diagram of blocks (and inter-connections)
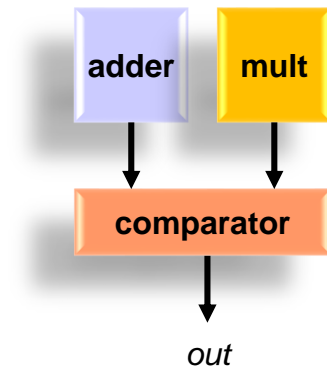
## 2. Circuit diagram



- Although it may not require details to the transistor level or gate level (e.g., NAND or NOR), it should have more circuit-type details if applicable
- Having said that, in some cases it may be the same as a block diagram



# Basic Diagrams
 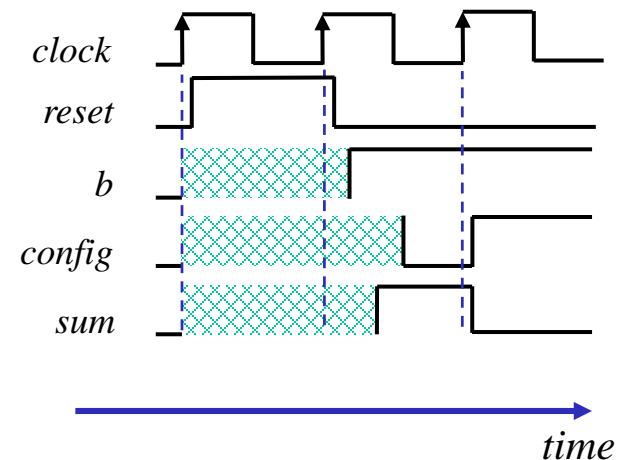
## 3. Timing diagram


- Logic level (voltage) versus time
- As a rule, the *clock* is at the top. Draw a small arrow on each active edge. Draw a light vertical line aligned with each active clock edge.
- Several common waveform features:
  - Simple single-bit signal 0/1 values
  - Multi-bit bus
  - Transition location or region where a signal, or signal(s) within a bus, changes value



# Basic Diagrams

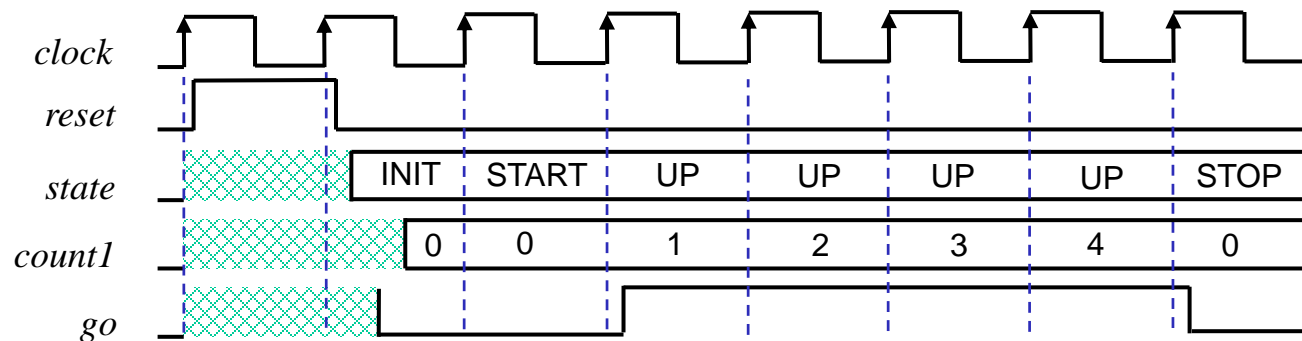
## 3. Timing Diagram continued

- Draw transitions of signals that come from a register a very short time after the active edge of the clock, not at the same time as the clock edge—this is for increased clarity however it also explicitly shows the “*clock-to-Q* delay”
- Timing diagrams may also show higher-level events such as state and counter values




# Basic Diagrams

## 4. State Diagram

 


## 5. Arithmetic Dot Diagrams

 

# Basic Diagrams
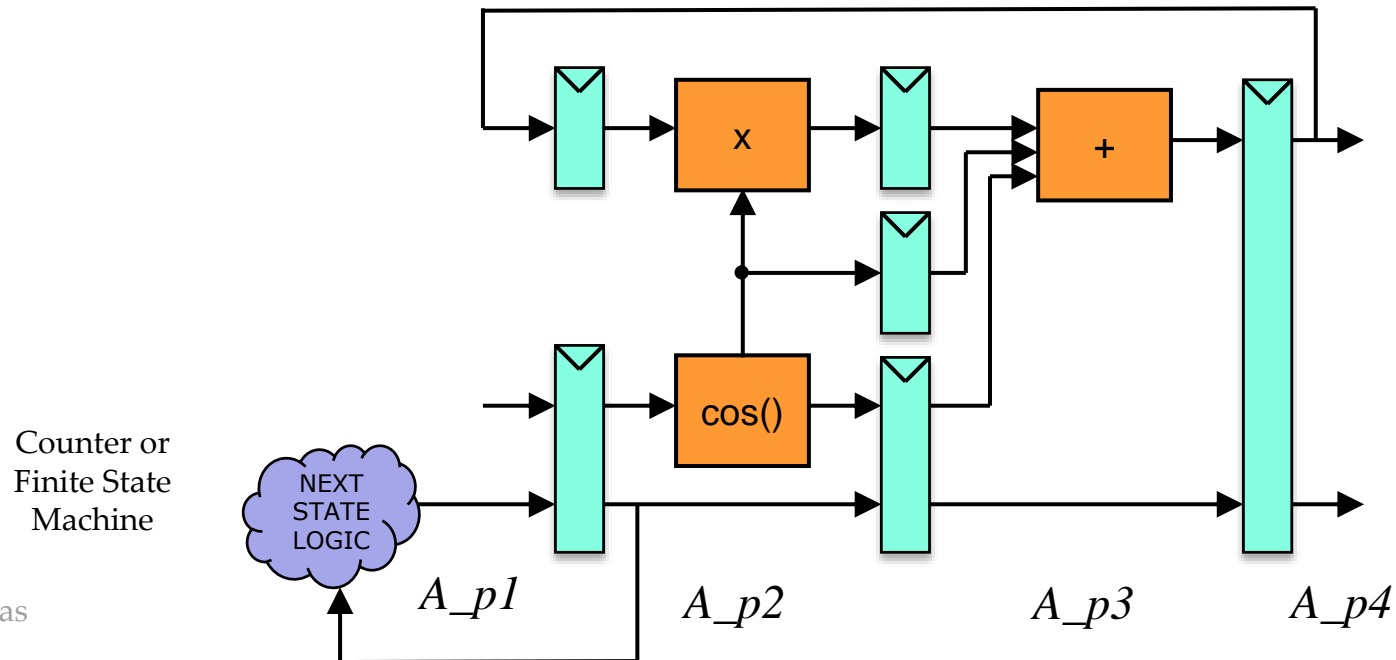
## 6. Pipelined Block Diagram

- All registers are aligned with others in the same pipeline stage
- “Reverse-flowing” signals are generally not pipelined
- It is often advisable to include a pipeline-stage notation in each signal’s name



# Basic Diagrams

## 7. Pipeline Diagram

- Useful for designing deeply-pipelined digital processors

