

BINARY MULTIPLICATION

Multipliers

- Multipliers are widely used in digital signal processing, generally more so than in general-purpose workloads
- Major categories of multiplier types
 - *Unsigned × Unsigned*
Also very useful for sign-magnitude data
 - *Signed 2's complement × Signed 2's complement*
Very useful for fixed-point 2's complement data
- Hardware is typically built in a manner broadly similar to how you would do it with paper and pencil
- The naming convention is somewhat unfortunate:

multiplier
× *multiplier*

Multipliers

- Example: 4-bit unsigned *multiplicand* “ a ” times 4-bit *multiplier* “ b ”
- b could be signed or unsigned
- $p_{xy} = a_x \times b_y$
 $= a_x \text{ AND } b_y$

		a_3	a_2	a_1	a_0	
	\times	b_3	b_2	b_1	b_0	
		p_{30}	p_{20}	p_{10}	p_{00}	$\leftarrow b_0$
	p_{31}	p_{21}	p_{11}	p_{01}	0	$\leftarrow b_1$
	p_{32}	p_{22}	p_{12}	p_{02}	0	$\leftarrow b_2$
	p_{33}	p_{23}	p_{13}	p_{03}	0	$\leftarrow b_3$


Multipliers

- Example: 4-bit signed 2's complement *multiplicand* “ a ” times 4-bit *multiplier* “ b ”
- b could be signed or unsigned
- s = partial product sign extension bits
- $p_{xy} = a_x \times b_y$
 $= a_x \text{ AND } b_y$

				a_3	a_2	a_1	a_0	
			\times	b_3	b_2	b_1	b_0	
s	s	s	s	p_{30}	p_{20}	p_{10}	p_{00}	$\leftarrow b_0$
s	s	s	p_{31}	p_{21}	p_{11}	p_{01}	0	$\leftarrow b_1$
s	s	p_{32}	p_{22}	p_{12}	p_{02}	0	0	$\leftarrow b_2$
s	$\overline{p_{33}}$	$\overline{p_{23}}$	$\overline{p_{13}}$	$\overline{p_{03}}$	0	0	0	$\leftarrow b_3$

3 Main Steps in Every Multiplier

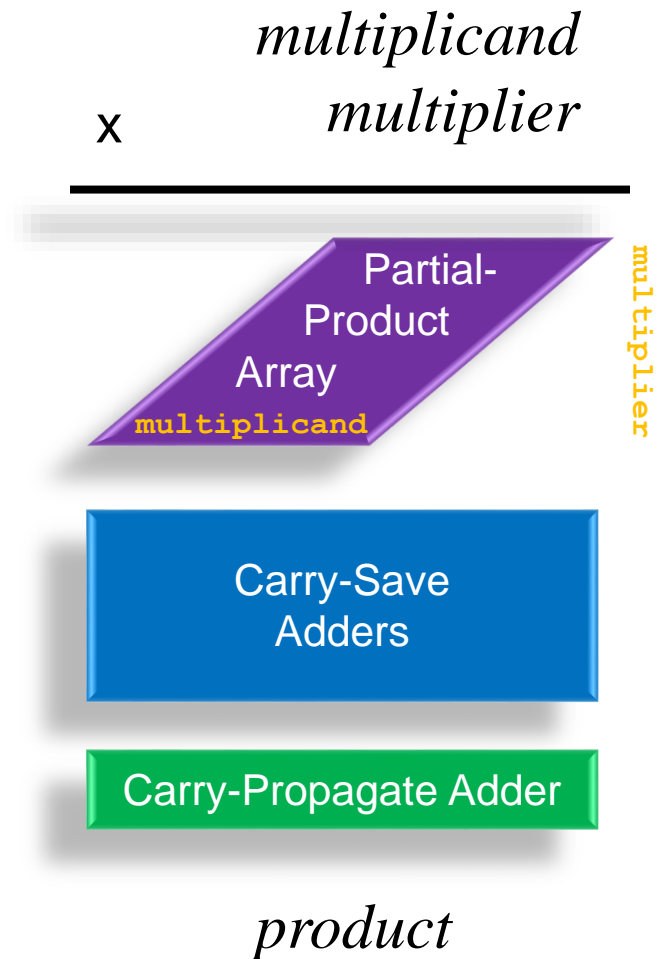
- 1) Generation of partial products
- 2) Reduction or “compression” of the partial product array (normally using carry-save addition) so that the product is composed of two words
 - Linear array addition
 - Tree addition (Wallace tree)
- 3) Final adder: Carry-propagate adder (CPA)
 - Converts the product in carry-save form into a single word form
 - Any style of CPA is fine though we probably favor faster ones



Straight-forward Partial Product Generation

- This is the simplest method to generate partial products
- Hardware looks at one bit of the *multiplier* (Y_i) at a time
- Partial products are copies of the *multiplicand* AND'd by bits of the *multiplier*
- Number of bits in the *multiplier*
= Number of partial products
= Number of terms/words/rows that must be added

Y_i	Partial product
0	0
1	$+x$ (= <i>multiplicand</i>)

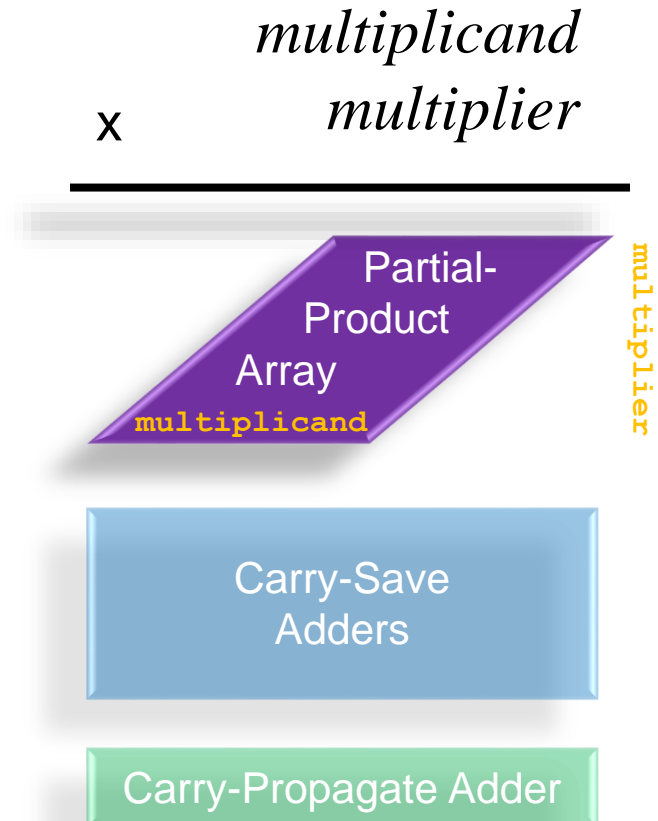

Straight-forward Partial Product Generation

- There are only two possible partial product results
- Two reasonable hardware solutions are:
 - a row of 2:1 muxes with zeros on one input
 - a row of AND gates (this should be more efficient)

$+x$

multiplicand


0

0

Y_i	Partial product
0	0
1	$+x (= \textit{multiplicand})$


Example unsigned 4-bit × 4-bit multiplication

 - Example: 4-bit unsigned *multiplicand* “a” 1100 times 4-bit *multiplier* “b” 1010
- $1100 \times 1010 = 12 \times 10 = 120$
- $1100 \times 1010 = (12 \times 8) + (12 \times 0) + (12 \times 2) + (12 \times 0) = 120$
- $1111000 = 64 + 32 + 16 + 8 = 120$ 😊



Example 2's complement 4-bit × 4-bit multiplication

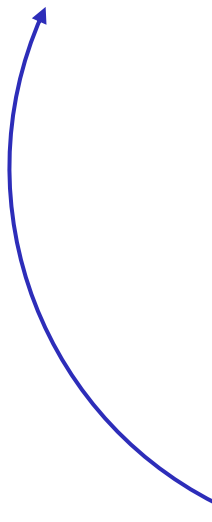- Example: 4-bit signed 2's complement *multiplicand* "a" 1100 times 4-bit *multiplier* "b" 1010
- $1100 \times 1011 = -4 \times -5 = +20$
- $1100 \times 1011 = (-4 \times -8) + (-4 \times 0) + (-4 \times 2) + (-4 \times 1) = +20$
- $00010100 = 16 + 4 = +20$ 😊



					1	1	0	0	
				×	1	0	1	1	
					<hr/>				
1	1	1	1	1	1	1	0	0	← 1
1	1	1	1	1	1	0	0	0	← 1
0	0	0	0	0	0	0	0	0	← 0
0	<u>1</u>	<u>1</u>	<u>0</u>	<u>0</u>	<u>1</u>	0	0	0	← 1
	<hr/>								
0	0	0	1	0	1	0	0		