

1. A transfer function magnitude at some frequency ω_1 is $|H(j\omega_1)| = 0.20$. What is this magnitude in dB?

$$|H(j\omega_1)| = \underline{\hspace{2cm}} \text{ dB}$$

$$\begin{aligned} \text{in dB: } 20 \log_{10} |\tilde{H}| &= 20 \log 0.2 \\ &= -13.98 \text{ dB} = -14 \text{ dB} \end{aligned}$$

2. a) A filter has a transfer function $H_1(j\omega) = \frac{10+j\omega}{j\omega}$. What is the magnitude $|H_1|$ of this transfer function [or the amplitude of (H_1)] at $\omega = 20$ rad/s ?

$$|H_1| = \underline{\hspace{2cm}}$$

$$|H_1| = \frac{|10+j20|}{|j20|} = \frac{\sqrt{10^2+20^2}}{20} = 1.12$$

b) What is the phase of this transfer function [or the angle (H_1)] at $\omega = 20$ rad/s ?

$$\text{angle}(H_1) = \underline{\hspace{2cm}}$$

//

$$\text{angle} \left(\frac{10+j20}{j20} \right) = \text{angle}(10+j20) - \text{angle}(j20)$$


$$= \tan^{-1} \frac{20}{10} - 90^\circ$$

$$= 63.4^\circ - 90^\circ = -26.6^\circ$$

3) What are the magnitude and phase of the complex number $-10 + j1$?

a) magnitude or amplitude = _____ (not in dB)

$$|-10 + j1| = \sqrt{-10^2 + 1^2}$$
$$= 10.05$$

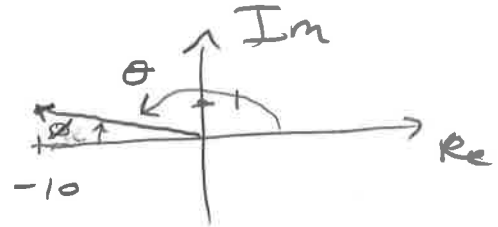

b) Phase or angle = _____ degrees

$$\phi = \tan^{-1} \frac{1}{10} = 5.7^\circ$$

$$\Theta = 180 - \phi = 174.3^\circ$$

complex number in 2nd quadrant

- 4: In lab, the signal generator is outputting a sinusoidal signal:
 $v(t) = B\cos(100t + 70^\circ)$. You measure this signal using a Digital Multimeter (DMM) and the DMM reads $2.0V_{rms}$.

a) What is the peak voltage of this sinusoidal signal? _____

$$\frac{\text{peak}}{\sqrt{2}} = \text{rms}$$

$$\Rightarrow \text{peak} = \sqrt{2}(\text{rms}) = \sqrt{2}(2.0) = 2.83V$$


"B"

b) What is the phasor representation for this signal? _____

$$\tilde{V} = B \angle 70^\circ = 2.83 \angle 70^\circ$$

$$\text{or } 2.83 e^{j70^\circ}$$

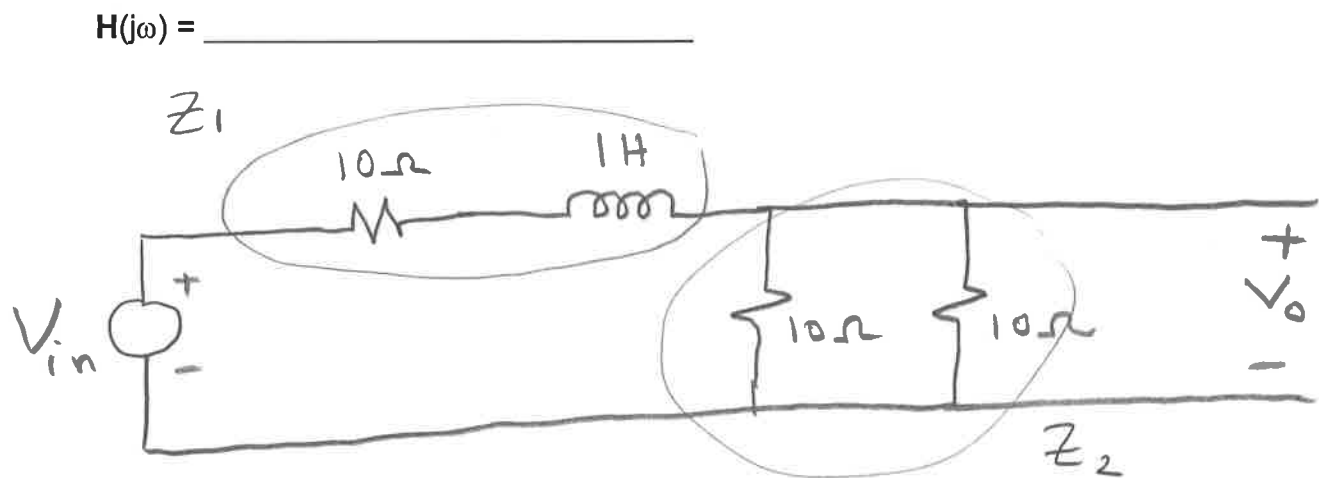5. Find the transfer function $H(j\omega) = \mathbf{V}_o(j\omega)/\mathbf{V}_{in}(j\omega)$ for the circuit below. (The answer should be in the form of a ratio of two complex expressions like 'a + jb', where a and/or b may be a function of ω .)







$$Z_1 = 10 + j\omega 1 = 10 + j\omega$$

$$Z_2 = \frac{10 \cdot 10}{10 + 10} = 5\Omega$$

$$\tilde{H} = \frac{V_o}{V_{in}} = \frac{Z_2}{Z_1 + Z_2} = \frac{5}{10 + j\omega + 5}$$

$$= \frac{5}{15 + j\omega}$$





6. a) Draw the approximate Bode magnitude (or amplitude) plot [$|H|$ in dB vs. ω on a log scale] for the transfer function $H(s) = \frac{10s}{1+s}$. (Set $s = j\omega$.) (A Bode plot using only straight-line segments is requested here.)

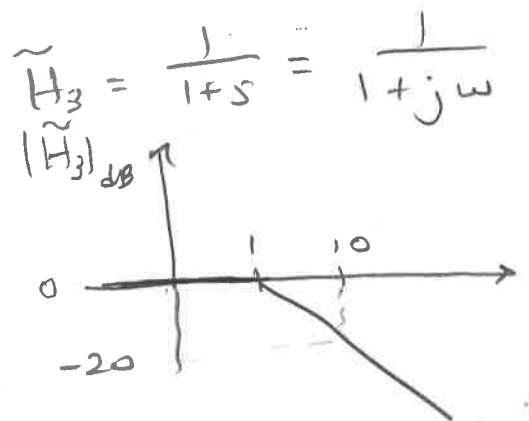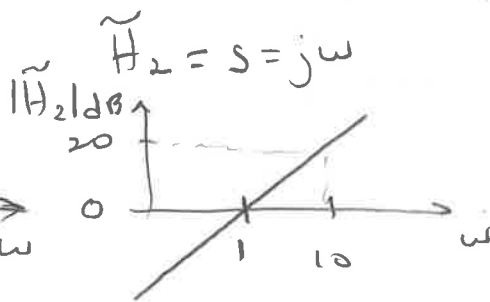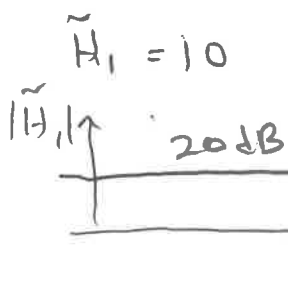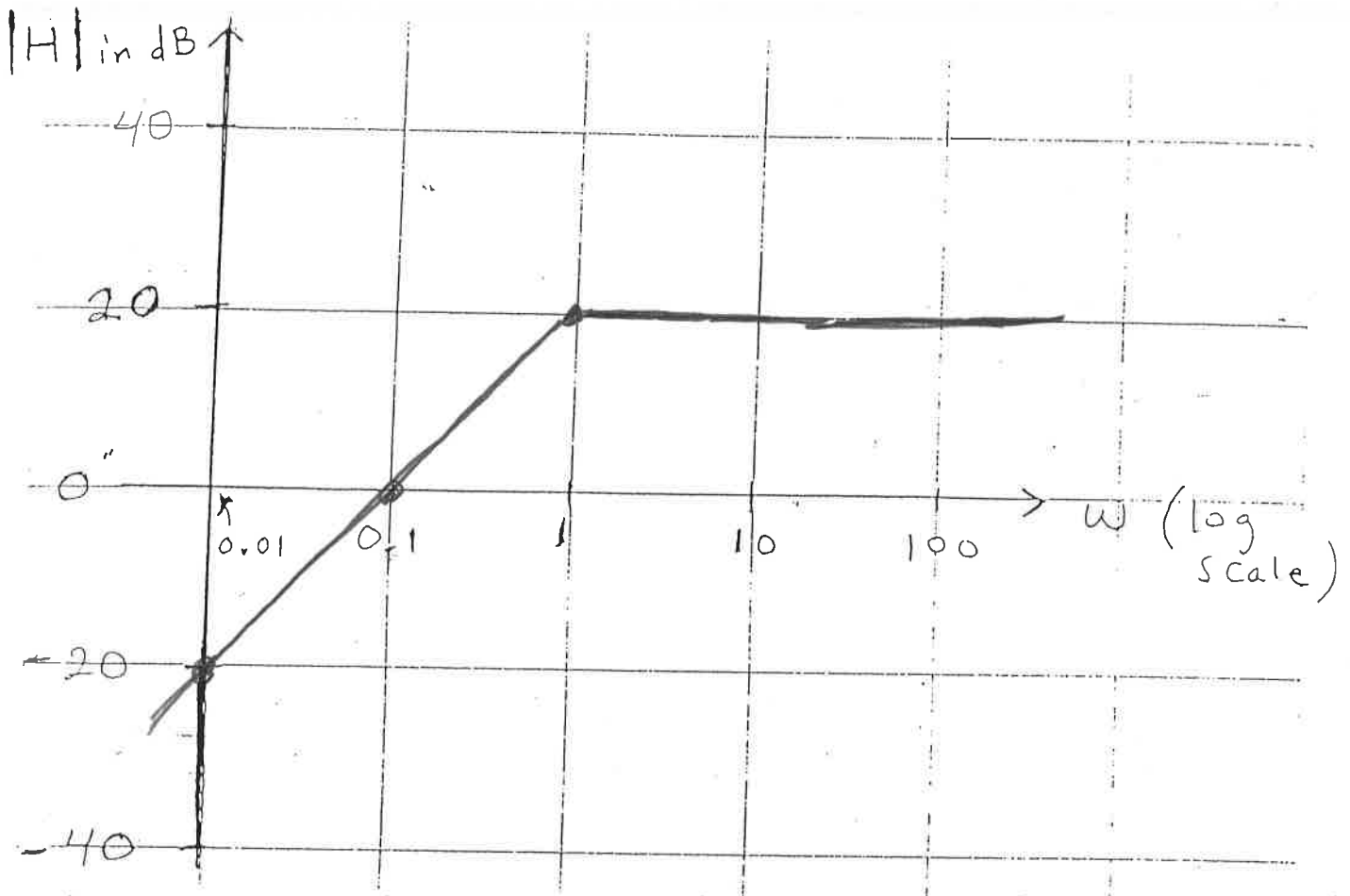

add these 3 plots
to get answer

6 (continued)

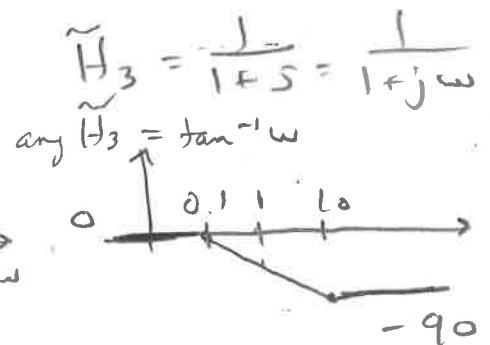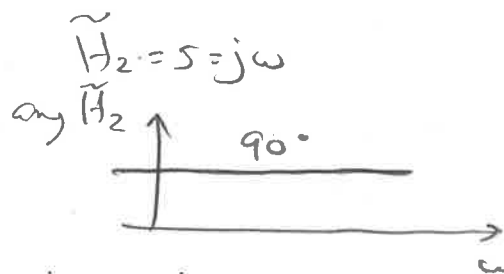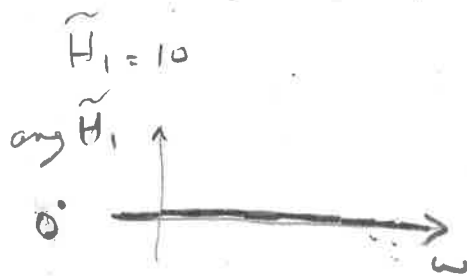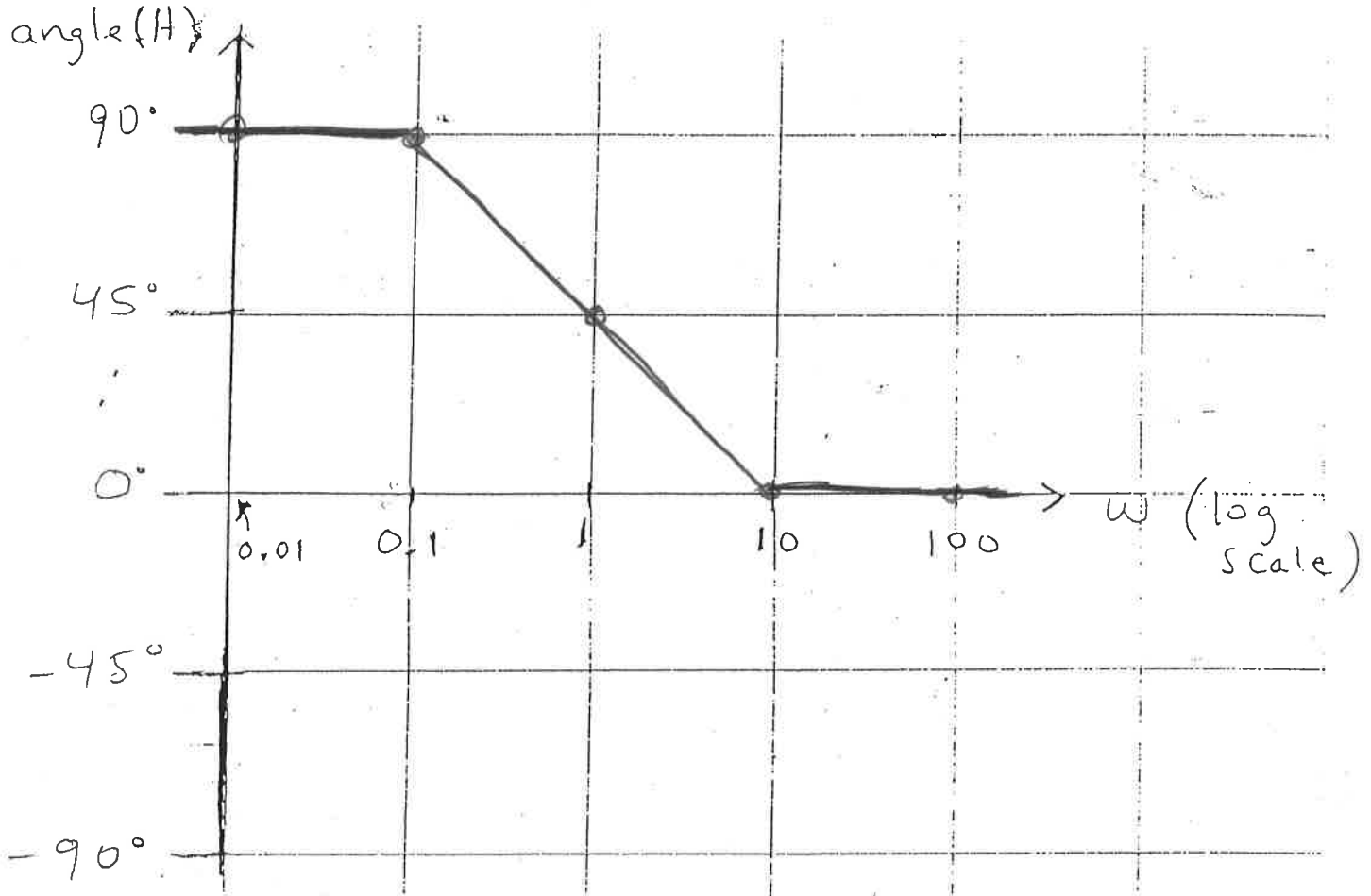b) Draw the approximate Bode phase (or angle) plot [$\angle(H)$ vs. ω on a log scale] for the transfer function $H(s) = \frac{10s}{1+s}$. (Set $s = j\omega$.) (A Bode plot using only straight-line segments is requested here.)




add these 3 plots

7. In the circuits below, assume the op amp is ideal.

a) For the circuit below, what R value gives $V_o / V_{in} = -12$

R = _____

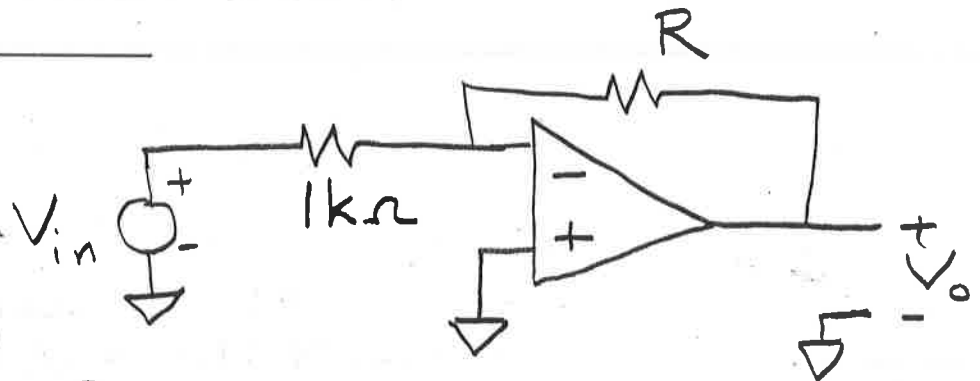


$$\frac{V_o}{V_{in}} = -\frac{R}{1k\Omega} = -12$$

$$\Rightarrow R = 12k\Omega$$

b) For the circuit below, what is the output voltage, V_o ? (The current source and voltage source are DC sources.)

$V_o =$ _____

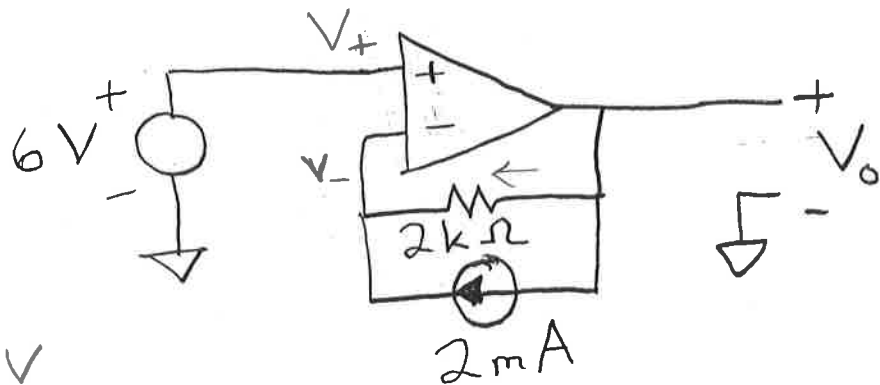

$$V_+ = V_- = 6V$$

$$\text{KCL: } 2mA + \frac{V_o - V_-}{2k\Omega} = 0$$

$$\begin{aligned} \Rightarrow V_o &= -2mA(2k\Omega) + V_- \\ &= -4V + 6V = 2V \end{aligned}$$