
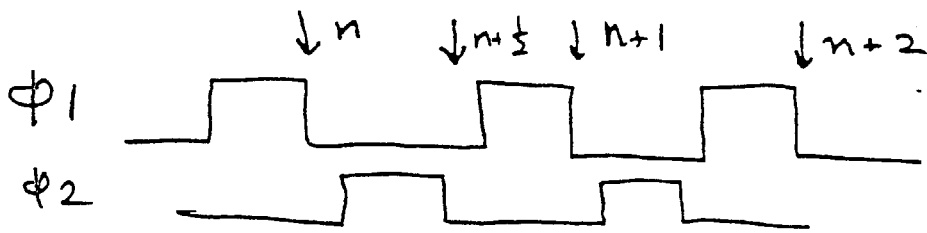


# DC output offset calculation:

P.H.

1) Due to op amp input offset voltage:

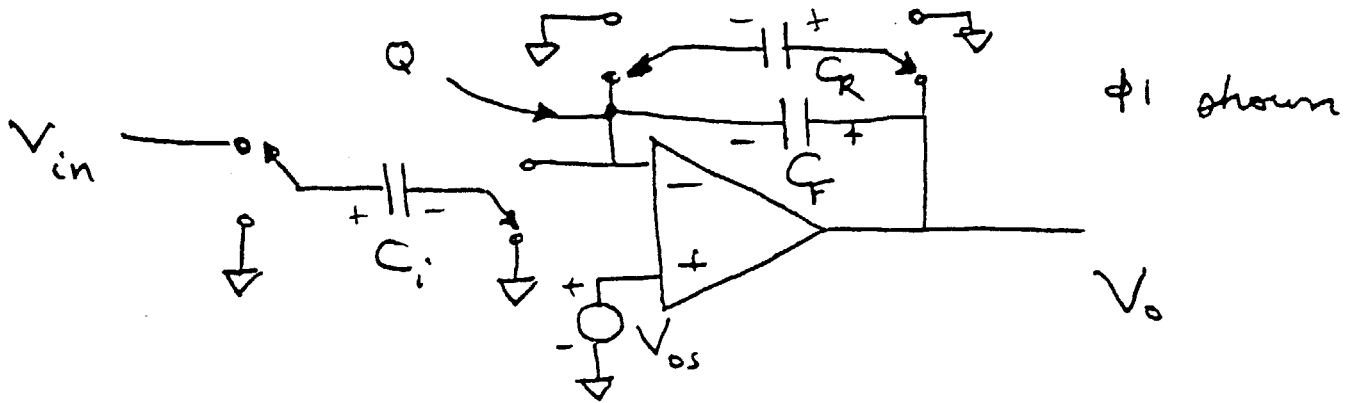

we/  $V_{in} = 0V, Q = 0c.$

$\phi_1$ , time  $n$ :

$$V_o(n) = V_{CF}(n) + V_{os}$$

$\phi_2$ , time  $n + \frac{1}{2}$ :

$$\left\{ \begin{array}{l} -Q_{Ci}(n) - Q_{CF}(n) = -Q_{Ci}(n + \frac{1}{2}) - Q_{CF}(n + \frac{1}{2}) \\ V_o(n + \frac{1}{2}) = \underbrace{V_{CF}(n) + \frac{C_i}{C_F} V_{os}}_{V_{CF}(n + \frac{1}{2})} + V_{os} \end{array} \right.$$


$\phi_1$ , time  $n + 1$ :

$$\left\{ \begin{array}{l} -Q_{CR}(n + \frac{1}{2}) - Q_{CF}(n + \frac{1}{2}) = -Q_{CR}(n + 1) - Q_{CF}(n + 1) \\ V_o(n + 1) = \underbrace{\frac{C_F}{C_F + C_R} V_{CF}(n + \frac{1}{2})}_{V_{CF}(n + 1)} + V_{os} \end{array} \right.$$

$$\therefore V_o(n + 1) = \frac{C_F}{C_F + C_R} \left[ V_o(n) - V_{os} + \frac{C_i}{C_F} V_{os} \right] + V_{os}$$

$$n \rightarrow \infty \Rightarrow V_o(\infty) = \left( 1 + \frac{C_i}{C_R} \right) V_{os}$$

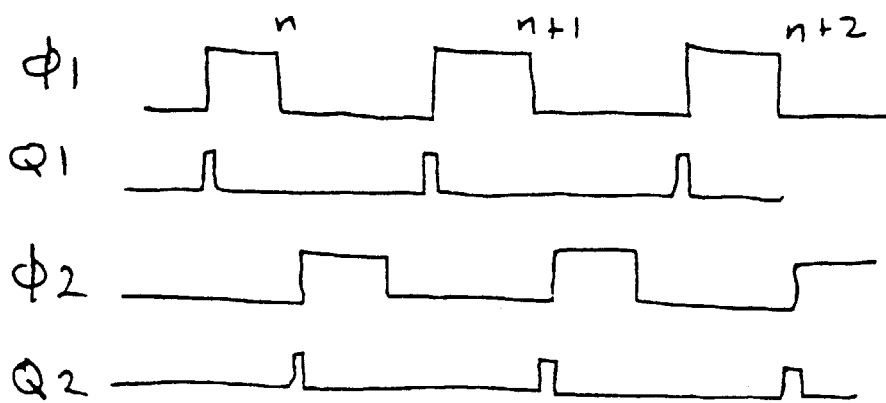2) Due to charge dumping in  $\ominus$  mode:



w/  $V_{in} = 0V$  and  $V_{os} = 0.0mV$ :

$$\phi_{1,n}: V_o(n)$$

$$\phi_{2, n+\frac{1}{2}}: V_o(n+\frac{1}{2}) = \frac{Q_2}{C_F} + V_o(n)$$

$$\phi_{1, n+1}: V_o(n+1) = \frac{Q_1}{C_F + C_R} + \frac{C_F}{C_F + C_R} V_o(n+\frac{1}{2})$$

$$\phi_{2, n+\frac{3}{2}}: V_o(n+\frac{3}{2}) = \frac{Q_2}{C_F} + V_o(n+1)$$

$$\text{on } \phi_{1}: V_o(n+1) = \frac{Q_1}{C_F + C_R} + \frac{Q_2}{C_F + C_R} + V_o(n) \frac{C_F}{C_F + C_R}$$

$$n \rightarrow \infty \Rightarrow V_o(\infty) = \frac{Q_1 + Q_2}{C_R}$$

$$\text{on } \phi_{2}: V_o(n+\frac{3}{2}) = \frac{Q_2}{C_F} + \frac{Q_1}{C_F + C_R} + \frac{C_F}{C_F + C_R} V_o(n+\frac{1}{2})$$

$$n \rightarrow \infty \Rightarrow V_o(\infty) = \frac{Q_1}{C_R} + \frac{Q_2}{\frac{C_F C_R}{C_F + C_R}}$$

