

# EEC 212

## Problem Set 4

Professor Hurst

### 1

Find an expression for  $(\frac{W}{L})_6$  in terms of  $(\frac{W}{L})_1$  that biases  $M_1$  at the edge of saturation, which assures maximum output swing if the cascoded current source in Figure 1 is used in the output stage of an op-amp. Take  $\lambda = 0$  and  $\gamma = 0$ .  $M_1$  through  $M_4$  all have the same  $(\frac{W}{L})$ .  $(\frac{W}{L})_5 = \frac{1}{9} (\frac{W}{L})_1$ .

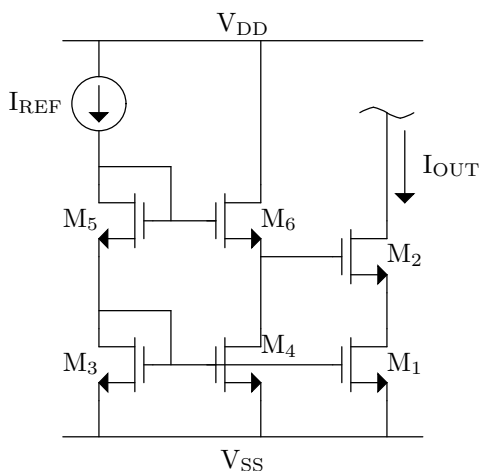


Figure 1: Current Source for Problem 1

### 2

(a) Use Blackman's impedance formula to find a formula for the output resistance of the current mirror in Figure 2. All transistors are in saturation and  $(\frac{W}{L})_1 = (\frac{W}{L})_2 = (\frac{W}{L})_3$ . Find  $R_{out} = fn(A, g_{m1}, r_{o1}, g_{m2}, r_{o2}, \dots)$ .

(b) What  $V_{BIAS}$  voltage gives the maximum output swing? Assume  $A \gg 1$ .

(c) What is  $R_{out}$  for the current source in Figure 3? All transistors are in saturation and  $(\frac{W}{L})_1 = (\frac{W}{L})_2 = (\frac{W}{L})_3 = (\frac{W}{L})_4$ .

### 3

(a) Use return-ratio feedback analysis to find the closed-loop gain,  $A_{CL} = \frac{v_{out}}{v_{in}}$ , and output resistance for the inverting amplifier in Figure 4. For the op-amp, take  $R_{in} = 1M\Omega$ ,  $R_{out} = 10k\Omega$ , and  $a_v = 200$ .

(b) By looking at the return ratio, show that the two-node feedback amp in Figure 5 is always stable if each impedance is either an R or a C.  $a_v$  is a constant voltage gain.

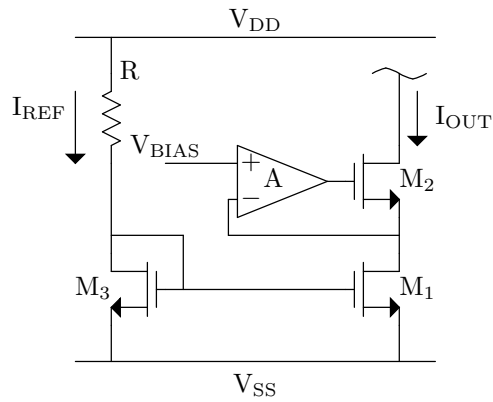


Figure 2: Current Source for Problem 2a.

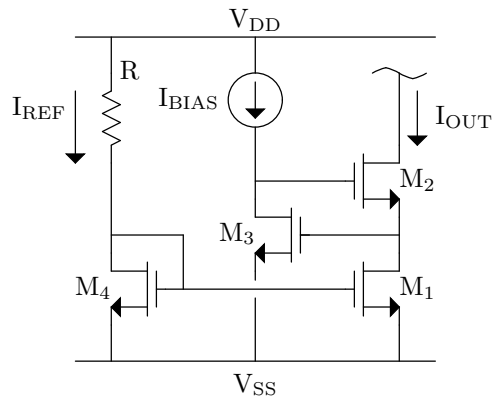


Figure 3: Current Source for Problem 2c.

4

Consider the fully differential circuit in Figure 6. For (a) and (b) find:

$$A'_{DM} = \frac{v_{od}}{v_{id}}, A'_{CM} = \frac{v_{oc}}{v_{ic}}, A'_{CM-DM} = \frac{v_{od}}{v_{ic}}, A'_{DM-CM} = \frac{v_{oc}}{v_{id}}$$

(a)  $R_1 = R_2 = 1k\Omega$ ,  $R_3 = R_4 = 5k\Omega$ , and an ideal differential op-amp with infinite differential mode gain and zero common mode gain.

(b)  $R_1 = 1.01k\Omega$ ,  $R_2 = 0.99k\Omega$ ,  $R_3 = R_4 = 5k\Omega$ , and the ideal op-amp in (a).

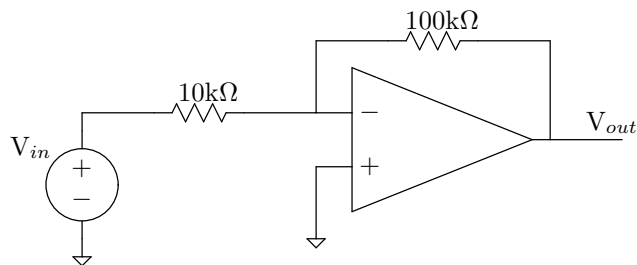


Figure 4: Amplifier for Problem 3a.

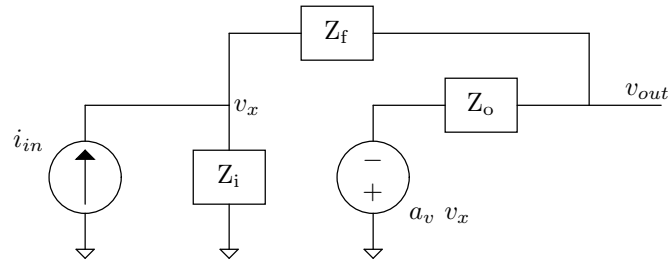


Figure 5: Circuit for Problem 3b.

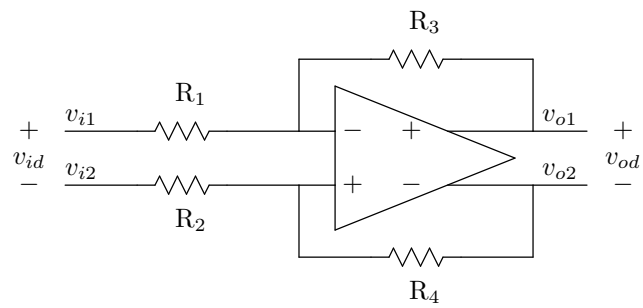


Figure 6: Circuit for Problem 4.

5. a) Compute the return ratio for the circuit in Fig. 7b, and show that it can be written as

$$R = \underbrace{\frac{G_m R_o}{1 + s R_o C_L'}}_{\text{"gain"} = -\frac{N_o}{N_x}} \cdot \underbrace{\frac{C_2}{C_2 + C_1 + C_{in}}}_{\text{"fb factor"} = \frac{N_o}{N_x}}$$

b) Assume  $R(0) = G_m R_o \gg 1$  and the feedforward is negligible ( $d \approx 0$ ).


Then  $A_{CL} = \frac{N_o}{N_{in}} \approx A_{\infty} \frac{R}{1+R}$

What is  $A_{\infty}$  in Fig 7a?


c) Show that the -3dB bandwidth is equal to the freq  $\omega_u'$  where  $|R(\omega_u')| = 1$ .  
Hint: see GHLM eqns 9.11-9.20 for 1 option.

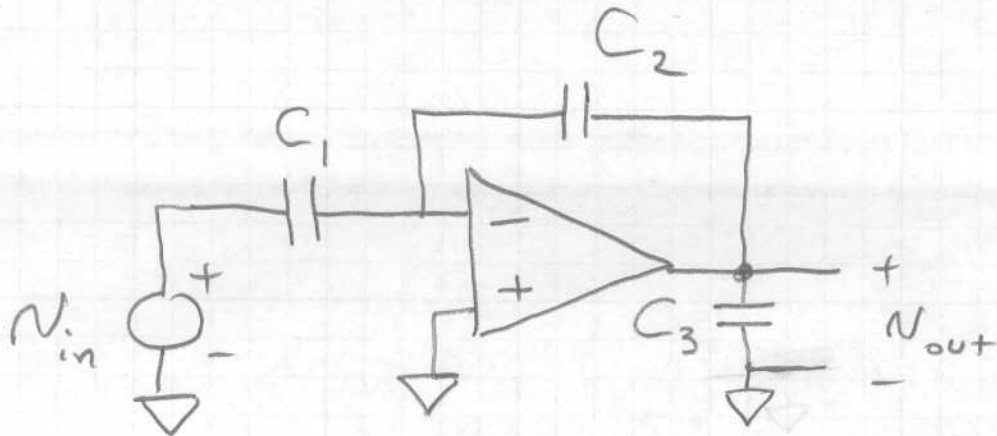d) How does  $\omega_u'$  change (increase, decrease, or no change) if  $C_L'$  increases?

If fb factor increases (assume  $C_L'$  does not change)? If  $R_o$  increases?



(a)

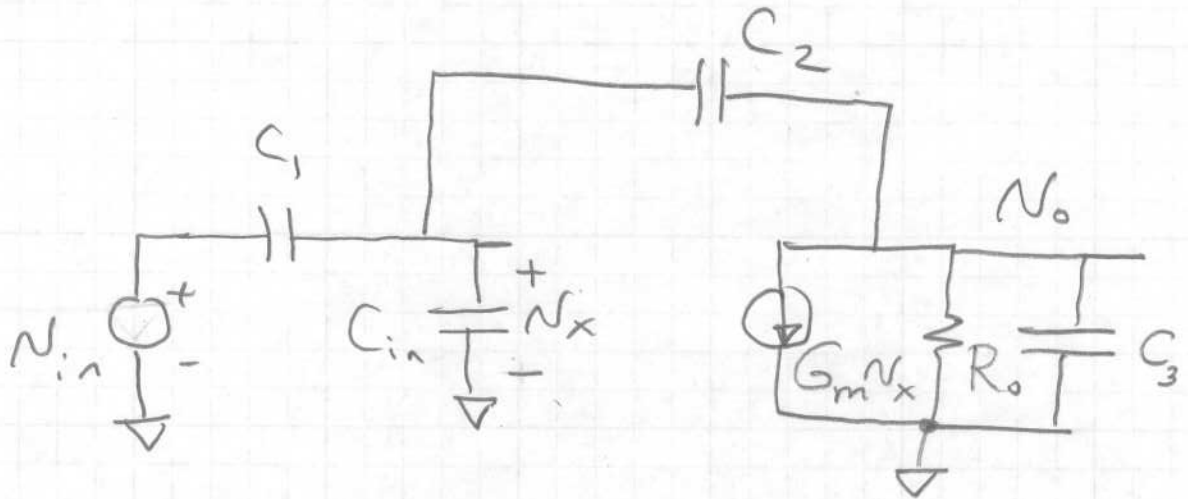

(b)

Fig 7 : a) Circuit b) SS model