

EEC 212

Problem Set 5

Professor Hurst

1

For the sample-and-hold circuit in Figure 1 estimate the $\frac{W}{L}$ value needed to give $R_{ON} \cdot C_H \leq 0.5 \mu\text{sec}$ for $V_{CK} = 5\text{V}$ and $V_{in} \leq 3\text{V}$. Assume $k' = 60 \frac{\mu\text{A}}{\text{V}^2}$ and $V_{T(MAX)} = 0.7\text{V}$ (including body effect).

 


Figure 1: Sample-and-Hold Circuit for Problem 1

2

A fully differential op-amp with CMFB is shown in Figure 2. All bodies of PMOS transistors are connected to V_{DD} , and all bodies of NMOS transistors are connected to V_{SS} . Let $X_d = 0$, and use the transistor sizes listed on table below as well as the transistor data in the SPICE models (see next page).

<i>Transistor</i>	W (μm)	L (μm)
M ₁₋₂ , M _{1C-2C}	64	0.8
M ₃₋₄ , M ₂₆₋₂₇ , M ₁₁	96	1.4
M ₂₁₋₂₄	6	0.8
M ₁₄ , M ₂₅ , M ₅₂	16	0.8
M ₁₃	1.4	0.8

- (a) Choose W values for M₁₂ and M₅₁ so that $|I_{D13}| = 20\mu\text{A}$. Use $L = 0.8\mu\text{m}$ for M₅₁ and $L = 1.4\mu\text{m}$ for M₁₂.
- (b) Use SPICE to find the low-frequency op-amp gain v_{od}/v_{id} , v_{oc}/v_{ic} , v_{od}/v_{ic} , and v_{oc}/v_{id} with the CMFB active. **NOTE:** To get HSPICE to compute the differential output voltage correctly using 'v(out1,out2)', you must include '.options acout=0' in your HSPICE input file. For the op-amp inputs, use $V_{IN(CM)} = -0.65\text{V}$.
- (c) Calculate the output slew rate dV_{od}/dt if a 4 pF capacitor is connected from each op-amp output to ground.
- (d) What is the differential output voltage swing of this op-amp? Assume that $V_{IN(CM)} = -0.65\text{V}$. (Ignore the body effect.)

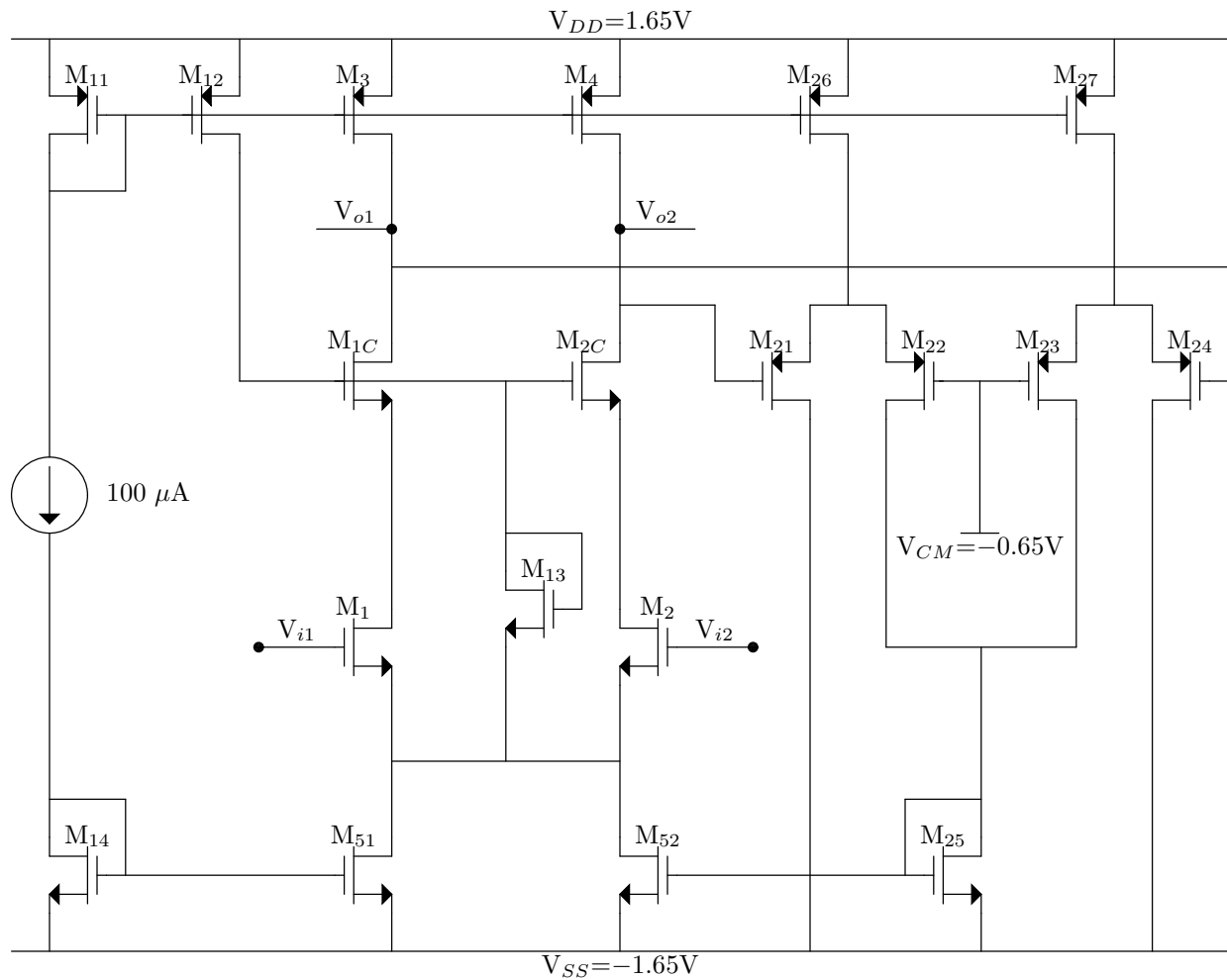


Figure 2: Op-amp for Problem 2

(e)** Repeat (b) when the input transistors are mismatched with $W_1 = 63 \mu m$ and $W_2 = 65 \mu m$.

(f)** Repeat (b) when the load transistors are mismatched with $W_3 = 95 \mu m$ and $W_4 = 97 \mu m$.

**Note: $V_{OS} \neq 0$ with mismatched transistors.

(g) It is possible to bias the op-amp without M_{51} . What change in device W/L should be made to M_{52} to keep the op-amp unchanged when M_{51} is deleted?

(h) Can you see any advantage to making the change described in (g)?

 


Figure 3: Circuit for Problem 3

3

During one clock phase in a SC filter, the op-amp in problem 2 is in the configuration shown in Figure 3.

(a) Apply a 1-V step as a differential input, using SPICE. What is the slew plus settle time to within 0.5% of the final value?

(b) What is the slew rate? How does this compare with the calculation of $\frac{\pm I_{B,IAS}}{C_L}$?

Note: You'll have to add DC feedback to this circuit; this feedback should not affect the circuit above about 10kHz. One way to do this is to put a very large resistor across each 1.5 pF cap: [e.g., rfb x y 1.0t].

SPICE MODELS: 0.4 μ m CMOS

```
.MODEL CMOSN NMOS LEVEL=3
+ TOX=0.8000E-08 XJ=0.150000U TPG=1 PHI=0.600000 DELTA=2.1370E-01
+ LD=9.0003E-08 VTO=0.60 GAMMA=0.5947 UO=450 THETA=1.9240E-01
+ RSH=1.7260E+01 KP=1.96E-04 NSUB=1.2706E+17 NFS=6.0410E+11
+ VMAX=1.8610E+05 ETA=2.1370E-02 KAPPA=8.4220E-02 CGDO=3.5E-10
+ CGSO=3.5E-10 CGBO=3.0251E-10 CJ=5.2E-04 MJ=0.59 CJSW=1.2E-10
+ MJSW=0.31 PB=0.98 ACM=3 HDIF=0.4u
```

```
.MODEL CMOSP PMOS LEVEL=3
+ TOX=0.8000E-08 XJ=0.150000U TPG=-1 PHI=0.600000 DELTA=2.0729E-01
+ LD=9.0000E-08 VTO=-0.80 GAMMA=0.5200 UO=137.3 THETA=1.6710E-01
+ RSH=3.6310E+00 KP=6.6E-05 NSUB=9.7132E+16 NFS=5.9890E+11
+ VMAX=3.0560E+05 ETA=1.8760E-02 KAPPA=5.9230E+00 CGDO=3.5E-10
+ CGSO=3.5E-10 CGBO=3.1661E-10 CJ=9.1191E-04 MJ=0.49 CJSW=1.2E-10
+ MJSW=0.201 PB=0.96 ACM=3 HDIF=0.4u
```

You can copy the SPICE MODELS file from: `/home/hurst/212/MOS_models_0.4um`