

EEC 212

Problem Set 6

Professor Hurst

Read: Chapter on Switched-Capacitor Circuits

1

A first-order switched capacitor high-pass filter is shown in Figure 1.

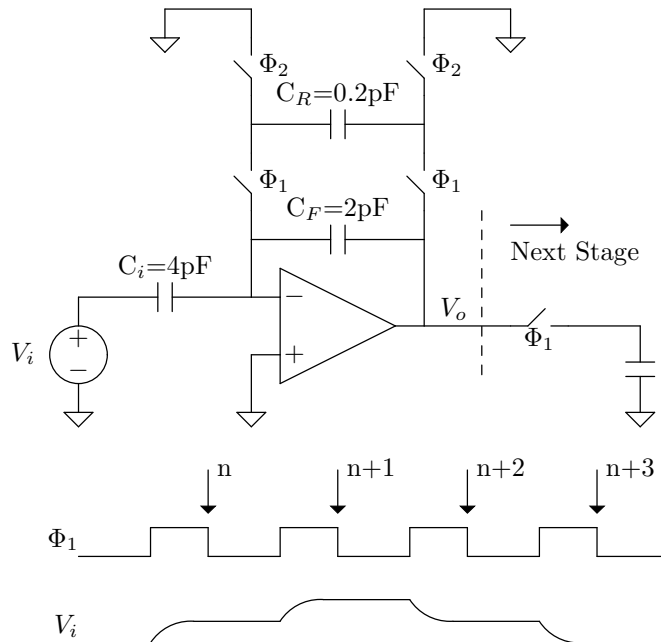


Figure 1: High-pass filter for Problem 1

- (a) Find $H(z) = \frac{V_o}{V_i}(z)$. Assume an ideal op-amp and V_o is to be sampled on Φ_1 .
- (b) What is the new pole location if the op-amp has a finite open-loop voltage gain of 200?

2

An R-C filter shown in Figure 2 is to be transformed into the S-C filter shown in Figure 3. Assume an ideal op-amp is used (e.g., $a \rightarrow \infty$).

- (a) If $f_S = 200\text{kHz}$, compute values for C_i and C_R using the approximation $R_{eqx} \approx 1/(f_S C_X)$.
- (b) Find $H(z) = \frac{V_o}{V_i}(z)$. What is the dc gain? What is the minimum gain? At what frequency is the minimum gain?
- (c) Verify the design using SWITCAP. Look at $H(z)$ using the command

SAMPLE OUTPUT IMPULSE

in SWITCAP. (See page 27 of the SWITCAP manual.)

(d) Plot $|\hat{H}(z = e^{j\omega T_s})|$ for Figure 3 and $|H(s = j\omega)|$ for Figure 2 on the same graph for $f = 0$ to $f = f_s$. Over what frequency range do the two plots differ by less than 20%?

 


Figure 2: R-C Filter for Problem 2

 


Figure 3: Transformed S-C Filter for Problem 2

3

Return ratio can be simulated using SPICE by breaking the loop at an arbitrary point and calculating 2 terms, RR'_V and RR'_I , which can be combined to find RR . (See attached, first 3 pages of a paper).

 


Figure 4: Circuit for Problem 3

(a) For the circuit in Figure 4, use SPICE to find the RR directly by breaking the loop at node 1. Print or plot the magnitude and phase of RR . Is this feedback circuits stable? What is the phase margin?

(b) Find the RR indirectly by breaking the loop at node 2 and finding $RR'_V = -v_r/v_d$ in Figure 4a of the attached paper and $RR'_I = -i_r/i_d$ in Figure 4b of the attached paper (use SPICE). Then RR can be found using Equation 3 in the paper. (Note: The return ratios are complex numbers.) Compare this answer with the answer you got in 3a. They should agree. [The return ratio can be found indirectly from SPICE simulations and some post processing. Potentially useful information on running simulations to find return ratio of a single-ended feedback circuit is on the 212 web page. It uses HSPICE and Linux post-processing scripts (that once worked but may not work now due to changes to HSPICE).]

There are three Appendices below:

Appendix A - Running SWITCAP

Appendix B - Sample SWITCAP input file

Appendix C - First 3 pages of this paper (the complete paper is available from the course web page):

P.J. Hurst and S.H. Lewis, **Determination of stability using return ratios in balanced fully differential feedback circuits**. *IEEE Transactions on Circuits and Systems II: Analog and Digital Signal Processing*, vol. 42, no. 12, pp. 805-817, Dec. 1995.

Appendix A: Running SWITCAP at UCD

Note: SWITCAP is not the most user-friendly program. Its error messages can be confusing, and sometimes a major error in the input file will produce no output. However, SWITCAP is simple, easy to learn and effective. So we'll use it.

To run SWITCAP: see "How to run SWITCAP1 on a Linux computer" on the ECE 212 web page. The SWITCAP manual can be accessed from the ECE 212 web page (see "SWITCAP Manual").

Appendix B: Sample SWITCAP Circuit

The sample SWITCAP circuit is shown on Figure 5 and the corresponding netlist, which is the SWITCAP input file, is below. Note that #CLK means 'non-overlapping complement of CLK'.

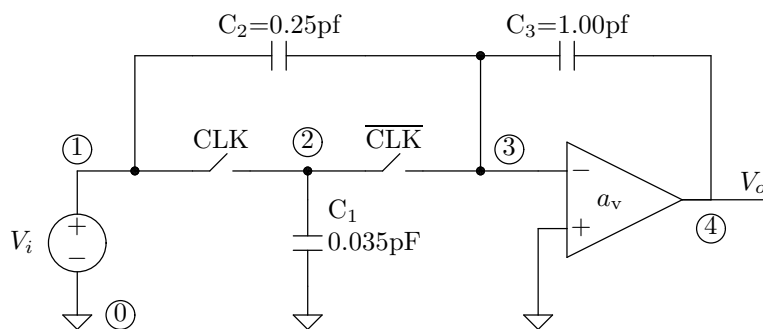


Figure 5: Sample SWITCAP problem ($a_v = 5500$)

Input netlist

TITLE: Sample SWITCAP Circuit;

TIMING;
 PERIOD 8E-6;
 CLOCK clk 1 (0 3/8);
 END;

CIRCUIT;
 S1 (1 2) clk;
 S2 (2 3) #clk;
 C1 (2 0) 0.035;
 C2 (1 3) 0.250;
 C3 (3 4) 1.000;
 E1 (4 0 0 3) 5500;
 V1 (1 0);
 END;

ANALYZE SSS;
 INFREQ 0.01 100000 LOG 15;
 SET V1 AC 1.0 0.0;
 PRINT VR(4) VI(4);
 PLOT VDB(4) VP(4);
 END;

END;