

# EEC 116 Fall 2011 Prelab #5

Rajeevan Amirtharajah  
Dept. of Electrical and Computer Engineering  
University of California, Davis

Issued: October 26, 2011  
Due: November 2, 2011, 4 PM in 2131 Kemper.

**Reading:** Rabaey Chapters 7.1-7.3 [1].

**Reference:** Kang and Leblebici Chapters 7 and 8 [2].

For **all** problems in this prelab assignment, assume we are using enhancement-type NMOS and PMOS transistors which have the characteristics shown in Table 1, unless otherwise specified. Also, assume **minimum** length devices unless otherwise specified.

Parameter	NMOS	PMOS
$V_{T0}$	0.5 V	-0.55 V
$\mu C_{ox}$	350 $\mu\text{A}/\text{V}^2$	125 $\mu\text{A}/\text{V}^2$
$\gamma$	0	0
$L_{min}$	0.180 $\mu\text{m}$	0.180 $\mu\text{m}$
$W_{min}$	0.450 $\mu\text{m}$	0.450 $\mu\text{m}$
$\lambda$	0.0 $\text{V}^{-1}$	0.0 $\text{V}^{-1}$
$C_g$	13.5 fF/ $\mu\text{m}^2$	13.5 fF/ $\mu\text{m}^2$
$C_d, C_s$	5.28 fF/ $\mu\text{m}$	5.28 fF/ $\mu\text{m}$
$V_{DD}$	1.8 V	

Table 1: Assumed Transistor Parameters.

## 1 Edge-Triggered Flip-Flop Design

For this problem, use the device parameters in Table 1.

**Problem 1.1** Redraw the schematic of Figure 1 at the transistor level and label the  $D$ ,  $clk$ ,  $\overline{clk}$ , and  $Q$  signals on the schematic such that the circuit operates as a **static positive edge-triggered flip-flop**.

**Problem 1.2** Choose sizes for the transistors in your schematic from Problem 1.1 based on equalizing the CMOS inverter rise and fall times. Make sure your sizes are integer multiples of  $\lambda = 90\text{nm}$ .

 


Figure 1: Negative Edge-Triggered Flip-Flop.

**Problem 1.3** Calculate the setup time  $t_{setup}$  and clock-to-Q propagation delay  $t_{clkQ}$  for the flip-flop you designed in Problem 1.2. Assume ideal step inputs for  $D$  and the true and complement versions of the clock. Assume a gate capacitance per unit area to ground  $C_g$  and a drain/source capacitance per unit width to ground  $C_d/C_s$  as shown in Table 1 and neglect all other capacitances. Use the average current method at the beginning and end points of the appropriate transitions.

## References

- [1] J. Rabaey, A. Chandrakasan, and B. Nikolic, *Digital Integrated Circuits: A Design Perspective*, 2nd ed. Upper Saddle River, New Jersey: Prentice-Hall, Inc., 2003.
- [2] S.-M. Kang and Y. Leblebici, *CMOS Digital Integrated Circuits: Analysis and Design*, 3rd ed. San Francisco: McGraw-Hill, Inc., 2003.