


**EEC 116 Lecture #2:
MOSFET Basics
Layout Introduction
CMOS Inverters**

**Rajeevan Amirtharajah Bevan Baas
University of California, Davis
Jeff Parkhurst
Intel Corporation**

Outline


- **Finish Lecture 1 Slides**
- **Switch Example**
- **MOSFET Structure**
- **MOSFET Regimes of Operation**
- **Scaling**
- **Parasitic Capacitances**

3D Perspective

 

nwell and pwell

- The “bodies” of the transistors

 

ndiffusion and pdiffusion


- **Source and Drain for each transistor**



Source: Omar Sattari

Polysilicon

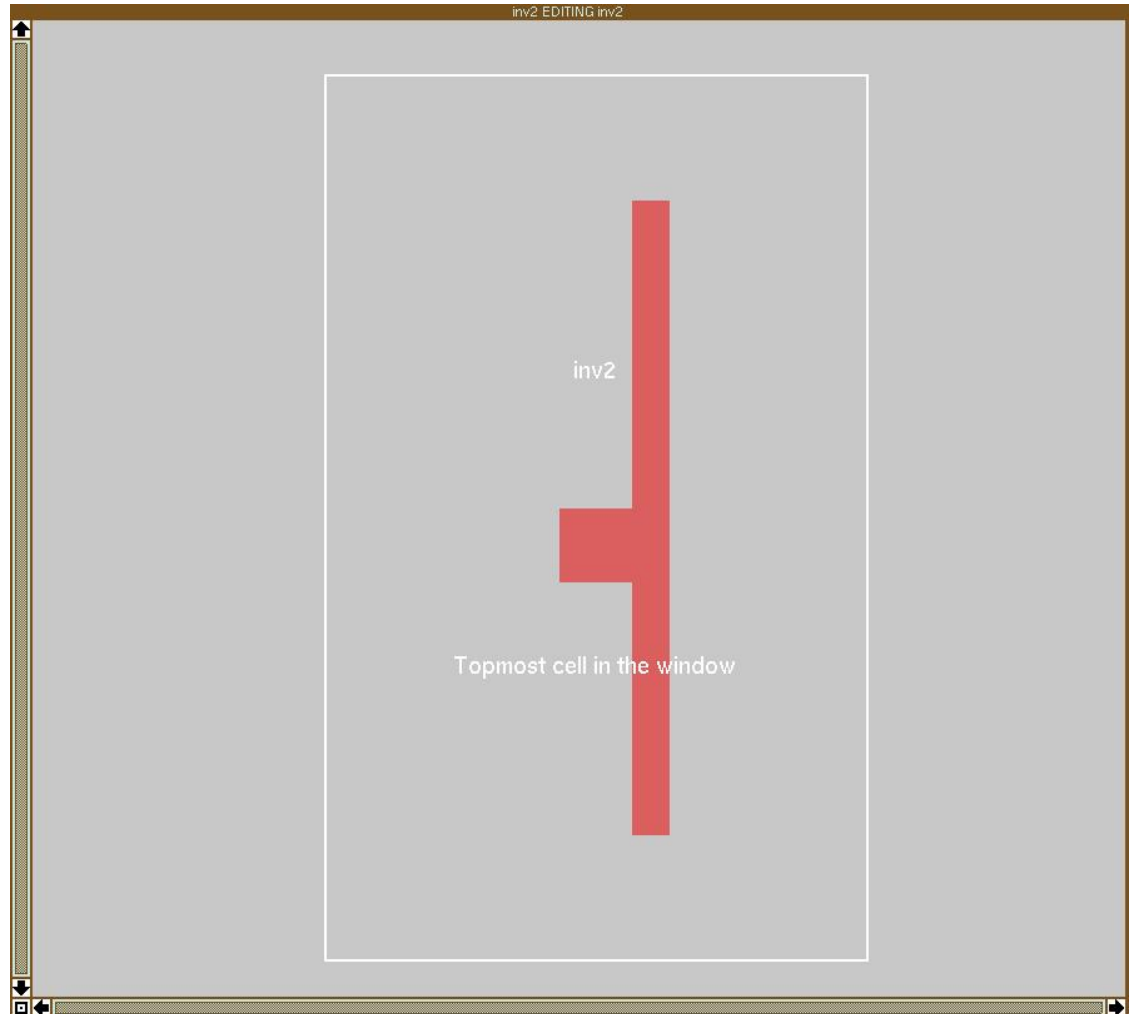
- Gate of transistors and for short-distance wiring



Source: Omar Sattari

Metal1

- First level of interconnect

 

Metal2


- **Second layer of interconnect**



Source: Omar Sattari


Building an Inverter: Starting with Well and Diffusion

 - **Place N-type and P-type diffusions**
 - Convention is to place PMOS on top and NMOS on bottom



Transistors

 
- poly crossing diffusion produces a transistor!
- Common gate here
- PMOS shown on top
- NMOS shown on bottom



Source: Omar Sattari

Metal1

 
- metal1 laid down but not yet connected
- Use metal for *Vdd* and *Gnd*
- Labels added
 - Extremely useful for testing
 - Documents design
 - Use “point” labels, not large area ones
 - Never use *global* labels that end in an “!”



Source: Omar Sattari

Metal2

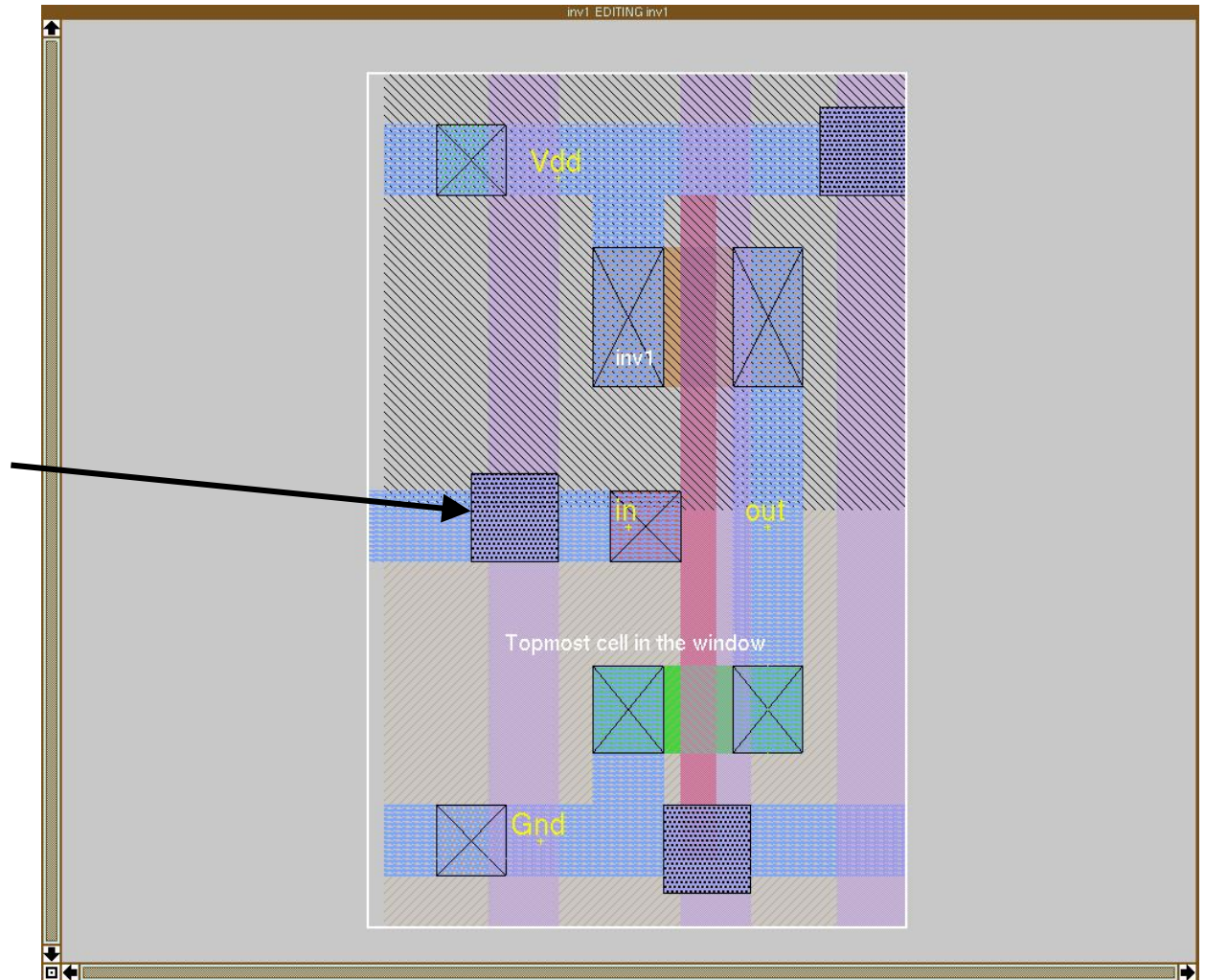- Use metal2 for longer distance routing
- Routes over the “top” of other circuits shown
- metal2 contacts connect metal1 and metal2 only



Source: Omar Sattari


Design Rules

- **Interface between designer and process (CMOS fabrication) engineer**
- **Guidelines for constructing fabrication masks**
- **Units commonly used**
 - Scalable design rules: lambda (λ) parameter (used in magic), or
 - Absolute dimensions (micron rules)
- **Common rule examples:**
 - Minimum width
 - Minimum separation same material
 - Minimum separation different material
- **Look for flashing markers in Cadence that show errors**


Design Rules

- **Mead and Conway, 1980**
 - “Lambda-based” scalable design rules
 - Allows full-custom designs to be easily reused from technology generation to technology generation
 - Lambda is roughly one half the minimum feature size
 - “1.0 μm technology” -> 1.0 μm min. length, lambda = 0.5 μm
 - “0.5 μm technology” -> 0.5 μm min. length, lambda = 0.25 μm
 - For our class, we are using a 0.18 μm technology so lambda is 0.09 μm
- **See lab handouts for URL to our scalable design rules on the MOSIS website**
- **We are using “SCMOS_DEEP” rules**



Example Intra-Layer Design Rules

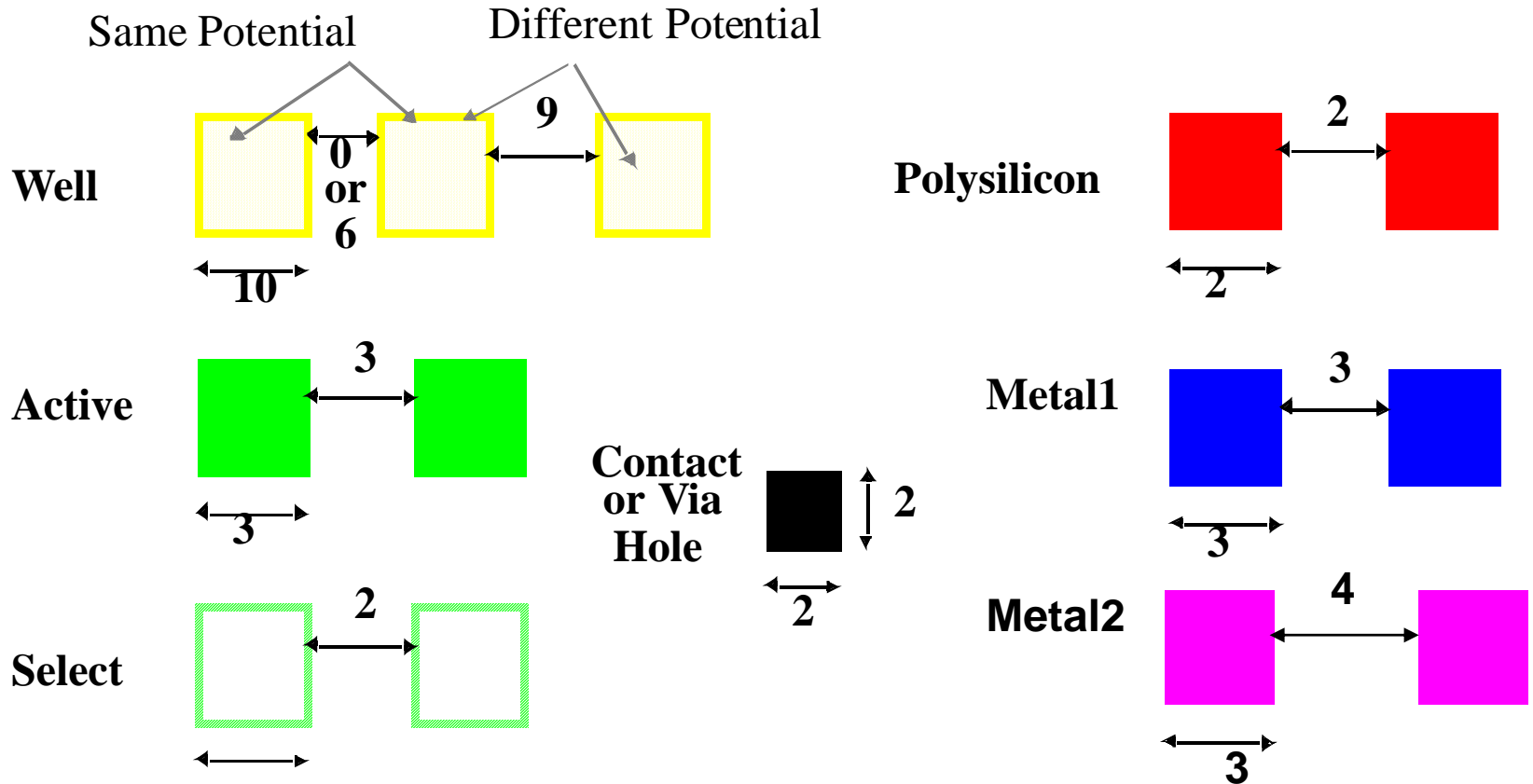


Example Design Rules: Transistor Layout

 

Example Design Rules: Vias and Contacts

 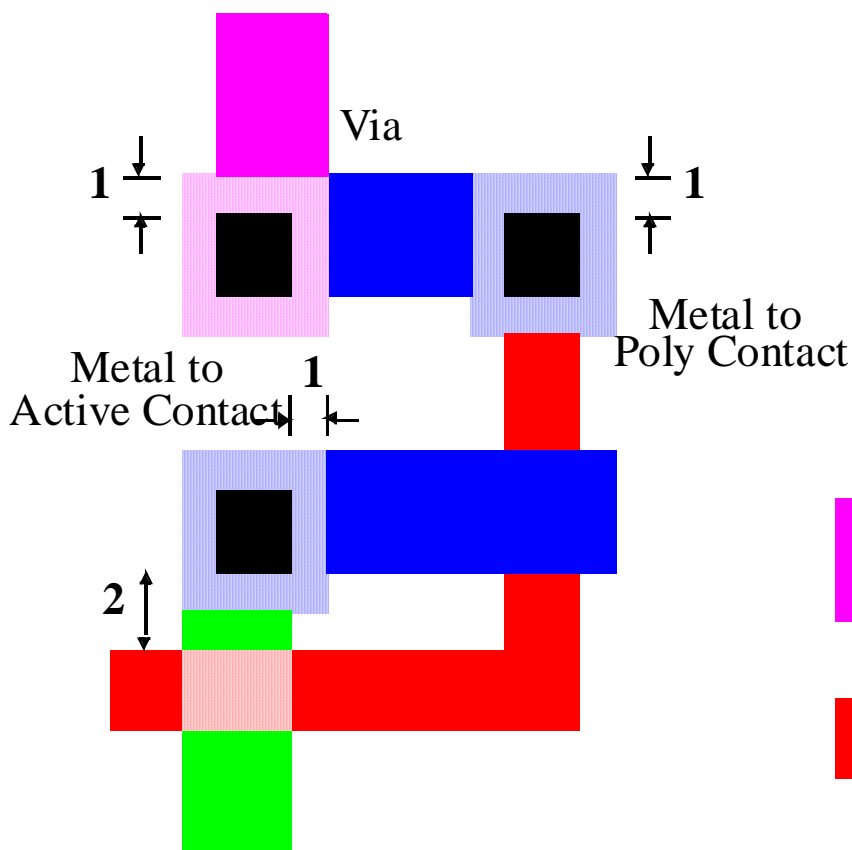

Design Rule Checker

 

In magic, white dots appear at the point of a DRC rule violation. Something similar occurs in Cadence.


poly_not_fet to all_diff minimum spacing = 0.14 um.

Place a box around white dots and press “y” to see what is causing an error

Accounting for VDSM Effects


- **VDSM = Very Deep Sub Micron**
 - Effects significant below 0.25 μm (0.18 μm , 130 nm, 90 nm, 65 nm, 45 nm)
- **Compensation made at the mask level**
 - OPC – Optical Proximity Correction
 - Occurs when different mask layers don't align properly
 - Test structures are used to characterize the process
 - Ability to adapt depends on the consistency of the error from process run to process run

Accounting for VDSM Effects: OPC

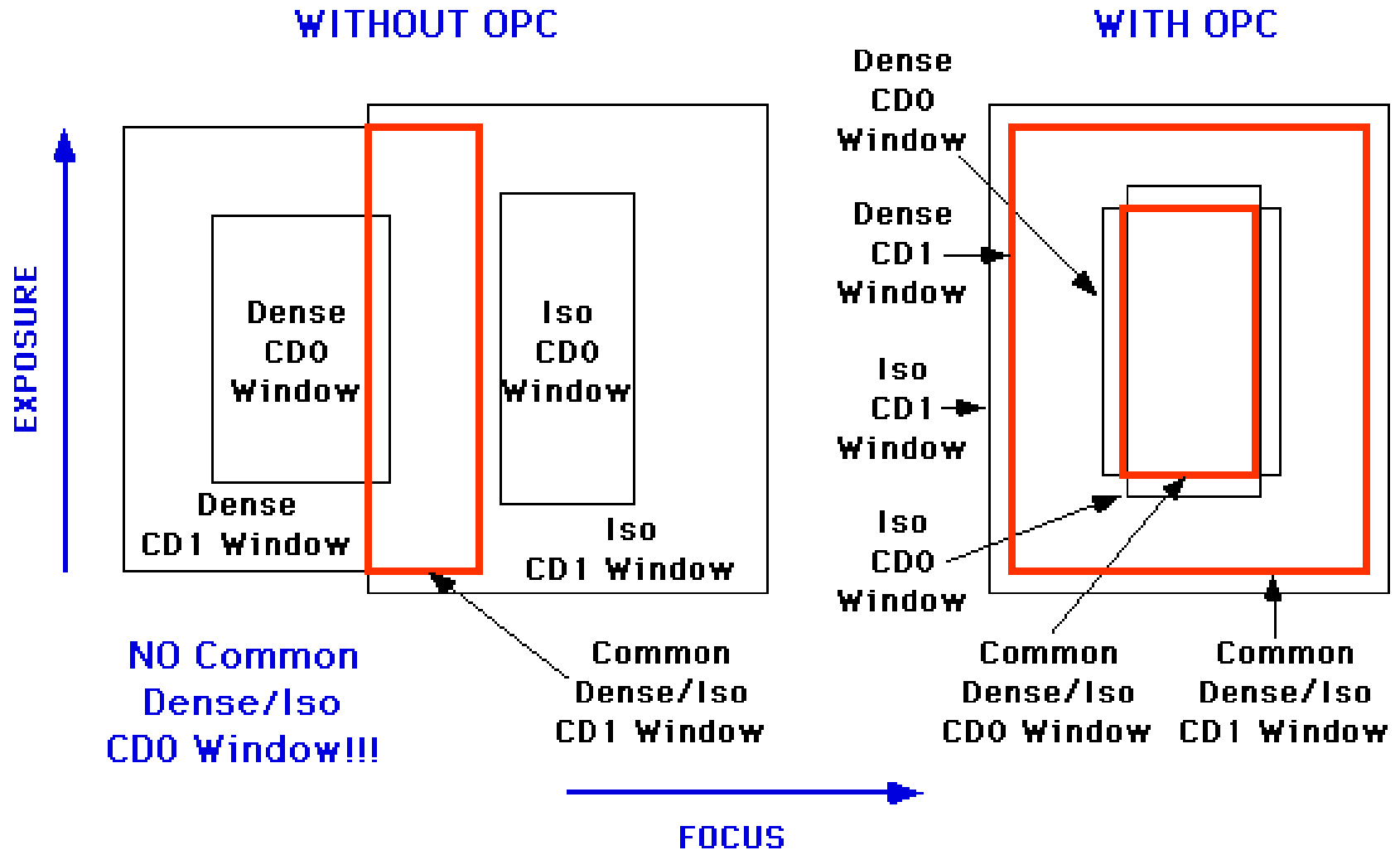

Accounting for VDSM Effects: Example

 
- Example of 2D OPC effects: rounded edges, narrowed lines



Uncorrected


Corrected

Compensating for VDSM Effects: Masks

 

Compensating for VDSM Effects: CAD

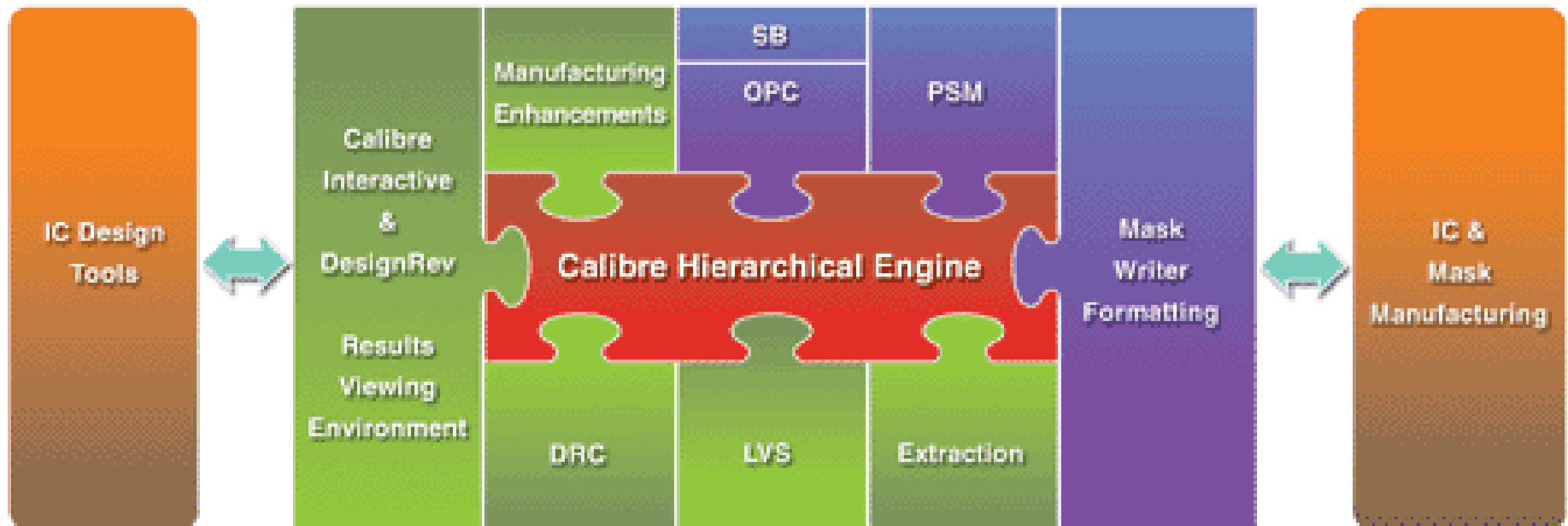- Flow to compensate is transparent to layout designer
- Layout design proceeds as normal



Mentor Graphics Flow


<http://www.mentor.com/calibre/datasheets/opc/html/>

References


- **“Design of VLSI Systems”**. A web based course located at: <http://turquoise.wpi.edu/webcourse/>
- **“Simplified Rule Generation for Automated Rules-Based Optical Enhancement”**, Otto et. al. On web at:
<http://www.jetlink.net/~ootto/bacus95/BACUS95Index.html>
- **Mark Anders and Jim Schantz of Intel Corporation**
- **Jan Rabaey, Lecture notes from his book “Digital Integrated Circuits, A Design Perspective”**

MOS Transistor Types

 - Rabaey Ch. 3 (Kang & Leblebici Ch. 3)
- Two transistor types (analogous to bipolar NPN, PNP)
 - NMOS: p-type substrate, n^+ source/drain, electrons are charge carriers
 - PMOS: n-type substrate, p^+ source/drain, holes are charge carriers




NMOS

 


PMOS

MOS Transistor Symbols

NMOS

 


PMOS

 

Note on MOS Transistor Symbols

 - **All symbols appear in literature**
 - Symbols with arrows are conventional in analog papers
 - PMOS with a bubble on the gate is conventional in digital circuits papers
- **Sometimes bulk terminal is ignored – implicitly connected to supply:**




- **Unlike physical bipolar devices, source and drain are usually symmetric**


MOS Transistor Structure

- Important transistor physical characteristics

 - Channel length $L = L_D - 2x_d$ (K&L $L = L_{\text{gate}} - 2L_D$)
- Channel width W
- Thickness of oxide t_{ox}




NMOS Transistor I-V Characteristics I

 

- **I-V curve vaguely resembles bipolar transistor curves**
 - Quantitatively very different
 - Turn-on voltage called Threshold Voltage V_T


NMOS Transistor I-V Characteristics II

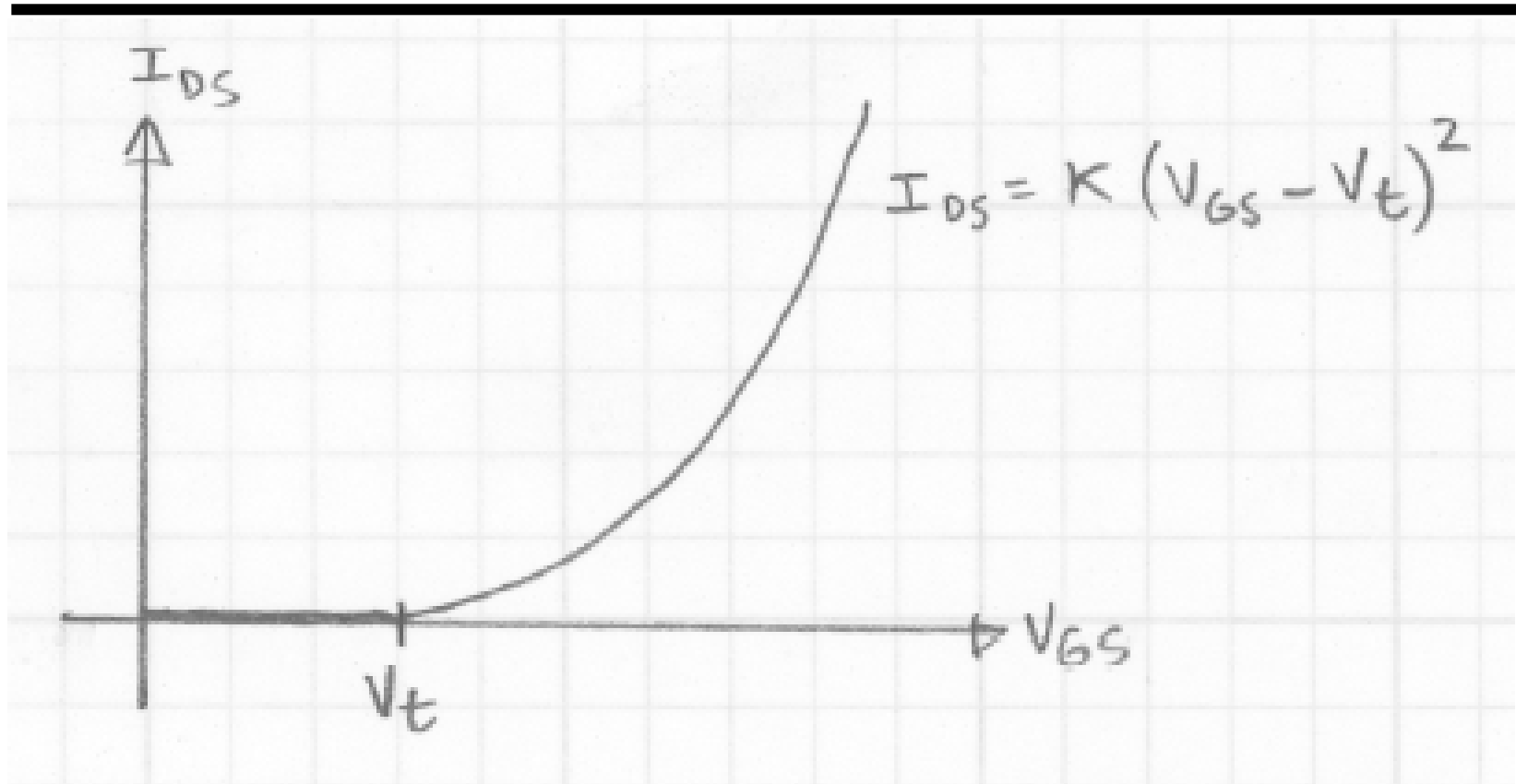

- **Drain current varies quadratically with gate-source voltage V_{GS} (in Saturation)**


MOS Transistor Operation: Cutoff

 - **Simple case: $V_D = V_S = V_B = 0$**
 - Operates as MOS capacitor ($C_g = \text{gate to channel}$)
 - Transistor in cutoff region
- **When $V_{GS} < V_{T0}$, depletion region forms**
 - No carriers in channel to connect S and D (Cutoff)



MOS Transistor Operation: Inversion

 - When $V_{GS} > V_{T0}$, inversion layer forms
- Source and drain connected by conducting n-type layer (for NMOS)
 - Conducting p-type layer in PMOS



Threshold Voltage Components

- Four physical components of the threshold voltage
 1. Work function difference between gate and channel (depends on metal or polysilicon gate): Φ_{GC}
 2. Gate voltage to invert surface potential: $-2\Phi_F$
 3. Gate voltage to offset depletion region charge: Q_B/C_{ox}
 4. Gate voltage to offset fixed charges in the gate oxide and oxide-channel interface: Q_{ox}/C_{ox}

$$C_{ox} = \frac{\epsilon_{ox}}{t_{ox}} \quad : \text{ gate oxide capacitance per unit area}$$

Threshold Voltage Summary

- If $V_{SB} = 0$ (no substrate bias):

$$V_{T0} = \Phi_{GC} - 2\phi_F - \frac{Q_{B0}}{C_{ox}} - \frac{Q_{ox}}{C_{ox}} \quad (\text{K\&L 3.20})$$

- If $V_{SB} \neq 0$ (non-zero substrate bias)

$$V_T = V_{T0} + \gamma \left(\sqrt{|-2\phi_F + V_{SB}|} - \sqrt{|2\phi_F|} \right) \quad (3.19)$$

- **Body effect (substrate-bias) coefficient:**

$$\gamma = \frac{\sqrt{2qN_A \epsilon_{Si}}}{C_{ox}} \quad (\text{K\&L 3.24})$$



- **Threshold voltage increases as V_{SB} increases!**

Threshold Voltage (NMOS vs. PMOS)

	NMOS	PMOS
Substrate Fermi potential	$\phi_F < 0$	$\phi_F > 0$
Depletion charge density	$Q_B < 0$	$Q_B > 0$
Substrate bias coefficient	$\gamma > 0$	$\gamma < 0$
Substrate bias voltage	$V_{SB} > 0$	$V_{SB} < 0$

Body Effect

  - **Body effect: Source-bulk voltage V_{SB} affects threshold voltage of transistor**
 - Body normally connected to ground for NMOS, Vdd (Vcc) for PMOS
 - Raising source voltage increases V_T of transistor
 - Implications on circuit design: series stacks of devices



MOS Transistor Regions of Operation

- Three main regions of operation
- **Cutoff**: $V_{GS} < V_T$
No inversion layer formed, drain and source are isolated by depleted channel. $I_{DS} \approx 0$
- **Linear (Triode, Ohmic)**: $V_{GS} > V_T$, $V_{DS} < V_{GS} - V_T$
Inversion layer connects drain and source.
Current is almost linear with V_{DS} (like a resistor)
- **Saturation**: $V_{GS} > V_T$, $V_{DS} \geq V_{GS} - V_T$
Channel is “pinched-off”. Current saturates (becomes independent of V_{DS} , to first order).

MOSFET Drain Current Overview

Saturation:
$$I_D = \frac{\mu C_{ox}}{2} \frac{W}{L} (V_{GS} - V_T)^2 (1 + \lambda V_{DS})$$


Linear (Triode, Ohmic):

$$I_D = \mu C_{ox} \frac{W}{L} \left((V_{GS} - V_T) V_{DS} - \frac{V_{DS}^2}{2} \right)$$

Cutoff:
$$I_D \approx 0$$

“Classical” MOSFET model, will discuss deep submicron modifications as necessary (Rabaey, Eqs. 3.25, 3.29)


Cutoff Region

 


- **For NMOS:** $V_{GS} < V_{TN}$
- **For PMOS:** $V_{GS} > V_{TP}$
- **Depletion region – no inversion**
- **Current between drain and source is 0**
 - Actually there is always some leakage (subthreshold) current

Linear Region

 - When $V_{GS} > V_T$, an inversion layer forms between drain and source
- Current I_{DS} flows from drain to source (electrons travel from source to drain)
- Depth of channel depends on V between gate and channel
 - Drain end narrower due to larger drain voltage
 - Drain end depth reduces as V_{DS} is increased



Linear Region I/V Equation Derivation

 

- **Gradual Channel Approximation:**
 - Assume dominant electric field in y -direction
 - Current is constant along channel
- **Integrate differential voltage drop $dV_c = I_D dR$ along y**

Linear Region I/V Equation

- Valid for continuous channel from Source to Drain

$$I_D = \mu_n C_{ox} \frac{W}{L} \left[(V_{GS} - V_T) V_{DS} - \frac{1}{2} V_{DS}^2 \right]$$


Device transconductance: $k_n = \mu_n C_{ox} \frac{W}{L}$

Process transconductance: $k'_n = \mu_n C_{ox}$

$$I_D = k'_n \frac{W}{L} \left[(V_{GS} - V_T) V_{DS} - \frac{1}{2} V_{DS}^2 \right]$$

Saturation Region

 - When $V_{DS} = V_{GS} - V_T$:
 - No longer voltage drop of V_T from gate to substrate at drain
 - Channel is “pinched off”
- If V_{DS} is further increased, no increase in current I_{DS}
 - As V_{DS} increased, pinch-off point moves closer to source
 - Channel between that point and drain is depleted
 - High electric field in depleted region accelerates electrons towards drain




Saturation I/V Equation

- **As drain voltage increases, channel remains pinched off**
 - Channel voltage remains constant
 - Current saturates (no increase with increasing V_{DS})
- **To get saturation current, use linear equation with $V_{DS} = V_{GS} - V_T$**

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TN})^2$$

MOS I/V Characteristics

 - I/V curve for ideal MOS device
- $V_{GS3} > V_{GS2} > V_{GS1}$



Channel Length Modulation

- In saturation, pinch-off point moves

- As V_{DS} is increased, pinch-off point moves closer to source
- Effective channel length becomes shorter
- Current increases due to shorter channel


$$L' = L - \Delta L$$

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TN})^2 (1 + \lambda V_{DS})$$

λ = channel length modulation coefficient

MOS I/V Curve Summary

I/V curve for non-ideal NMOS device:

 

MOS I/V Equations Summary

Cutoff $V_{GS} < V_{TN}$ $\Rightarrow I_D = 0$
 $V_{GS} > V_{TP}$

Linear

$$\begin{aligned} V_{GS} \geq V_{TN}, \quad V_{DS} < V_{GS} - V_{TN} \\ V_{GS} \leq V_{TP}, \quad V_{DS} > V_{GS} - V_{TP} \end{aligned} \Rightarrow I_D = \mu C_{ox} \frac{W}{L} \left[(V_{GS} - V_T) V_{DS} - \frac{1}{2} V_{DS}^2 \right]$$

Saturation

$$\begin{aligned} V_{GS} \geq V_{TN}, \quad V_{DS} \geq V_{GS} - V_{TN} \\ V_{GS} \leq V_{TP}, \quad V_{DS} \leq V_{GS} - V_{TP} \end{aligned} \Rightarrow I_D = \frac{1}{2} \mu C_{ox} \frac{W}{L} (V_{GS} - V_T)^2 (1 + \lambda V_{DS})$$

Note: if $V_{SB} \neq 0$, need to recalculate V_T from V_{T0}


A Fourth Region: Subthreshold

Subthreshold:
$$I_D = I_S e^{\frac{V_{GS}}{n kT/q}} \left(1 - e^{-\frac{V_{DS}}{kT/q}} \right)$$

- **Sometimes called “weak inversion” region**
- **When V_{GS} near V_T , drain current has an exponential dependence on gate to source voltage**
 - Similar to a bipolar device
- **Not typically used in digital circuits**
 - Sometimes used in very low power digital applications
 - Often used in low power analog circuits, e.g. quartz watches

Inverter Operation

 - **Inverter is simplest digital logic gate (1 input, 1 output)**




In	Out
0	1
1	0

- **Many different circuit styles possible**
 - Resistive-load
 - NMOS and Pseudo-NMOS
 - CMOS
- **Important static and dynamic characteristics**
 - Speed (delay through the gate)
 - Power consumption
 - Robustness (tolerance to noise)
 - Area and process cost

Inverter Model: Voltage Transfer Curve

 
Voltage transfer curve (VTC): plot of output voltage V_{out} vs. input voltage V_{in}



Ideal digital inverter:


- When $V_{in}=0$, $V_{out}=V_{dd}$
- When $V_{in}=V_{dd}$, $V_{out}=0$
- Infinitely sharp transition region at inverter switching threshold

Actual Inverter: V_{OH} and V_{OL}

 

- V_{OH} and V_{OL} represent the “high” and “low” output voltages of the inverter
- V_{OH} = output voltage when $V_{in} = '0'$ (V Output High)
- V_{OL} = output voltage when $V_{in} = '1'$ (V Output Low)
- Ideally,
 - $V_{OH} = V_{DD}$
 - $V_{OL} = 0\text{ V}$

VOL and VOH

 

- **In transfer function terms:**

- $V_{OL} = f(V_{OH})$

- $V_{OH} = f(V_{OL})$


- f = inverter transfer function

- **Difference ($V_{OH} - V_{OL}$) is the *voltage swing* of the gate**

- *Full-swing logic* swings from ground to V_{DD}

- Other families with smaller swings


Inverter Switching Threshold

 

Inverter switching threshold:


- Point where voltage transfer curve intersects line $V_{out} = V_{in}$
- Represents the point at which the inverter switches state
- Normally, $V_M \approx V_{DD}/2$
- Sometimes other thresholds desirable

Noise Margins

 

- V_{IL} and V_{IH} measure effect of input voltage on inverter output
- V_{IL} = largest input voltage recognized as logic '0'
- V_{IH} = smallest input voltage recognized as logic '1'
- Defined as point on VTC where slope = -1

Noise Margins and Robustness

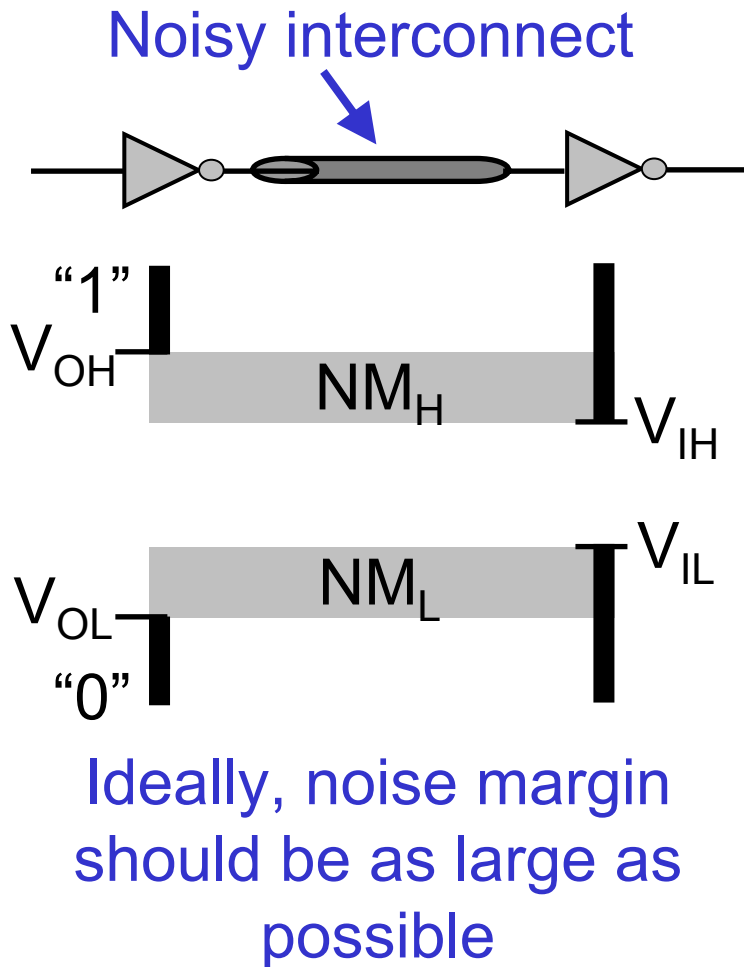

- Noise margin is a measure of the *robustness* of an inverter

$$- N_{ML} = V_{IL} - V_{OL}$$

$$- N_{MH} = V_{OH} - V_{IH}$$

- Models a chain of inverters.
Example:

- First inverter output is V_{OH}
- Second inverter recognizes input $> V_{IH}$ as logic ‘1’
- Difference $V_{OH} - V_{IH}$ is “safety zone” for noise

Noise Margin Motivation

- Why are V_{IL} , V_{IH} defined as unity-gain point on VTC curve?

- Assume there is noise on input voltage V_{in}


$$V_{out} = f(V_{in} + V_{noise})$$

- First-order Taylor series approximation:

$$V_{out} = f(V_{in}) + \frac{dV_{out}}{dV_{in}} V_{noise}$$


- If gain (dV_{out}/dV_{in}) > 1 , noise will be amplified.
- If gain < 1 , noise is filtered. Therefore V_{IL} , V_{IH} define regions where gain < 1

Inverter Time Response

 

- Propagation delay measured from 50% point of V_{in} to 50% point of V_{out}
- $t_{pHL} = t_1 - t_0$, $t_{pLH} = t_3 - t_2$, $t_p = \frac{1}{2}(t_{pHL} + t_{pLH})$



Rise and Fall Time

 

- **Fall time:** measured from 90% point to 10% point
 - $t_F = t_1 - t_0$
- **Rise time:** measured from 10% point to 90% point
 - $t_R = t_3 - t_2$
- **Alternately, can define 20%-80% rise/fall time**

Ring Oscillator

  
- **Ring oscillator circuit:** standard method of comparing delay from one process to another
- **Odd-number n of inverters connected in chain:** oscillates with period T (usually $n \gg 5$)



$$T = t_{plh1} + t_{phl1} + t_{plh2} + t_{phl2} + t_{plh3} + t_{phl3} + \dots$$

$$T = 2nt_p, \quad f = \frac{1}{T} = \frac{1}{2nt_p}, \quad t_p = \frac{1}{2nf}$$

Inverter as Amplifier

 

- For V_{in} between V_{IL} and V_{IH} , inverter gain > 1
- Acts as a linear amplifier (often very high gain)
- Logic levels '0' and '1' correspond to saturating amplifier output (output is pegged to high or low supply)
- Resistive load inverter same circuit as common source amplifier

Next Topic: Inverters

- **Inverter Characteristics**
 - Transfer functions, noise margins, resistive and nonlinear loads
- **CMOS Inverters**
- **MOSFET Scaling**
- **MOSFET Capacitances**