

EEC 116 Lecture #3: CMOS Inverters MOS Scaling


**Rajeevan Amirtharajah
University of California, Davis
Jeff Parkhurst
Intel Corporation**

Outline

- **Review: Inverter Transfer Characteristics**
- **Lecture 3: Noise Margins, Rise & Fall Times, Inverter Delay**
- **CMOS Inverters: Rabaey 1.3.2, 5 (Kang & Leblebici, 5.1-5.3 and 6.1-6.2)**

Review: Inverter Voltage Transfer Curve

 
Voltage transfer curve (VTC): plot of output voltage V_{out} vs. input voltage V_{in}



Ideal digital inverter:


- When $V_{in}=0$,
 $V_{out}=V_{dd}$
- When $V_{in}=V_{dd}$,
 $V_{out}=0$
- Sharp transition region

Review: Actual Inverter Output Levels

 

- V_{OH} and V_{OL} represent the “high” and “low” output voltages of the inverter
- V_{OH} = output voltage when $V_{in} = '0'$ (V Output High)
- V_{OL} = output voltage when $V_{in} = '1'$ (V Output Low)
- Ideally,
 - $V_{OH} = V_{dd}$
 - $V_{OL} = 0\text{ V}$

Review: VOL and VOH

 

- In transfer function terms:

- $V_{OL} = f(V_{OH})$

- $V_{OH} = f(V_{OL})$


- f = inverter transfer function

- **Difference ($V_{OH} - V_{OL}$) is the *voltage swing* of the gate**

- *Full-swing logic* swings from ground to V_{DD}

- Other families with smaller swings

Review: Inverter Switching Threshold

 

Inverter switching threshold:

- Point where voltage transfer curve intersects line $V_{out} = V_{in}$
- Represents the point at which the inverter switches state
- Normally, $V_M \approx V_{DD}/2$
- Sometimes other thresholds desirable

VTC Mathematical Definitions

- **V_{OH} is the output high level of an inverter**

$$V_{OH} = VTC(V_{OL})$$

- **V_{OL} is the output low level of an inverter**

$$V_{OL} = VTC(V_{OH})$$

- **V_M is the switching threshold**

$$V_M = V_{IN} = V_{OUT}$$

- **V_{IH} is the lowest input voltage for which the output will be \geq the input (worst case '1')**

$$dVTC(V_{IH})/dV_{IH} = -1$$

- **V_{IL} is the highest input voltage for which the output will be \leq the input (worst case '0')**

$$dVTC(V_{IL})/dV_{IL} = -1$$

Noise Margin and Delay Definitions

- **NM_L is the difference between the highest acceptable '0' and the lowest possible '0'**

$$NM_L = V_{IL} - V_{OL}$$


- **NM_H is the difference between the lowest acceptable '1' and the highest possible '1'**

$$NM_H = V_{OH} - V_{IH}$$


- **t_{PHL} is the propagation delay from the 50% point of the input to the output when the output goes from high to low**
- **t_{PLH} is the propagation delay from the 50% point of the input to the output when the output goes from low to high**
- **t_p is the average propagation delay**
- **t_R is the rise time (usually 10% to 90%)**
- **t_F is the fall time (usually 90% to 10%)**

CMOS Inverter

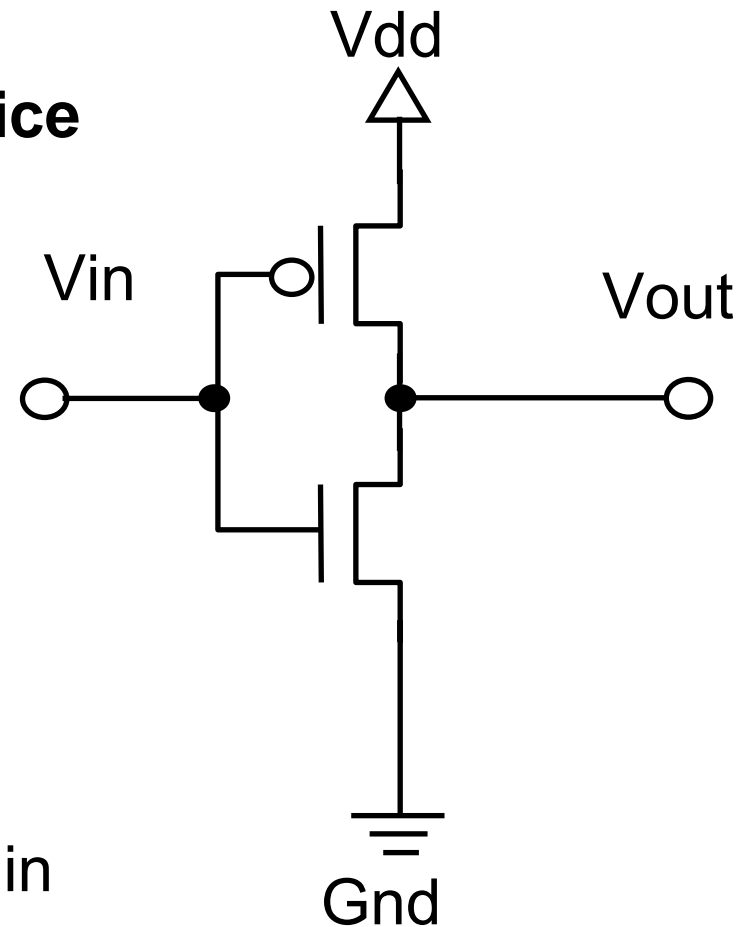- **Complementary NMOS and PMOS devices**
- **In steady-state, only one device is on (no static power consumption)**
- **$V_{in}=1$: NMOS on, PMOS off**
 - $V_{out} = V_{OL} = 0$
- **$V_{in}=0$: PMOS on, NMOS off**
 - $V_{out} = V_{OH} = V_{dd}$
- **Ideal V_{OL} and V_{OH} !**
- **Ratioless logic: output is independent of transistor sizes in steady-state**



CMOS Inverter: VTC

 

- Output goes completely to V_{dd} and Gnd
- Sharp transition region


CMOS Inverter Operation

- **NMOS transistor:**


- Cutoff if $V_{in} < V_{TN}$
- Linear if $V_{out} < V_{in} - V_{TN}$
- Saturated if $V_{out} > V_{in} - V_{TN}$

- **PMOS transistor**

 
- Cutoff if $(V_{in} - V_{DD}) > V_{TP} \rightarrow V_{in} > V_{DD} + V_{TP}$
- Linear if $(V_{out} - V_{DD}) > V_{in} - V_{DD} - V_{TP} \rightarrow V_{out} > V_{in} - V_{TP}$
- Sat. if $(V_{out} - V_{DD}) < V_{in} - V_{DD} - V_{TP} \rightarrow V_{out} < V_{in} - V_{TP}$



CMOS Inverter VTC: Device Operation

 

CMOS Inverter VTC: Device Sizing

 

- Increase W of PMOS
 k_p increases
VTC moves to right
- Increase W of NMOS
 k_n increases
VTC moves to left
- For $V_M = V_{DD}/2$
 $k_n = k_p$
 $2W_n \approx W_p$

Effects of V_M adjustment

- **Result from changing k_p/k_n ratio:**
 - Inverter threshold $V_M \neq V_{DD}/2$
 - Rise and fall delays unequal
 - Noise margins not equal
- **Reasons for changing inverter threshold**
 - Want a faster delay for one type of transition (rise/fall)
 - Remove noise from input signal: increase one noise margin at expense of the other
 - Interfacing other types of logic (with different swings)

CMOS Inverter: V_{IL} Calculation

- **KCL (NMOS saturation, PMOS linear):**

$$\frac{k_n}{2} (V_{GS,n} - V_{T0,n})^2 = \frac{k_p}{2} [2(V_{GS,p} - V_{T0,p})V_{DS,p} - V_{DS,p}^2]$$

$$\frac{k_n}{2} (V_{in} - V_{T0,n})^2 = \frac{k_p}{2} [2(V_{in} - V_{DD} - V_{T0,p})(V_{out} - V_{DD}) - (V_{out} - V_{DD})^2]$$

- **Differentiate and set dV_{out}/dV_{in} to -1**

$$k_n (V_{in} - V_{T0,n}) = k_p \left[(V_{in} - V_{DD} - V_{T0,p}) \frac{dV_{out}}{dV_{in}} + (V_{out} - V_{DD}) - (V_{out} - V_{DD}) \frac{dV_{out}}{dV_{in}} \right]$$

$$k_n (V_{IL} - V_{T0,n}) = k_p (2V_{out} - V_{IL} + V_{T0,p} - V_{DD})$$

$$V_{IL} = \frac{2V_{out} + V_{T0,p} - V_{DD} + k_R V_{T0,n}}{1 + k_R} \quad k_R = \frac{k_n}{k_p}$$

- **Solve simultaneously with KCL to find V_{IL}**

CMOS Inverter: V_{IH} Calculation

- **KCL:** $\frac{k_n}{2} \left[2(V_{GS,n} - V_{T0,n})V_{DS,n} - V_{DS,n}^2 \right] = \frac{k_p}{2} (V_{GS,p} - V_{T0,p})^2$

$$\frac{k_n}{2} \left[2(V_{in} - V_{T0,n})V_{out} - V_{out}^2 \right] = \frac{k_p}{2} (V_{in} - V_{DD} - V_{T0,p})^2$$

- **Differentiate and set dV_{out}/dV_{in} to -1**

$$k_n \left[(V_{in} - V_{T0,n}) \frac{dV_{out}}{dV_{in}} + V_{out} - V_{out} \frac{dV_{out}}{dV_{in}} \right] = k_p (V_{in} - V_{DD} - V_{T0,p})$$

$$k_n (2V_{out} - V_{IH} + V_{T0,p}) = k_p (V_{IH} - V_{DD} - V_{T0,p})$$

$$V_{IH} = \frac{V_{DD} + V_{T0,p} + k_R (2V_{out} + V_{T0,n})}{1 + k_R} \quad k_R = \frac{k_n}{k_p}$$

- **Solve simultaneously with KCL to find V_{IH}**

CMOS Inverter: V_M Calculation

- **KCL (NMOS & PMOS saturated):**

$$\frac{k_n}{2} (V_{GS,n} - V_{T0,n})^2 = \frac{k_p}{2} (V_{GS,p} - V_{T0,p})^2$$

$$\frac{k_n}{2} (V_{in} - V_{T0,n})^2 = \frac{k_p}{2} (V_{in} - V_{DD} - V_{T0,p})^2$$

- **Solve for $V_M = V_{in} = V_{out}$**

$$V_M = \frac{V_{T0,n} + \sqrt{\frac{1}{k_R} (V_{DD} + V_{T0,p})}}{1 + \sqrt{\frac{1}{k_R}}} \quad k_R = \frac{k_n}{k_p}$$

CMOS Inverter: Achieving Ideal V_M

$$V_{TH} = \frac{V_{T0,n} + \sqrt{\frac{1}{k_R}} (V_{DD} + V_{T0,p})}{1 + \sqrt{\frac{1}{k_R}}} \quad k_R = \frac{k_n}{k_p}$$

- **Ideally, $V_M = V_{DD}/2$** $k_{R,ideal} = \left(\frac{V_{DD}/2 + V_{T0,p}}{V_{DD}/2 + V_{T0,n}} \right)^2$

- **Assuming $V_{T0,n} = V_{T0,p}$, $k_{R,ideal} = 1$**

$$\frac{\left(\frac{W}{L}\right)_p}{\left(\frac{W}{L}\right)_n} = \frac{\mu_n}{\mu_p} \approx 2.5$$

CMOS Inverter: V_{IL} and V_{IH} for Ideal V_M

- Assuming $V_{T0,n} = -V_{T0,p}$, and $k_R = 1$,

$$V_{IL} = \frac{1}{8} (3V_{DD} + 2|V_{T0}|)$$

$$V_{IH} = \frac{1}{8} (5V_{DD} - 2|V_{T0}|)$$

$$V_{IL} + V_{IH} = V_{DD}$$

$$NM_L = V_{IL} - V_{OL} = V_{IL}$$

$$NM_H = V_{OH} - V_{IH} = V_{DD} - V_{IH} = V_{IL}$$

MOSFET Scaling Effects

- Rabaey Section 3.5 (Kang & Leblebici Section 3.5)
 - **Scaling provides enormous advantages**
 - Scale linear dimension (channel length) by factor $S > 1$
 - Better area density, yield, performance
 - **Two types of scaling**
 - Constant field scaling (full scaling)
 - $A' = A/S^2$; $L' = L/S$; $W' = W/S$; $I_D' = I_D/S$; $P' = P/S^2$;
 $V_{dd}' = V_{dd}/S$
 - Power Density $P'/A' =$ stays the same
 - Constant voltage scaling
 - $A' = A/S^2$; $L' = L/S$; $W' = W/S$; $I_D' = I_D * S$; $P' = P * S$;
 $V_{dd}' = V_{dd}$
 - Power Density $P'/A' = S^3 * P$ (Reliability issue)
- Change these two
- This changed as well

Short Channel Effects

- **As geometries are scaled down**
 - V_T (effective) goes lower
 - Effective channel length decreases
 - Sub-threshold I_{ds} occurs
 - Current goes from drain to source while $V_{gs} < V_t$
 - T_{ox} is scaled which can cause reliability problems
 - Can't handle large V_g without hot electron effects
 - Changes the V_t when carriers imbed themselves in the oxide
 - Interconnects scale
 - Electromigration and ESD become issues

MOSFET Capacitances


- Rabaey Section 3.3 (Kang & Leblebici Section 3.6)

- **Oxide Capacitance**


- Gate to Source overlap
- Gate to Drain overlap
- Gate to Channel

- **Junction Capacitance**

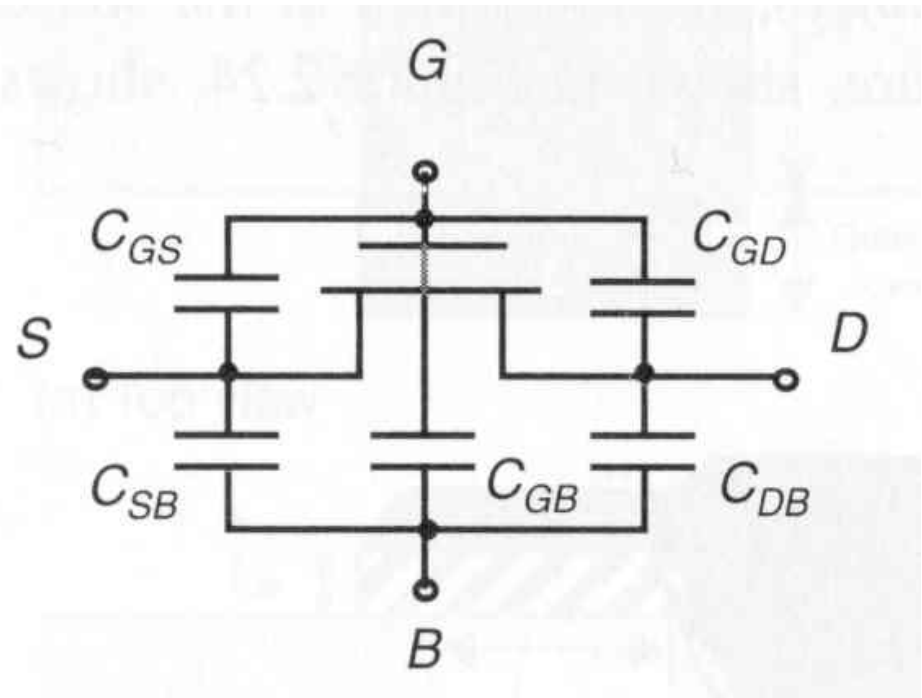- Source to Bulk junction
- Drain to Bulk junction



Oxide Capacitances: Overlap

 

- **Overlap capacitances**


- Gate electrode overlaps source and drain regions
- x_d is overlap length on each side of channel
- $L_{\text{eff}} = L_{\text{drawn}} - 2x_d$ (effective channel length)
- Overlap capacitance:

$$C_{GSO} = C_{GDO} = C_{ox} W x_d \quad \text{Assume } x_d \text{ equal on both sides}$$

Total Oxide Capacitance

- **Total capacitance consists of 2 components**

 - Overlap capacitance
- Channel capacitance



- **Cutoff:**

- No channel connecting to source or drain

- $C_{GS} = C_{GD} = C_{ox} W x_d$

- $C_{GB} = C_{ox} W L_{eff}$

- Total Gate Capacitance = $C_G = C_{ox} W L$

Oxide Capacitances: Channel

- **Linear mode**

- Channel spans from source to drain
- Channel Capacitance split equally between S and D

$$C_{GS} = \frac{1}{2} C_{ox} WL_{eff} \quad C_{GD} = \frac{1}{2} C_{ox} WL_{eff} \quad C_{GB} = 0$$

- Total Gate capacitance $C_G = C_{ox} WL$

- **Saturation regime**


- Channel is pinched off: Channel Capacitance --

$$C_{GD} = Wx_d C_{ox} \quad C_{GS} = \frac{2}{3} C_{ox} WL_{eff} + C_{ox} Wx_d \quad C_{GB} = 0$$


- Total Gate capacitance:

$$C_G = \frac{2}{3} C_{ox} WL_{eff} + 2x_d WC_{ox}$$

Oxide Capacitances: Channel

 

Junction Capacitance

 

Reverse-biased P-N junctions!
Capacitance depends on reverse-bias voltage.

Junction Capacitance

For a P-N junction:

$$C_j = \frac{A}{2} \sqrt{\frac{2q\epsilon}{V_0 - V} \frac{N_d N_a}{N_d + N_a}}$$

If $V=0$, cap/area =

$$C_{j0} = \sqrt{\frac{q\epsilon_{Si}}{2V_0} \frac{N_d N_a}{N_d + N_a}}$$

General form:

$$C_j = \frac{AC_{j0}}{\left(1 - \frac{V}{V_0}\right)^m}$$

**m = grading coefficient (0.5 for abrupt junctions)
(0.3 for graded junctions)**

Junction Capacitance

- **Junction with substrate**
 - Bottom area = $W * L_S$ (length of drain/source)
 - Total cap = C_j
- **Junction with sidewalls**
 - “Channel-stop implant”
 - Perimeter = $2L_S + W$
 - Area = $P * X_j$
 - Total cap = C_{jsw}
- **Total junction cap $C = C_j + C_{jsw}$**

Junction Capacitance

- **Voltage Equivalence Factor**

- Creates an average capacitance value for a voltage transition, defined as $\Delta Q/\Delta V$

$$C_{eq} = \frac{-AC_{j0}V_0}{(V_2 - V_1)(1-m)} \left(\left(1 - \frac{V_2}{V_0}\right)^{1-m} - \left(1 - \frac{V_1}{V_0}\right)^{1-m} \right) = AK_{eq}C_{j0}$$

$$K_{eq} = \frac{-2\sqrt{V_0}}{(V_2 - V_1)} \left(\sqrt{V_0 - V_2} - \sqrt{V_0 - V_1} \right) \quad (\text{abrupt junction only})$$

$$C_{db} = AK_{eq}C_{j0} + PX_j K_{eqsw} C_{jsw0}$$

Example: Junction Cap

- **Consider the following NMOS device**
 - Substrate doping: $N_A = 10^{15} \text{ cm}^{-3}$
 - Source/drain doping: $N_D = 2 \times 10^{20} \text{ cm}^{-3}$
 - Channel-stop doping: 10X substrate doping
 - Drain length $L_D = 1\mu\text{m}$
 - Transistor $W = 10\mu\text{m}$
 - Junction depth $X_j = 0.5\mu\text{m}$, abrupt junction
- **Find capacitance of drain-bulk junction when drain voltage = 3V**

Next Time: AC Characteristics

- **CMOS Inverters**
 - AC Characteristics: Designing for speed