

EEC 116 Lecture #6: Sequential Logic

Rajeevan Amirtharajah
University of California, Davis
Jeff Parkhurst
Intel Corporation

Announcements

- **Lab 3 extended, same due date as Lab 4**
- **HW4 issued today**


Outline

- **Review: Arithmetic**
- **Finish Transmission Gate Circuits and Multipliers**
- **Sequential MOS Logic Circuits: Rabaey, 7.1-7.3 (Kang & Leblebici, 8.1-8.5)**
- **Next Topic: Latchup and Layout Guidelines**

Sequential Logic Basic Definition



- **Combinational circuits' output is a function of the circuit inputs and a delay time**
 - Examples: NAND, NOR, XOR, adder, multiplier
- **Sequential circuits' output is a function of the circuit inputs, previous circuit state, and a delay time**
 - Examples: Latches, flip-flops, FSMs, pipelined adders and multipliers, microprocessors
 - Sequential elements are critical to implementing techniques such as feedback or blocks such as memory

Sequential Logic Example: Mealy FSM

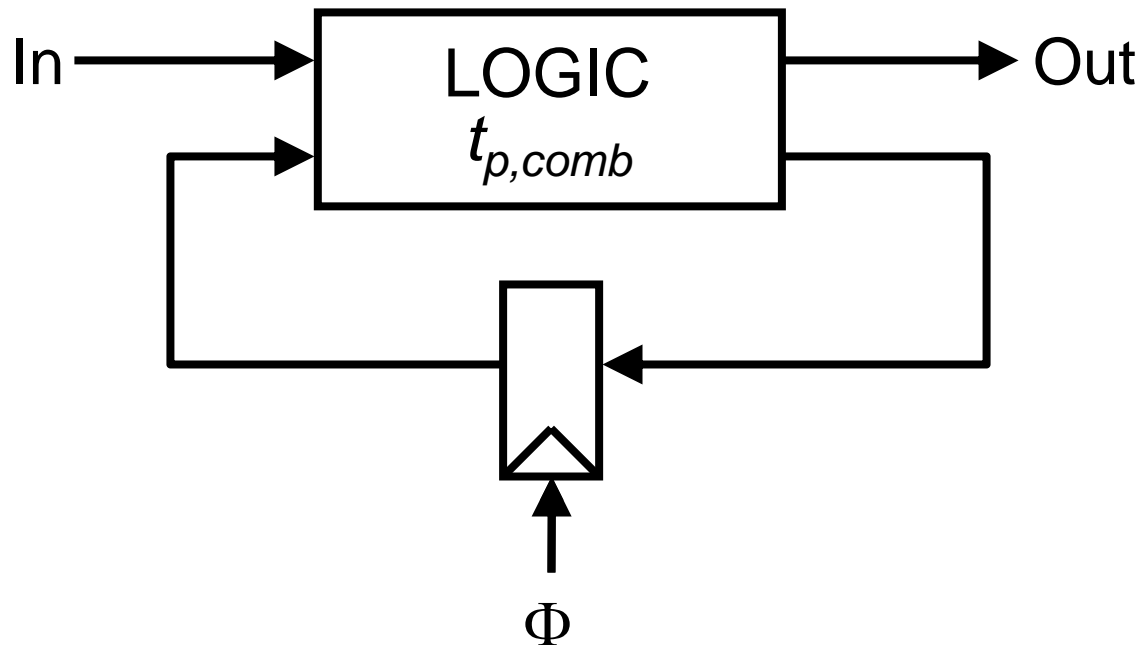


- **Two information storage mechanisms**
 - Positive feedback-based (static) circuits
 - Charge storage-based (dynamic) circuits
- **Clock signal Φ controls timing of state (memory) updates**

Positive Feedback: Bistability

  

Metastability

 


Gain should be larger than 1 in the transition region

Bistable Elements

- **Bistable elements have two stable states or operation modes**
- **Cross-coupled inverters are the most basic bistable element**
 - Circuit forms the basis of latches and SRAM memory
 - Stable points on the VTC are those with the lowest energy
 - Points with high energy are unstable, perturbations are amplified

Set-Reset (SR) Latch

 
- **Change inverters to NAND or NOR gates, with second inputs = S(set) and R(reset)**



- **Allows control of the state of the bistable element**
- **One input state is not allowed**
- **Gating S and R with the clock prevents the latch from responding except during one phase of the clock cycle**

SR Latch

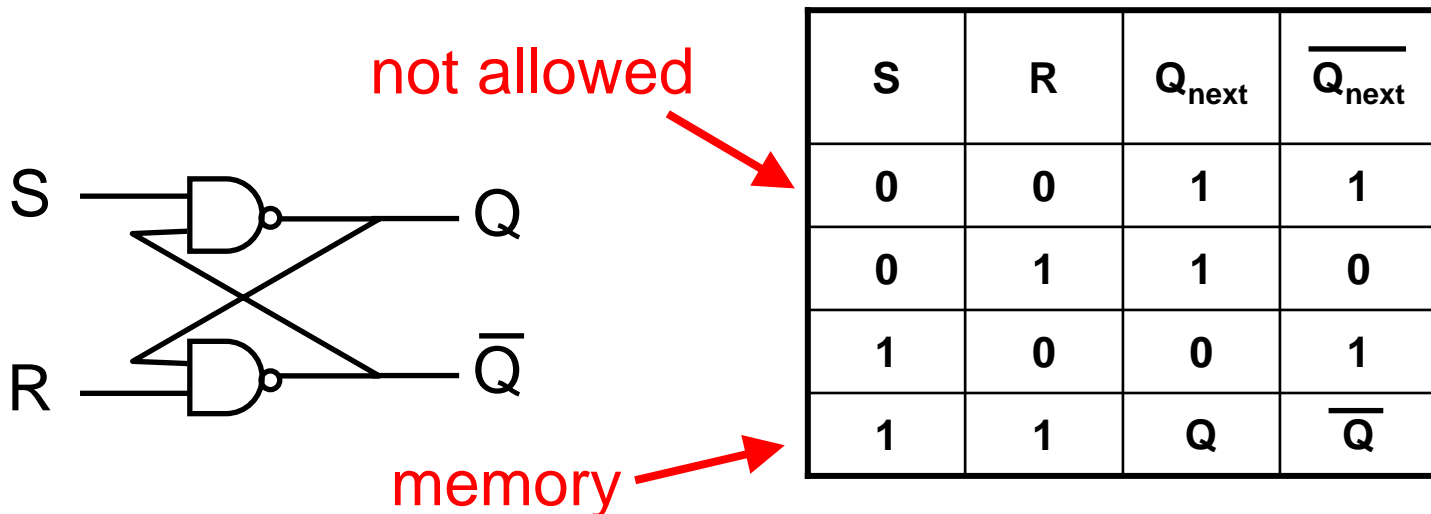- **Sequential circuits:** circuits which “store state”: circuits with memory elements
- **Latches:** store previous output value for certain input combinations
- **SR latch (NAND-based):**




Other Latches

- **Clocked SR latch**
 - Adds clock input. Latch output can only be set/reset when $\text{clk}=1$ (or $\text{clk}=0$)
- **Other latch types:**
 - JK latch: Removes “not allowed” state – e.g., toggles when inputs are both 1
 - T latch: Toggles when T input = 1
 - D latch: Output = D input


Latch Circuits

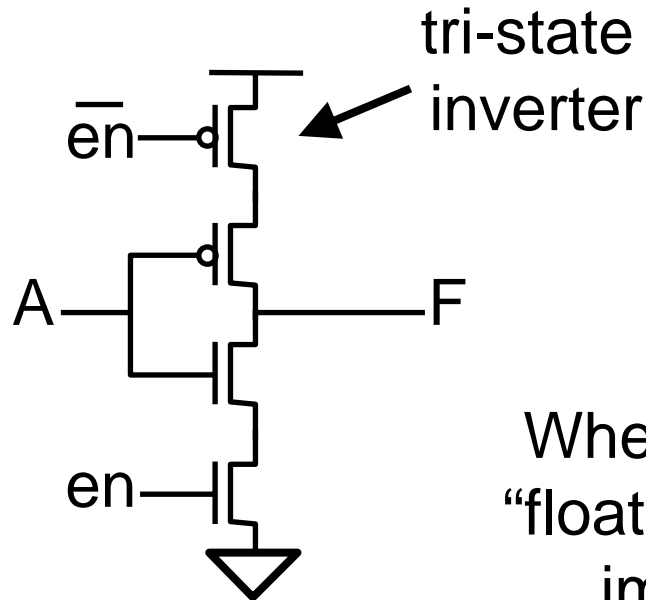- **Many methods for implementing latches**
 - Standard CMOS gates (cross-coupled NAND, etc)
 - Transmission gates
 - Tri-state inverters




When $en=0$, F is “floating”, i.e. high impedance

Positive Dynamic Transmission Gate Latch

 


- No feedback devices
- Data stored on input capacitance of inverter I_0
- Dynamic logic issues apply: leakage, capacitive coupling, charge sharing

Transmission Gate Positive Static Latch

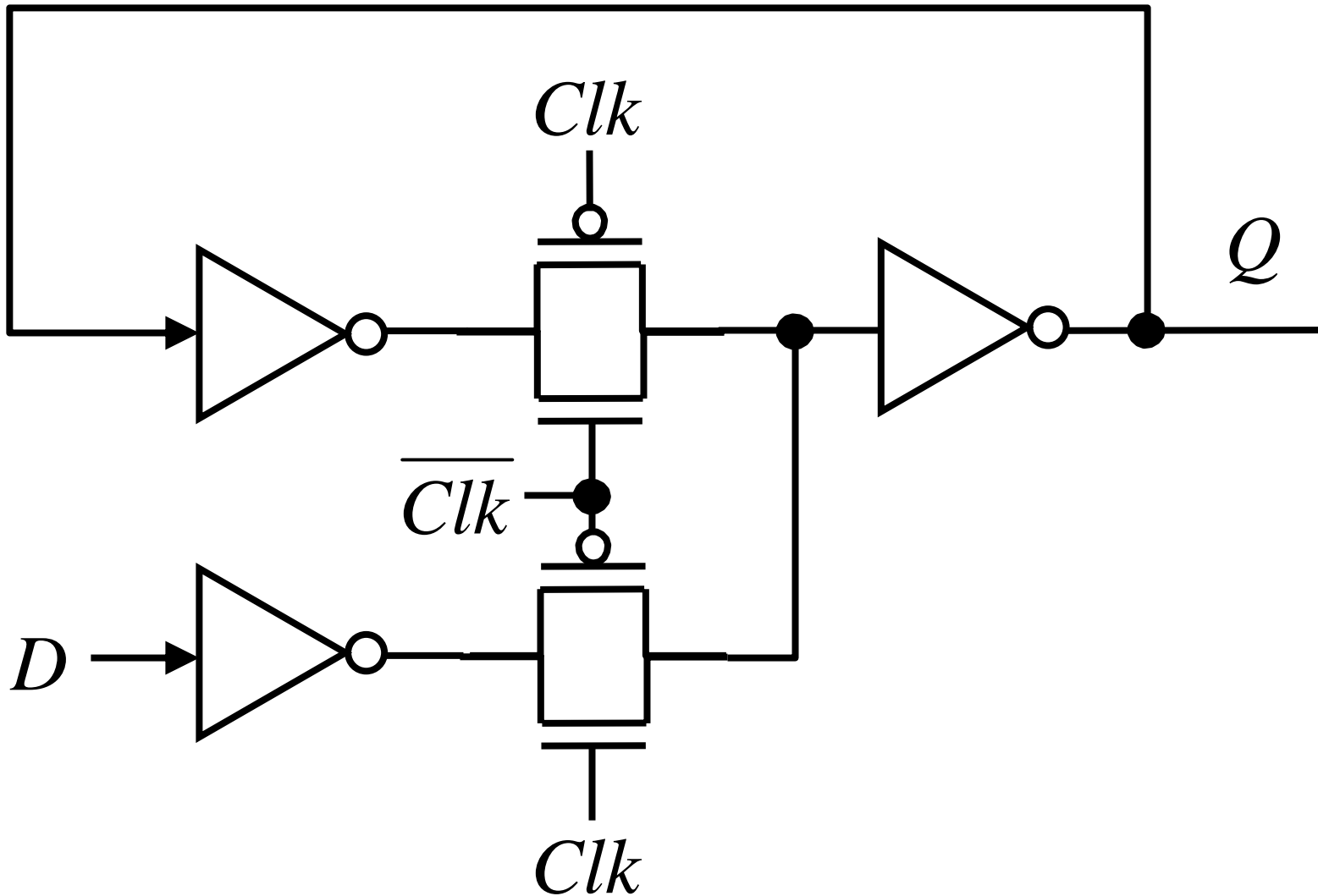

NMOS Pass Gate Positive Static Latch

 

- Fewer devices, less area, lower clock load
- Threshold drop on internal nodes implies more static power, less noise margin


Master-Slave Flip-Flop

- **By cascading two level-sensitive latches, one type of edge triggered flip-flop is created**
- **JK latch can be used for first stage so that no input combinations are invalid**
- **SR latch is then used for the second stage because inputs cannot be invalid**
- **Rather than using logic gate-based latches, can cascade latches such as above (e.g., transmission gate dynamic or static latches)**


Edge-Triggered Flip-Flops

- **Types of latches/flip-flops:**
 - *Level-sensitive*: output is set when clock is a certain level (0 or 1)
 - *Edge-triggered*: output can only be set on a clock edge (rising or falling)
- **Advantages of edge-triggered flip-flops:**
 - Data only needs to be stable at clock edge
 - Reduces *race conditions*: potential errors where an input data change travels through multiple latches during their “transparent” phase


“Safest” Edge-Triggered Flip-Flop

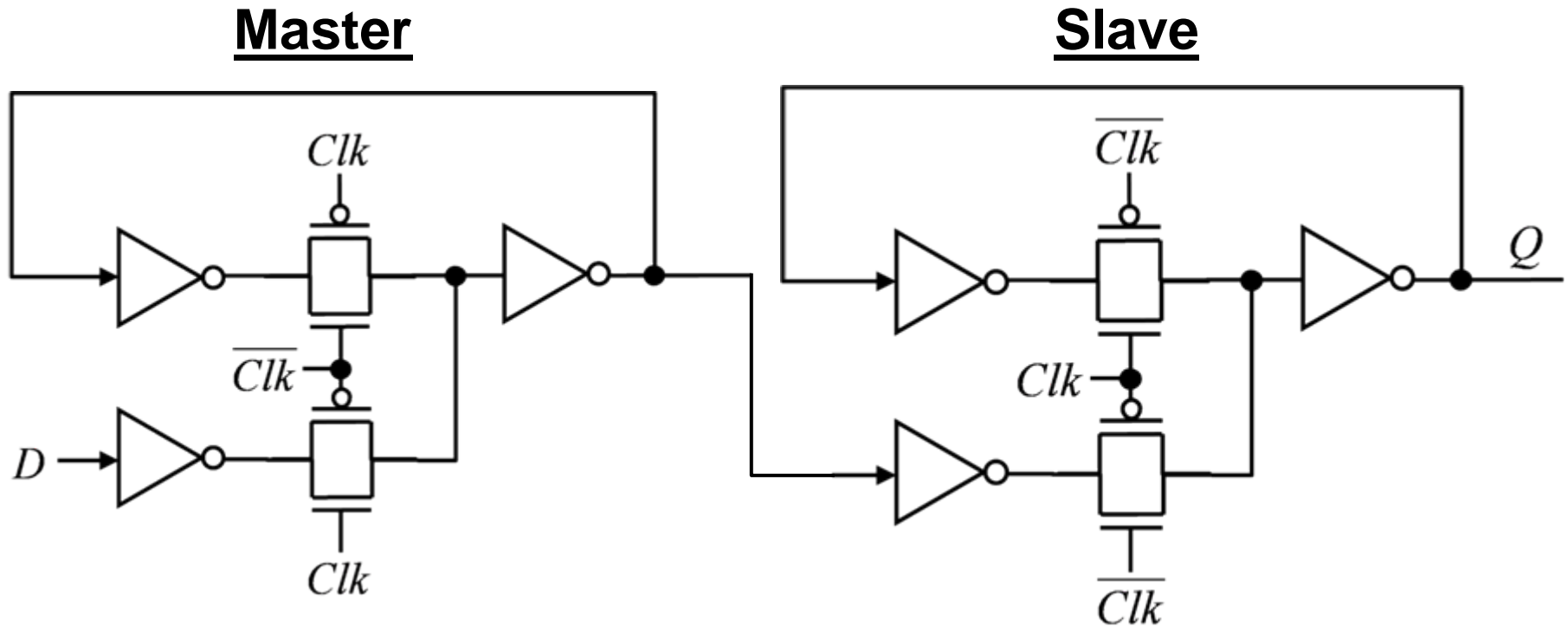

Edge-Triggered Flip-Flop Timing Diagram

 

Dynamic Positive Edge-Triggered FF

 


- No feedback devices
- Data stored on input capacitances of inverters I0 and I1
- Dynamic logic issues apply: leakage, capacitive coupling, charge sharing

Clocked Circuit Timing


- **Timing definitions:**
 - Clock-to-Q or Propagation Delay (t_{clkQ}): delay of flip-flop from clock edge to output Q
 - Setup Time (t_{setup}): amount of time *before* clock edge that data has to be stable. If data arrives after this time, it will not be latched correctly.
 - Hold Time (t_{hold}): amount of time *after* clock edge that data has to be stable.
- **It is possible to trade off setup and hold time with flip-flop circuit design**
 - Modify data and clock timing relationship by delaying one of the two signals

Flip-Flop: Timing Definitions

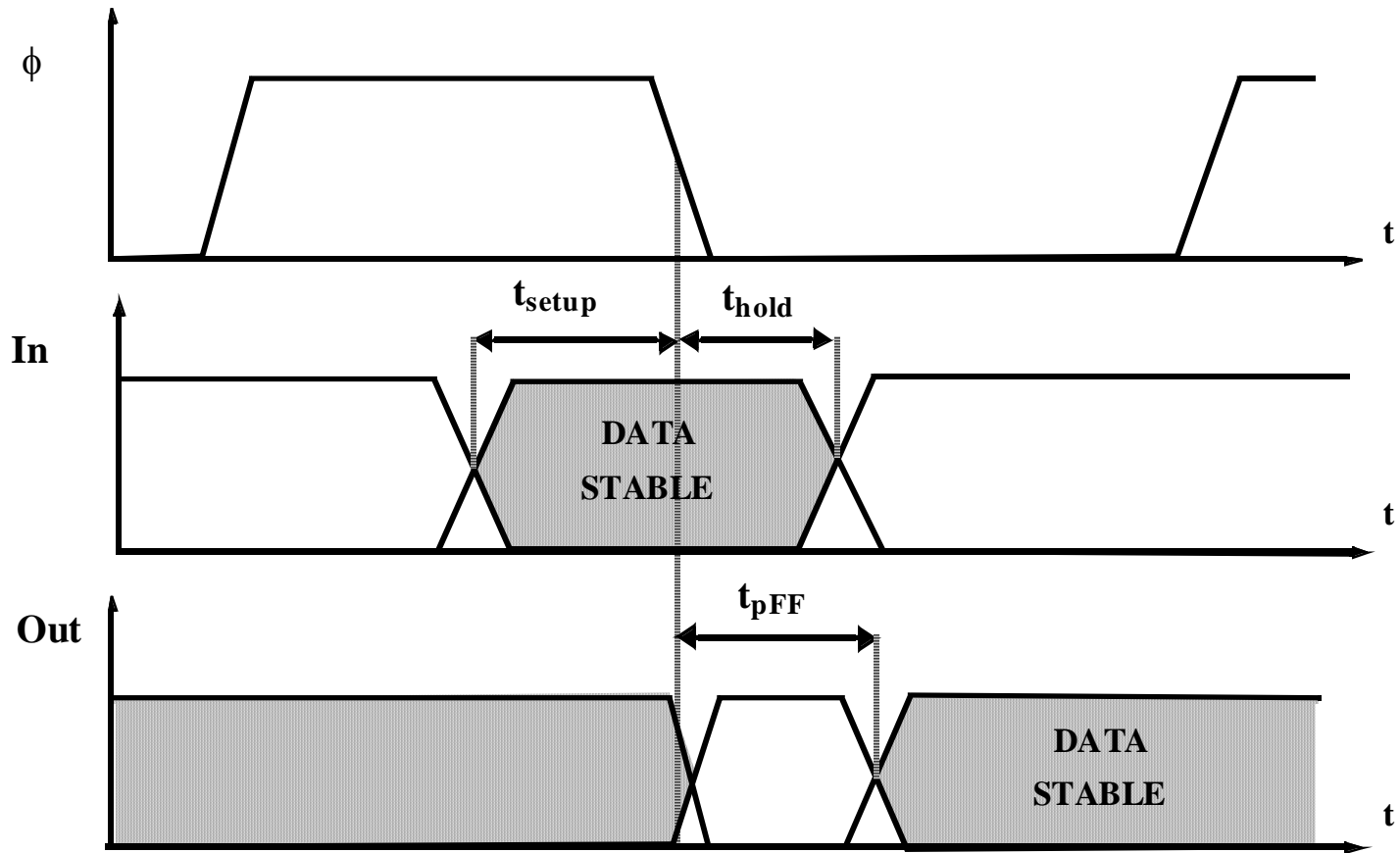

From Digital Integrated Circuits – Jan Rabaey Notes


Maximum Clock Frequency

 

$$t_{pFF} + t_{p,comb} + t_{setup} < T = \frac{1}{f}$$


- **Signals must propagate out of flip-flop, through combinational logic, and be stable before next clock edge (clock period = T, clock frequency = f)**

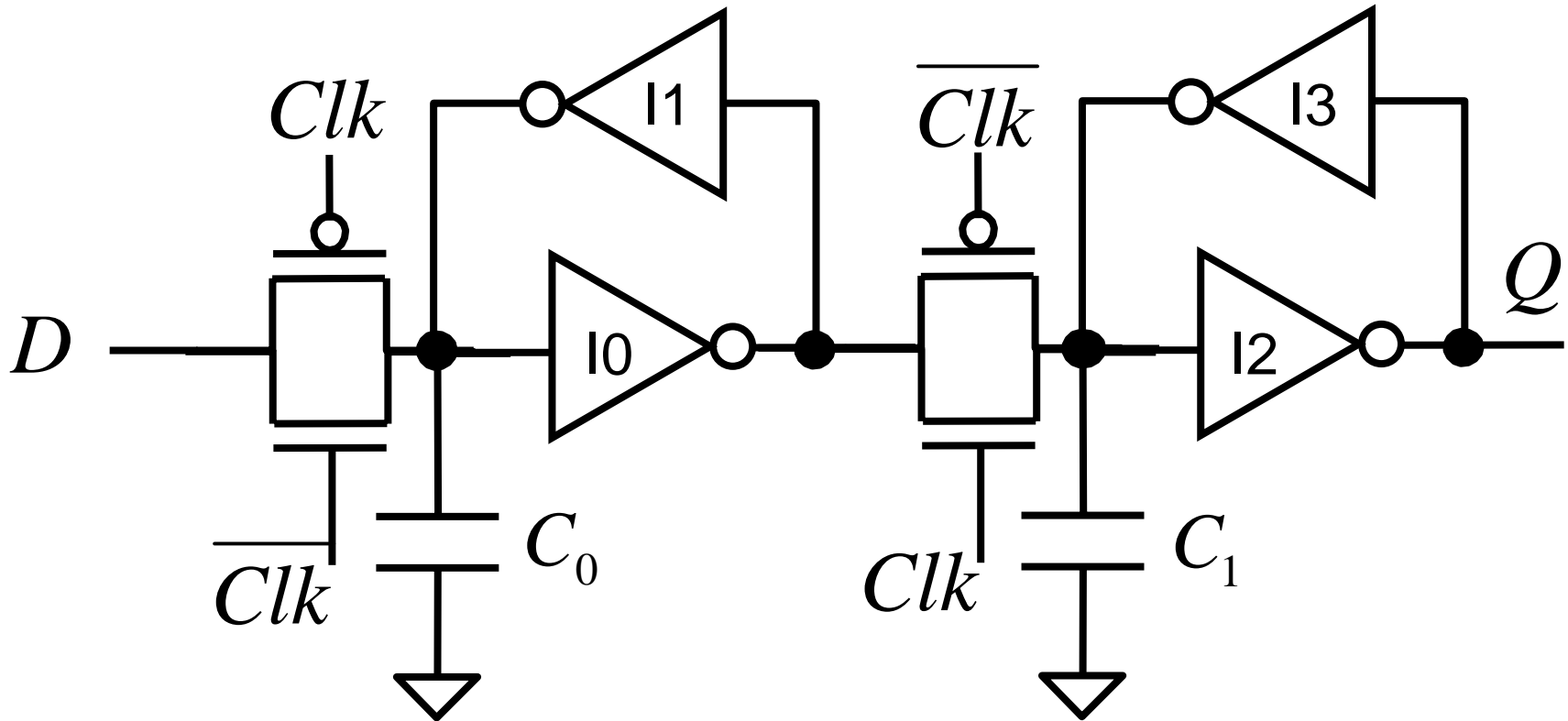Staticized Dynamic Positive Edge-Triggered FF




- Use weak feedback inverters to enhance robustness
- Returns to reduced clock load static flip-flop with same sizing issues

Clock Overlap Failures

 


1. Both high simultaneously, race condition from D to Q
2. Node A can be driven simultaneously by D and B

Race Through and Feedback Paths

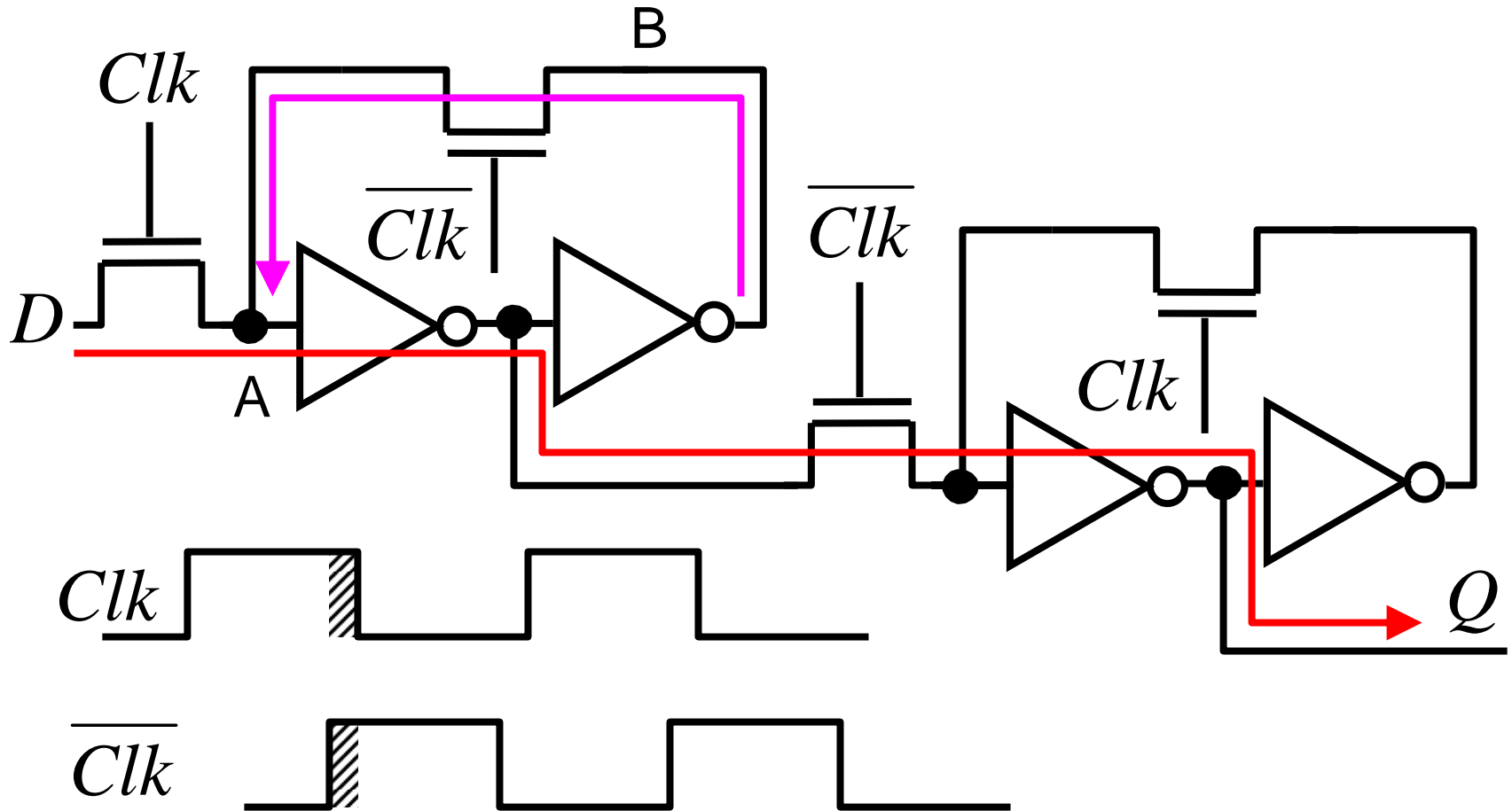


1. Both high simultaneously, race condition from D to Q
2. Node A can be driven simultaneously by D and B

Nonoverlapping Clocks Methodology

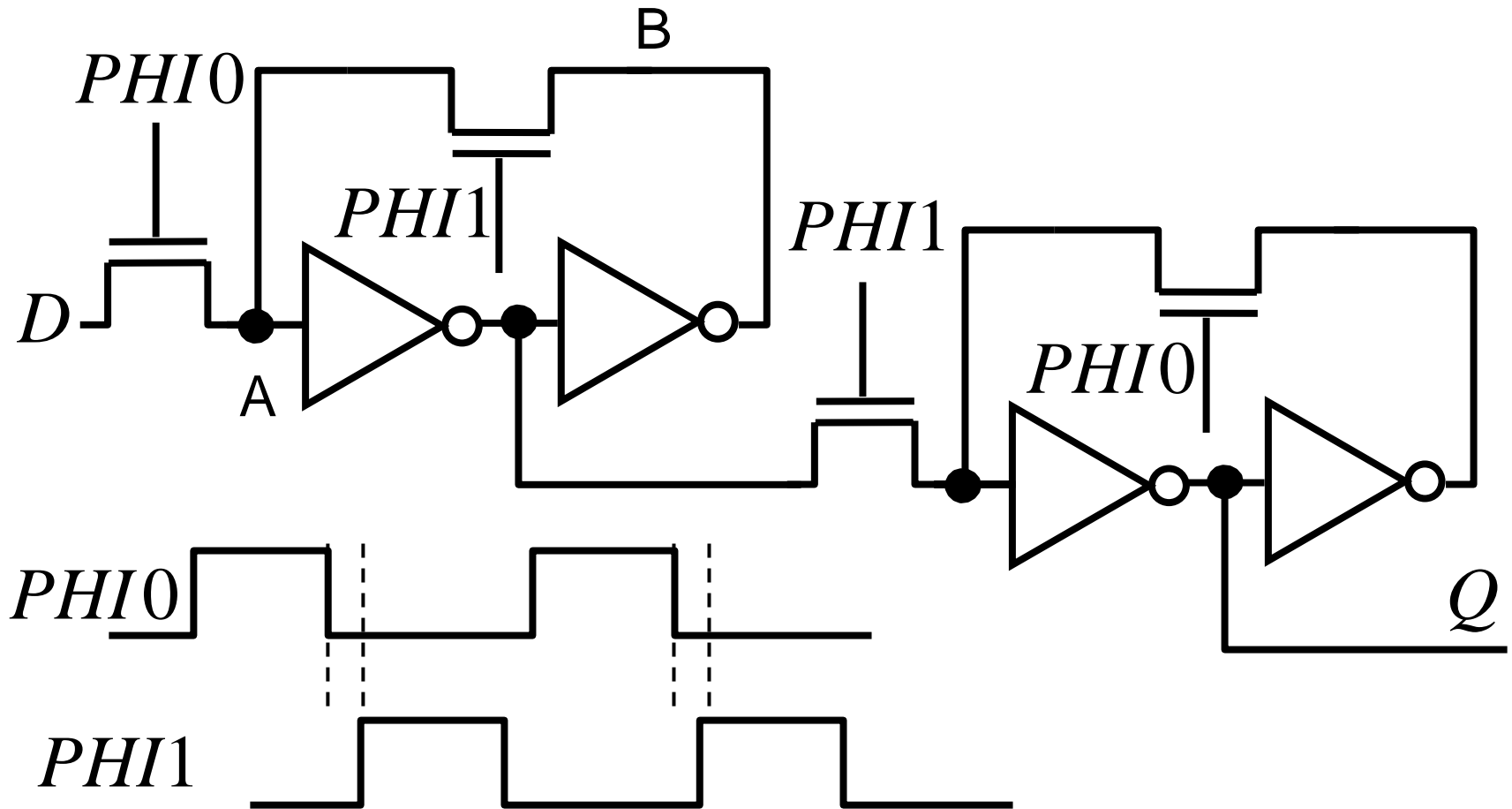


- **Guarantee nonoverlap period long enough**
- **Note: internal nodes left high Z during nonoverlap**

C²MOS Edge Triggered Flip-Flop

 


- **Tristate inverters eliminate clock overlap race condition**

Zero-Zero Overlap Condition

 

- **Both phases low simultaneously enables opposite nets**

High-High Overlap Condition

 


- **Both phases high simultaneously enables opposite nets**

C²MOS Design

- **Clock overlap problems eliminated as long as rise and fall times remain fast**
 - Slow rise / fall times imply pullup and pulldown nets on simultaneously resulting in potential errors, static power
- **Dynamic flip-flop style leaves output high Z**
 - Must take care when using since output wire could be exposed to many more noise sources than internal nodes
- **Mix and match styles by using C²MOS as master and other types of latch as slave**
- **Clock load small, but potentially larger than transmission gate dynamic latches due to PMOS sizing**

Pipelining

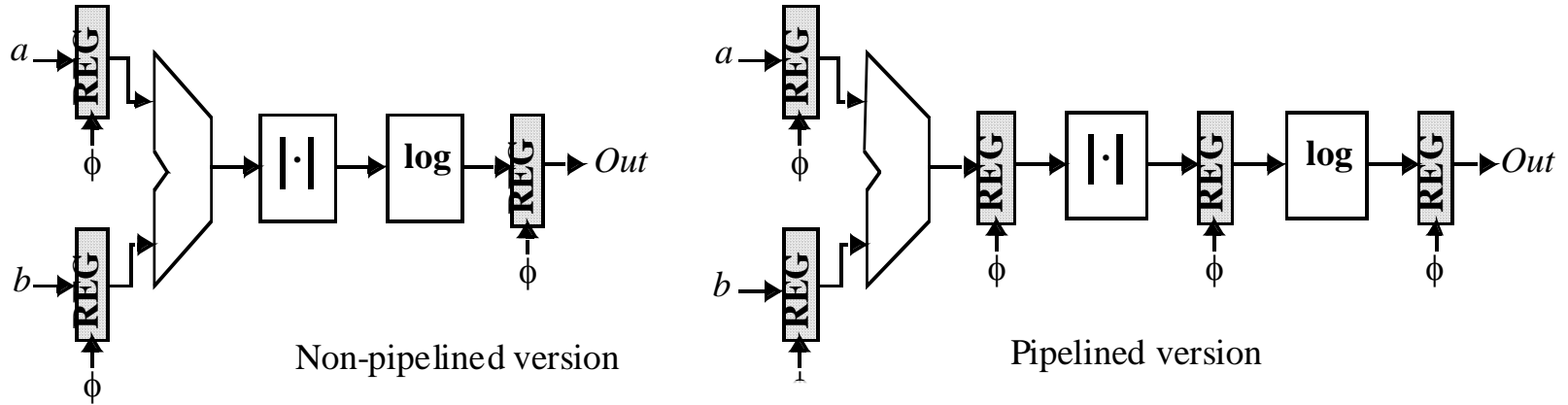

Non-pipelined version

Pipelined version

Clock Period	Adder	Absolute Value	Logarithm
1	$a_1 + b_1$		
2	$a_2 + b_2$	$ a_1 + b_1 $	
3	$a_3 + b_3$	$ a_2 + b_2 $	$\log(a_1 + b_1)$
4	$a_4 + b_4$	$ a_3 + b_3 $	$\log(a_2 + b_2)$
5	$a_5 + b_5$	$ a_4 + b_4 $	$\log(a_3 + b_3)$

From Digital Integrated Circuits – Jan Rabaey Notes

Next Topic: Latchup and Layout Guidelines

- **Latchup**
- **Minimizing area**
- **Managing complexity**