 


# 1. Transparent Latch

## Problem 1.1



We want the latch to be transparent when  $clk$  is positive, so we put  $clk$  at the gates of the NMOS's and  $clk\_bar$  at the gates of the PMOS's. The feedback inverter makes it static instead of dynamic.

## Problem 1.2

Since the output equals the input after some delay, we imagine the input  $D$  at  $V_{DD}$  and the output  $Q$  low before the  $clk$  signal goes high. We're given the  $t_{pLH}$  for the second inverter which is the delay for the output to go from GND to  $0.5 V_{DD}$ . Assuming that  $t_{pLH2}$  is the time from when the input changes to its 50% value till the output rises to the 50% value, the  $t_{pLH}$  from the input to the output is approximately  $t_{HL1} + t_{pLH2}$  because we need the time it takes the voltage at the capacitor  $V_{C0}$  or the input to the second inverter to become  $0.5 V_{DD}$ . We don't have to calculate the full fall time for the first inverter.

Using the average current method,  $\tau_{pHL1} = \frac{C_{load}\Delta V}{I_{avg}}$  where  $\Delta V$  is  $0.5V_{DD}$ .


$$I_{avg} = \frac{1}{2} [I(V_{in} = 1.8, V_{C0} = 1.8) + I(V_{in} = 1.8, V_{C0} = 0.9)]$$

Saturation since

$$V_{DS} \geq V_{GS} - V_{T,n}$$

Linear since

$$V_{DS} < V_{GS} - V_{T,n}$$

 

We can treat the two NMOS in series as one NMOS with an effective length of  $2*L$ .

$$I_{avg} = \frac{k_n}{4} [(V_{GS} - V_{T,n})^2 + 2(V_{GS} - V_{T,n})V_{DS} - V_{DS}^2] = \frac{300\mu A}{4} \frac{0.45}{2 * 0.180} [1.2^2 + 2(1.2)(0.9) - 0.9^2] = 262 \mu A$$

$$\tau_{HL} = \frac{97 \text{ fF} \cdot 0.9 \text{ V}}{262 \text{ } \mu\text{A}} = 333 \text{ ps}$$

$$t_{pLH} = 333 \text{ ps} + 45 \text{ ps} = 378 \text{ ps}$$

You can also use the 2<sup>nd</sup> approximation using the saturation current, which gives  $\tau_{HL} = 323 \text{ ps}$  and

$$t_{pLH} = 323 \text{ ps} + 45 \text{ ps} = 368 \text{ ps}.$$

### Problem 1.3

The same can be done as in the previous problem, but for the output falling from high to low and the input low before clock goes high. Therefore, we will focus on the PMOS in the first inverter, and the second inverter has  $t_{pHL} = 45 \text{ ps}$ .


$$I_{avg} = \frac{1}{2} [I(V_{in} = 0, V_{C_0} = 0) + I(V_{in} = 0, V_{C_0} = 0.9)]$$

Saturation since

$$|V_{DS}| \geq |V_{GS}| - |V_{T,p}|$$

Linear since

$$|V_{DS}| < |V_{GS}| - |V_{T,p}|$$

 

$$I_{avg} = \frac{k_p}{4} [(V_{GS} - V_{T,p})^2 + 2(V_{GS} - V_{T,p})V_{DS} - V_{DS}^2]$$

$$= \frac{100 \mu\text{A}}{4} \frac{1.44}{2 \cdot 0.180} [(-1.1)^2 + 2(-1.1)(-0.9) - (-0.9)^2] = 238 \mu\text{A}$$

$$\tau_{pLH1} = \frac{97 \text{ fF} \cdot 0.9 \text{ V}}{238 \text{ } \mu\text{A}} = 367 \text{ ps}$$

$$t_{pHL} = 367 \text{ ps} + 45 \text{ ps} = 412 \text{ ps}$$

Using the second average current approximation,  $t_{pHL} = 360 \text{ ps} + 45 \text{ ps} = 405 \text{ ps}$


### Problem 1.4

The Master stage latch in the flip-flop determines when a signal is "let in" or is the first of the two cascaded latches. In this case since the flip-flop is negative edge triggered, meaning that the output will hold the input value when the clock goes low, the master latch is active when the clock is high. The setup time is the time the input has to be stable before the active edge so that it can propagate to the input of the slave stage and be held. In this case, the longest possible propagation delay will determine the setup time. The longest propagation delay we see from the ideal clock pulse to the output changing to the 50% value is 412 ps. To be more conservative so that output reaches GND and since it's an ideal clock, it would most likely take another 45 ps resulting in a setup time of 457 ps.

## 2. Flip-Flop

2.1 The Active Low signal  $\overline{CLR}$  drives the gate of transistor  $P_7$ . if  $\overline{CLR}$  is set to "0", transistor  $P_7$  pulls the gates of  $P_5$  &  $N_5$  up to  $V_{DD}$ . this sets a low or clears Q and does not rely on the clock therefore it is Asynchronous.

2.2

 

$$I_P = I_{N1} \Rightarrow \frac{K_H}{2} (V_m - V_{TH})^2 = \frac{K_D}{2} (V_{DD} - V_m - |V_{TP}|)^2$$

$$\frac{K_H}{K_P} (V_m - V_{TH})^2 = (V_{DD} - V_m - |V_{TP}|)^2$$

$$\sqrt{\frac{K_H}{K_P}} (V_m - V_{TH}) = (V_{DD} - V_m - |V_{TP}|) \Rightarrow \sqrt{\frac{K_H}{K_P}} V_m + V_m = V_{DD} + \sqrt{\frac{K_H}{K_P}} V_{TH} - |V_{TP}|$$

$$\text{Solve for } V_m = \frac{V_{DD} + \sqrt{\frac{K_H}{K_P}} V_{TH} - |V_{TP}|}{1 + \sqrt{\frac{K_H}{K_P}}}$$

The only difference between the CMOS stage and the inverter is the ratio of  $K_H/K_P$


for the inverter

$$\frac{K_H}{K_P} = \frac{300 \mu A/\mu^2 \cdot 1.4/0.6}{100 \mu A/\mu^2 \cdot 2.0/0.6} = \frac{800}{466} = 1.7$$

for the CMOS

$$\frac{K_H}{K_P} = \frac{300 \mu A/\mu^2 \cdot 1.4/1.2}{100 \mu A/\mu^2 \cdot 2.0/1.2} = \frac{400}{233} = 1.7$$

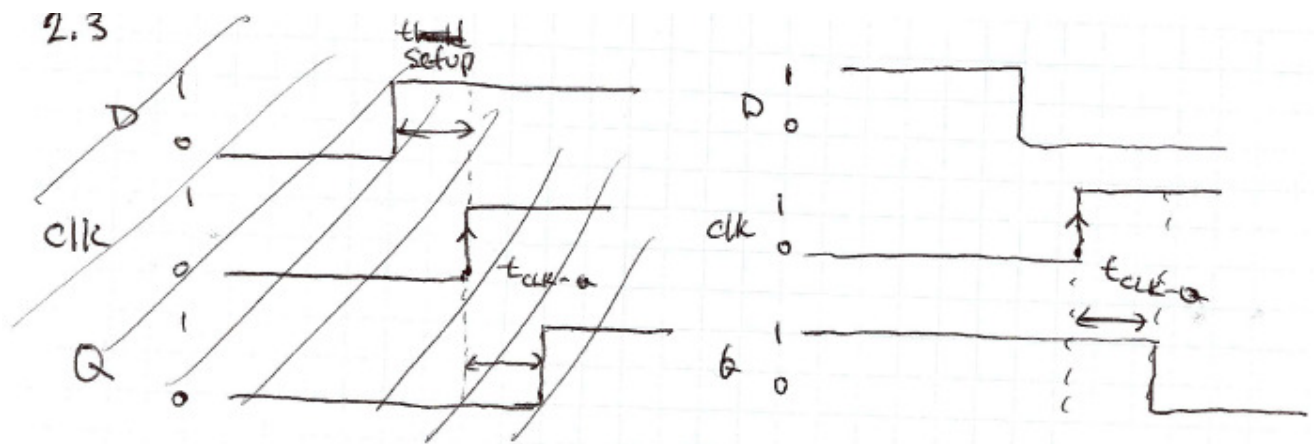The Ratio of  $K_H/K_P$  is equal so the thresholds ( $V_m$ ) are equal.



When the clock is low, the storage node formed by the gates of transistors  $N_1$  &  $P_1$  is discharged when the signal  $D$  ~~falls~~ is low.

After the clock rises, the "0" stored on the gates of  $N_1$  &  $P_1$  is passed to  $Q$ .

When the clock signal is high the  $C^{2}mos$  stage drives the inverter formed by transistors  $N_5$  &  $P_5$  to a logic "1".

~~This inverter~~ then drives the output  $Q$  low.

From this we see that we need to compute the delay through the  $C^{2}mos$  stage & the inverter.



the total delay will be

$$t_{\text{clk-to-q}} = T_{\text{PLH}}^{\text{CMOS}} + T_{\text{PHL}}^{\text{INV}}$$

to find these we need to determine the loading capacitance & the average current for both individually.

$$T_{\text{PLH}}^{\text{CMOS}} = \frac{C \Delta V}{I_{\text{AVG}}}$$

$$\Delta V = \cancel{V_{DD} - V_{SS}} \quad V_{SS} \rightarrow V_{DD}/2 \quad 10\% \text{ to } V_{DD} \rightarrow 90\% \text{ to } V_{DD}$$

$$I_{\text{AVG}} = \frac{1}{2} (I_{\text{sat,P}} + I_{\text{lin,P}})$$

$$I_{\text{sat,P}} = \frac{K_P}{2} (V_{DD} - |V_{TP}|)^2$$

$$K_P = \mu_p C_{ox} \cdot \frac{2.8}{1.2} = 233 \text{ mA/V}^2$$

$$I_{\text{sat,P}} = \frac{233.3 \text{ mA/V}^2}{2} (1.8 - 1 - 0.7)^2 = 141 \text{ mA}$$

Note:  $2L$  is the effective length.

$$I_{\text{lin,P}} = K_P \left[ (V_{GS} - |V_{TP}|) V_{DS} - \frac{V_{DS}^2}{2} \right]$$

Linear when  $V_{DS} < V_{GS} - V_{TP}$   $V_{GS} = V_{DD}$


$$\text{Assume mid point } V_{DS} = \frac{V_{DD} - |V_{TP}|}{2} = \frac{1.8 - 1 - 0.7}{2} = 0.65$$

$$I_{\text{lin,P}} = 233 \text{ mA/V}^2 \left[ (1.8 - 1 - 0.7) 0.65 - \frac{1}{2} 0.65^2 \right]$$

$$I_{\text{lin,P}} = 233 \text{ mA/V}^2 \cdot 0.503 \text{ V}^2 = 117.5 \text{ mA}$$

$$I_{avg_P} = \frac{141 \mu A + 117.5 \mu A}{2} \approx 129.25 \mu A$$

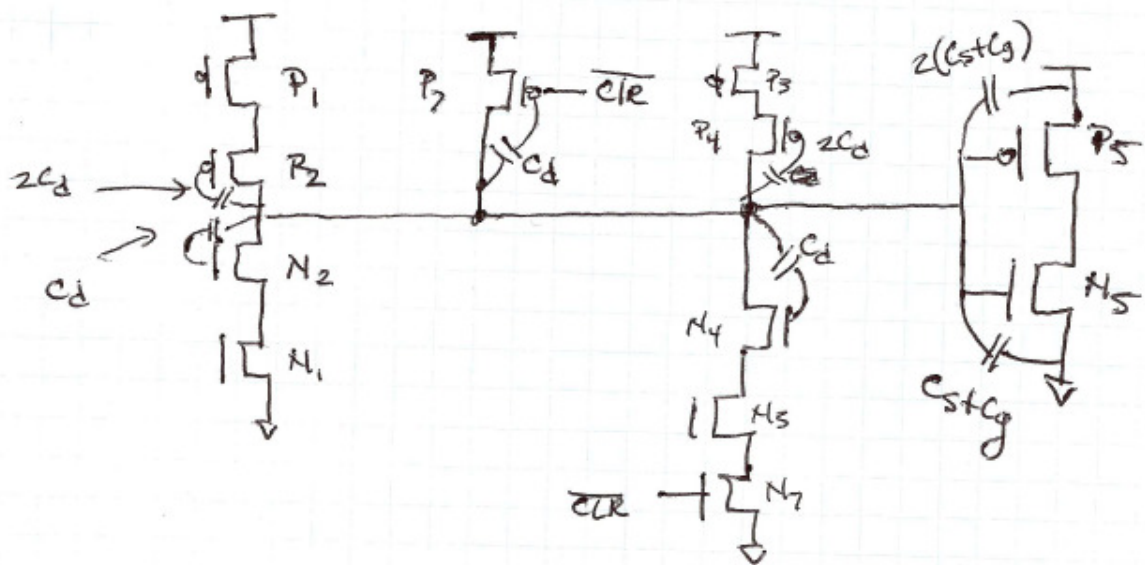Next we need to find the total capacitance connected to the output of the CMOS stage.



All PMOS devices have capacitances which are  $2\times$  larger as they have twice the area.

$$C = 7C_d + 3C_s + 3C_g = 10C_s + 3C_g$$

$$C = 10 \cdot 10fF + 3 \cdot 15fF = 145fF$$

$$T_{PLH_{CMOS}} = \frac{145fF \cdot 0.9V}{129.25 \mu A} \approx 1 \mu s$$

$$t_{PHL_{INV}} = \frac{C_{INV}}{I_{avg}}$$

$$I_{avg} = \frac{1}{2} (I_{sat,N} + I_{LW,N})$$

$$I_{sat,N} = \frac{k_N}{2} (V_{GS} - V_{TN})^2$$

$$k_N = \mu_n C_{ox} \frac{W}{L} = 200 \mu A/V^2$$

$$I_{sat,N} = \frac{k_N}{2} (1.8 - 0.6)^2 = 504 \mu A$$

$$I_{LW,N} = k_N \left[ (V_{GS} - V_{TN}) V_{DS} - \frac{1}{2} V_{DS}^2 \right]$$

Assume mid point  $V_{DS} = \frac{V_{DD} - V_{TN}}{2} = 0.6$

$$I_{LW,N} = 200 \mu A/V^2 \left[ (1.8 - 0.6) 0.6 - \frac{1}{2} 0.6^2 \right] = 378 \mu A$$


$$I_{avg,N} = \frac{504 \mu A + 378 \mu A}{2} = 441 \mu A$$

$$2C_D + 2C_S + 2C_G$$

$$C = 6C_D + 3C_S + 3C_G$$

$$C = 9C_S + 3C_G$$

$$C = 135 fF$$

 


$$t_{PHL_{INV}} =$$

$$\frac{135 fF \cdot 0.9V}{441 \mu A} = 0.276 ns$$

$$t_{clk-Q} = 1.276 ns$$

### 3. Mixed Combinational and Sequential Logic

$$F = A(B + C)$$

 

$$\text{For } t_{\text{fall}} = t_{\text{rise}}, \mu_n W_n = \mu_p W_p$$

$$\Rightarrow W_p = \frac{\mu_n}{\mu_p} W_n = 2.5 W_n$$

Other solutions possible ...