

# **EEC 118 Lecture #11: CMOS Design Guidelines Alternative Static Logic Families**

**Rajeevan Amirtharajah  
University of California, Davis**

**Jeff Parkhurst  
Intel Corporation**


# Outline

---

- **Finish Arithmetic Discussion**
- **Review: Static CMOS Sizing**
- **Design Guidelines for CMOS**
- **Pseudo-NMOS Logic: Rabaey 6.2**
- **Pass Transistor Circuits: Rabaey 6.2 (Kang & Leblebici 9.1-9.2)**
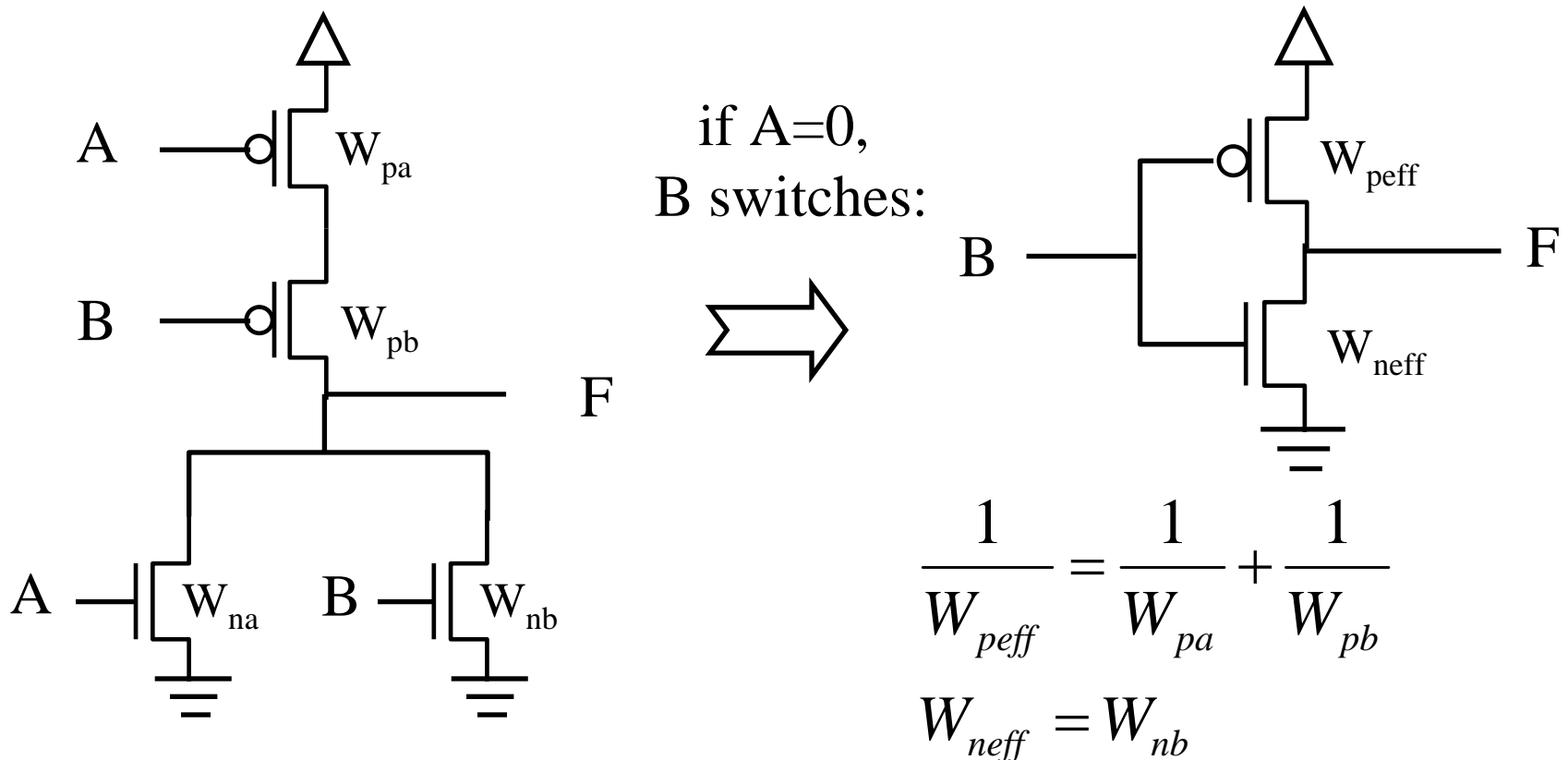
# Review: CMOS Sizing

- Equivalent inverter approach: replace transistors which are “on” with equivalent transistor
- Use equivalent inverter to find  $V_M$ , delays, etc.




# Review of Sizing

---

- **Gate delays depend on which inputs switch**
  - Normally sized for worst-case delay
  - Best-case (fastest) delay also important due to race conditions in a pipelined datapath
- **Switching threshold  $V_M$  normally considers all inputs switching**
- **Delay estimation**
  - Combine switching transistors into equivalent inverter

## Example: NAND gate

---

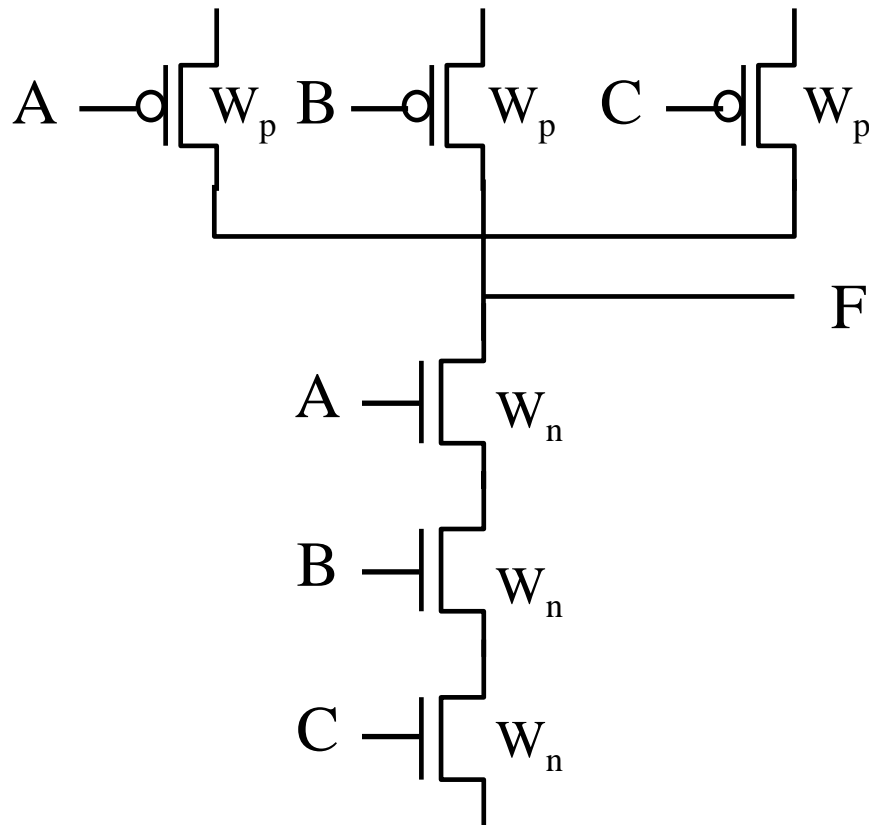

- **Circuit:**

- Load cap  $C_L = 400\text{fF}$
- PMOS  $W/L = 2$
- NMOS  $W/L = 1$
- $k_n' = 200 \text{ mA/V}^2$
- $k_p' = 80 \text{ mA/V}^2$
- $V_T = 0.5\text{V}$

- **1<sup>st</sup>: Find delay of inverter**
- **2<sup>nd</sup>: Find delay of NAND**

# Equivalent Inverter

---

- **Problems with equivalent inverter method:**
  - Need to take into account load capacitance  $C_L$ 
    - Depends on number of transistors connected to output (junction capacitances)
    - Even transistors which are off (not included in equivalent inverter) contribute to capacitance (i.e. PMOS Drain Capacitance)
  - Need to include capacitance in intermediate stack nodes (NMOS caps). Worst-case: need to charge/discharge all nodes
  - Body effect of stacked transistors

# Load Capacitance

---

- **Output capacitance includes junction caps of all transistors on output**
- **Reducing load capacitance**
  - Minimize number of transistors on output node
  - Tapering transistor stacks:
    - Wider transistors closest to power and ground nodes, narrower at output
    - Transistors closest to power nodes carry more current

# Intermediate Node Capacitances

---

- **Internal capacitances in CMOS gates are charged and discharged**
  - Depends on input pattern
  - Increases delay of gate
- **Simple analysis**
  - Combine internal capacitances into output load
  - Assumes all capacitances charged and discharged fully
- **Effect on delay analysis**
  - Gate delay depends on timing of inputs!



# CMOS Design Guidelines I

---

- **Transistor sizing**
  - Size for worst-case delay, threshold, etc
  - Tapering: transistors near power supply are larger than transistors near output
- **Transistor ordering**
  - Critical signal is defined as the latest-arriving signal to input of gate of interest.
  - Put critical signals closest to output
    - Stack nodes are discharged by early signals
    - Reduced body effect on top transistor

# CMOS Design Guidelines II

---

- **Limit *fan-in* of gate**
  - Fan-in: number of gate inputs
  - Affects size of transistor stacks
  - Normally fan-in limit is 3-4
- **Convert large multi-input gates into smaller chain of gates**
- **Limit *fanout* of gate**
  - Fanout: number of gates connected to output
  - Capacitive load: affects gate delay
- **NANDs are better than NORs**
  - Series NMOS devices less area, capacitance than equivalent series PMOS devices

# CMOS Disadvantages

---

- **For N-input CMOS gate,  $2N$  transistors required**
  - Each input connects to an NMOS and PMOS transistor
  - Large input capacitance: limits fanout
- **Large fan-in gates: always have long transistor stack in PUN or PDN**
  - Limits pullup or pulldown delay
  - Requires very large transistors
- **Single-stage gates are inverting**


# Pseudo-NMOS Logic

---

- **Pseudo-NMOS:** replace PMOS PUN with single “always-on” PMOS device (grounded gate)
- **Same problems as true NMOS inverter:**
  - $V_{OL}$  larger than 0 V
  - Static power dissipation when PDN is on
- **Advantages**
  - Replace large PMOS stacks with single device
  - Reduces overall gate size, input capacitance
  - Especially useful for wide-NOR structures
 
# Pseudo-NMOS Inverter Circuit

- Replace PUN or resistor with “always-on” PMOS transistor
- Easier to implement in standard process than large resistance value
- PMOS load transistor:
  - On when  $V_{GS} < V_{TP} \rightarrow V_{GS} = -V_{DD}$ : transistor always on
  - Linear when  $V_{DS} > V_{GS} - V_{TP} \rightarrow V_{out} - V_{DD} > -V_{DD} - V_{TP} \rightarrow V_{out} > -V_{TP}$
  - Saturated when  $V_{DS} < V_{GS} - V_{TP} \rightarrow V_{out} - V_{DD} < -V_{DD} - V_{TP} \rightarrow V_{out} < -V_{TP}$




Remember:  
 $V_T \text{ (PMOS)} < 0$
 
# Pseudo-NMOS Inverter: $V_{OH}$

---

- $V_{OH}$  for pseudo-NMOS inverter:
  - $V_{in} = 0$
  - NMOS in cutoff: no drain current
- **Result:  $V_{OH}$  is  $V_{DD}$  (as in resistive-load inverter or CMOS inverter case)**



# Pseudo-NMOS Inverter: $V_{OL}$

---

- **Find  $V_{OL}$  of pseudo-NMOS inverter:**

- $V_{in} = V_{DD}$ : NMOS on in linear mode (assume  $V_{OL} < V_{DD} - V_{Tn}$ )

$$I_{Dn} = k_n \left[ (V_{DD} - V_{Tn})V_{OL} - \frac{1}{2}V_{OL}^2 \right]$$

- PMOS on in saturation mode (assume)

$$I_{Dp} = \frac{1}{2} k_p (-V_{DD} - V_{Tp})^2 \quad (\text{neglecting } \lambda)$$

- Setting  $I_{dn} = I_{dp}$ :


$$\frac{1}{2} k_n V_{OL}^2 - k_n (V_{DD} - V_{Tn})V_{OL} + \frac{1}{2} k_p (-V_{DD} - V_{Tp})^2 = 0$$

- **Key point:  $V_{OL}$  is not zero**


- Depends on thresholds, sizes of N and P transistors

# Pseudo NMOS Inverter: I/V Curves

I/V curve for NMOS:

 



I/V curve for PMOS:

 

- Plot of  $-I_{DS}$  vs  $-V_{DS}$  since current is from source to drain
- Only one curve since  $V_{GS}$  fixed




# Pseudo NMOS Inverter: VTC

  

- **Similar VTC to resistive-load inverter**
  - Sharper transition region, smaller area
- **VOL worse than CMOS inverter**

# Transmission Gate Logic


---

 

- **NMOS and PMOS connected in parallel**
- **Allows full rail transition – ratioless logic**
- **Equivalent resistance relatively constant during transition**
- **Complementary signals required for gates**
- **Some gates can be efficiently implemented using transmission gate logic (XOR in particular)**

# Equivalent Transmission Gate Resistance


---

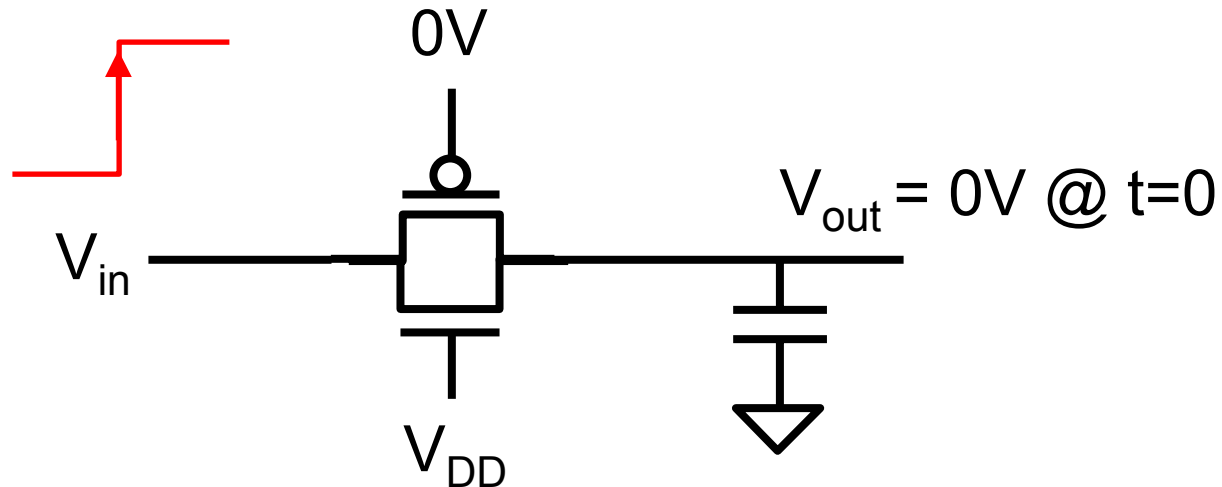

- **For a rising transition at the output (step input)**
  - NMOS sat, PMOS sat until output reaches  $|V_{TP}|$
  - NMOS sat, PMOS lin until output reaches  $V_{DD} - V_{TN}$
  - NMOS off, PMOS lin for the final  $V_{DD} - V_{TN}$  to  $V_{DD}$  voltage swing
 
# Equivalent Resistance

- Equivalent resistance  $R_{eq}$  is parallel combination of  $R_{eq,n}$  and  $R_{eq,p}$
- $R_{eq}$  is relatively constant



# Resistance Approximations

---

- **To estimate equivalent resistance:**
  - Assume both transistors in linear region
  - Ignore body effect
  - Assume voltage difference ( $V_{DS}$ ) is small

$$R_{eq,n} \approx \frac{1}{k_n (V_{DD} - V_{tn})} \qquad R_{eq,p} \approx \frac{1}{k_p (V_{DD} - |V_{tp}|)}$$

$$R_{eq} \approx \frac{1}{k_n (V_{DD} - V_{tn}) + k_p (V_{DD} - |V_{tp}|)}$$

# Equivalent Resistance – Region 1

---

- **NMOS saturation:**

$$R_{eq,n} = \frac{(V_{DD} - V_{out})}{\frac{1}{2} k_n (V_{DD} - V_{out} - V_{tn})^2}$$

- **PMOS saturation:**

$$R_{eq,p} = \frac{(V_{DD} - V_{out})}{\frac{1}{2} k_p (-V_{DD} - V_{tp})^2}$$

## Equivalent Resistance – Region 2

---

- **NMOS saturation:**

$$R_{eq,n} = \frac{(V_{DD} - V_{out})}{\frac{1}{2} k_n (V_{DD} - V_{out} - V_{tn})^2}$$

- **PMOS linear:**

$$\begin{aligned} R_{eq,p} &= \frac{2(V_{DD} - V_{out})}{k_p \left( 2(V_{DD} - |V_{TP}|)(V_{DD} - V_{out}) - (V_{DD} - V_{out})^2 \right)} \\ &= \frac{2}{k_p \left[ 2(V_{DD} - |V_{TP}|) - (V_{DD} - V_{out}) \right]} \end{aligned}$$

## Equivalent Resistance – Region 3

---

- **NMOS cut off:**

$$R_{eq,n} = \infty$$

- **PMOS linear:**

$$R_{eq,p} = \frac{2}{k_p \left[ 2(V_{DD} - |V_{TP}|) - (V_{DD} - V_{out}) \right]}$$




# Transmission Gate Logic

---

- **Useful for multiplexers (select between multiple inputs) and XORs**
- **Transmission gate implements logic function  $F = A$  if  $S$** 
  - If  $S$  is 0, output is floating, which should be avoided
  - Always make sure one path is conducting from input to output
- **Only two transmission gates needed to implement  $A\bar{S} + \bar{A}S$** 
  - Transmission Gate 1:  $A$  if  $\bar{S}$
  - Transmission Gate 2:  $\bar{A}$  if  $S$

# Transmission Gate XOR


---

 

- If  $S = 0$ ,  $F = A$  and when  $S = 1$ ,  $F = \sim A$


# Transmission Gate Multiplexer

---

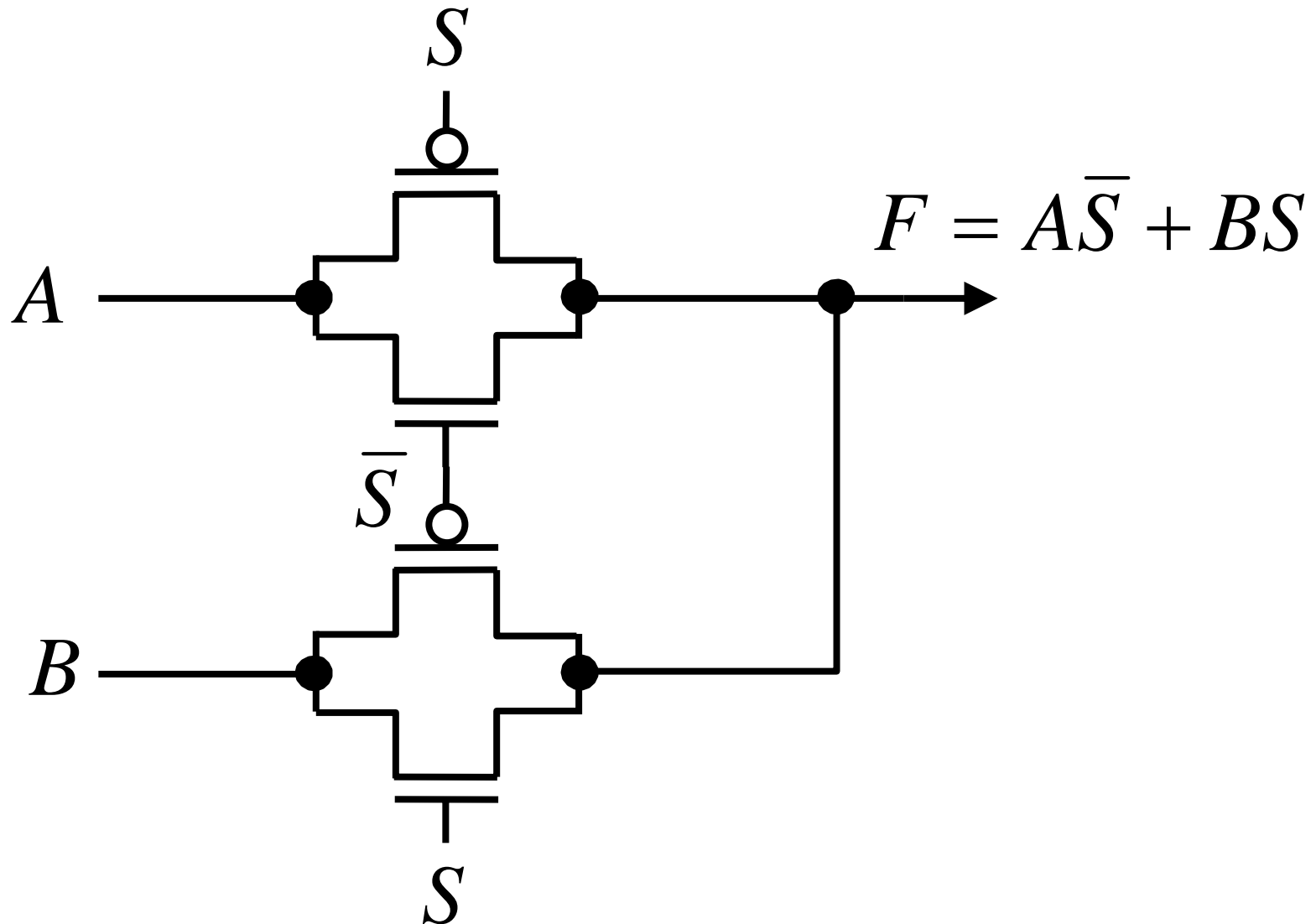

# Full Transmission Gate Logic

---

 

- PMOS devices in parallel with NMOS transistors pass full  $V_{DD}$  (only one logic path shown above)
- Requires more devices, but each can be sized smaller than static CMOS
- Output inverter reduces impact of fanout

# Next Topic: Dynamic Circuits

---

- **Extend dynamic sequential circuit idea to logic circuits**
  - Improved speed
  - Reduced area
  - Challenging to design: timing and noise issues, charge sharing, leakage
  - Preferred design style for high performance circuits