

EEC 118 Lecture #12: Dynamic Logic


**Rajeevan Amirtharajah
University of California, Davis**

**Jeff Parkhurst
Intel Corporation**

Outline


- **Today: Alternative MOS Logic Styles**
- **Dynamic MOS Logic Circuits: Rabaey 6.3 (Kang & Leblebici, 9.4-9.6)**

Review: Transmission Gate XOR

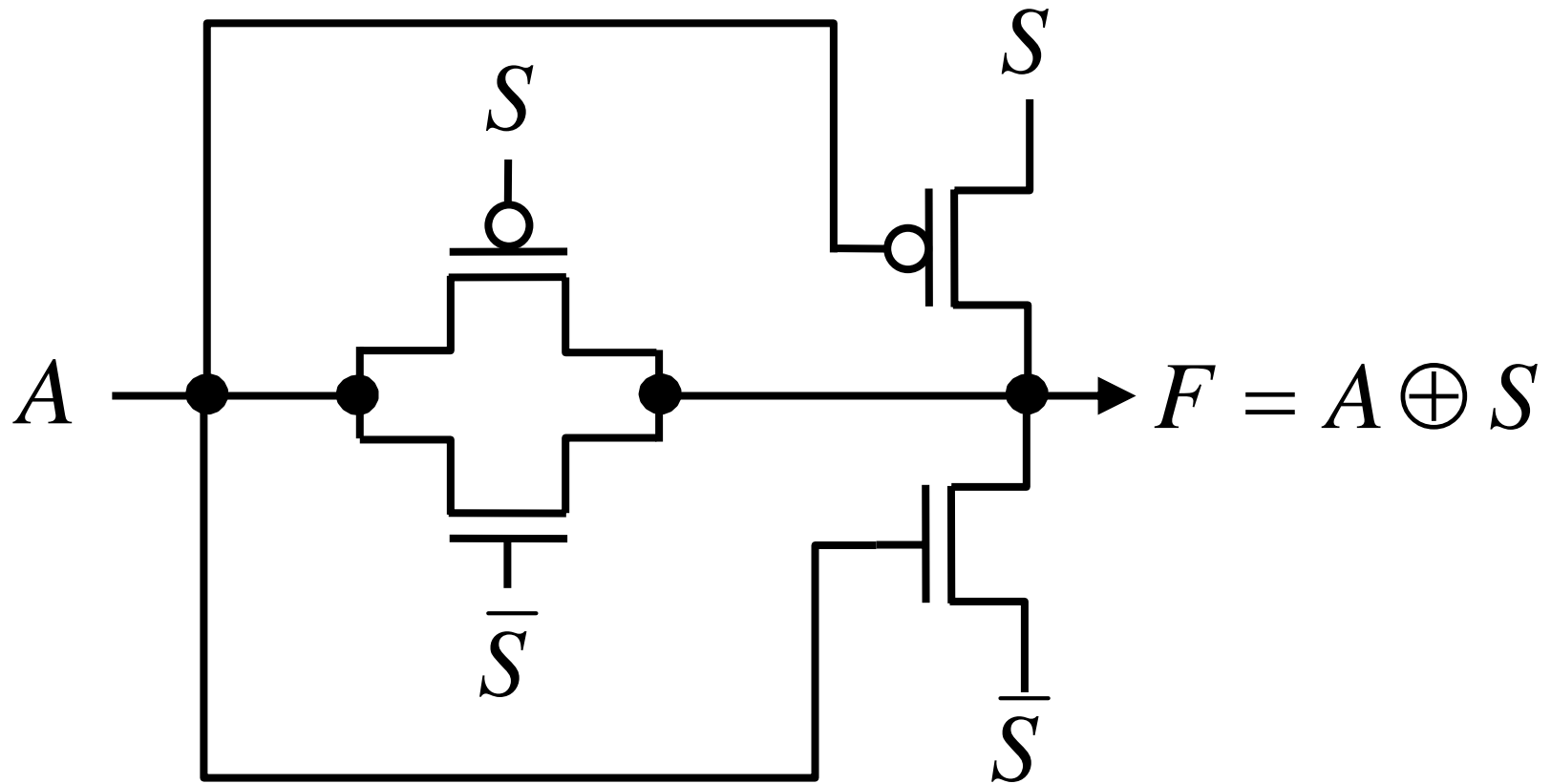


- If $S = 0$, $F = A$ and when $S = 1$, $F = \sim A$

Review: Transmission Gate Multiplexer

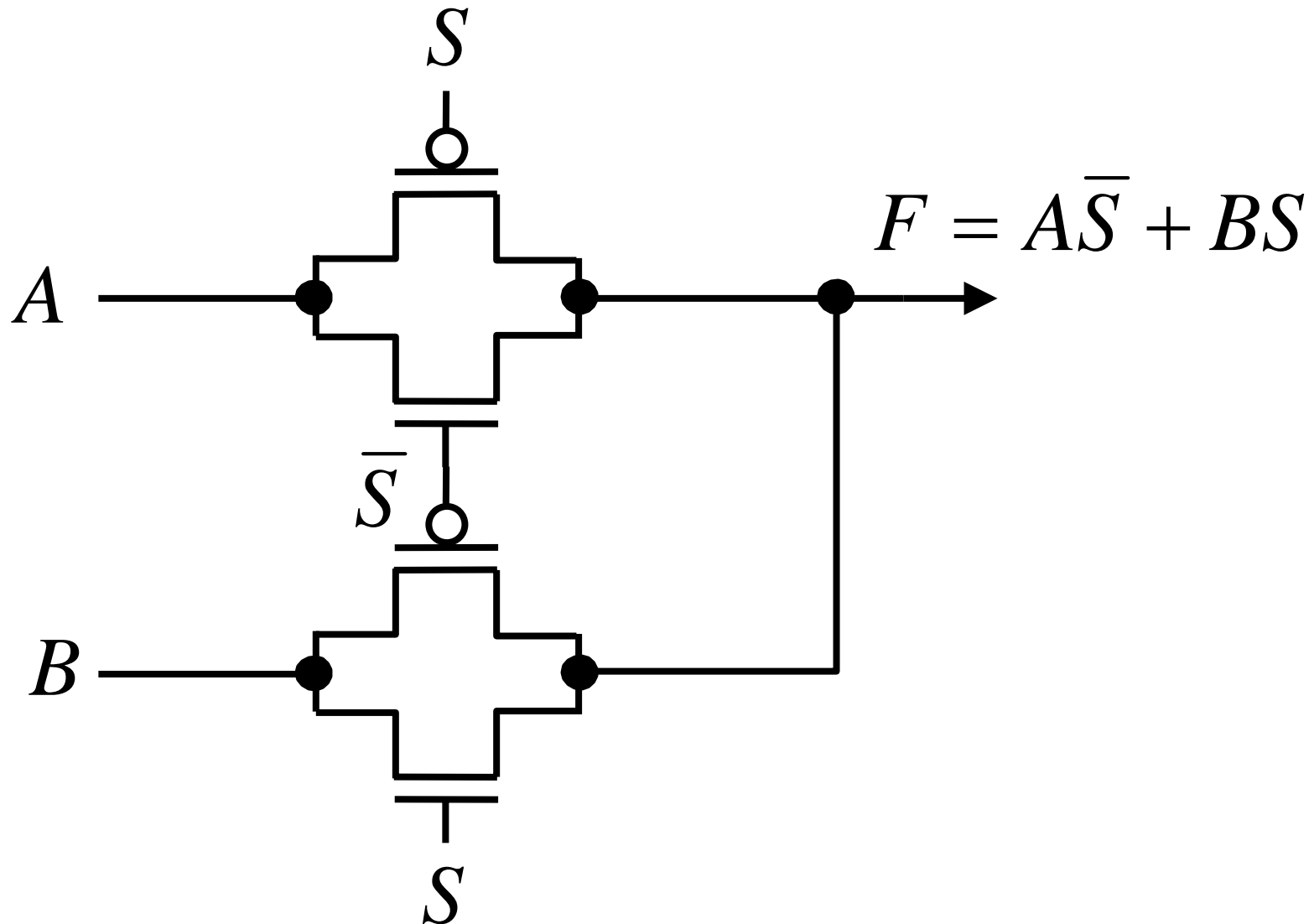

Dynamic CMOS

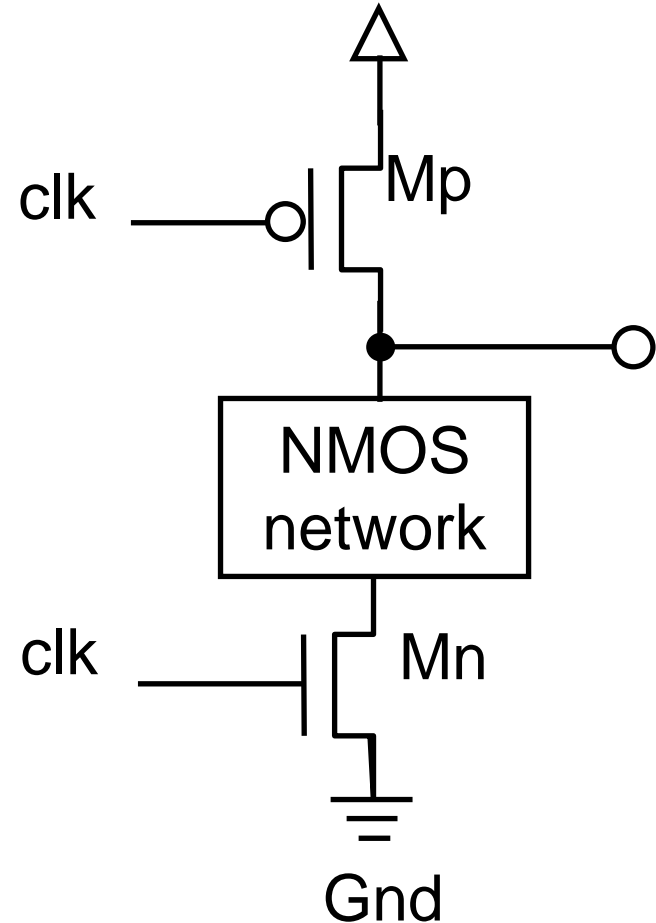
- **Operation**
 - Clk low during Pre-charge
 - Mp is on while Mn is off
 - Output charged to Vdd
 - Clk high during evaluate
 - Mn is on while Mp is off
 - Output pulled down according to PDN function
- **PDN design same as static CMOS**



Dynamic CMOS Tradeoffs

- **Advantages:**

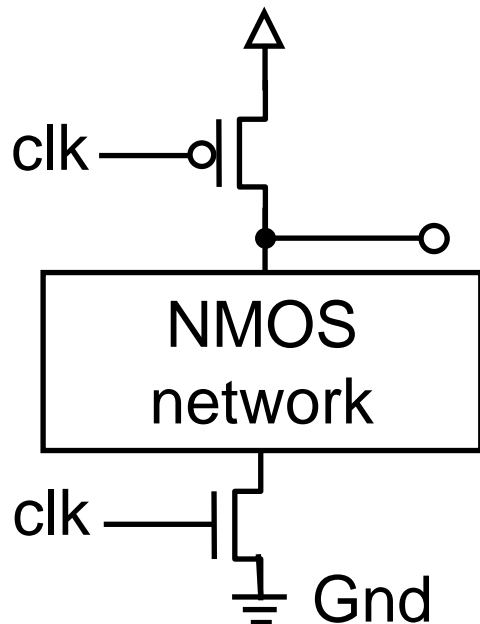
- Faster – why?
 - Reduced input load
 - No switching contention
- Less layout area



- **Disadvantages:**

- Multiple stage issues
- Charge leakage
- Charge sharing
- Capacitive coupling
- Cannot be cascaded
- Complicated timing/clocking
- Higher power
- Lower noise margins
- Does not scale well with process

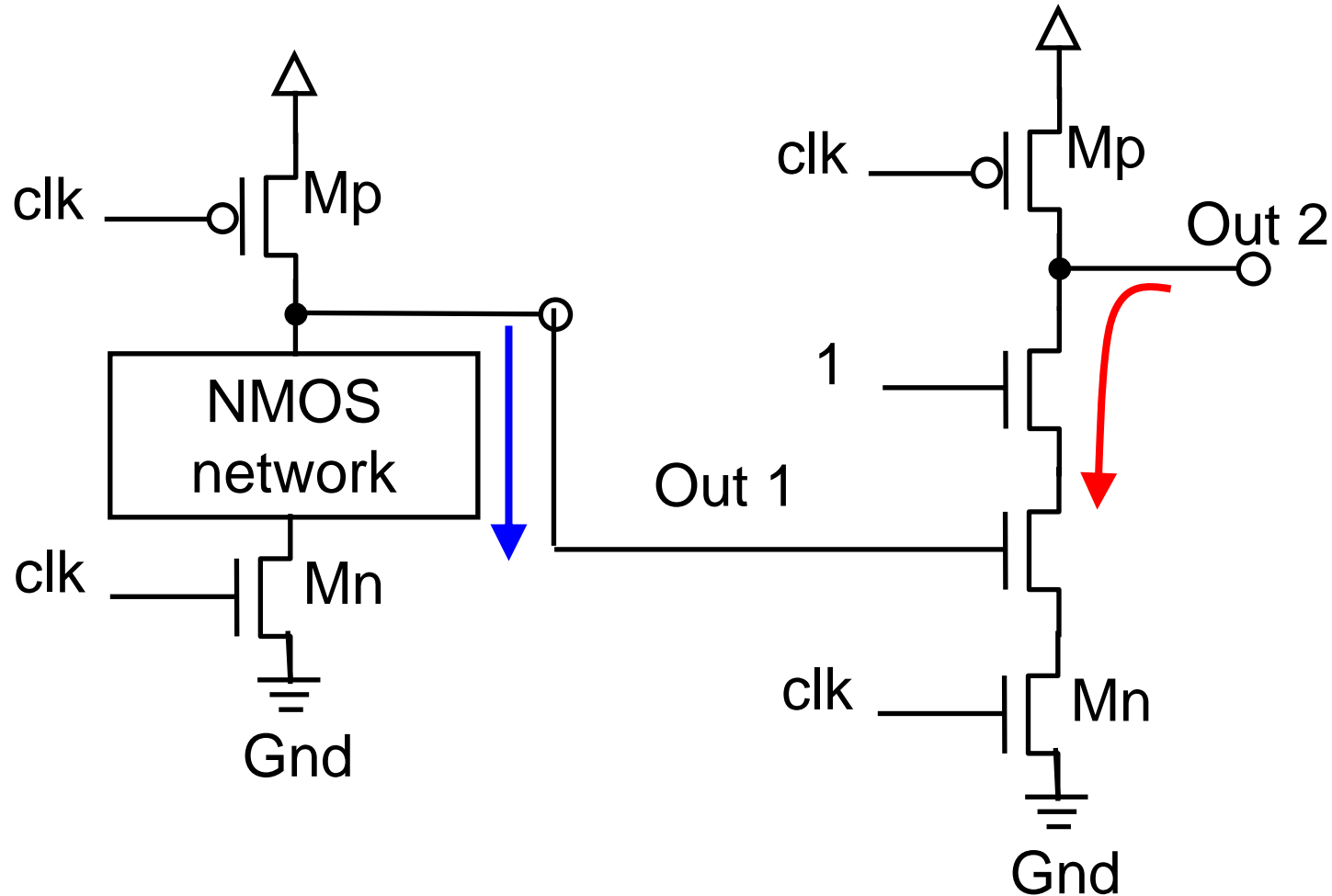Multiple Stage Issue: Output Discharge Race



- **During pre-charge stage, inputs to second gate are all high: Out 2 could discharge before Out 1 discharges**


Cascading Multiple Stages

- During pre-charge stage, inputs to second gate are all high
 - At the beginning of evaluate stage, Out 2 is discharged.
 - Out 1 goes through its evaluation stage concurrently and goes low
 - Hence out 2 was supposed to be high, but already discharged.
 - Dynamic logic driven by the same clock cannot *be cascaded directly*

Charge Sharing

- Output is floating after $\text{clk} = '1'$ if inputs are $'0'$
- If upper transistors in a stack switch, the intermediate and output node voltages will be equalized, possibly leading to a drop in the output voltage = noise
- Final output (initial charge distributed over both capacitors):
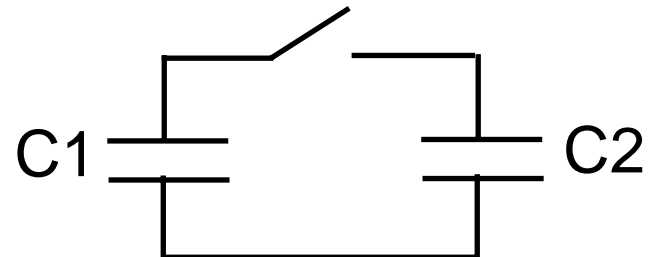
$$V = (C_1 V_1 + C_2 V_2) / (C_1 + C_2)$$




Charge Leakage & Capacitive Coupling

- **Output is floating after $\text{clk} = '1'$ if inputs are $'0'$**
- **Since the current is not 0 when transistors are in cutoff, current can leak charge away from the output when all inputs are $'0'$**
- **Changes in input signals couple to the output and intermediate nodes, also resulting in voltage drops**

Noise Solutions

- **Charge sharing:**
 - Ensure the output capacitance is large enough such that the voltage drop is minimal
 - Precharge internal stack nodes to V_{DD}
 - Pre-discharging internal stack nodes can increase performance, but worsens noise
- **Charge leakage/sharing and capacitive coupling:**
 - Add a keeper PMOS (weak P pullup) – increased evaluation contention

Domino Logic

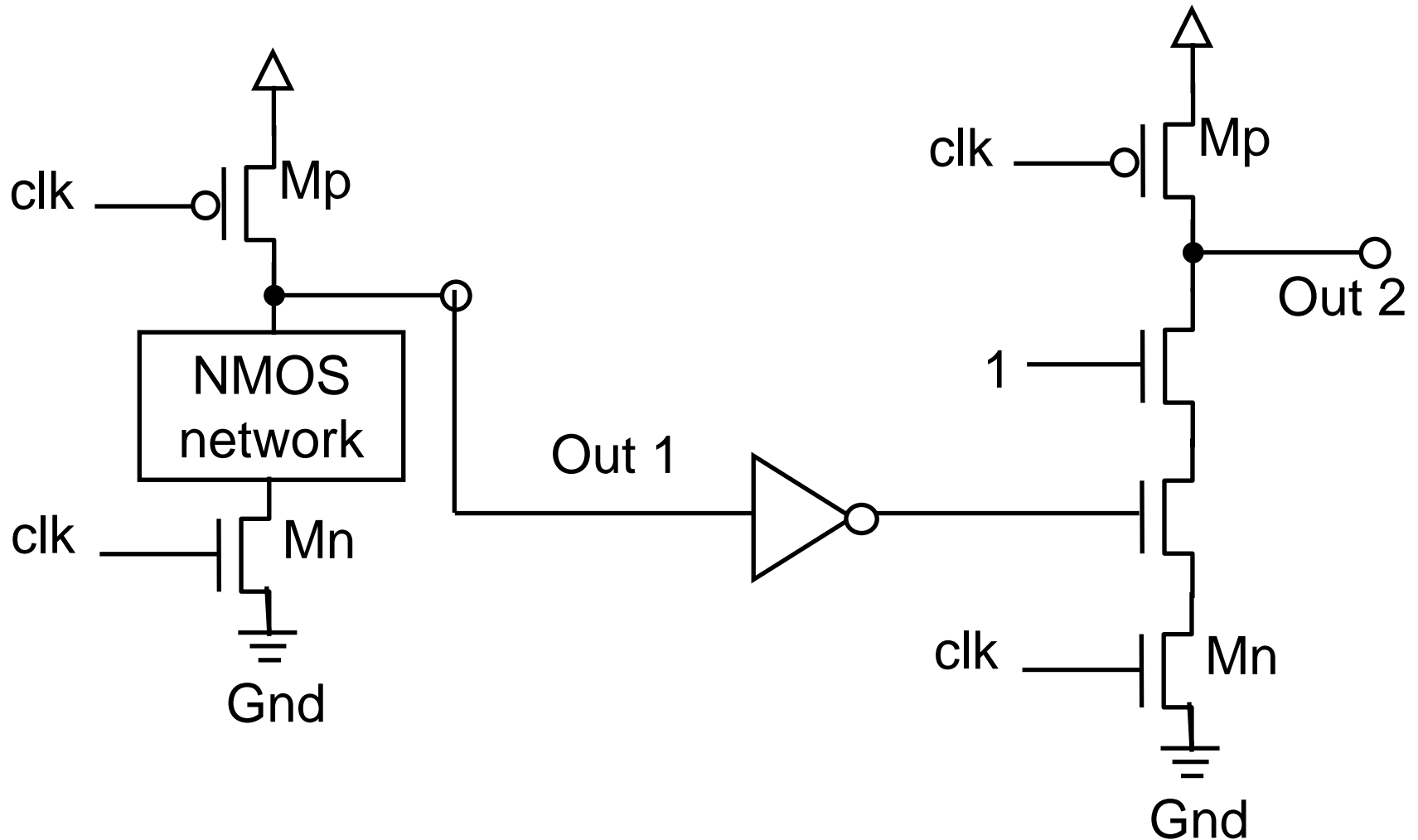

Domino Logic

- **Add an inverter between dynamic gates**
 - Inverter drives the gate's fanout – increased performance
- **Sometimes the inverter is replaced with a more complex static CMOS gate**
 - Incorporates more logic per stage to improve speed
- **Static CMOS gate improves overall circuit dynamic noise margins**

Cascading Domino


- **For gates with all inputs coming from other domino gates, the bottom NMOS transistor can be eliminated**
 - Why? All inputs will be '0' during precharge and can only transition from '0' to '1' during evaluate due to inverter between stages...
 - Results in increased performance due to decreased stack height
 - Precharge now depends on input precharge time

Dynamic Logic Power

- **Power depends upon switching activity**
 - Switching activity depends upon the probability of a ‘1’ input
- $$P_{avg} = \frac{1}{T} C_{load} V_{DD}^2 = C_{load} V_{DD}^2 f$$
- Effective capacitance C_{load} is doubled when the gate evaluates because the gate must later precharge
 - Frequency must be multiplied by the probability that an evaluation will occur
- **Power is usually higher for domino logic except when it replaces prior logic with very high activity factors**

Bottom Line

- **Tradeoff between performance and power exists**
- **Many things can go wrong from a design standpoint (high risk)**
 - Charge sharing, noise, leakage currents, race conditions
- **Debugging challenge, especially in deep submicron**
 - Leakage currents put lower bound on clock frequency for testing
- **Best to use dynamic logic only when necessary**
 - High performance circuits such as microprocessor critical paths

 

NORA Logic

- **Solves problem of cascading dynamic gates, but is vulnerable to noise**
 - Alternate P-dynamic and N-dynamic stages
 - Both clk and $\overline{\text{clk}}$ required
 - Lose some of the speed benefits due to added PUNs

Zipper Logic

- **Like NORA logic...but,**
 - PMOS precharge and NMOS pre-discharge weakly on during evaluation stage...

Variations on the Domino Theme


- **Multiple-Output Domino**

- Exploit situation when certain outputs are subsets of other outputs to reduce area
- Precharge intermediate nodes in PDN and follow with inverters to drive other N-block dynamic gates


- **Compound Domino**

- Use complex static CMOS gates (NANDs, NORs) on outputs of multiple dynamic gates in parallel
- Replaces large fanin domino gates with lower fanin gates
- Capacitive coupling from static gate outputs to dynamic gate outputs an issue

Multiple Output Domino CMOS Logic

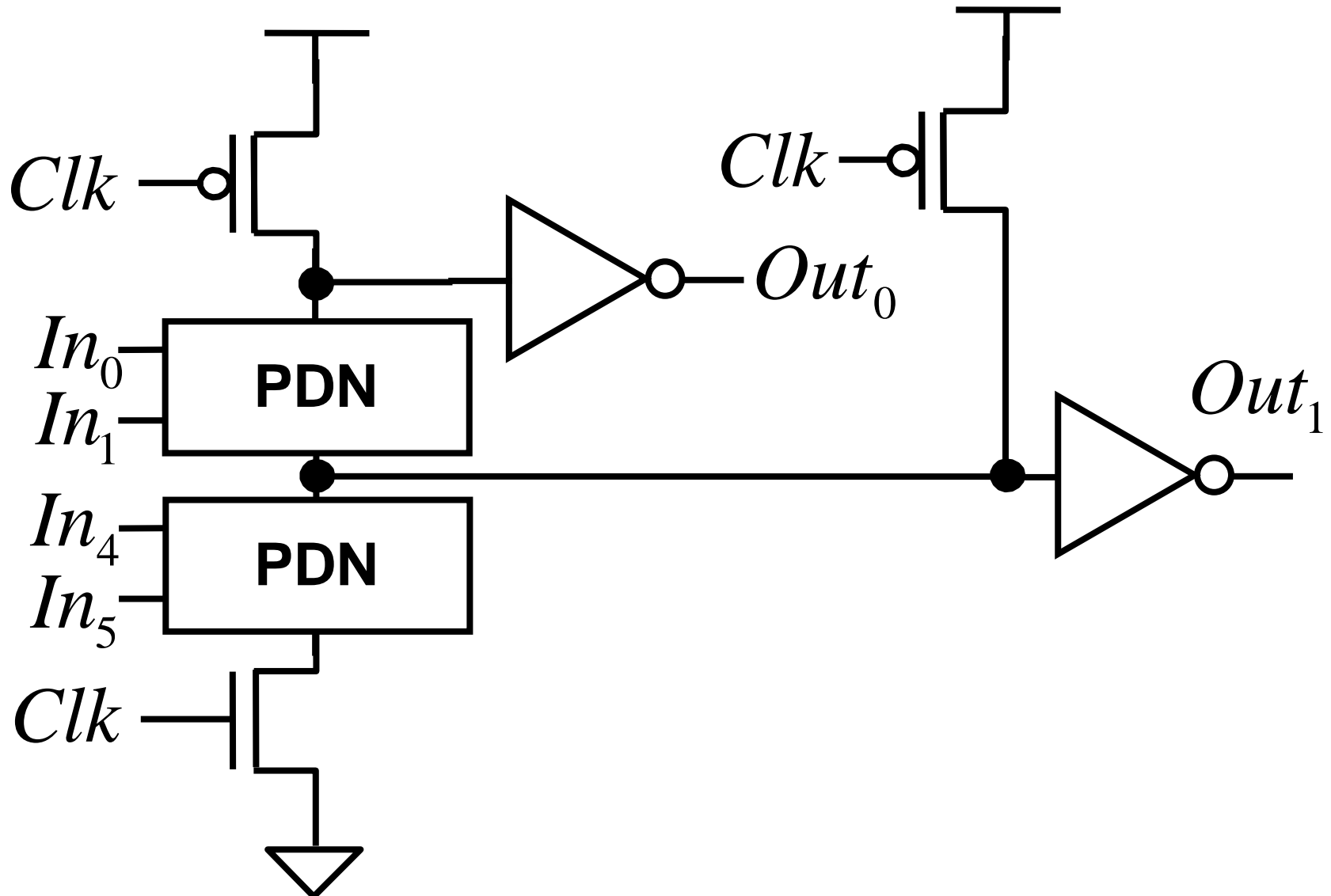

Compound Domino CMOS Logic

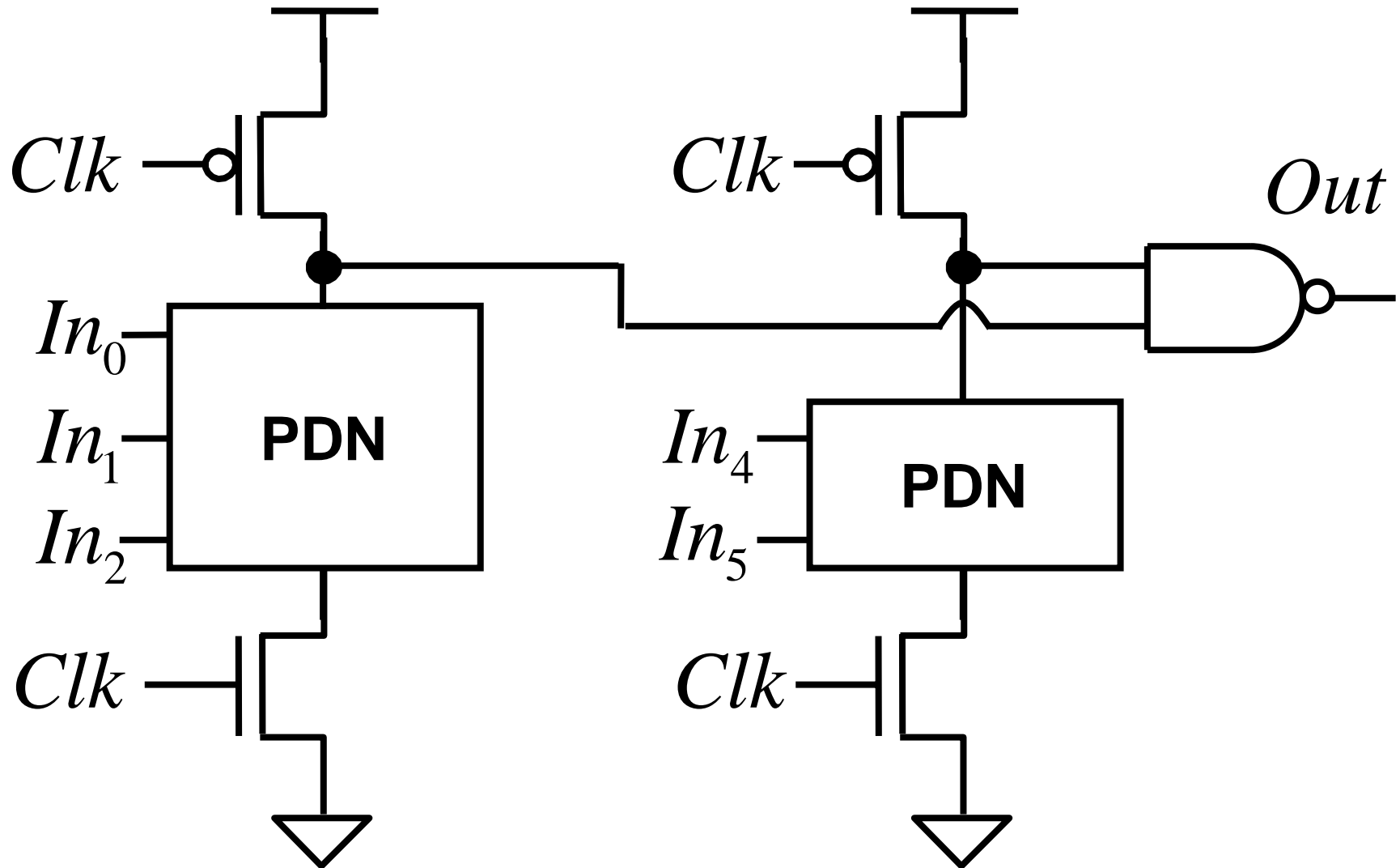

Next Topic: Memories

- **Memory principles and circuits**
 - ROM: Read Only Memory
 - RWM (Read/Write Memory) or RAM (Random Access Memory)
 - DRAM, SRAM
 - Nonvolatile memories (Flash, PROM, EEPROM)