 


---

# Arithmetic Building Blocks

## Chapter 11 Rabaey




# Announcements

---

- Today: wrap up dynamic circuits, start discussing arithmetic circuits
- Homework 6 – due next Monday
- Lab 5 (simulation) – starts this week
- Midterms handed back on Wednesday

# A Generic Digital Processor

 

# Building Blocks for Digital Architectures

---

## **Datapath (Arithmetic Unit)**

- Bit-sliced datapath (adder , multiplier, shifter, comparator, etc.)

## **Memory**

- RAM, ROM, Buffers, Shift registers


## **Control**

- Finite state machine (PLA, random logic.)
- Counters

## **Interconnect**


- Switches
- Arbiters
- Bus

# Bit-Sliced Design

 


**Tile identical processing elements**

# Full Adder

 

$A$	$B$	$C_i$	$S$	$C_o$	<i>Carry status</i>
0	0	0	0	0	delete
0	0	1	1	0	delete
0	1	0	1	0	propagate
0	1	1	0	1	propagate
1	0	0	1	0	propagate
1	0	1	0	1	propagate
1	1	0	0	1	generate
1	1	1	1	1	generate

# The Binary Adder

 


$$S = A \oplus B \oplus C_i$$

$$= A\bar{B}\bar{C}_i + \bar{A}B\bar{C}_i + \bar{A}\bar{B}C_i + ABC_i$$

$$C_o = AB + BC_i + AC_i$$

# The Ripple-Carry Adder

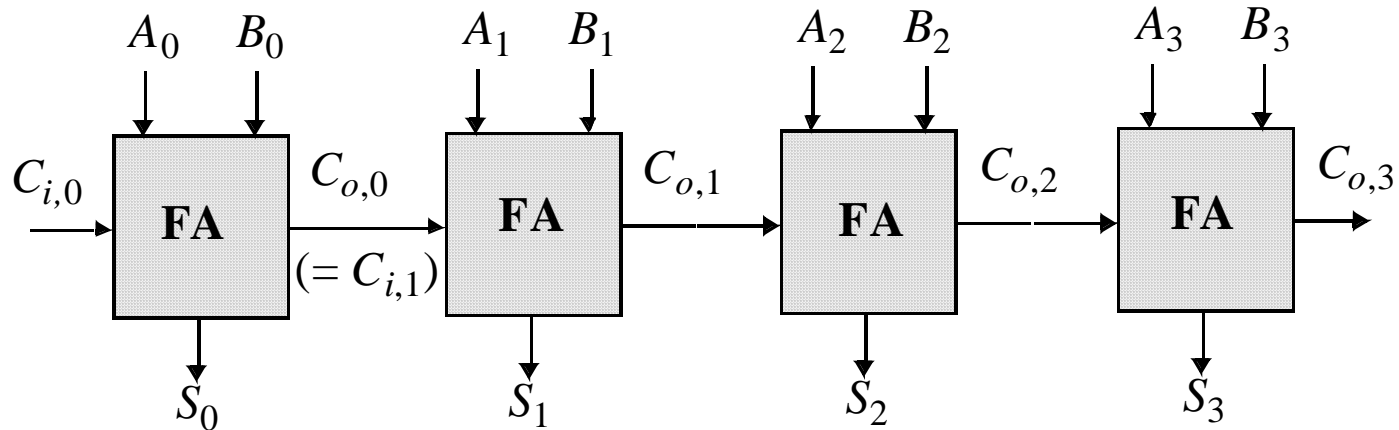

**Worst case delay linear with the number of bits**


$$t_d = O(N)$$

$$t_{\text{adder}} \approx (N - 1)t_{\text{carry}} + t_{\text{sum}}$$

**Goal: Make the fastest possible carry path circuit**



# Complimentary Static CMOS Full Adder

 


**28 Transistors**

Arithmetic
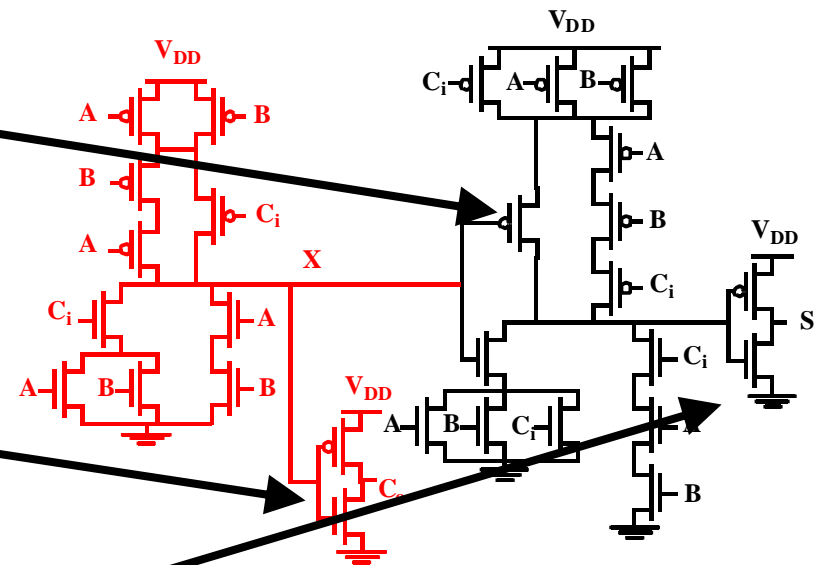
# A Closer Look

- Drawbacks

- » Tall PMOS Stack
  - Slows down circuit
- »  $C_o$  load is 2 diffusion and 6 gate capacitances
- »  $C_i$  goes through the extra output inverter to  $C_o$ 
  - Could optimize with next stage
- » Sum generation has extra inverter on output
  - Not the critical path




28 Transistors

- Positive

- »  $C_i$  closest to output node


# Inversion Property

 

$$\bar{S}(A, B, C_i) = S(\bar{A}, \bar{B}, \bar{C}_i)$$

$$\bar{C}_o(A, B, C_i) = C_o(\bar{A}, \bar{B}, \bar{C}_i)$$

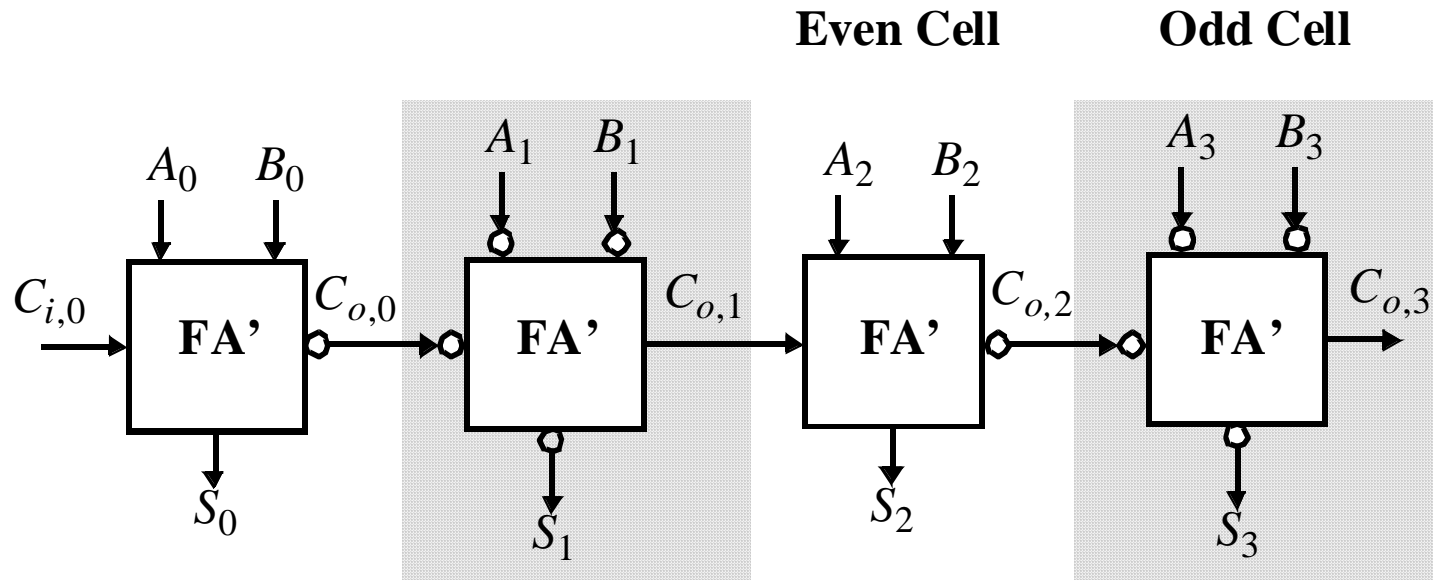
# Minimize Critical Path by Reducing Inverting Stages



**Exploit Inversion Property**

**Note: need 2 different types of cells**

# Applying Inversion Property

 

With the next stage, invert  $\bar{A}$  and  $\bar{B}$ . You will get as outputs  $S$  and  $C$ ...so take away inverters on these outputs.

# Express Sum and Carry as Function of P, G, D

Define 3 new variable which ONLY depend on A, B

**Generate (G) = AB**  $C_0 = 1$  if  $G = 1$

**Propagate (P) = A  $\oplus$  B**  $C_0 = C_i$  if  $P = 1$

**Delete =  $\bar{A} \bar{B}$**   $C_0 = 0$  if  $D = 1$


$$C_o(G, P) = G + PC_i$$

$$S(G, P) = P \oplus C_i$$

A	B	$C_i$	S	$C_o$	Carry status
0	0	0	0	0	delete
0	0	1	1	0	delete
0	1	0	1	0	propagate
0	1	1	0	1	propagate
1	0	0	1	0	propagate
1	0	1	0	1	propagate
1	1	0	0	1	generate
1	1	1	1	1	generate

Can also derive expressions for S and  $C_o$  based on  $D$  and  $P$

# A Better Structure: the Mirror Adder

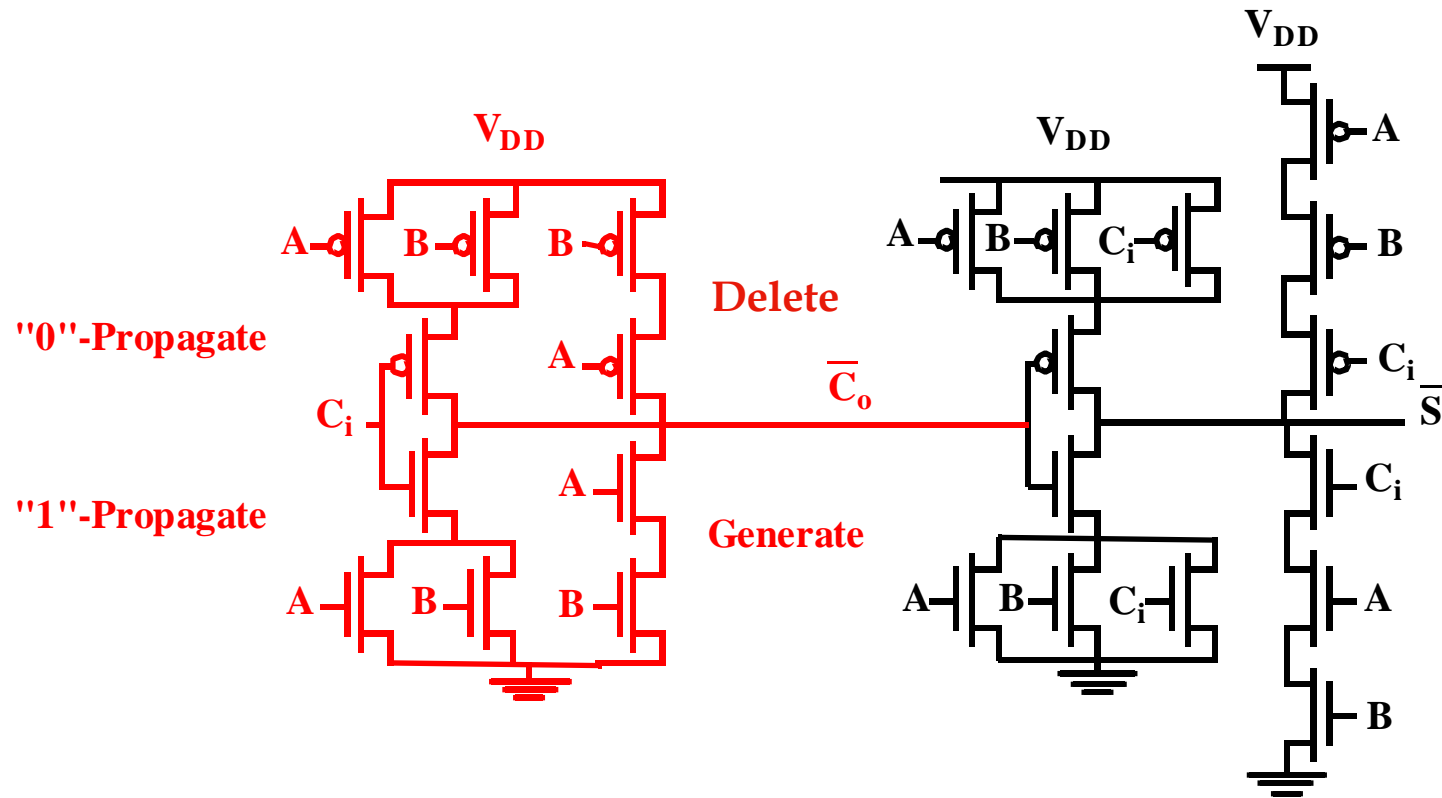

24 transistors

# The Mirror Adder I

- The NMOS and PMOS chains are **completely symmetrical**. This guarantees identical rising and falling transitions if the NMOS and PMOS devices are properly sized. A maximum of two series transistors can be observed in the carry-generation circuitry.
- When laying out the cell, the most critical issue is the minimization of the capacitance at node  $C_o$ . The reduction of the diffusion capacitances is particularly important.
- The capacitance at node  $C_o$  is composed of four diffusion capacitances, two internal gate capacitances, and six gate capacitances in the connecting adder cell .



# The Mirror Adder II

---


- The transistors connected to  $C_i$  are placed closest to the output.
  - Fastest for late arriving inputs,  $C_i$  tends to arrive late
- Only the transistors in the carry stage have to be optimized for optimal speed. All transistors in the sum stage can be minimal size.

# Adder Architectures

---


- In addition to optimizing each full adder cell and exploiting inversion property, we can also reorganize the add computation to speed things up
- Basic idea is to overlap propagating the carry with computing the Propagate and Generate functions
- Discuss three basic architectures
  - Carry-Bypass
  - Carry-Select
  - Carry-Lookahead

# Carry-Bypass Adder

 


Idea: If ( $P_0$  and  $P_1$  and  $P_2$  and  $P_3 = 1$ )  
then  $C_{o,3} = C_{i,0}$ , else “kill” or “generate”.

# Carry-Bypass Adder (cont.)

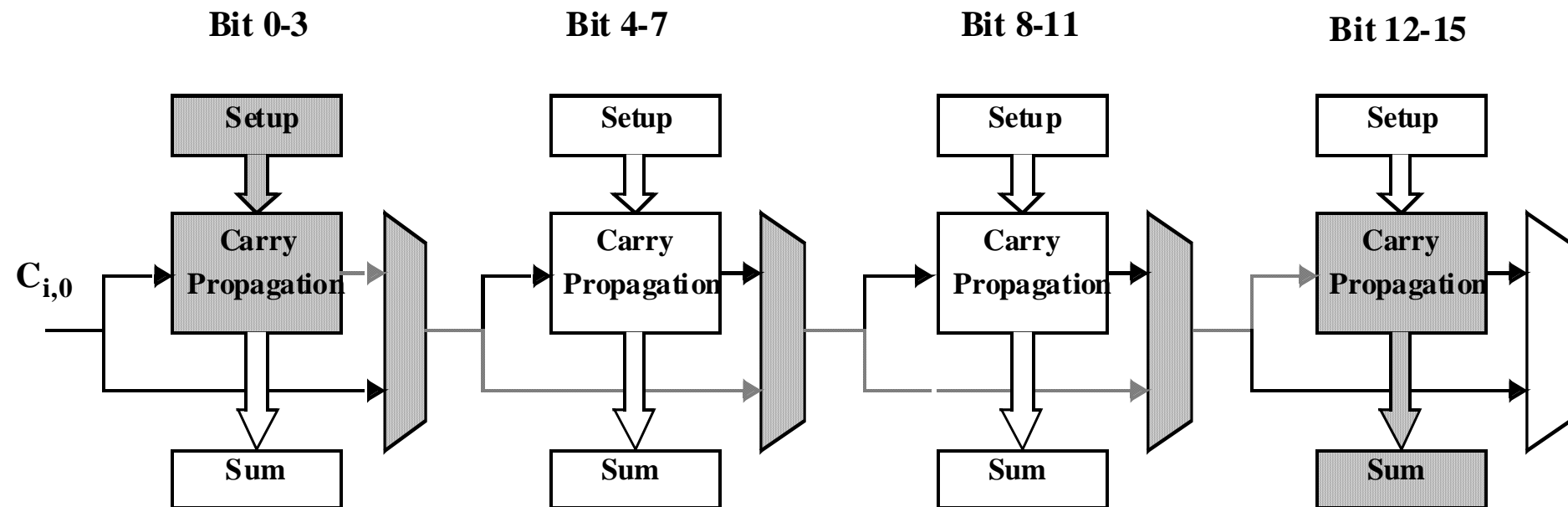


**Note that this is done at the expense of a MUX in the carry delay path !!**

# Carry Ripple vs. Carry Bypass

 


**Essentially greater than 4 bits is needed to overcome the overhead of the MUX**


# Carry-Select Adder

 

# Carry Select Adder: Critical Path

 

# Linear Carry Select

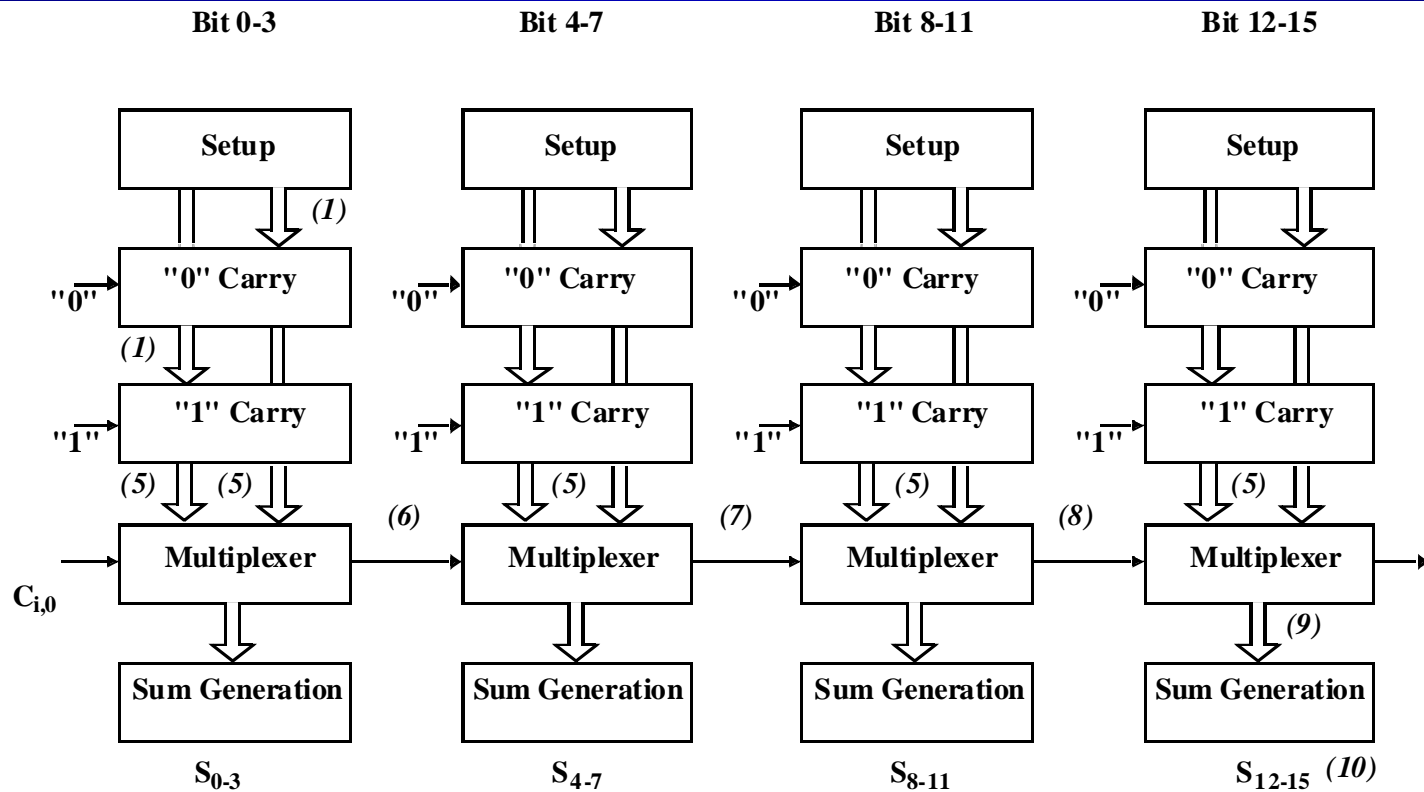

$$t_{add} = t_{setup} + \left(\frac{N}{M}\right)t_{carry} + Mt_{mux} + t_{sum}$$




# Carry-Select Adder Observations

---


- The inputs to the final multiplexer are steady long before the Mux select ( $C_i$ ) arrives
  - » Path is the same as is the number of bits
- Would be helpful to try and even out the delays so that the critical path is balanced between inputs and Mux select.
  - » Make logic simpler with the least significant bits by reducing the number of bits handled in the FA or half adder (HA). HA is FA without  $C_i$  (2 ins, 2 outs)
  - » Add bits progressively as you move to the MSB

# Square Root Carry Select

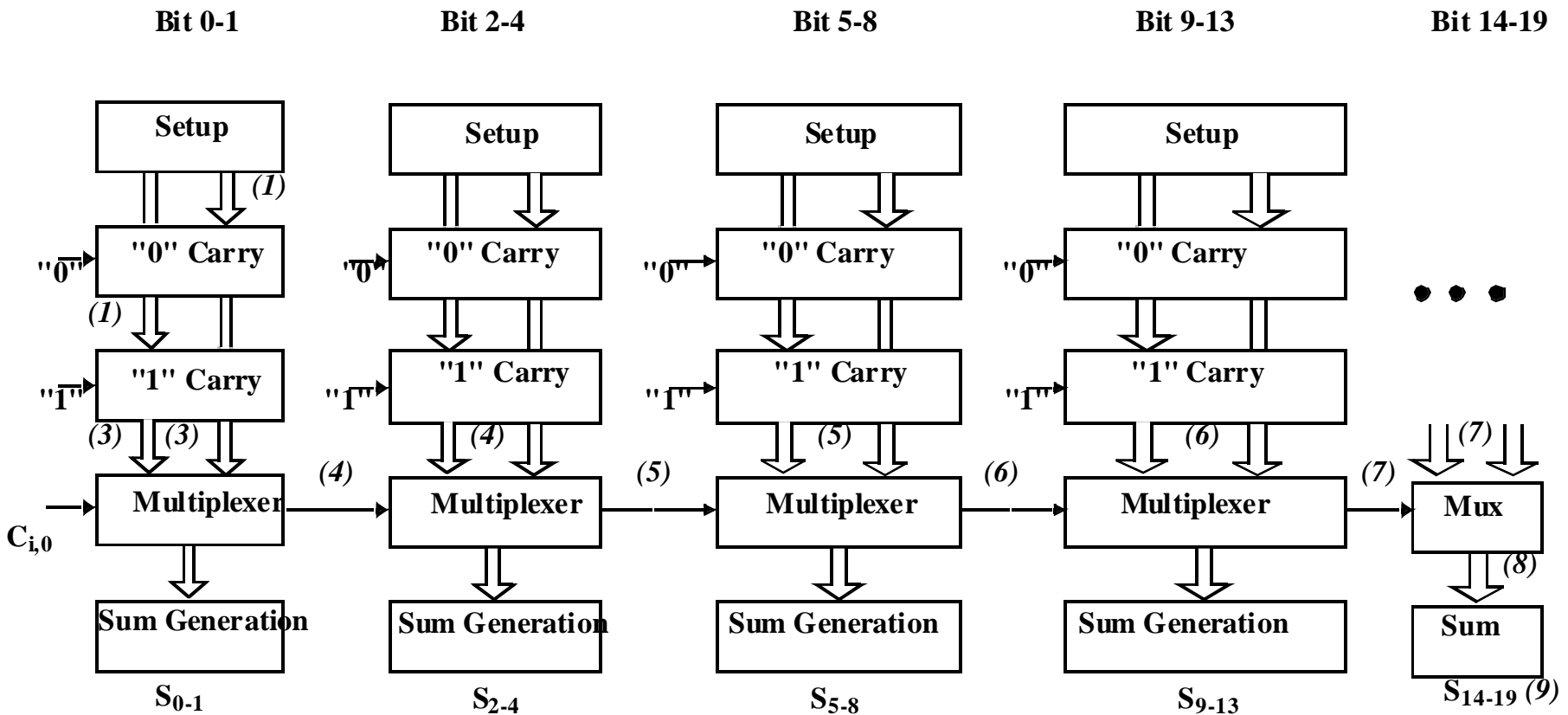


$$t_{add} = t_{setup} + P \cdot t_{carry} + (\sqrt{2N})t_{mux} + t_{sum}$$


# Adder Delays: Comparison

 

# Carry Look Ahead: Basic Idea

 

# Look-Ahead: Topology

 

- **No more than  $N = 4$  bits**
- **Delay still increases linearly with number of bits**
- **Capacitance, resistance too high for  $N > 4$**

# Binary Multiplication

$$\begin{aligned} Z &= \mathbf{X} \times \mathbf{Y} = \sum_{k=0}^{M+N-1} Z_k 2^k \\ &= \left( \sum_{i=0}^{M-1} X_i 2^i \right) \left( \sum_{j=0}^{N-1} Y_j 2^j \right) \\ &= \sum_{i=0}^{M-1} \left( \sum_{j=0}^{N-1} X_i Y_j 2^{i+j} \right) \end{aligned}$$

**with**

$$\begin{aligned} \mathbf{X} &= \sum_{i=0}^{M-1} X_i 2^i \\ \mathbf{Y} &= \sum_{j=0}^{N-1} Y_j 2^j \end{aligned}$$

# Binary Multiplication


$$\begin{array}{r} \phantom{\times} \phantom{10} 101010 \\ \times \phantom{10} \phantom{10} 1011 \\ \hline \phantom{10} 101010 \\ \phantom{10} 101010 \\ \phantom{10} 000000 \\ \phantom{10} 101010 \\ \hline 111001110 \end{array}$$

**AND operation**

**Partial Products**


The diagram illustrates the binary multiplication of 101010 and 1011. The first step is the AND operation, which produces four partial products: 101010, 101010, 000000, and 101010. These are then summed to produce the final product, 111001110. The partial products are highlighted with a grey background, and an arrow points from the label 'AND operation' to the first partial product.

# The Array Multiplier

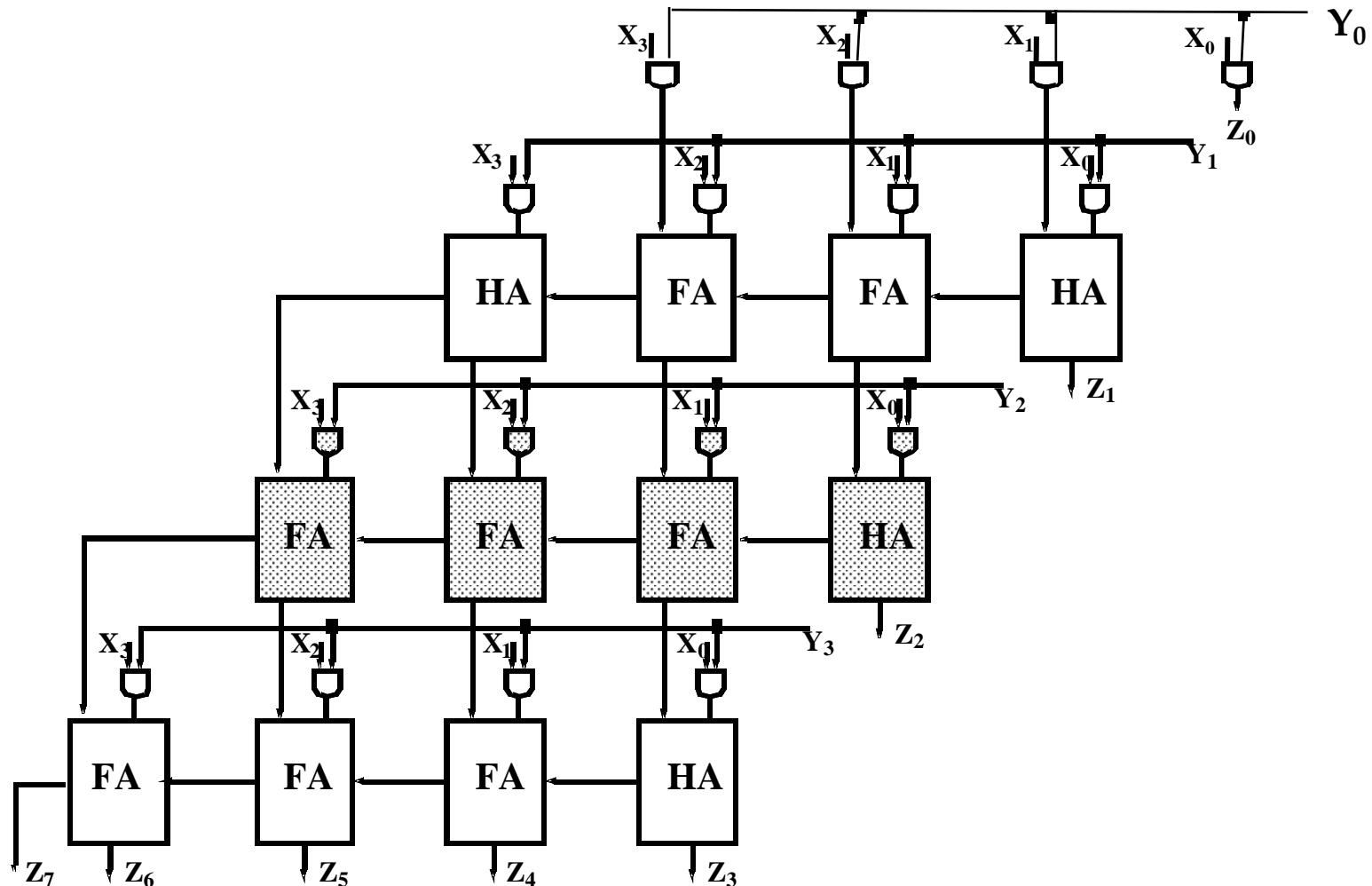





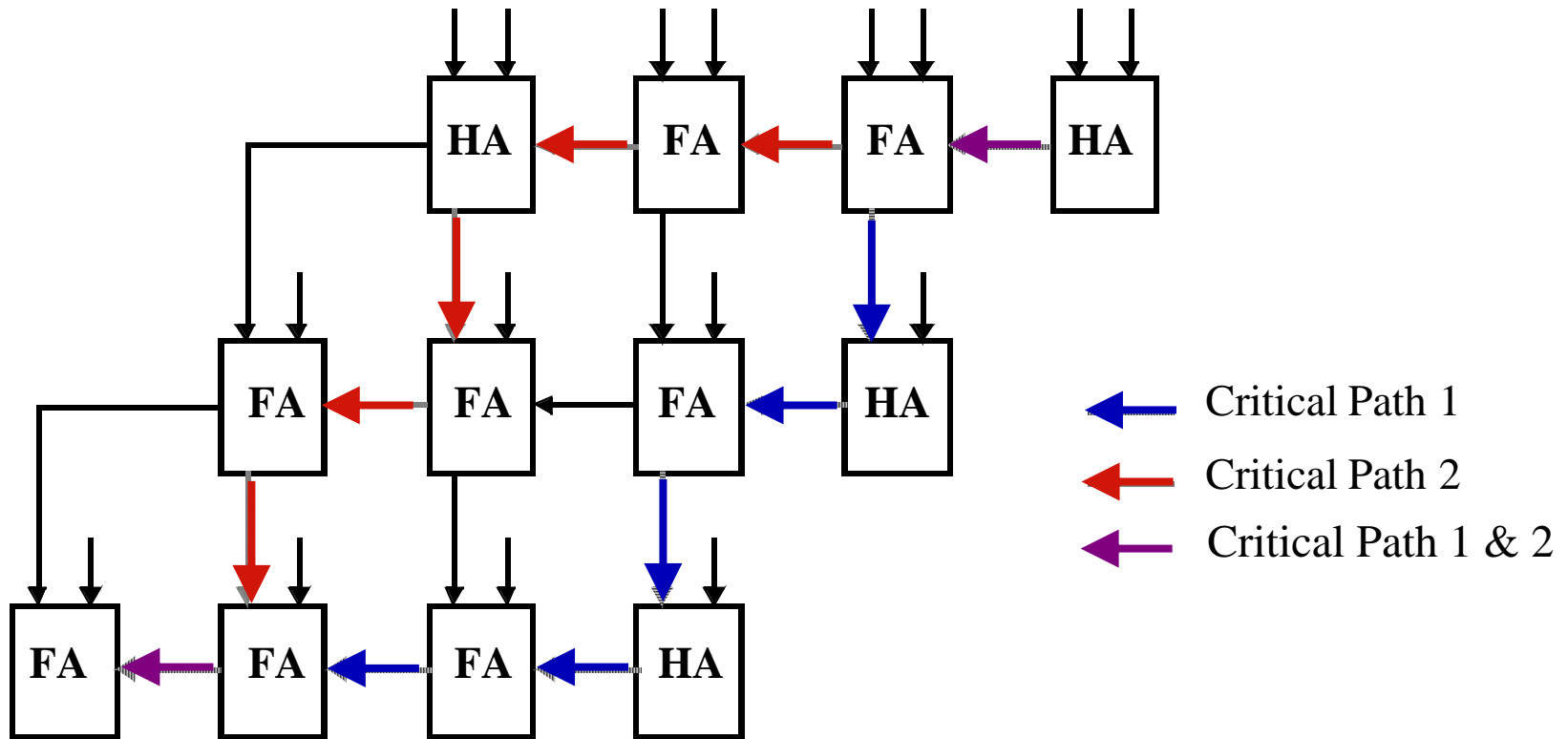
# The MxN Array Multiplier: Critical Path




$$t_{mult} \approx [(M-1) + (N-2)]t_{carry} + (N-1)t_{sum} + t_{and}$$

# Adder Cells in Array Multiplier

   

**Identical Delays for Carry and Sum**

# Multiplier Floorplan

 


# Array Multiplier Reflections

---

- Many equal critical paths
  - » Very hard to optimize by transistor sizing
- We could pass the carry bits diagonally down instead of across
  - » Output does not change
  - » Need to add an extra stage to accommodate this

# Carry Save Multiplier

 


Vector Merging Adder

$$t_{mult} = (N - 1)t_{carry} + t_{and} + t_{merge}$$
 
# The Tree Multiplier


- Note that the partial products layout looks as follows:



- Note that we can rearrange and add the partial products differently
- Reduce number of adder circuits and logic depth
- FA compresses  $3b$  to  $2b$ , HA has  $2b$  in and  $2b$  out


# Tree Multiplier

- Re arranging

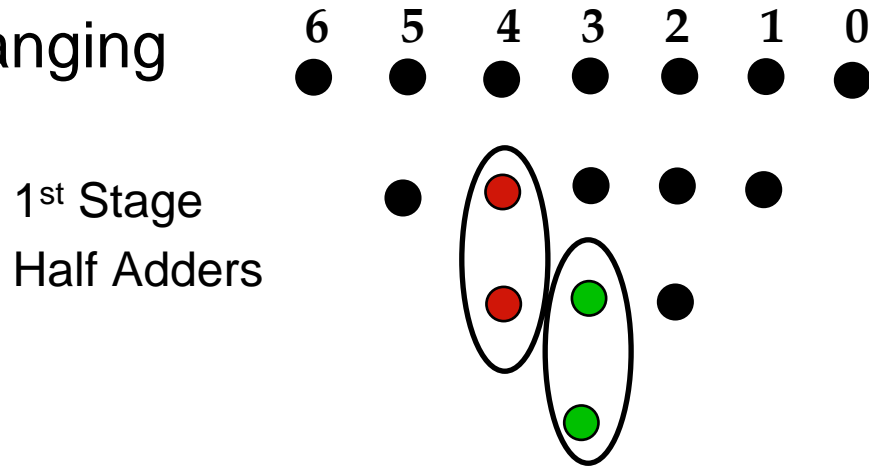

# Tree Multiplier


- Re arranging

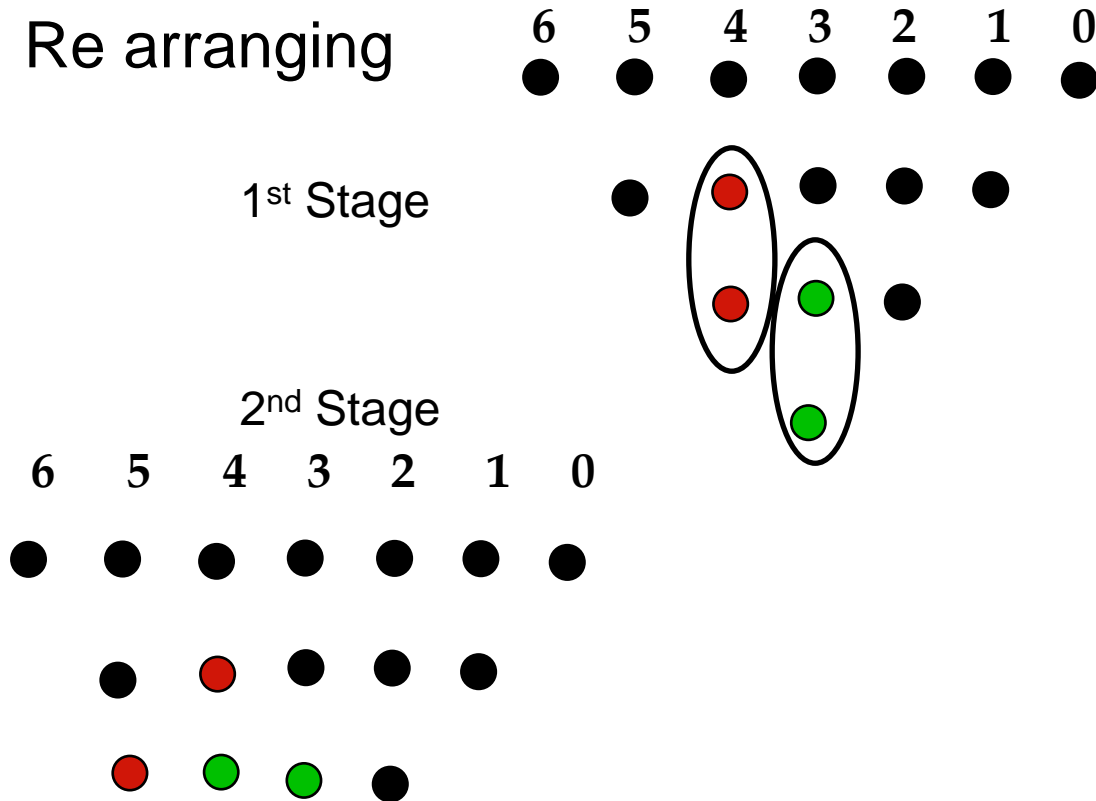




# Tree Multiplier

- Re arranging

 


# Tree Multiplier

- Re arranging

 


# Tree Multiplier

- Re arranging

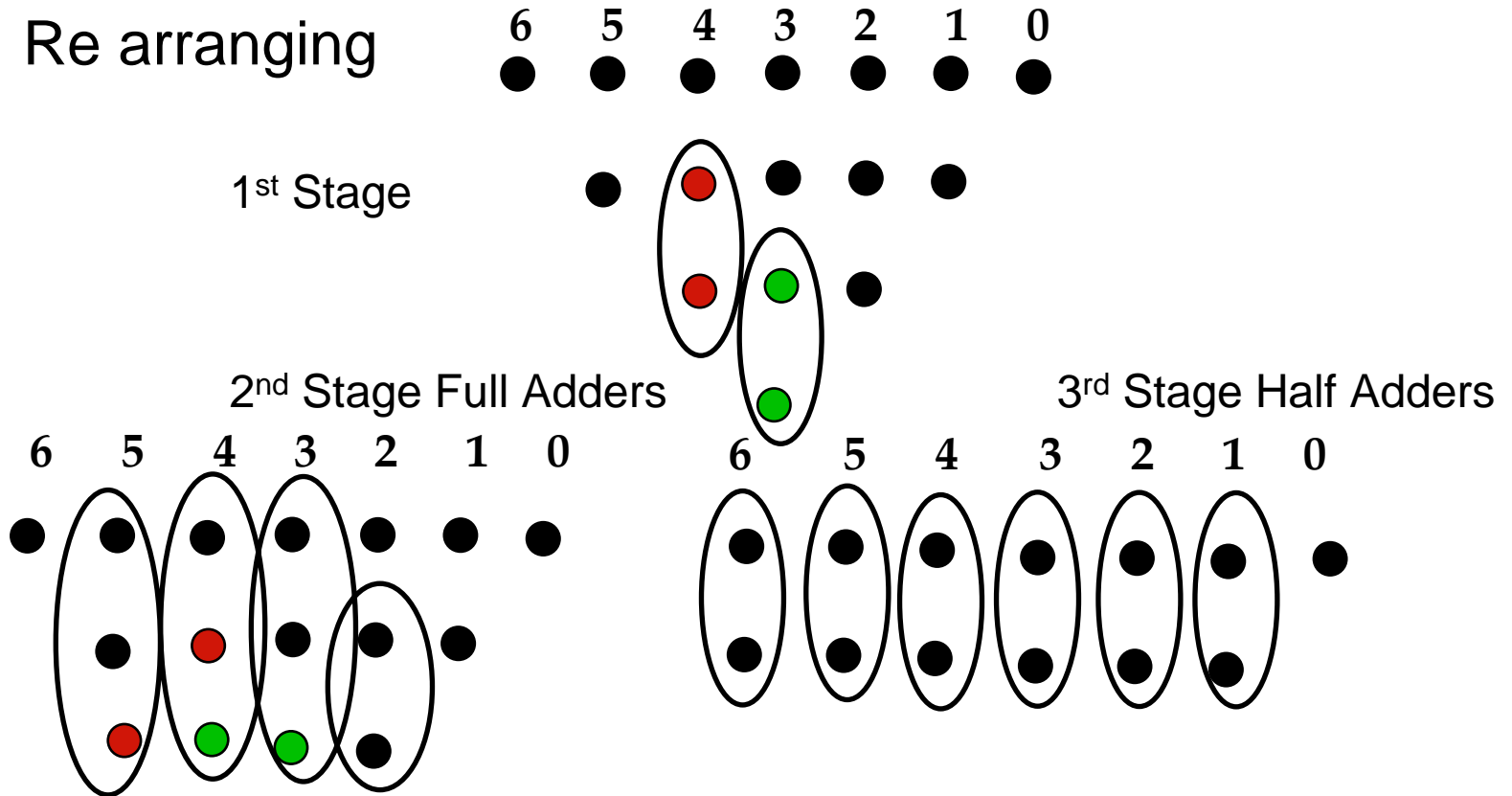

# Wallace-Tree Multiplier

 

# Multipliers: Summary

---

- Optimization goals different than Adder
  - » Identify critical path
  - » More system level optimization than individual cell optimization