

# **EEC 118 Lecture #4: CMOS Inverters**

**Rajeevan Amirtharajah**  
**University of California, Davis**  
**Jeff Parkhurst**  
**Intel Corporation**

# Announcements

---

- **Lab 2 this week, report due next week**
- **Lab 1 reports due this week at lab section**
- **HW 2 due this Friday at 4 PM in box, Kemper 2131**


# Outline

---

- **Review: Inverter Transfer Characteristics**
- **Lecture 3: Noise Margins, Rise & Fall Times, Inverter Delay**
- **CMOS Inverters: Rabaey 1.3.2, 5 (Kang & Leblebici, 5.1-5.3 and 6.1-6.2)**
 
# Review: Inverter Voltage Transfer Curve

Voltage transfer curve (VTC): plot of output voltage  $V_{out}$  vs. input voltage  $V_{in}$




## Ideal digital inverter:

- When  $V_{in}=0$ ,  
 $V_{out}=V_{dd}$
- When  $V_{in}=V_{dd}$ ,  
 $V_{out}=0$
- Sharp transition region

# Review: Actual Inverter Output Levels


---

 

- $V_{OH}$  and  $V_{OL}$  represent the “high” and “low” output voltages of the inverter
- $V_{OH}$  = output voltage when  $V_{in} = '0'$  (V Output High)
- $V_{OL}$  = output voltage when  $V_{in} = '1'$  (V Output Low)
- Ideally,
  - $V_{OH} = V_{dd}$
  - $V_{OL} = 0\text{ V}$

# Review: VOL and VOH

---

 

- In transfer function terms:

- $V_{OL} = f(V_{OH})$

- $V_{OH} = f(V_{OL})$


- $f$  = inverter transfer function

- **Difference ( $V_{OH} - V_{OL}$ ) is the *voltage swing* of the gate**

- *Full-swing logic* swings from ground to  $V_{dd}$

- Other families with smaller swings

# Review: Inverter Switching Threshold

 

## Inverter switching threshold:

- Point where voltage transfer curve intersects line  $V_{out} = V_{in}$
- Represents the point at which the inverter switches state
- Normally,  $V_M \approx V_{DD}/2$
- Sometimes other thresholds desirable

# VTC Mathematical Definitions

---

- **$V_{OH}$  is the output high level of an inverter**

$$V_{OH} = VTC(V_{OL})$$

- **$V_{OL}$  is the output low level of an inverter**

$$V_{OL} = VTC(V_{OH})$$

- **$V_M$  is the switching threshold**

$$V_M = V_{IN} = V_{OUT}$$

- **$V_{IH}$  is the lowest input voltage for which the output will be  $\geq$  the input (worst case '1')**

$$dVTC(V_{IH})/dV_{IH} = -1$$

- **$V_{IL}$  is the highest input voltage for which the output will be  $\leq$  the input (worst case '0')**

$$dVTC(V_{IL})/dV_{IL} = -1$$



# Noise Margin and Delay Definitions

---

- **$NM_L$  is the difference between the highest acceptable '0' and the lowest possible '0'**

$$NM_L = V_{IL} - V_{OL}$$


- **$NM_H$  is the difference between the lowest acceptable '1' and the highest possible '1'**

$$NM_H = V_{OH} - V_{IH}$$



- **$t_{PHL}$  is the propagation delay from the 50% point of the input to the output when the output goes from high to low**
- **$t_{PLH}$  is the propagation delay from the 50% point of the input to the output when the output goes from low to high**
- **$t_p$  is the average propagation delay**
- **$t_R$  is the rise time (usually 10% to 90%)**
- **$t_F$  is the fall time (usually 90% to 10%)**
 
# CMOS Inverter

- **Complementary NMOS and PMOS devices**
- **In steady-state, only one device is on (no static power consumption)**
- **$V_{in}=1$ : NMOS on, PMOS off**
  - $V_{out} = V_{OL} = 0$
- **$V_{in}=0$ : PMOS on, NMOS off**
  - $V_{out} = V_{OH} = V_{dd}$
- **Ideal  $V_{OL}$  and  $V_{OH}$ !**
- **Ratioless logic: output is independent of transistor sizes in steady-state**



# CMOS Inverter: VTC

 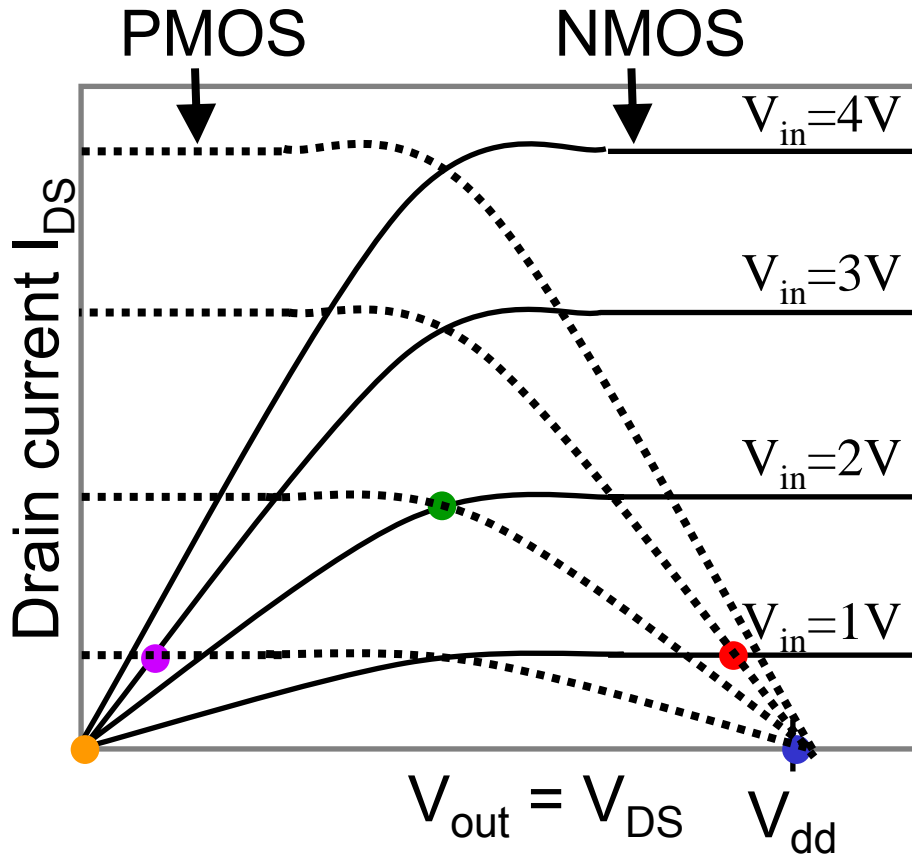

- Output goes completely to  $V_{dd}$  and  $Gnd$
- Sharp transition region

# CMOS Inverter Operation


---

- **NMOS transistor:**


- Cutoff if  $V_{in} < V_{TN}$
- Linear if  $V_{out} < V_{in} - V_{TN}$
- Saturated if  $V_{out} > V_{in} - V_{TN}$

- **PMOS transistor**

 
- Cutoff if  $(V_{in} - V_{DD}) > V_{TP} \rightarrow V_{in} > V_{DD} + V_{TP}$
- Linear if  $(V_{out} - V_{DD}) > V_{in} - V_{DD} - V_{TP} \rightarrow V_{out} > V_{in} - V_{TP}$
- Sat. if  $(V_{out} - V_{DD}) < V_{in} - V_{DD} - V_{TP} \rightarrow V_{out} < V_{in} - V_{TP}$



# CMOS Inverter VTC: Device Operation

 

# CMOS Inverter VTC: Device Sizing

 

- Increase  $W$  of PMOS  
 $k_p$  increases  
VTC moves to right
- Increase  $W$  of NMOS  
 $k_n$  increases  
VTC moves to left
- For  $V_M = V_{DD}/2$   
 $k_n = k_p$   
 $2W_n \approx W_p$

# Effects of $V_M$ adjustment

---

- **Result from changing  $k_p/k_n$  ratio:**
  - Inverter threshold  $V_M \neq V_{DD}/2$
  - Rise and fall delays unequal
  - Noise margins not equal
- **Reasons for changing inverter threshold**
  - Want a faster delay for one type of transition (rise/fall)
  - Remove noise from input signal: increase one noise margin at expense of the other
  - Interfacing other types of logic (with different swings)

# CMOS Inverter: $V_{IL}$ Calculation

- **KCL (NMOS saturation, PMOS linear):**

$$\frac{k_n}{2} (V_{GS,n} - V_{T0,n})^2 = \frac{k_p}{2} [2(V_{GS,p} - V_{T0,p})V_{DS,p} - V_{DS,p}^2]$$

$$\frac{k_n}{2} (V_{in} - V_{T0,n})^2 = \frac{k_p}{2} [2(V_{in} - V_{DD} - V_{T0,p})(V_{out} - V_{DD}) - (V_{out} - V_{DD})^2]$$

- **Differentiate and set  $dV_{out}/dV_{in}$  to  $-1$**

$$k_n (V_{in} - V_{T0,n}) = k_p \left[ (V_{in} - V_{DD} - V_{T0,p}) \frac{dV_{out}}{dV_{in}} + (V_{out} - V_{DD}) - (V_{out} - V_{DD}) \frac{dV_{out}}{dV_{in}} \right]$$

$$k_n (V_{IL} - V_{T0,n}) = k_p (2V_{out} - V_{IL} + V_{T0,p} - V_{DD})$$

$$V_{IL} = \frac{2V_{out} + V_{T0,p} - V_{DD} + k_R V_{T0,n}}{1 + k_R} \quad k_R = \frac{k_n}{k_p}$$

- **Solve simultaneously with KCL to find  $V_{IL}$**



# CMOS Inverter: $V_{IH}$ Calculation

- **KCL:**  $\frac{k_n}{2} \left[ 2(V_{GS,n} - V_{T0,n})V_{DS,n} - V_{DS,n}^2 \right] = \frac{k_p}{2} (V_{GS,p} - V_{T0,p})^2$

$$\frac{k_n}{2} \left[ 2(V_{in} - V_{T0,n})V_{out} - V_{out}^2 \right] = \frac{k_p}{2} (V_{in} - V_{DD} - V_{T0,p})^2$$

- **Differentiate and set  $dV_{out}/dV_{in}$  to  $-1$**

$$k_n \left[ (V_{in} - V_{T0,n}) \frac{dV_{out}}{dV_{in}} + V_{out} - V_{out} \frac{dV_{out}}{dV_{in}} \right] = k_p (V_{in} - V_{DD} - V_{T0,p})$$

$$k_n (2V_{out} - V_{IH} + V_{T0,p}) = k_p (V_{IH} - V_{DD} - V_{T0,p})$$

$$V_{IH} = \frac{V_{DD} + V_{T0,p} + k_R (2V_{out} + V_{T0,n})}{1 + k_R} \quad k_R = \frac{k_n}{k_p}$$

- **Solve simultaneously with KCL to find  $V_{IH}$**

# CMOS Inverter: $V_M$ Calculation

---

- **KCL (NMOS & PMOS saturated):**

$$\frac{k_n}{2} (V_{GS,n} - V_{T0,n})^2 = \frac{k_p}{2} (V_{GS,p} - V_{T0,p})^2$$

$$\frac{k_n}{2} (V_{in} - V_{T0,n})^2 = \frac{k_p}{2} (V_{in} - V_{DD} - V_{T0,p})^2$$

- **Solve for  $V_M = V_{in} = V_{out}$**

$$V_M = \frac{V_{T0,n} + \sqrt{\frac{1}{k_R} (V_{DD} + V_{T0,p})}}{1 + \sqrt{\frac{1}{k_R}}} \quad k_R = \frac{k_n}{k_p}$$

# CMOS Inverter: Achieving Ideal $V_M$

$$V_{TH} = \frac{V_{T0,n} + \sqrt{\frac{1}{k_R}} (V_{DD} + V_{T0,p})}{1 + \sqrt{\frac{1}{k_R}}} \quad k_R = \frac{k_n}{k_p}$$

- **Ideally,  $V_M = V_{DD}/2$**   $k_{R,ideal} = \left( \frac{V_{DD}/2 + V_{T0,p}}{V_{DD}/2 + V_{T0,n}} \right)^2$

- **Assuming  $V_{T0,n} = V_{T0,p}$ ,  $k_{R,ideal} = 1$**   

$$\frac{\left(\frac{W}{L}\right)_p}{\left(\frac{W}{L}\right)_n} = \frac{\mu_n}{\mu_p} \approx 2.5$$

# CMOS Inverter: $V_{IL}$ and $V_{IH}$ for Ideal $V_M$

---

- Assuming  $V_{T0,n} = -V_{T0,p}$ , and  $k_R = 1$ ,

$$V_{IL} = \frac{1}{8} (3V_{DD} + 2|V_{T0}|)$$

$$V_{IH} = \frac{1}{8} (5V_{DD} - 2|V_{T0}|)$$

$$V_{IL} + V_{IH} = V_{DD}$$

$$NM_L = V_{IL} - V_{OL} = V_{IL}$$

$$NM_H = V_{OH} - V_{IH} = V_{DD} - V_{IH} = V_{IL}$$

# Next Time: AC Characteristics & Fabrication

---

- **CMOS Inverters**
  - AC Characteristics: Designing for speed