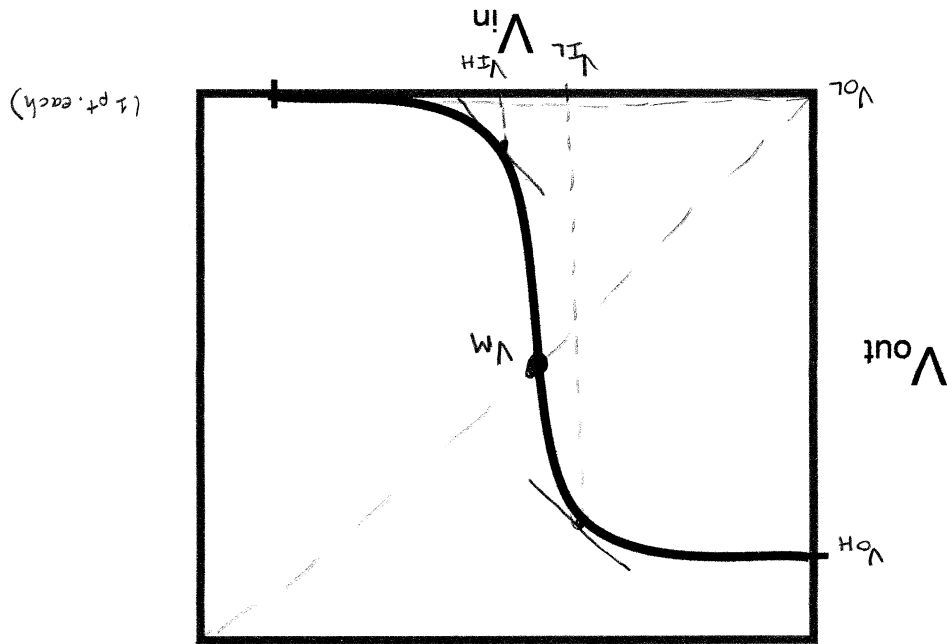



Name: Solutions

Lab Section: \_\_\_\_\_

**Problem 1 (5 points)** Label the following points on the Voltage Transfer Curve below:  $V_{OH}$ ,  $V_{OL}$ ,  $V_{IH}$ ,  $V_{IL}$ , and  $V_M$ . Indicate any other lines that are necessary to define the preceding voltage points.



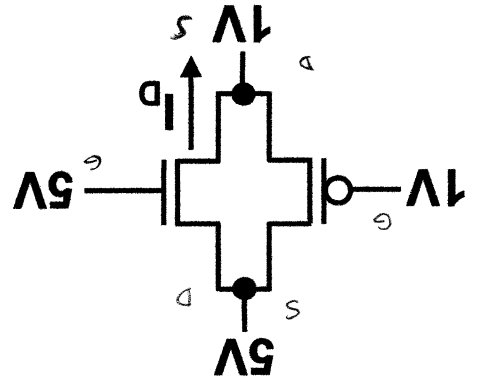**Problem 2 (5 points)** For the following circuit, find the current  $I_D$  given:  $W^p/L^p = 300 \times 10^{-6} \text{ A/V}^2$ ,  $V_{Tn} = 1.1 \text{ V}$ ,  $\mu_n C_{ox} = 100 \times 10^{-6} \text{ A/V}^2$ ,  $V_{Tp} = -0.9 \text{ V}$ ,  $\mu_p C_{ox} = 100 \times 10^{-6} \text{ A/V}^2$ ,  $\lambda = 0$ ,  $\gamma = 0$ ,  $V_{DD} = 5 \text{ V}$ . Show all work to receive full credit.



NMOS:  $V_{GS} = 4 \text{ V}$ ,  $V_{DS} = 4 \text{ V} > V_{GS} - V_T = 2.9 \text{ V} \Rightarrow \text{sat.}$

$$I_N = \frac{\mu_n C_{ox}}{2} \left(\frac{W}{L}\right)^N (V_{GS} - V_T)^2$$

$$= \frac{300 \mu\text{A/V}^2}{2} (1)^N (2.9)^2 = 1.262 \text{ mA} \quad (2 \text{ pts.})$$

PMOS:  $V_{GS} = -4 \text{ V}$ ,  $V_{DS} = -4 \text{ V} < V_{GS} - V_T = -3.1 \text{ V} \Rightarrow \text{sat.}$

$$I_P = \frac{\mu_p C_{ox}}{2} \left(\frac{W}{L}\right)^P (V_{GS} - V_T)^2$$

$$= \frac{100 \mu\text{A/V}^2}{2} (1)^P (3.1)^2 = 0.481 \text{ mA} \quad (2 \text{ pts.})$$

$$I_D = I_N + I_P$$

$$= \boxed{1.743 \text{ mA}} \quad (1 \text{ pt.})$$