

① a) $V_0 = 3 - V_t - (V_{GS} - V_t)$; $V_{GS} - V_t = \sqrt{\frac{2I}{K' \frac{W}{L}}}$; $K' = \mu_n C_{ox}$
 $C_{ox} = \frac{3.9 \times 8.854 \times 10^{-14}}{250 \times 10^{-8} \text{ cm}} = 1.38 \times 10^{-7} \frac{\text{F}}{\text{cm}^2} = 1.38 \frac{\text{fF}}{\mu^2}$
 $K' = \mu_n C_{ox} = 650 \frac{\text{cm}^2}{\text{Vs}} \cdot 1.38 \times 10^{-7} \frac{\text{F}}{\text{cm}^2} = 89.7 \mu\text{A/V}^2 \approx 90 \mu\text{A/V}^2$
 $\therefore V_{GS} - V_t = \sqrt{\frac{2(200)}{90(10)}} \approx 0.67 \text{ V} \rightarrow V_0 = 3 - 0.7 - 0.67 = \boxed{1.63 \text{ V}}$

$\frac{V_0}{V_i} = \frac{g_m r_o}{1 + g_m r_o}$; $r_o = \infty$ because $\lambda = 0 \rightarrow \frac{V_0}{V_i} = 1$

b) V_t affects V_0 and vice versa, solve iteratively

$V_t = V_{t0} + \gamma \left(\sqrt{2\phi_F + V_{SB}} - \sqrt{2\phi_F} \right)$
 $\gamma = \frac{\sqrt{2q\epsilon_N A}}{C_{ox}} = \frac{\sqrt{2(1.6 \times 10^{-19})(11.7 \times 8.854 \times 10^{-14})(2 \times 10^{15})}}{1.38 \times 10^{-7}} = 0.19 \sqrt{\text{V}}$
 $V_{SB} = V_0$ - use answer from (a) to start; $\phi_F = V_T \ln \frac{N_A}{n_i} = 26 \text{ mV} \ln \frac{2 \times 10^{15}}{1.5 \times 10^{10}} \approx 0.3$

$V_t = 0.7 + 0.19 \left(\sqrt{0.6 + 1.63} - \sqrt{0.6} \right) = 0.84 \text{ V}$

So $V_0 = 3 - 0.84 - 0.67 = 1.49$ Try Again

$V_t = 0.7 + 0.19 \left(\sqrt{0.6 + 1.49} - \sqrt{0.6} \right) = 0.83$ - Not much change - OK

So $V_0 = 3 - 0.83 - 0.67 \approx \boxed{1.5 \text{ V}}$

$\frac{V_0}{V_i} = \frac{g_m}{g_m + g_{mb}} = \frac{1}{1 + \chi}$; $\chi = \frac{\gamma}{2\sqrt{2\phi_F + V_{SB}}} = \frac{0.19}{2\sqrt{0.6 + 1.5}} \approx 0.07$
 $= \frac{1}{1 + 0.07} \approx \boxed{0.93}$

c) Use V_0 from (b) at first $\rightarrow I = 200 \mu\text{A} + \frac{1.5}{100\text{k}} \approx 215 \mu\text{A}$

$V_0 = 3 - 0.83 - \sqrt{\frac{2(215)}{90 \cdot 10}} = \boxed{1.48 \text{ V}}$ (Not much change from

(b) so don't bother to recalculate V_t .)

To find $a_v = \frac{V_0}{V_i}$, use $a_v' = \text{OCV}_G$ from (b) = 0.93

$a_v' \left(\text{Circuit with } R = 100\text{k} \right) \Rightarrow a_v' = a_v' \frac{100\text{k}}{100\text{k} + r_{out}'}$

$r_{out}' = 1/(g_m + g_{mb}) = 1/g_m(1 + \chi)$; $g_m = \sqrt{2IK' \frac{W}{L}} = \sqrt{2(215)90 \cdot 10} = 0.62 \text{ mA/V}$
 $r_{out}' = \frac{1}{0.62(1.07)} = 1.5 \text{ k}\Omega \Rightarrow a_v' = 0.93 \frac{100}{101.5} = \boxed{0.92}$

d) Use V_0 from (c) at first $\rightarrow I = 200 + \frac{1.48}{10\text{k}} = 348 \mu\text{A}$

$V_0 = 3 - 0.83 - \sqrt{\frac{2(348)}{90 \cdot 10}} = 1.29 \text{ V}$

$V_t = 0.7 + 0.19 \left(\sqrt{0.6 + 1.29} - \sqrt{0.6} \right) = 0.81 \text{ V}$

$I = 200 + \frac{1.29}{10\text{k}} = 329 \mu\text{A}$

$V_0 = 3 - 0.81 - \sqrt{\frac{2(329)}{90 \cdot 10}} = \boxed{1.33 \text{ V}}$

$a_v' = 1/(1 + \chi)$; $\chi = 0.19 / (2\sqrt{0.6 + 1.33}) = 0.07 \rightarrow a_v' \approx 0.93$

$r_{out}' = 1/[g_m(1 + \chi)]$; $g_m = \sqrt{2(329)90(10)} = 0.77 \text{ mA/V}$

$r_{out}' = \frac{1}{0.77(1.07)} = 1.2 \text{ k}\Omega \rightarrow a_v = 0.93 \frac{10\text{k}}{11.2\text{k}} = \boxed{0.83}$

② I'll send my SPICE file to anyone who wants it.
 Please send me e-mail if you want it but did not get it.
 ANSWER: $V_0 = 1.32 \text{ V}$ $\frac{V_0}{V_i} = 0.835$ (very close to)
 (hand calcs)

③

$$R_i \rightarrow \infty$$

$$G_m = g_{m1} = \sqrt{2(40)(100)(250)} \approx 2.1 \text{ mA/V}$$

$$R_o \approx (g_{m2} + g_{mb2}) R_{D2} R_{O1} = g_{m2} (1 + \lambda) R_{D2} R_{O1}$$



$$R_{O1} = R_{O2} = \frac{1}{\lambda I} = \frac{10}{250} = 40 \text{ k}\Omega$$

$$R_o \approx 2.1 (1 + 0.1) (40 \text{ k})^2 \approx 3.7 \text{ meg}\Omega$$

$$OCV_6 = -G_m R_o = 2.1 \text{ m} (3.7 \text{ meg})$$

$$\approx -7700$$

④

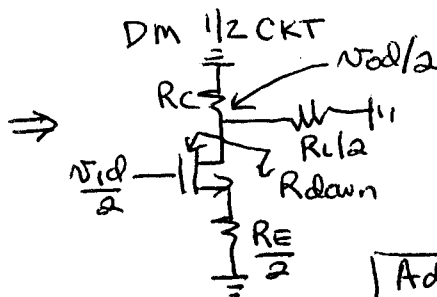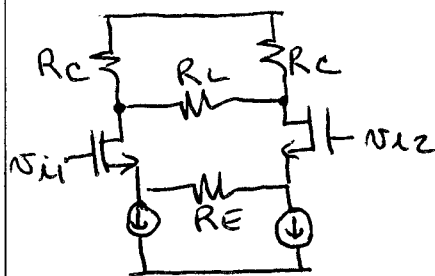


$$A_{dm} = -G_m R_o$$

$$G_m = \frac{g_m}{1 + g_m \frac{R_E}{2}}$$

$$R_o = R_c \parallel R_{L/2} \parallel R_{down}$$

$$A_{dm} = - \frac{g_m (R_c \parallel R_{L/2})}{1 + g_m \frac{R_E}{2}}$$

CM 1/2 CKT

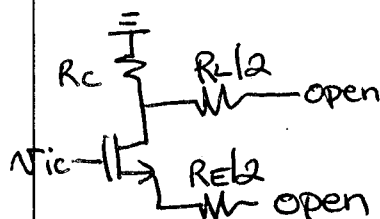

Since the resistance connected to the source $\rightarrow \infty$, G_m here = 0 and $A_{cm} = 0$

⑤

From Table 2.4 $\mu_n C_{ox} = 450 \times \frac{3.9 \times 8.854 \times 10^{-14}}{0.08 \times 10^{-5}} = 194 \text{ }\mu\text{A/V}^2 = K'$

$$\Delta I_d = 0.85 I_{TAIL} = \frac{K'}{2} \frac{W}{L_{eff}} (0.2) \sqrt{\frac{2 I_{TAIL}}{\frac{K'}{2} \frac{W}{L_{eff}}} - (0.2)^2} \quad \text{EQ(1)}$$

Also $G_m = 1.0 \frac{\text{mA}}{\text{V}} = \sqrt{I_{TAIL} K' \frac{W}{L_{eff}}} \quad \text{EQ(2)} \rightarrow K' \frac{W}{L_{eff}} = \frac{1 \times 10^{-6} \text{ A/V}^2}{I_{TAIL}}$

So we have 2 equations and 2 unknowns (I_{TAIL} and $\frac{W}{L_{eff}}$)

Substitute (2) into (1)

$$0.85 I_{TAIL} = \frac{1 \times 10^{-6}}{2 I_{TAIL}} (0.2) \sqrt{\frac{2 I_{TAIL}}{1 \times 10^{-6} / 2 I_{TAIL}} - (0.2)^2}$$

Solve for I_{TAIL}^2 : $7.225 \times 10^{13} I_{TAIL}^4 - 4 \times 10^6 I_{TAIL}^2 + 0.04 = 0$

$$I_{TAIL}^2 = \frac{4 \times 10^6 \pm \sqrt{(4 \times 10^6)^2 - 4(7.225 \times 10^{13})(0.04)}}{2(7.225 \times 10^{13})} = 2.768 \times 10^{-8} \pm 1.458 \times 10^{-8}$$

$$I_{TAIL}^2 = 4.226 \times 10^{-8} \text{ or } 1.310 \times 10^{-8}$$

$$I_{TAIL} = 205.6 \text{ }\mu\text{A} \text{ or } 114.4 \text{ }\mu\text{A}$$

If $I_{TAIL} = 205.6 \text{ }\mu\text{A}$, $\frac{W}{L_{eff}} = \frac{1 \times 10^{-6}}{194 \times 10^{-6} (205.6 \times 10^{-6})} = 25.1$

If $I_{TAIL} = 114.4 \text{ }\mu\text{A}$, $\frac{W}{L_{eff}} = \frac{1 \times 10^{-6}}{194 \times 10^{-6} (114.4 \times 10^{-6})} = 45.0$

If $I_{TAIL} = 205.6 \text{ }\mu\text{A}$, $V_{OV} = \sqrt{\frac{2(I_{TAIL}/2)}{K' W/L_{eff}}} = \sqrt{\frac{205.6}{194(25)}} = 0.206 \text{ V}$

If $I_{TAIL} = 114.4 \text{ }\mu\text{A}$, $V_{OV} = \sqrt{\frac{2(I_{TAIL}/2)}{K' W/L_{eff}}} = \sqrt{\frac{114.4}{194(45)}} = 0.114 \text{ V}$

This overdrive is too small because the range would be only $\pm \sqrt{2}(0.114)$ which is 162 mV which is less than the 200 mV input

$$L_{eff} = L_{drawn} - 2L_d - x_d = 1 \text{ }\mu\text{m} - 2(0.09) - 0 = 0.82 \text{ }\mu\text{m}$$

$$I_{TAIL} = 205.6 \text{ }\mu\text{A} \quad \frac{W}{L_{eff}} = \frac{W}{0.82 \text{ }\mu\text{m}} = 25.1 \Rightarrow 20.6 \text{ }\mu\text{m} = W$$