
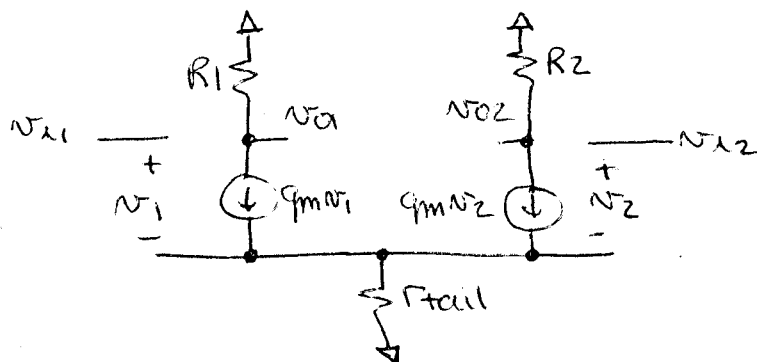
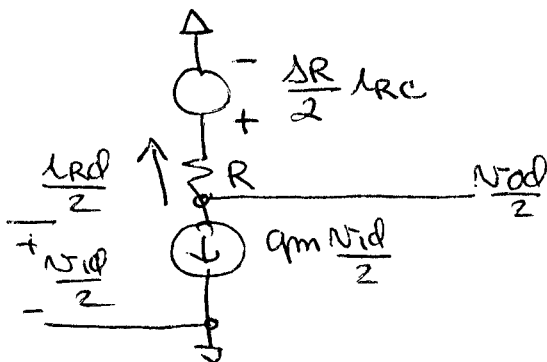
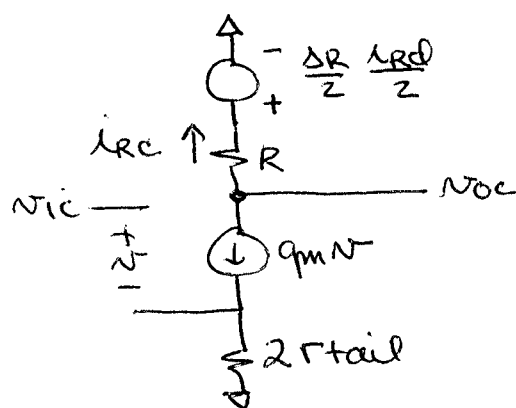
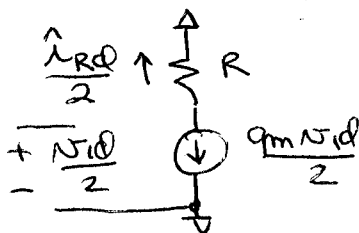


④

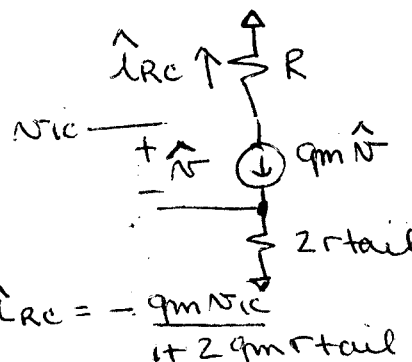

$$\text{Let } R = \frac{R_1 + R_2}{2}$$

$$\Delta R = R_1 - R_2$$

EXACT DM $\frac{1}{2}$ CKTEXACT CM $\frac{1}{2}$ CKTDM $\frac{1}{2}$ CKT WITHOUT MISMATCHCM $\frac{1}{2}$ CKT WITHOUT MISMATCH

$$\frac{\hat{I}_{RD}}{2} = -g_m \frac{V_{id}}{2}$$

$$\hat{I}_{RC} = -\frac{g_m V_{ic}}{1 + 2g_m r_{tail}}$$

FROM EXACT $\frac{1}{2}$ CKTS

$$\frac{V_{od}}{2} = \frac{\Delta R}{2} I_{RC} + R \frac{\hat{I}_{RD}}{2} \approx \frac{\Delta R}{2} \hat{I}_{RC} + R \frac{\hat{I}_{RD}}{2} = -\frac{\Delta R}{2} \frac{g_m V_{ic}}{1 + 2g_m r_{tail}} - R g_m \frac{V_{id}}{2}$$

$$\therefore A_{dm} \approx -g_m R = -1(10) = -10$$

$$A_{cm-dm} \approx \frac{-g_m \Delta R}{1 + 2g_m r_{tail}} = \frac{-1(0.2)}{1 + 2(1)(1000)} \approx -1 \times 10^{-4}$$

$$V_{oc} = \frac{\Delta R}{2} \frac{I_{RC}}{2} + R I_{RC} \approx \frac{\Delta R}{2} \frac{\hat{I}_{RC}}{2} + R \hat{I}_{RC} = -\frac{\Delta R}{2} \frac{g_m V_{ic}}{1 + 2g_m r_{tail}} - R g_m \frac{V_{ic}}{2}$$

$$\therefore A_{cm-cm} \approx \frac{-g_m \Delta R}{4} = \frac{-1(0.2)}{4} = -0.05$$

$$A_{cm} \approx \frac{-g_m R}{1 + 2g_m r_{tail}} = \frac{-1(10)}{1 + 2(1)(1000)} \approx -0.005$$

$$\frac{A_{dm}}{A_{cm}} \approx \frac{10}{0.005} = 2000$$

$$\frac{A_{dm}}{A_{cm-dm}} \approx \frac{10}{1 \times 10^{-4}} = 100,000$$

$$\frac{A_{dm}}{A_{cm-cm}} \approx \frac{10}{0.05} = 200$$

⑤ From Table 2.4, $K' = \mu_n C_{ox}$

$$= \frac{450 \times 3.9 \times 8.86 \times 10^{-14}}{0.08 \times 10^{-5}} = 194 \mu A/V^2$$

$$I_{out} = 50 \mu A (1 + \lambda \Delta V_{DS})$$

From condition (c), $\lambda \Delta V_{DS} \leq 0.01$ and $\Delta V_{DS} = 1V \Rightarrow \lambda \leq 0.01 V^{-1}$

From conditions (a) and (b)

$$50 \mu A = \frac{K'}{2} \frac{W}{L_{eff}} (V_{GS} - V_t)^2 \quad \text{where } V_{GS} - V_t = 0.2V$$

$$50 \mu = \frac{194}{2} \frac{W}{L_{eff}} (0.2)^2 \Rightarrow \frac{W}{L_{eff}} = 12.9$$

$$\lambda \leq \frac{1}{100V} \quad \text{Also from Table 2.4 } \frac{d\lambda/dV_{DS}}{dV_{DS}} = 0.02$$

$$\lambda = \frac{1}{V_A} = \frac{d\lambda/dV_{DS}}{L_{eff}} \leq \frac{1}{100V} \Rightarrow L_{eff} \geq 2 \mu m$$

$$L_{drawn} = L_{eff} + 2L_d + x_d \quad \text{where } x_d = 0 \text{ (given)} \\ L_d = 0.09 \mu m \text{ (Table 2.4)}$$

$$L_{drawn} = 2 \mu m + 2(0.09) = 2.18 \mu m \approx 2.2 \mu m$$

The minimum length that satisfies the constraints minimizes the required gate area

$$\text{Then } W = 12.9 \times 2.2 \mu m = \boxed{28 \mu m}$$