

$$\textcircled{1} \quad V_{EB2} = V_T \ln \frac{I_{C2}}{I_{S2}} = V_T \ln \frac{I_{E2}}{I_{S2}} \text{ because base current is ignored}$$

$$I_{E2} = \frac{\Delta V_{EB}}{R_3}$$

Now double I_{S1} & I_{S2} . ΔV_{EB} is constant. See (4.272)
Therefore $I_{E2} < I_{C2}$ are constant

So V_{EB2} changes by $V_T \ln \frac{1}{2} = -18 \text{ mV}$

$$\text{From (4.248)} \quad V_{EB2} = V_{G0} - V_T [(\gamma - \alpha) \ln T - \ln (EG)]$$

$$\begin{aligned} \frac{dV_{EB2}}{dT} &= -V_T \frac{(\gamma - \alpha)}{T} - (\gamma - \alpha) \ln T \frac{V_T}{T} + \frac{V_T}{T} \ln (EG) \\ &= \underbrace{-V_T (\gamma - \alpha)}_{T} - V_T [(\gamma - \alpha) \ln T - \ln (EG)] + V_{G0} - V_{G0} \\ &= \frac{V_{EB2} - V_{G0} - V_T (\gamma - \alpha)}{T} \end{aligned}$$

Under nominal conditions, the slope of the V_{EB2} term and the slope of the ΔV_{EB} term at the output are set equal in magnitude and opposite in polarity at 25°C to set $T_{CF} = 0$. However, under the specified conditions, V_{EB2} has fallen by 18 mV , and its slope has fallen by $\frac{18 \text{ mV}}{25 + 273} = \frac{18}{298} = 60 \frac{\mu\text{V}}{\text{K}} = 60 \frac{\mu\text{V}}{\text{C}}$

Since V_{EB2} contributes directly to the output, [see (4.266)], the output slope changes by the same amount.

$$\text{Therefore } \left. \frac{dV_{OUT}}{dT} \right|_{T=25^\circ\text{C}} = -60 \frac{\mu\text{V}}{\text{C}}$$

\textcircled{2} With I_{S1} and I_{S2} doubled from the nominal value but the gain equal to the nominal value, SPICE gives

$$\left. \frac{dV_{OUT}}{dT} \right|_{T=25^\circ\text{C}} = -58 \frac{\mu\text{V}}{\text{C}}$$

With the gain readjusted so that $V_{OUT} = \text{target}$ at 25°C , $\left. \frac{dV_{OUT}}{dT} \right|_{T=25^\circ\text{C}} = 0$

Therefore, the case of $I_S \neq \text{nominal}$ can be corrected by trimming the gain to set the output equal to the target.

③

Because $m_3 = m_4$, $|ID_3| = |ID_4| = ID_1 = ID_2 = I_{BIAS}$

$$\text{KVL: } V_{GS1} - V_{GS2} = I_{BIAS} R$$

$$\text{Ignore body effect } \rightarrow V_{t1} = V_{t2}$$

$$V_{OV1} - V_{OV2} = I_{BIAS} R$$

$$\sqrt{\frac{2I_{BIAS}}{m_n C_{ox}(W/L)_1}} - \sqrt{\frac{2I_{BIAS}}{m_n C_{ox}(W/L)_2}} = I_{BIAS} R$$


$$\sqrt{\frac{2I_{BIAS}}{m_n C_{ox}}} \left\{ \sqrt{\frac{1}{(W/L)_1}} - \sqrt{\frac{1}{(W/L)_2}} \right\} = I_{BIAS} R$$

$$I_{BIAS} = \frac{2}{m_n C_{ox} R^2} \left\{ \sqrt{\frac{1}{(W/L)_1}} - \sqrt{\frac{1}{(W/L)_2}} \right\}^2$$

As $T \uparrow$, $R \uparrow$ and $m_n \downarrow$ ($m_n \propto T^{-n}$). These effects tend to cancel. The precise behavior depends on the exact dependence of m_n and R versus T .

④

Small signal model

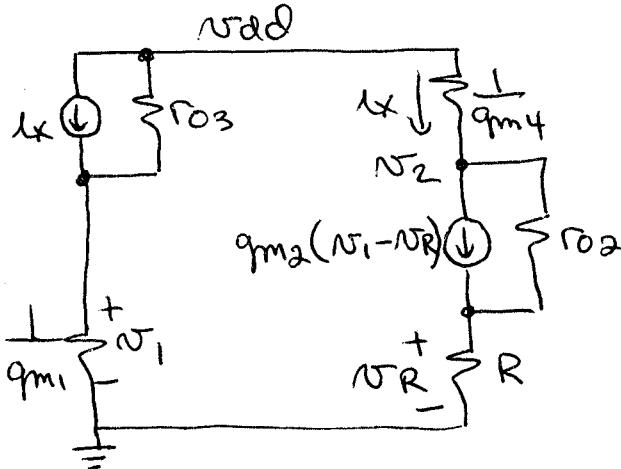

$$\text{KCL: } I_x = \frac{N_1 - N_{dd}}{R_{03}} + N_1 q_{m1}$$

$$\rightarrow N_1 \left(\frac{1}{R_{03}} + q_{m1} \right) = I_x + \frac{N_{dd}}{R_{03}}$$

$$N_2 = N_{dd} - \frac{I_x}{q_{m4}} = N_R + N_{R02}$$

$$= I_x R + [I_x - q_{m2} (N_1 - N_R)] R_{02}$$

$$\text{So } N_{dd} - \frac{I_x}{q_{m4}} =$$

$$I_x R + I_x R_{02} - q_{m2} R_{02} N_1 + q_{m2} R_{02} I_x R$$

$$N_{dd} = I_x \left(R + R_{02} + q_{m2} R_{02} R + \frac{1}{q_{m4}} \right) - \frac{q_{m2} R_{02} \left(I_x + \frac{N_{dd}}{R_{03}} \right)}{q_{m1} + 1/R_{03}}$$

$$N_{dd} \left(1 + \frac{q_{m2} R_{02}}{1 + q_{m1} R_{03}} \right) = I_x \left(R + R_{02} + q_{m2} R_{02} R + \frac{1}{q_{m4}} \right) - \frac{q_{m2} R_{02} R_{03}}{1 + q_{m1} R_{03}}$$

Assume $R_{02} \approx R_{03}$

$$\frac{I_{bias}}{N_{dd}} = \frac{I_x}{N_{dd}} \approx \frac{1 + \frac{q_{m2}}{q_{m1}}}{q_{m2} R_{02} R}$$

The use of cascodes on the top and bottom would reduce $\frac{I_{bias}}{N_{dd}}$ by another factor of $q_{m2} R_0$