

- (7.1) ① Similar to GHLom 7.1 but replace BJTs with MOS Transistors
 $g_m = \sqrt{2(60)(\frac{100}{1.6})(500 \mu A)} = 1.9 \text{ mA/V}$; $A_v \approx -g_m R_L = -g_m (5K) = -9.7$
 $f_T = g_m / [2\pi(C_{gs} + C_{gd})]$; $C_{gsi} = \frac{2}{3} W \cdot L_{eff} C_{ox} = \frac{2}{3}(100)(1.6) C_{ox}$
 $C_{ox} = \frac{1.9 \text{ mA/V}}{2\pi(106.7 + 20)(20)} 36 \text{ Hz} = 0.7 \text{ fF}/\mu^2$
 $C_{gs} = (106.7 + 20) 0.7 = 89 \text{ fF}$; $C_{gd} = 20(0.7) = 14 \text{ fF}$
- (a) Use Miller Effect for $|P_1| = \frac{1}{2\pi(R_S)[C_{gs} + C_{gd}(1 - A_v)]} = \frac{1}{2\pi(10K)[89 + 14(10.7)]} = 67 \text{ MHz}$
- (b) DO NOT use Miller Effect to calculate 2nd POLE!
 From EQ 7.26, $|P_2| = \frac{1}{2\pi P_1 R_L R_S C_{gd} C_{gs}} = \frac{1}{2\pi(2\pi \times 67 \text{ MHz})(5K)(10K)(14 \text{ fF})(89 \text{ fF})} = 6 \text{ GHz}$
- (7.4) ② SPICE gives 63 MHz and 4.5 GHz, (It doesn't zero C_{db} , as I did above)
 The given C_{ox} here is the same as that calculated in ①.
 So the result here is the same as in ① except that C_{db} is included here
 $V_0 = 10 - 0.5(5K) = 7.5 \text{ V}$; $C_{db0} = 5(100)(0.4) + 100(0.4) = 240 \text{ fF}$
 $C_{db} = \frac{240}{\sqrt{1 + 7.5/0.6}} = 65 \text{ fF}$
 So the output time constant = $5K(65 \text{ fF}) = 0.3 \text{ ns}$ } $f_{-3dB} = \frac{1}{2\pi(2.7 \text{ ns})} = 59 \text{ MHz}$
 The time constant in ① = $1/(2\pi(67 \text{ MHz})) = 2.4 \text{ ns}$
- (7.26) ③ Iterate to find bias current, Start w/ $V_{ov3} = 0$
 Then $I_3 \approx (10 - V_{t1})/30K = 9/30K = 300 \mu A$; $V_{ov3} = \sqrt{\frac{2(300)}{60 \cdot 100/(2 - 0.4 - 1)}} = 0.24 \text{ V}$
 Then $I_3 \approx (10 - 1 - 0.24)/30K \approx 290 \mu A$
 V_{ov3} still = 0.24V so this is close enough
- Now $V_{DS2} = 10 \text{ V}$, $V_{DS3} = 1.24 \text{ V} \rightarrow \Delta V_{DS} = 8.8 \text{ V} \rightarrow I_1 = I_2 = 290(1 + \frac{8.8}{100}) = 315 \mu A$
 $g_{m1} = \sqrt{2(20)(200)(0.6)(315)} = 2.0 \text{ mA/V}$; $r_{o1} = 50/315 = 160 \text{ K}\Omega$
 $g_{m2} = \sqrt{2(60)(100)(0.6)(315)} = 2.5 \text{ mA/V}$; $r_{o2} = 100/315 = 320 \text{ K}\Omega$
 $g_{m3} = \sqrt{2(60)(100)(0.6)(290)} = 2.4 \text{ mA/V}$; $r_{o3} = 100/290 = 340 \text{ K}\Omega$
- (a) $A = -(1/g_{m1}) g_{m1}(r_{o1} || r_{o2}) = -160 \text{ K} || 320 \text{ K} \approx -110 \text{ K}\Omega$
 $C_{gs1} = \frac{2}{3}(200)(0.6)(0.7) + 200(0.2)(0.7) = 84 \text{ fF}$
 $R(C_{gs1}) = 1/g_{m1} = 500 \Omega$; $T_{gs1} = (0.084)(0.5) = 0.04 \text{ ns}$ (very small)
- $C_{db01} = 5(200)(0.2) + 200(0.2) = 240 \text{ fF}$
 $C_{db02} = 5(100)(0.4) + 100(0.4) = 240 \text{ fF}$
 So $C_{db1} = C_{db2} = \frac{240}{\sqrt{1 + 10/0.6}} \approx 57 \text{ fF}$ } $T_{db1-2} = 2(0.057)110 \text{ K} = 12.5 \text{ ns}$
 Also $R(C_{db1}) = R(C_{db2}) = r_{o1} || r_{o2} = 110 \text{ K}\Omega$
- $C_{gd2} = W L_d C_{ox} = 100(0.2)(0.7) = 14 \text{ fF}$
 $R(C_{gd2}) = (1/g_{m3}) || r_{o3} || 30K + r_{o1} || r_{o2} + g_{m2}[\frac{1}{g_{m3}} || r_{o3} || 30K][r_{o1} || r_{o2}]$
 $\approx 2(r_{o1} || r_{o2}) = 220 \text{ K}\Omega$; $T_{gd2} = 0.014(220) = 3 \text{ ns}$
- $C_{gd1} = W L_d C_{ox} = 206(0.2)(0.7) = 28 \text{ fF}$
 $R(C_{gd1}) = 1/g_{m1} + r_{o1} || r_{o2} + (1/g_{m1}) g_{m1}(r_{o1} || r_{o2})$
 $\approx 2(r_{o1} || r_{o2}) = 220 \text{ K}\Omega$; $T_{gd1} = 0.028(220) = 6.2 \text{ ns}$
- So $f_{-3dB} \approx 1/(2\pi \sum T) = 1/(2\pi(6.2 + 12.5 + 3)) = 7.3 \text{ MHz}$
- Note that none of the time constants dominates here

$$f_{-3dB} \approx \frac{1}{2\pi(4400\text{ns})} = \boxed{36\text{ KHz}}$$

(a)  M_1 = source follower with perfect current source, $\lambda = 0$, and no body effect. $\rightarrow$ Gain = 1
 M_2 = CS AMP
 $\frac{v_{od}}{v_{id}} = -g_{m2}(5k) = \boxed{-9.6}$
 $g_{m1} = \sqrt{2(60)(100)(1.6)(10)} = 270 \mu A/V$
 $g_{m2} = \sqrt{2(60)(100)(1.6)(500)} = 1.9 mA/V$

(b) Since $M1$ is an ideal source follower, its gain = 1. Therefore, the voltage across C_{gs1} doesn't change. So ignore C_{gs1} . Note that if you include C_{gs1} , ZUTC only predicts the pole. (It ignores the zero.)

$$C_{gd1} = W L d C_{ox1} = 100(0.2)(0.7) = 14 \text{ fF}$$

$$R(C_{gd1}) = 10 \text{ K}\Omega; T_{gd1} = 0.014(10) = 0.14 \text{ ns}$$

$$C_{sbo1} = 5(100)(0.4) + \underline{100(0.4)} = 240 \text{ fF}; \text{ Need DC Voltage at Source of } M1$$

$$V_{S1} = 0 - V_{t1} - V_{OV1}; V_{OV1} = \sqrt{2(10)/(60 \cdot 100/1.6)} = 0.07 \text{ V}$$

$$V_{S1} = 0 - 1 - 0.07 = -1.07 \text{ V}$$

$$Csb_1 = 240 / \sqrt{1 + (-1.07 - (-6)) / 0.6} = 80 \text{ fF}$$

$$R(C_{sb1}) = 1/qm_1 = 3.7 \text{ K}\Omega ; T_{csb1} = 0.08(3.7) = 0.30 \text{ ns}$$

$$C_{gs2} = 23(100)(1.6)(0.7) + 100(0.2)(0.7) \approx 90 \text{ fF}$$

$$R(Cgs_2) = 1/gm_1 = 3.7 K\Omega; T_{Cgs_2} = 0.09(3.7) = 0.33 ns$$

$$C_{db02} = 5(100)(0.4) + 100(0.4) = 240 \text{ fF} ; \text{ Need DC } V_{D2}$$

$$V_{D_2} = 6 - 5K(0.5mA) = 3.5V$$

$$Cdb_2 = 240 / \sqrt{1 + (3.5 + 6) / 0.6} \approx 60 \text{ ft}$$

$$R_{Cdb_2} = 5k\Omega; \quad \tau_{db_2} = 0.06(5k) = 0.30 \text{ ns}$$

$$C_{ad_2} = w L d \cos^2 i = 100 (0.2) (0.7) = 14 \text{ tF}$$

$$R(C_g d_2) = 1/gm_1 + 5k + gm_2(1/gm_1)5k = 44k\Omega; T_{gd_2} = 0.014(44) = 0.62 ns$$

$$f_{-3dB} \approx 1/[2\pi(0.14 + 0.30 + 0.33 + 0.30 + 0.62)] = 94 \text{ MHz}$$

COMMENT: In working ZUTC problems, it pays to be careful, organized, & neat.