

EEC 210 Fall 2008 Midterm

Rajeevan Amirtharajah
Dept. of Electrical and Computer Engineering
University of California, Davis

November 13, 2008

Name:

Instructions: This test consists of 4 problems and 14 pages, including the cover sheet. Please make sure that you have all of them. This is an open-book, open-notes test. State any assumptions you make and show complete work to receive credit. The time limit is 80 minutes. The problems are weighted as shown below:

Grading: *Solutions*

Problem	Maximum	Score
1	13	
2	13	
3	12	
4	12	
Total	50	

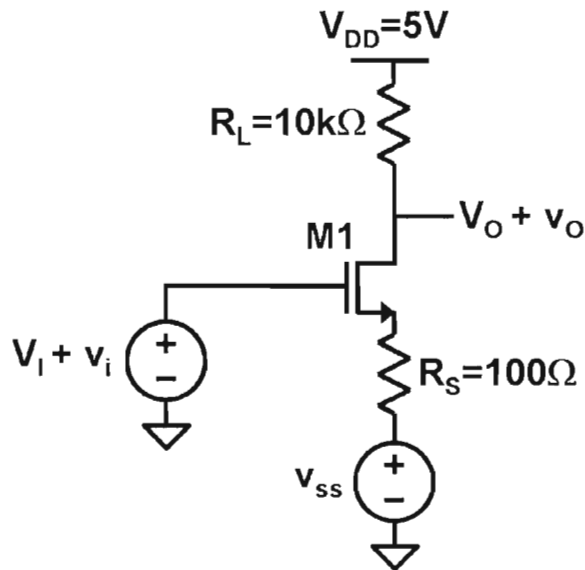


Figure 1: Resistive load amplifier.

1 Resistive Load Amplifier

Figure 1 shows a resistively loaded amplifier. Source v_{ss} is a small-signal source only. For this problem, use the transistor parameters in Table 1.

Parameter	NMOS
V_t	1 V
L_d	0
X_d	0
k'	$300 \mu\text{A}/\text{V}^2$
γ	0
W/L	16/3
λ	$1/100 \text{ V}^{-1}$

Table 1: Problem 1 Transistor Parameters.

Problem 1.1 (4 points) Find the large-signal input voltage V_I such that the large-signal output voltage $V_O = 3\text{V}$. You may ignore channel length modulation for this part.

$$V_O = 3\text{V} \Rightarrow I_D = \frac{V_{DD} - V_O}{R_L} = \frac{2\text{V}}{10\text{k}\Omega} = 0.2\text{mA}, \quad V_{GS} = V_I + I_D R_S \quad (1\text{pt.})$$

$$0.2\text{mA} = \frac{k'}{2} \left(\frac{W}{L}\right) (V_{GS} - V_t)^2 = \frac{300\mu\text{A}/\text{V}^2}{2} \left(\frac{16}{3}\right) (V_I - (0.2\text{mA})(100\Omega) - 1\text{V})^2 \quad (2\text{pts.})$$

$$\boxed{V_I = 1.52 \text{ V}} \quad (1\text{pt.})$$

Problem 1.1 (cont.)

$$\text{or } V_{ov} = \sqrt{\frac{2 I_D}{k' (W/L)}} = \sqrt{\frac{2 (200 \mu A)}{300 \frac{\mu A}{V^2} \left(\frac{16}{3}\right)}} = 0.5 V \quad (1 \text{ pt.})$$

$$V_I = I_D R_S + V_t + V_{ov} = (200 \mu A)(100 \Omega) + 1 V + 0.5 V \quad (1 \text{ pt.})$$

$$\boxed{V_I = 1.52 V} \quad (1 \text{ pt.})$$

Problem 1.2 (4 points) Find the small-signal voltage gain $a_{v1} = \frac{v_o}{v_i}$.

CS Amp w/ Degeneration

$$a_{v1} = G_m (R_o \parallel R_L) \quad g_m = \sqrt{2 I_D k' \left(\frac{W}{L}\right)} = \sqrt{2 (200 \mu A) \left(\frac{300 \mu A}{V^2}\right) \left(\frac{16}{3}\right)} \quad (1 \text{ pt.})$$

$$= 0.8 \text{ mS}$$

$$r_o = \frac{1}{\lambda I_D} = \frac{1}{(0.01 V^{-1})(200 \mu A)} = 500 \text{ k}\Omega$$


$$G_m = \frac{g_m}{1 + (g_m + \underset{0}{g_{mb}}) R_S + \frac{R_S}{r_o}} \simeq \frac{g_m}{1 + (g_m) R_S} = 741 \mu S \quad (1 \text{ pt.})$$

$$R_o = R_S + r_o (1 + g_m R_S) \simeq r_o (1 + g_m R_S) = 540 \text{ k}\Omega \quad (1 \text{ pt.})$$

$$R_o \parallel R_L = 9818 \Omega$$

$$a_{v1} = (741 \mu S)(9818 \Omega) = \boxed{7.28} \quad (1 \text{ pt.})$$

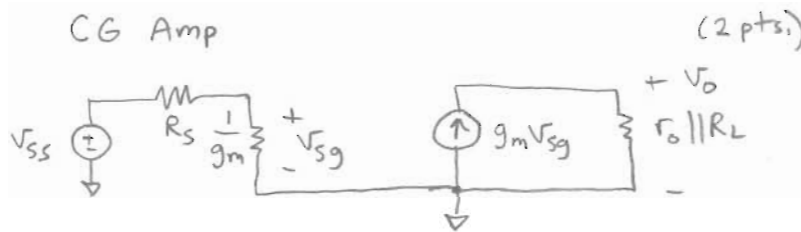Problem 1.3 (4 points) Find the small-signal voltage gain $a_{v2} = \frac{v_o}{v_{ss}}$.



$$\begin{aligned} \frac{v_o}{v_{ss}} &= g_m (r_o \parallel R_L) \frac{1/g_m}{R_s + 1/g_m} \\ &= \frac{(r_o \parallel R_L)}{R_s + 1/g_m} \quad (1 \text{ pt.}) \end{aligned}$$

$$a_{v2} = \frac{(500 \text{ k}\Omega \parallel 10 \text{ k}\Omega)}{100 \Omega + \frac{1}{800 \mu\text{S}}} = \frac{9800}{1350} = \boxed{7.26} \quad (1 \text{ pt.})$$

Problem 1.4 (1 point) Find the power supply rejection ratio $\left| \frac{a_{v1}}{a_{v2}} \right|$.

$$\text{PSRR}^- = \frac{7.28}{7.26} = \boxed{1.00} !$$


2 Differential Amplifier

Figure 2 shows the circuit schematic for a differential amplifier. For this problem, use the transistor parameters in Table 2. Assume that all transistors are biased in saturation and the following circuit parameters: $I_{TAIL} = 400\mu A$, $R_{TAIL} = 500\text{ k}\Omega$, $R_S = 50\Omega$, $(W/L)_1 = (W/L)_2 = 10$, $(W/L)_3 = (W/L)_4 = 8$.

Parameter	NMOS	PMOS
V_t	1 V	-1 V
L_d	0	0
X_d	0	0
k'	$400\text{ }\mu A/V^2$	$100\text{ }\mu A/V^2$
χ	0.25	0.25
λ	0.01 V^{-1}	0.01 V^{-1}

Table 2: Problem 2 Transistor Parameters.

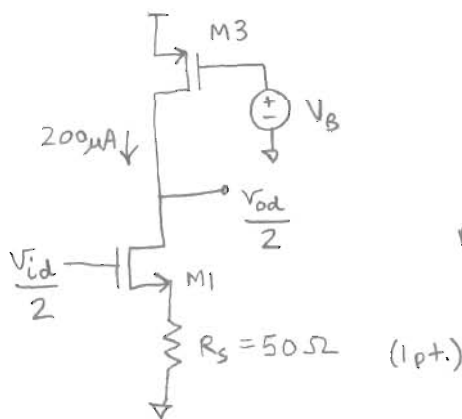Problem 2.1 (4 points) Draw and label the small-signal differential-mode half circuit, and find the differential-mode gain, $\frac{v_{od}}{v_{id}}$, where $v_{id} = v_{i1} - v_{i2}$ and $v_{od} = v_{o1} - v_{o2}$.



CS Amp w/ degen.

$$I_D = 200\text{ }\mu A$$

$$\frac{v_{od}}{v_{id}} = G_m (R_o \parallel r_{o3})$$

$$g_m = \sqrt{k' \left(\frac{W}{L}\right) I_D} = \sqrt{2 \cdot 400\text{ }\mu A/V^2 \cdot 10 \cdot 200\text{ }\mu A} = 1.26\text{ mS}$$

$$r_{o1} = \frac{1}{\lambda I_D} = \frac{1}{(0.01\text{ V}^{-1}) (200\text{ }\mu A)} = r_{o3} = 500\text{ k}\Omega \quad (1\text{ pt.})$$

$$G_m = \frac{g_m}{1 + (1 + \chi) g_m R_S + \frac{R_S}{r_o}} \approx \frac{g_m}{1 + (1 + \chi) g_m R_S} = 1.17\text{ mS} \quad (1\text{ pt.})$$

$$R_o = R_S + r_{o1} [1 + (1 + \chi) g_m R_S] = 539\text{ k}\Omega$$

$$\frac{v_{od}}{v_{id}} = (1.17\text{ mS}) (539\text{ k}\Omega \parallel 500\text{ k}\Omega) = \boxed{303} \quad (1\text{ pt.})$$


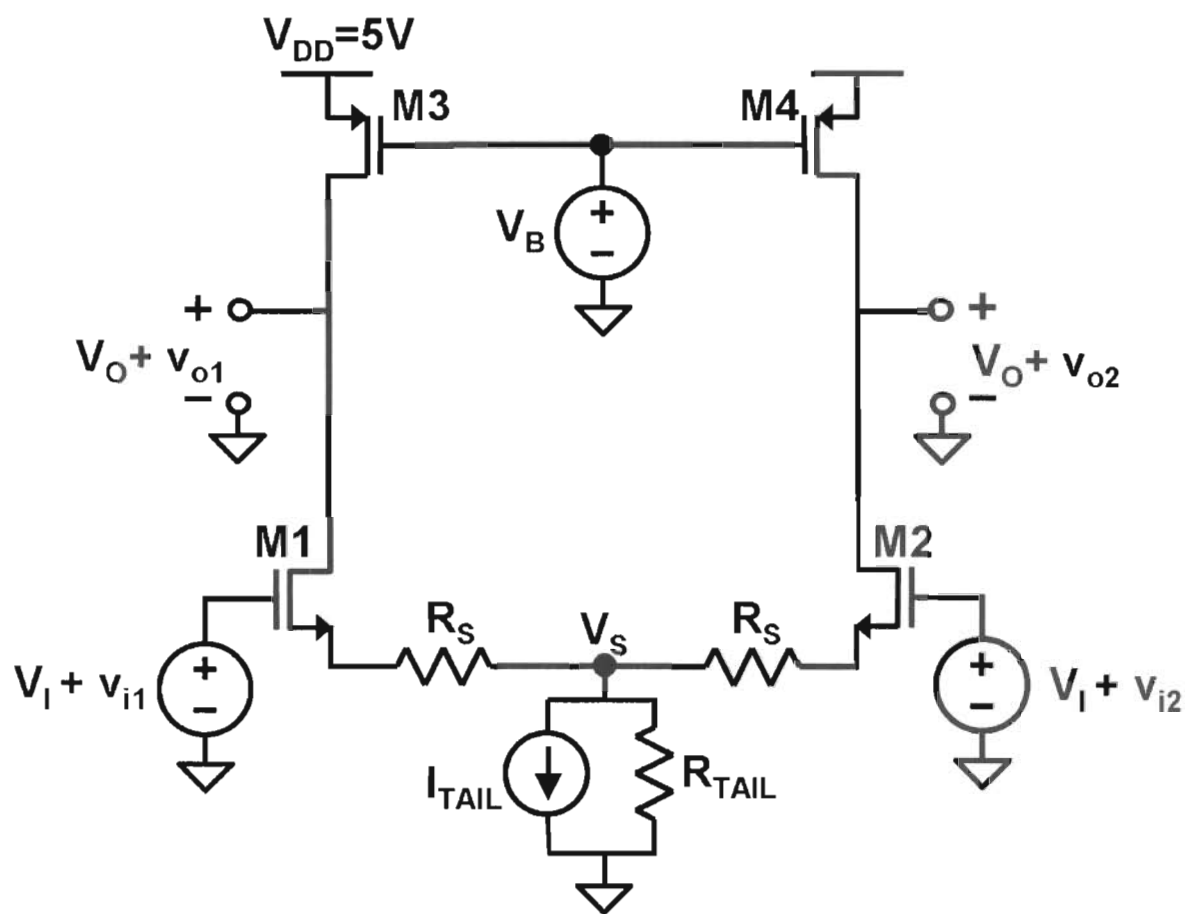


Figure 2: Differential amplifier.

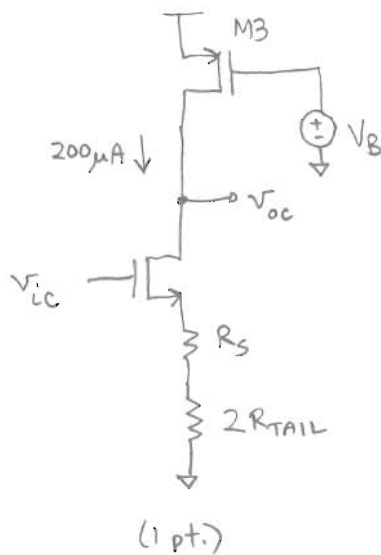Problem 2.2 (4 points) Draw and label the small-signal common-mode half circuit, and find the common-mode gain, $\frac{v_{oc}}{v_{ic}}$, where $v_{ic} = 0.5(v_{i1} + v_{i2})$ and $v_{oc} = 0.5(v_{o1} + v_{o2})$.



CS Amp w/ degeneration

$$\frac{v_{oc}}{v_{ic}} = G_m (R_o \parallel r_{o3})$$

$$G_m = \frac{g_m}{1 + (1+\chi)g_m(R_S + 2R_{TAIL}) + \frac{R_S + 2R_{TAIL}}{r_{o1}}} = 798 \text{ nS} \quad (1 \text{ pt.})$$

$$R_o = R_S + 2R_{TAIL} + r_{o1}(1 + (1+\chi)g_m(R_S + 2R_{TAIL})) = 789 \text{ M}\Omega \quad (1 \text{ pt.})$$

$$\frac{v_{oc}}{v_{ic}} \approx G_m r_{o3} = (798 \text{ nS})(500 \text{ k}\Omega) = \boxed{0.399} \quad (1 \text{ pt.})$$

Problem 2.3 (2 points) Find the common-mode rejection ratio (CMRR).

$$\left| \frac{v_{od}/v_{id}}{v_{oc}/v_{ic}} \right| = \frac{303}{0.399} = \boxed{760} \quad (1 \text{ pt.})$$

(1 pt.)

Problem 2.4 (3 points) Find the large-signal common-mode input voltage V_I assuming $V_{DS1} = V_{DS2} = 1.5V$ and the current through R_{TAIL} is $2\mu A$.

$$R_{TAIL} = 500 k\Omega, I_{R_{TAIL}} = 2\mu A \Rightarrow V_S = 1V$$

$$\begin{aligned} I_{DS1} &= (200\mu A + 1\mu A) = \frac{K'}{2} \left(\frac{W}{L}\right) (V_{GS1} - V_t)^2 (1 + \lambda V_{DS1}) \quad (2 \text{ pts.}) \\ &= \frac{K'}{2} \left(\frac{W}{L}\right) (V_I - V_S - V_t)^2 (1 + \lambda V_{DS1}) \\ &= \frac{400\mu A/V^2}{2} (10) (V_I - 1V - 1V)^2 (1 + 0.01 V^{-1} (1.5V)) \end{aligned}$$

$$\text{Solve for } V_I = V_{ov1} + V_S + V_t = 0.315V + 2V$$

$$V_I = \boxed{2.32V} \quad (\text{ignore } R_S \text{ since } V_{R_S} = 10mV) \quad (1 \text{ pt.})$$

$$\text{or} \\ 2.33V \quad \text{if } I R_S \text{ included}$$

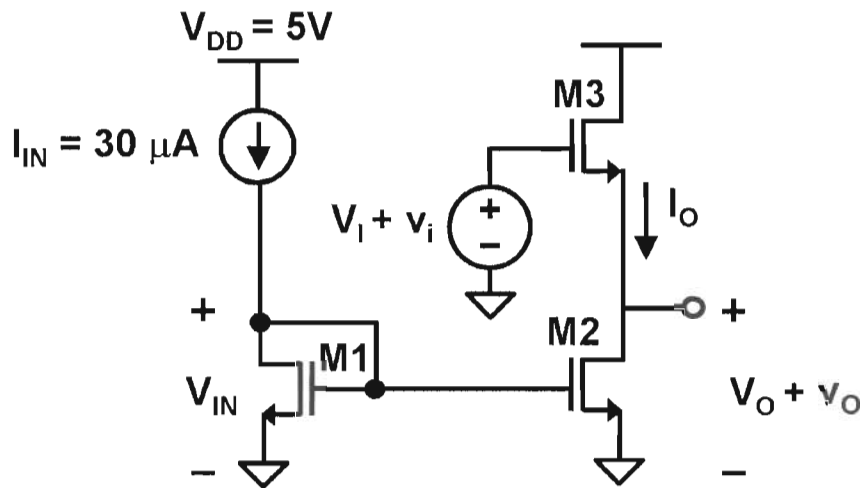


Figure 3: Active load amplifier.

3 Active Load Amplifier

Figure 3 shows an actively loaded amplifier circuit. For this problem, use the transistor parameters in Table 3. For the circuit in Figure 3, assume the following circuit parameters: $(W/L)_1 = 2$, $(W/L)_2 = 20$, and $(W/L)_3 = 30$.

Parameter	NMOS	PMOS
V_t	1 V	-1 V
L_d	0	0
X_d	0	0
k'	$300 \mu\text{A}/\text{V}^2$	$100 \mu\text{A}/\text{V}^2$
χ	0.2	0
λ	0.02 V^{-1}	0.02 V^{-1}

Table 3: Problem 3 Transistor Parameters.

Problem 3.1 (4 points) Find the large-signal input voltage V_I required to make the systematic current gain error 0. You can ignore λ when calculating the large-signal current.

$$V_{IN} = V_t + V_{ov1} = V_t + \sqrt{\frac{2I_D}{k' \left(\frac{W}{L}\right)_1}} = 1\text{V} + \sqrt{\frac{2 \cdot 30\mu\text{A}}{300\mu\text{A}/\text{V}^2 \cdot 2}} = 1.32\text{V} \quad (1 \text{ pt.})$$

$$I_D = 10 \cdot I_{IN} = 300\mu\text{A} \quad (1 \text{ pt.})$$

$$\text{Want } V_O = V_{IN} \text{ for 0 systematic offset} \Rightarrow V_O = V_I - V_{GS3} \Rightarrow V_I = V_{IN} + V_{GS3}$$

$$V_{GS3} = V_t + \sqrt{\frac{2I_D}{k' \left(\frac{W}{L}\right)_3}} = 1\text{V} + \sqrt{\frac{2(300\mu\text{A})}{300\mu\text{A}/\text{V}^2 \cdot 30}} = 1.26\text{V} \quad (2 \text{ pts.})$$

Problem 3.1 (cont.)

$$V_I = \boxed{2.57 \text{ V}} \quad (1 \text{ pt.})$$

Problem 3.2 (3 points) Find the minimum large-signal input voltage $V_I(MIN)$.

$$V_{I(MIN)} = V_{O(MIN)} + V_{GS3} = V_{OV2} + V_{GS3} \quad (1 \text{ pt.})$$

$$V_{OV2} = V_{OV1} = \sqrt{\frac{2 \cdot (30 \mu\text{A})}{\frac{300 \mu\text{A}}{\sqrt{2}} (2)}} = 0.32 \text{ V} \quad (1 \text{ pt.})$$

$$V_{I(MIN)} = 1.26 \text{ V} + 0.32 \text{ V} = \boxed{1.58 \text{ V}} \quad (1 \text{ pt.})$$

Problem 3.3 (2 points) Find the output resistance R_o .

Source Follower w/ active load

$$R_o = \frac{1}{g_m + g_{mb} + \frac{1}{r_o} + \frac{1}{R_L}} \quad (1 \text{ pt.})$$

$$\begin{aligned} g_{m3} &= \sqrt{2k' \left(\frac{W}{L}\right)_3 I_o} = \sqrt{2 \left(\frac{300 \mu\text{A}}{\text{V}^2}\right) (30) (300 \mu\text{A})} \\ &= 2.32 \text{ mS} \\ r_{o3} = r_{o2} &= \frac{1}{\lambda I_o} = \frac{1}{(0.02 \text{ V}^{-1}) (300 \mu\text{A})} \\ &= 167 \text{ k}\Omega \end{aligned}$$

$$R_o = \frac{1}{(1+\chi)g_{m3} + \frac{1}{r_{o3}} + \frac{1}{r_{o2}}} = \frac{1}{(1+0.2)(2.32 \text{ mS}) + \frac{2}{167 \text{ k}\Omega}} = \boxed{357 \Omega} \quad (1 \text{ pt.})$$

Problem 3.4 (3 points) Find the small-signal voltage gain $a_v = \frac{v_o}{v_i}$.

$$a_v = \frac{v_o}{v_i} = g_m R_o = (2.32 \text{ mS})(357 \Omega) = \boxed{0.828} \approx \frac{1}{1+\chi} \quad (2 \text{ pts.})$$

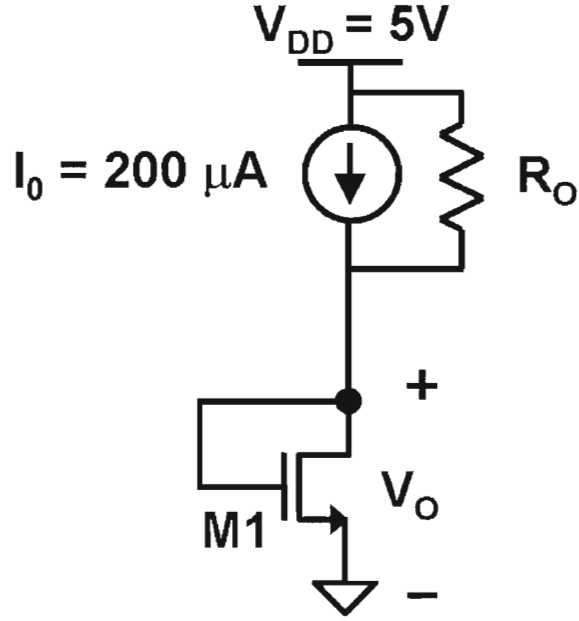


Figure 4: Voltage reference.

4 Voltage Reference

Figure 4 shows a proposed temperature and supply voltage-independent voltage reference circuit. For this problem, use the transistor parameters in Table 4. Note the temperature dependence of V_t and k' .

Parameter	NMOS	PMOS
V_t	1 V	-1 V
$\frac{dV_t}{dT}$	-2.3 mV/K	-3 mV/K
L_d	0	0
X_d	0	0
k'	$100 \mu A/V^2 \left(\frac{T}{300K} \right)^{-1.5}$	$50 \mu A/V^2$
γ	0	0
λ	0	0

Table 4: Problem 4 Transistor Parameters.

Problem 4.1 (5 points) Find W/L such that $\frac{dV_O}{dT} = 0$ at $T = 300\text{K}$ in the limit as $R_O \rightarrow \infty$.

$$V_O = V_{GS1} = V_t + V_{OV1} = V_t + \sqrt{\frac{2I_O}{k'(W/L)_1}} = V_t + \sqrt{\frac{2I_O}{(W/L)_1}} (k')^{-1/2} \quad (2 \text{ pts.})$$

$$V_O = V_t + \sqrt{\frac{2I_O}{(W/L)_1}} \frac{(100\mu\text{A}/V^2)^{-1/2}}{(300\text{K})^{3/4}} T^{3/4}$$

$$\frac{dV_O}{dT} = \frac{dV_t}{dT} + \sqrt{\frac{2I_O}{(W/L)_1}} \frac{(100\mu\text{A}/V^2)^{-1/2}}{(300\text{K})^{3/4}} \frac{3T^{-1/4}}{4}$$

$$\left. \frac{dV_O}{dT} \right|_{T=300\text{K}} = 0 = -2.3\text{mV/K} + \frac{5\text{mV/K}}{\sqrt{(W/L)_1}} \Rightarrow \left(\frac{W}{L} \right)_1 = \left(\frac{5\text{mV/K}}{2.3\text{mV/K}} \right)^2 \quad (2 \text{ pts.})$$

$$\left(\frac{W}{L} \right)_1 = \boxed{4.73} \quad (1 \text{ pt.})$$

Problem 4.2 (3 points) Find the target output voltage V_O at the operating point found in Problem 4.1.

$$V_O = V_t + \sqrt{\frac{2 I_O}{k'(W/L)}} = 1V + \sqrt{\frac{2 \cdot 200 \mu A}{100 \frac{\mu A}{V^2} (4.73)}} = \boxed{1.92 V} \quad (1 \text{ pt.})$$

(2 pts.)

Problem 4.3 (4 points) Suppose $R_O = 100k\Omega$. Find the approximate power supply gain $\frac{\Delta V_O}{\Delta V_{DD}}$ assuming $V_{DD} \gg V_O$. Hint: $(1+x)^{\frac{1}{2}} \approx 1 + \frac{x}{2}$ for small x .

$$V_O = V_t + \sqrt{\frac{2 I_{TOT}}{k'(W/L)}} = V_t + \sqrt{\frac{2}{k'(W/L)}} \left(I_O + \frac{V_{DD} - V_O}{R_O} \right)^{1/2} \quad (1 \text{ pt.})$$

$$\approx V_t + \sqrt{\frac{2 I_O}{k'(W/L)}} \left(1 + \frac{V_{DD}}{2 I_O R_O} \right) \quad (1 \text{ pt.})$$

$$\frac{\Delta V_O}{\Delta V_{DD}} \approx \sqrt{\frac{2 I_O}{k'(W/L)}} \frac{1}{2 R_O} = \sqrt{\frac{2 (200 \mu A)}{100 \frac{\mu A}{V^2} (4.73)}} \cdot \frac{1}{2 \cdot 100k\Omega (200 \mu A)} \quad (1 \text{ pt.})$$

$$= \boxed{2.3 \%} \quad (1 \text{ pt.})$$

Small-signal approach:

$$\frac{\Delta V_O}{\Delta V_{DD}} = \frac{1/g_m}{R_O + 1/g_m}$$

$$\approx \boxed{2.06 \%}$$

$$g_m = \sqrt{2 k' \left(\frac{W}{L} \right) I_{TOT}} = \sqrt{2 \left(\frac{100 \mu A}{V^2} \right) (4.73) (200 \mu A + \frac{5V}{100k\Omega})}$$

$$= 486 \mu S$$