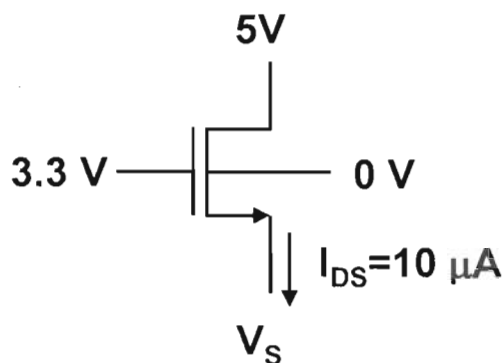


Name: Solutions

Lab Section: \_\_\_\_\_

**Problem 1 (5 points)** For the following transistor, find the value of  $V_S$  which produces the indicated  $I_{DS}$  given:  $W_n = 0.5 \mu\text{m}$ ,  $L_n = 0.1 \mu\text{m}$ ,  $V_{T,n} = 1 \text{ V}$ ,  $\mu_n C_{ox} = 0.5 \times 10^{-4} \text{ A/V}^2$ ,  $\lambda = 0$ ,  $\gamma = 0$ . Show all work to receive full credit.



$$V_{DS} = 5\text{V} - V_S > 3.3\text{V} - V_S - V_{T,n} = 2.3\text{V} - V_S \Rightarrow \text{saturation} \quad (1 \text{ pt.})$$

$$I_{DS} = \frac{\kappa'_n}{2} \frac{W}{L} (V_{GS} - V_{T,n})^2 (1 + \lambda V_{DS}) \quad (1 \text{ pt.})$$

$$V_{GS} = V_{T,n} + \sqrt{\frac{2 I_{DS}}{\kappa'_n W/L}} = 1\text{V} + \sqrt{\frac{2 (10 \mu\text{A})}{0.5 \times 10^{-4} \text{ A/V}^2 (5)}} \quad (1 \text{ pt.})$$

$$V_{GS} = 1.283\text{V} \quad (1 \text{ pt.})$$

$$V_S = V_G - V_{GS} = 2.017\text{V}$$

$$\boxed{V_S = 2.02\text{V}} \quad (1 \text{ pt.})$$

**Problem 2 (2 points)** Suppose  $\lambda = 0.1 \text{ V}^{-1}$ . What is the new current  $I_{DS}$  for the  $V_S$  you found above?

$$\begin{aligned} I_{DS} &= \frac{\kappa'_n}{2} \left(\frac{W}{L}\right) (V_{GS} - V_{T,n})^2 (1 + \lambda V_{DS}) \\ &= \frac{500 \mu\text{A/V}^2}{2} \left(\frac{5}{1}\right) (1.283\text{V} - 1\text{V})^2 (1 + 0.1 \text{ V}^{-1} (5 - 2.02\text{V})) \quad (1 \text{ pt.}) \end{aligned}$$

$$\boxed{\text{New } I_{DS} = 13 \mu\text{A}} \quad (1 \text{ pt.})$$