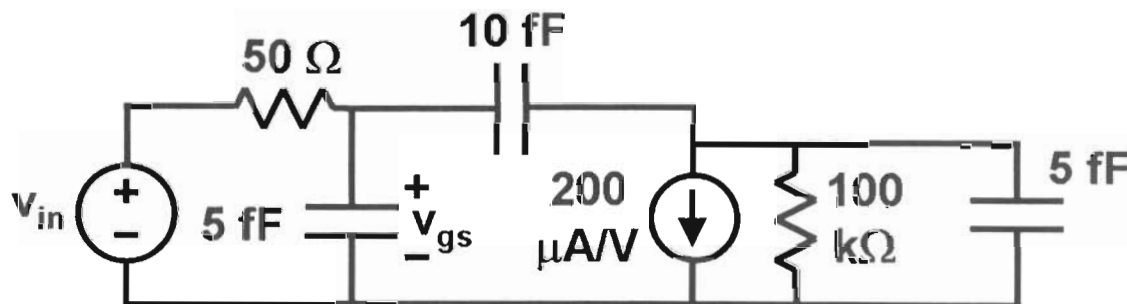


Name: Solutions


Lab Section: _____

Problem 1 (10 points) For the following small-signal model of a MOS amplifier, use the method of Zero-Value Time Constants (Open-Circuit Time Constants) to estimate the dominant pole location. Use the Miller Approximation to simplify your analysis. Show all work and express your final answer in Hz.



$$|A_v|^{(DC)} = g_m r_o = (200 \mu A/V)(100 k\Omega) = 20 \quad (2 \text{ pts.})$$

Miller Approx:

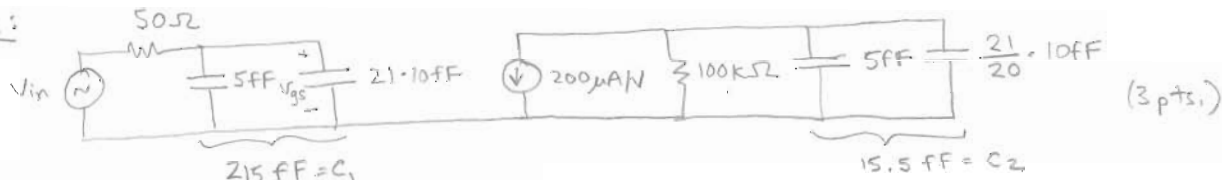

$$R_{EQ1} = 50 \Omega \quad \tau_1 = (215 \text{ fF})(50 \Omega) = 10.75 \text{ ps} \quad (1 \text{ pt.})$$

$$R_{EQ2} = 100 k\Omega \quad \tau_2 = (100 k\Omega)(15.5 \text{ fF}) = 1.55 \text{ ns} \quad (1 \text{ pt.})$$

$$f_{\text{pole}} = \left(\frac{1}{2\pi} \right) \left(\frac{1}{\sum \tau_i} \right) = \frac{1}{2\pi (1.56 \text{ ns})} = 102 \text{ MHz} \quad (2 \text{ pts.})$$

Harder Way:

$$R_1 = 50 \Omega, C_1 = 5 \text{ fF} \Rightarrow \tau_1 = 0.25 \text{ ps}$$

$$R_2 = 100 k\Omega, C_2 = 5 \text{ fF} \Rightarrow \tau_2 = 0.5 \text{ ns}$$

$$R_3 = r_o + R_I(1 + g_m r_o) = 101 k\Omega, C_3 = 10 \text{ fF} \Rightarrow \tau_3 = 1.01 \text{ ns}$$

$$f_{\text{pole}} = \frac{1}{2\pi} \frac{1}{\sum \tau_i} = \frac{1}{2\pi} \frac{1}{1.51 \text{ ns}} = 105 \text{ MHz}$$

$$f_{\text{POLE}} (\text{Hz}) = \boxed{102 \text{ MHz}} \quad (1 \text{ pt.})$$