

EEEC 216 Lecture #5: Low Power Circuits 2

**Rajeevan Amirtharajah
University of California, Davis**


Outline

- **Announcements**
- **Review: Static, Ratioed, and Pass Gate CMOS Logic**
- **Dynamic Logic**
- **Impact of Internal Circuit Nodes**
- **Sizing**
- **Clocking Styles Overview**
- **Static Latches and Flip-Flops**

Outline


- Announcements
- **Review: Static, Ratioed, and Pass Gate CMOS Logic**
- Dynamic Logic
- Impact of Internal Circuit Nodes
- Sizing
- Clocking Styles Overview
- Static Latches and Flip-Flops

Static CMOS Logic

 

- **Pull-Up network consists of PMOS devices connected complementary to NMOS Pull-Down network**


Complex Gate Example

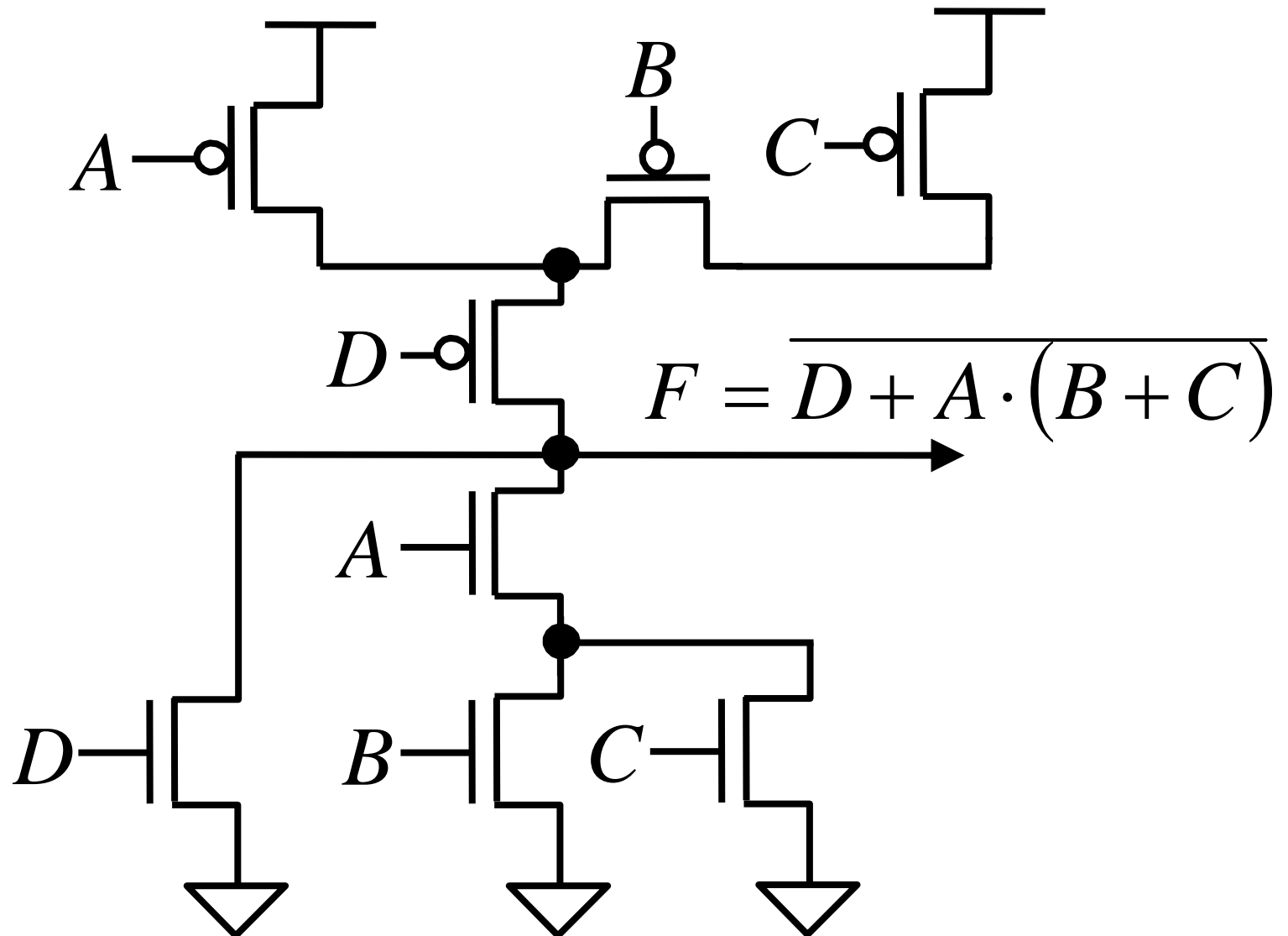

Static CMOS for Low Power

- **Dynamic power and short circuit current applies**
 - Mismatched delays can lead to glitching, increased dynamic power
 - Dynamic logic eliminates glitches, short circuit
- **Only static power due to leakage**
- **Fully complementary design has high noise margin**
 - $V_{OH} = V_{DD}$, $V_{OL} = GND$
 - Design style more scalable to lower supply voltages
 - Implies lower threshold voltages can be used also
- **PMOS devices may degrade performance**
 - High input capacitance, slow series P-stacks

Ratioed Logic Styles

 


- **Pull-Up network replaced by simple (often resistive) load**

Ratioed Logic for Low Power

- **Dynamic power and static current applies**
 - Mismatched delays can lead to glitching, increased dynamic power
 - Conducts current as long as output is low
- **Reduced noise margin because of resistance ratios**
 - $V_{OH} = V_{DD}$, $V_{OL} = V_{DD} R_{PDN} / (R_L + R_{PDN})$
 - Could increase leakage in load gates whose NMOS gates are at V_{OL} instead of ground
- **Reduced transistor count decreases input capacitance**
- **Low-to-High transition speed determined by load (could be faster or slower than series PMOS)**
- **Most useful for high fan-in gates**

 Differential Cascode Voltage Switch Logic




- **PDN1 ON implies PDN2 OFF pulls Out low, turning on PMOS which pulls complement high**

DCVSL Summary for Low Power


- **Differential logic style**
 - Generating both polarities of output can improve speed (eliminates inverters)
 - Extra noise immunity to common-mode noise
 - Convenient for self-timed (asynchronous) logic design
- **Still a ratioed logic style, even though outputs transition rail-to-rail**
 - PMOS must be sized carefully to ensure functionality
 - Pulldown networks must overcome PMOS on other side
- **Short circuit current flows while outputs are switching (pulldown fighting opposite side PMOS)**
- **Twice the number of NMOS inputs compared to single-ended ratioed logic styles, higher input capacitance**

Complementary Pass Transistor Logic

 

- Since complementary signals needed anyway, can create a fully differential version of pass gate logic

CPL Basic Gates: AND / NAND

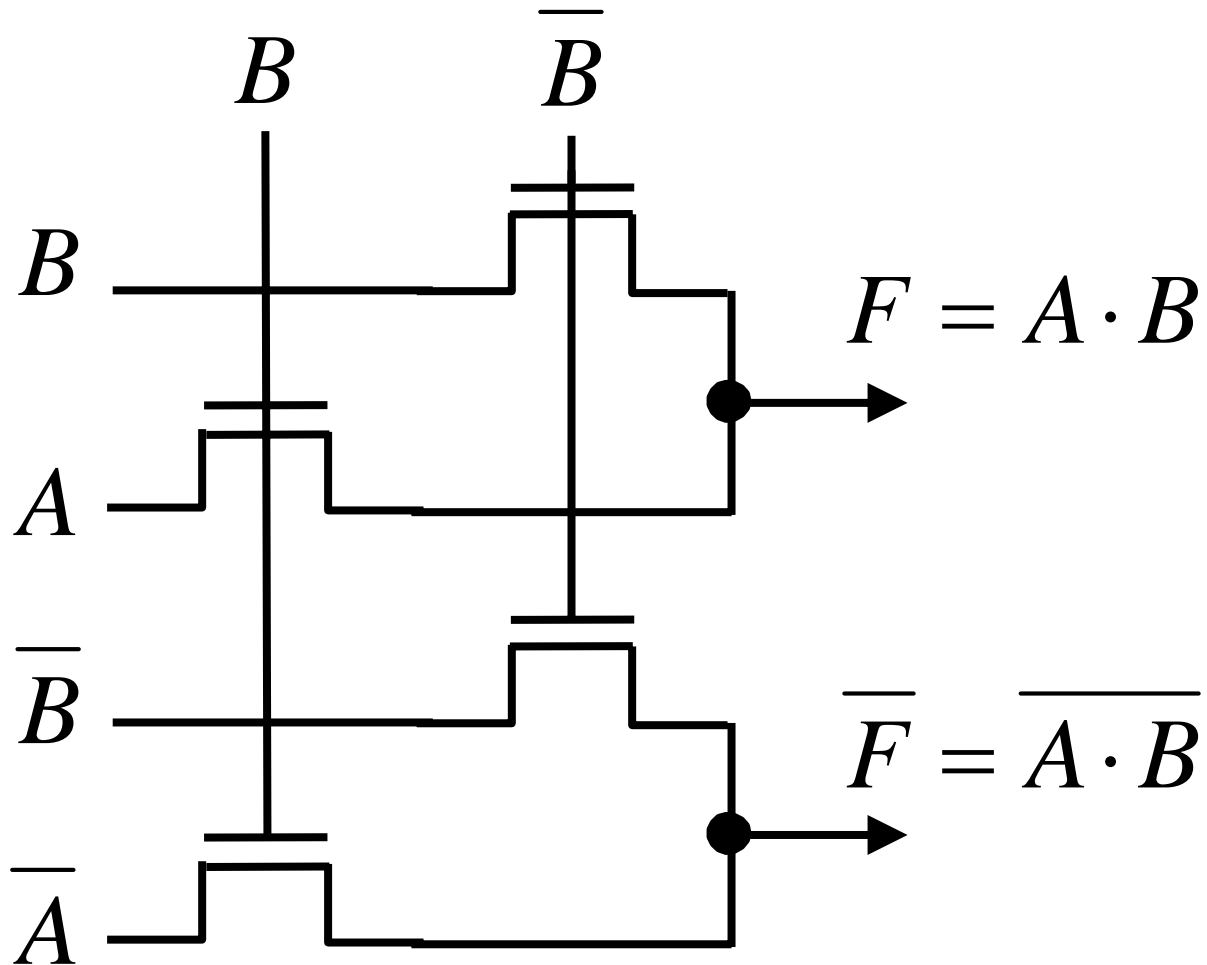

CPL Summary for Low Power

- **Fully differential signals**
 - Requires more devices, but simplifies complex gates like XOR, full adder; eliminates extra inverters
- **Static logic style**
 - Output nodes always have a low impedance path to V_{DD} and GND
 - Improves resilience to noise events
- **Very modular design style**
 - All gates share same fundamental topology: only inputs are permuted to implement other logic functions
- **Energy is low (good PDP) but speed is poor (bad EDP)**
 - Series transistors have high resistance
 - Circuit techniques necessary to overcome V_{Tn} drops

Outline

- Announcements
- Review: Static, Ratioed, and Pass Gate CMOS Logic
- **Dynamic Logic**
- Impact of Internal Circuit Nodes
- Sizing
- Clocking Styles Overview
- Static Latches and Flip-Flops


Summary of CMOS Logic Styles

- **Nonclocked Logic**
 - Does not require clock for proper logic operation (although clocks may be required for state operation)
 - Static CMOS, ratioed logic, DCVSL, Pass-Gate logic
- **Clocked Logic**
 - Periodic signal required for correct logic operation as well as for state (latches and flip-flops)
 - Dynamic logic (domino, NP-CMOS)
- **Clocked styles faster in general, but also consume more power (can be observed in Power-Delay Product)**


Dynamic CMOS Logic Concepts

- **Precharge Phase**
 - Output node charged to reference voltage and left floating before evaluation
 - Load capacitance “stores” the precharge value
- **Evaluation Phase**
 - Path to change the output node voltage energized by turning on evaluation transistor
 - Depending on inputs, load capacitance “written” with final value (changed from precharge value or left unchanged)
- **Inputs must make at most one transition during evaluation**
- **Output can be left high impedance, unlike static CMOS**

Dynamic CMOS Logic

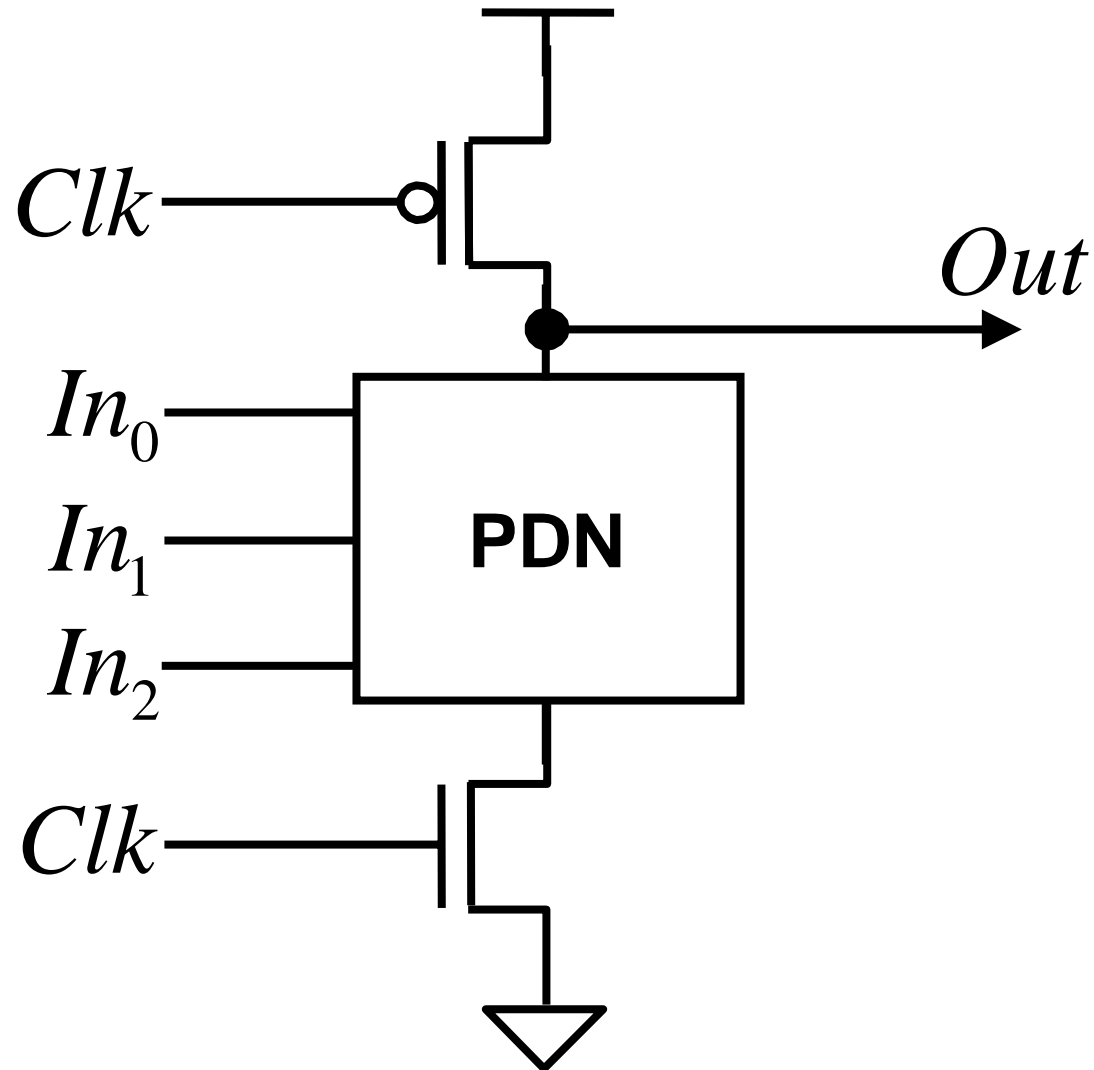

Dynamic CMOS Two-Input NAND Gate

 


- **PMOS precharges (Clk low), NMOS evaluates (Clk high)**

Dynamic CMOS Logic Gate Properties


- **Logic function implemented by NMOS pulldown network**
 - Design of PDN identical to static CMOS
- **Number of transistors for N-input dynamic gate is $N+2$ ($2N$ for static CMOS gate)**
 - Lower area, lower input capacitance
- **Nonratioed logic family: sizing of PMOS device independent of sizing of PDN**
 - Wider devices imply faster precharge, more clock power
- **Gates only consume dynamic power**
 - Ideally, no static current path exists when gate evaluates
- **Fast! Reduced input capacitance, all current to output**

Cascading Dynamic CMOS N-blocks

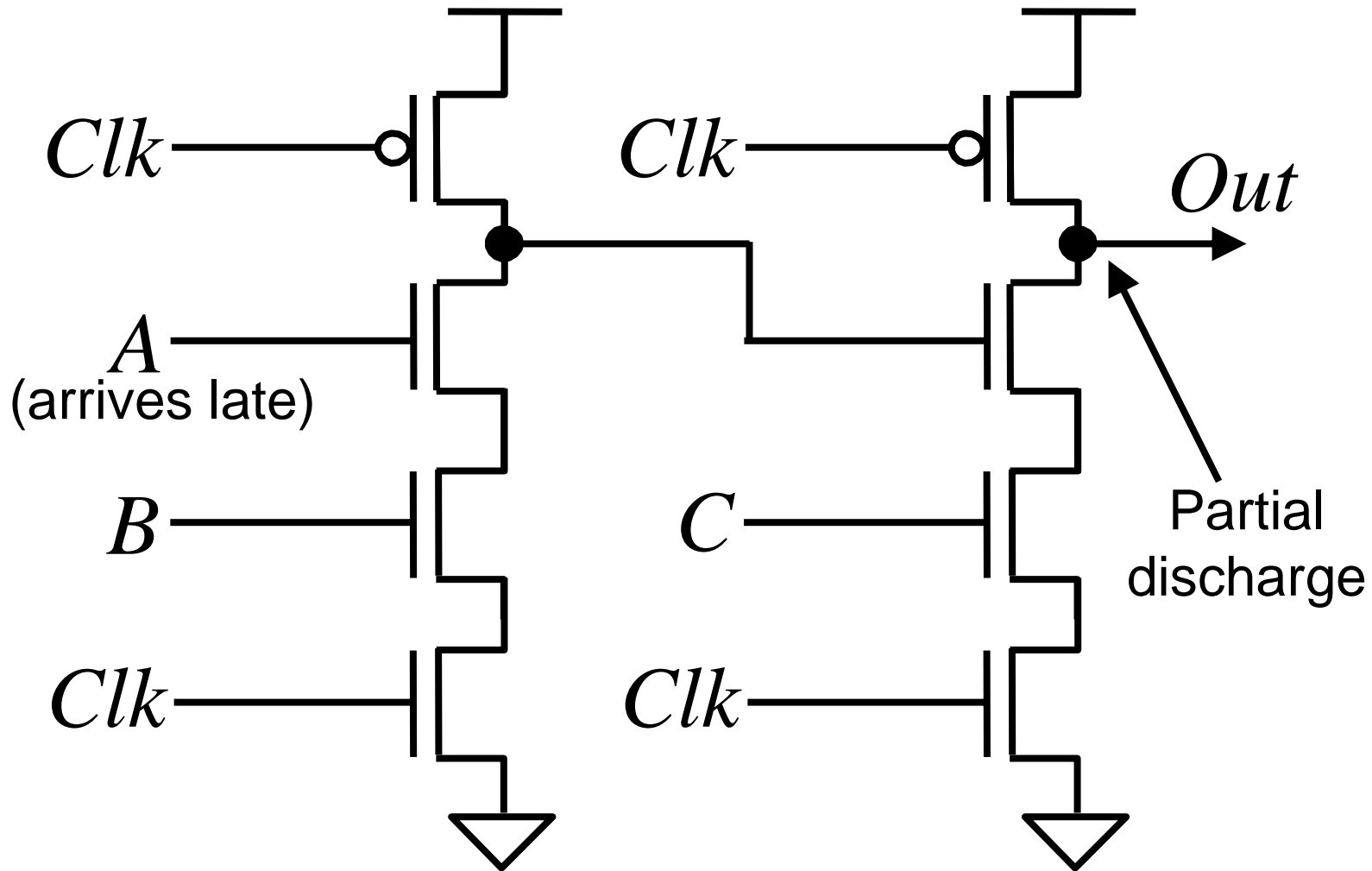


- **Problem: late arriving inputs cause false output discharge**

Domino CMOS Logic

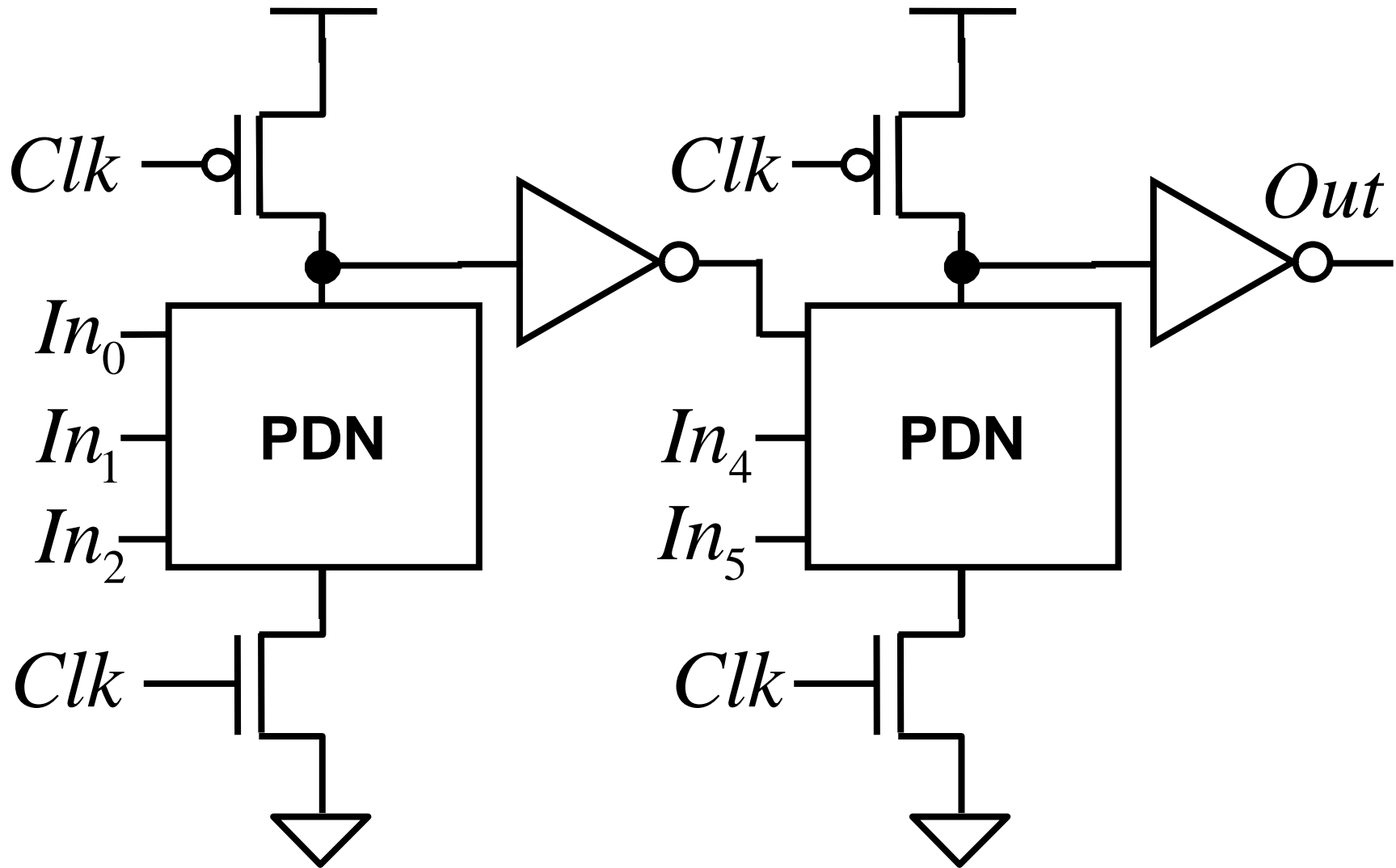

NP-CMOS Logic

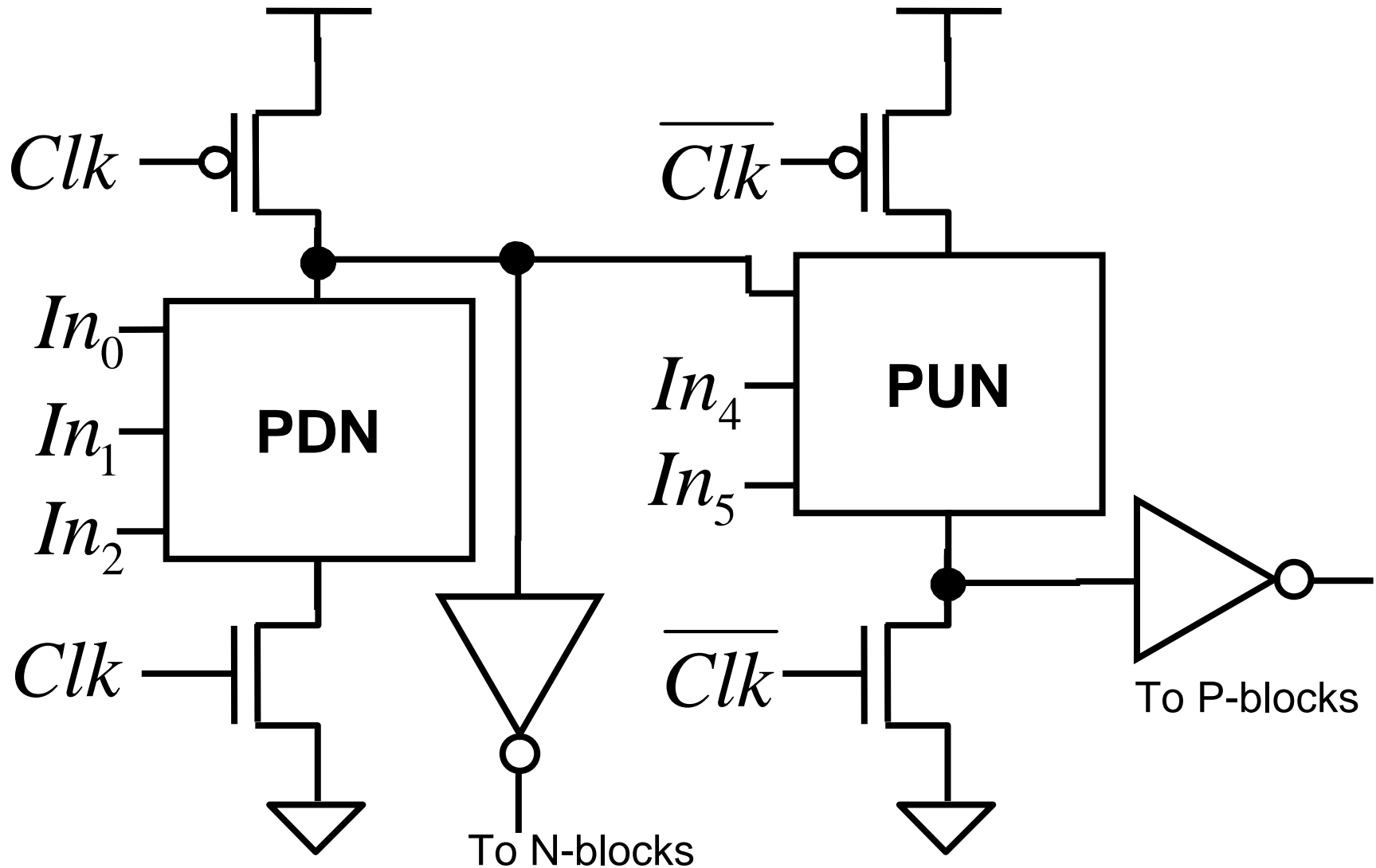

Variations on the Domino Theme


- **Multiple-Output Domino**

- Exploit situation when certain outputs are subsets of other outputs to reduce area
- Precharge intermediate nodes in PDN and follow with inverters to drive other N-block dynamic gates


- **Compound Domino**

- Use complex static CMOS gates (NANDs, NORs) on outputs of multiple dynamic gates in parallel
- Replaces large fanin domino gates with lower fanin gates
- Capacitive coupling from static gate outputs to dynamic gate outputs an issue

Multiple Output Domino CMOS Logic

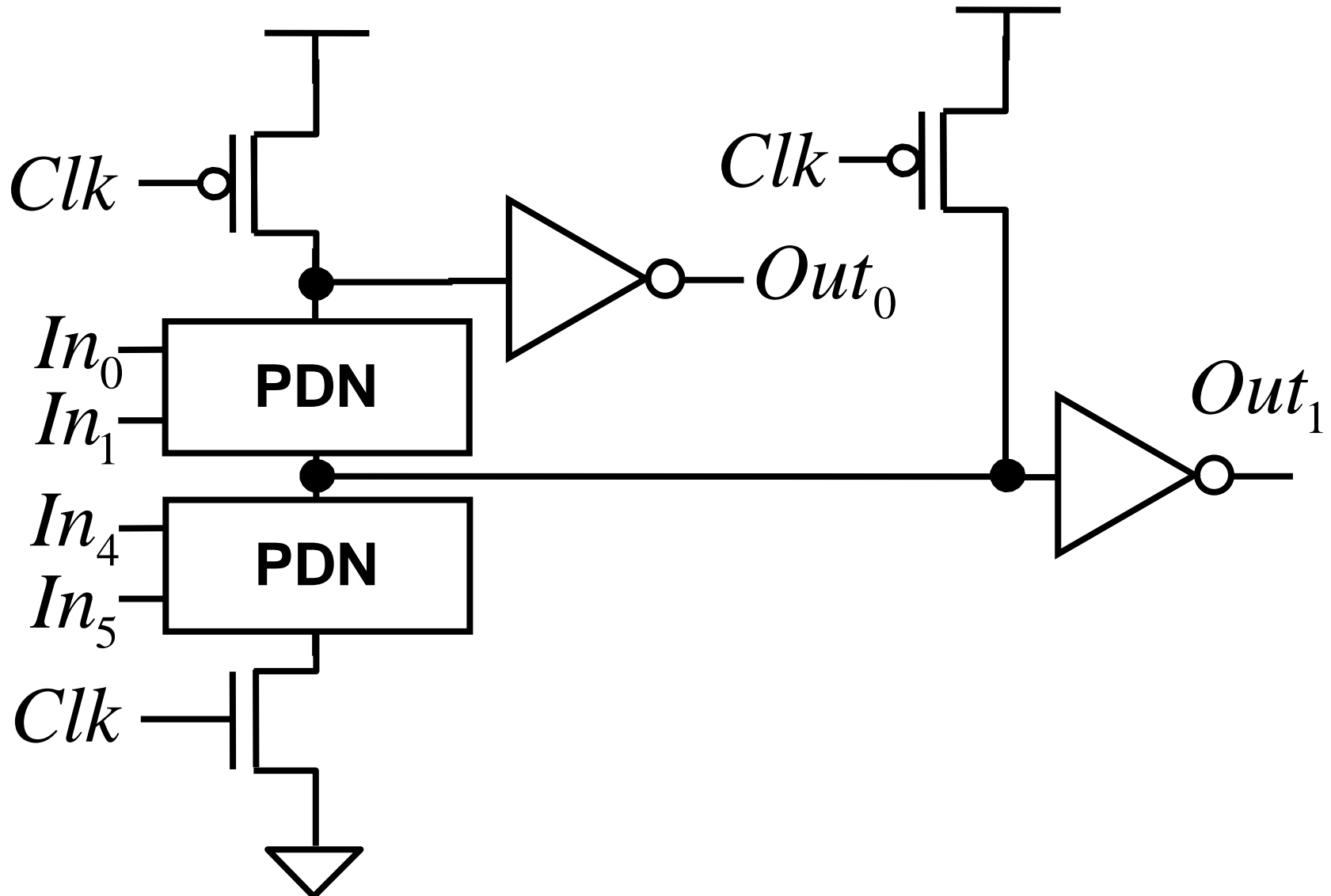

Compound Domino CMOS Logic

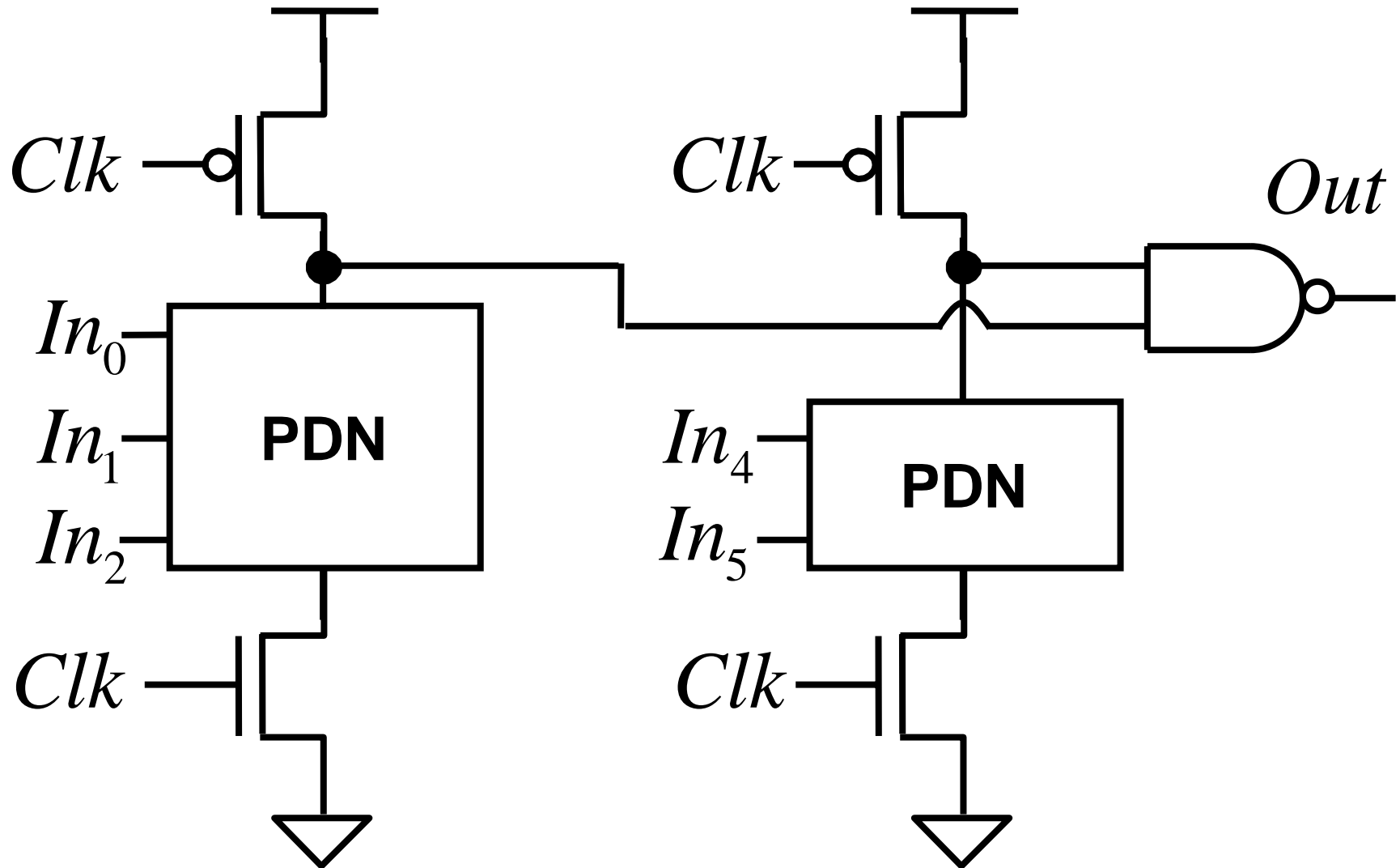

Dynamic Gate Activity Factor

Static Gate Activity Factor Equation:

$$\alpha_{0 \rightarrow 1} = p_0 p_1 = p_0 (1 - p_0)$$

- **Dynamic logic has higher activity due to periodic precharge and discharge**
- **Output transition probability independent of input state, dependent on input probabilities**
- **Output makes low-high transition if discharged during previous evaluate phase:**

$$\alpha_{0 \rightarrow 1} = p_0 = \frac{N_0}{2^N}$$

- **N_0 is the number of 0s in truth table output column**

Dynamic Logic Design for Low Power

- **Advantages for low power**
 - Lower physical capacitance since fewer devices used to implement given logic function
 - Input loading lower since no dual PMOS devices
 - Gates *must* allow only one transition for correct operation (i.e., no glitching!)
 - No short circuit power since pullup path not enabled when evaluating output
- **Disadvantages for low power**
 - Higher clock power since guaranteed clock node transition
 - More than minimal number of devices for implementation
 - Higher switching activity as shown earlier

Signal Integrity Issues in Dynamic Design

- **Charge leakage**
 - High impedance nodes can lose charge due to leakage
 - Can be offset by adding feedback devices to trickle charge the nodes and maintain state
- **Charge sharing**
 - Parasitic capacitances on intermediate nodes in PDN can pull charge from output node, degrading output state
- **Capacitive coupling**
 - High impedance nodes sensitive to adjacent node transitions coupling in noise
- **Clock feedthrough**
 - Capacitive coupling between clock input and output node


Closing Thoughts on Dynamic Logic

- **Dynamic logic is an aggressive design style**
 - Performance can be very good, very fast circuits
 - Noise issues require care to guarantee correct operation
 - Sensitivity to noise impedes aggressive voltage scaling
 - Leakage may require “staticizing” gate anyway using feedback to prevent output level degrading
 - Cannot reduce clock frequency arbitrarily for testing
 - Must evaluate power tradeoffs carefully during design

Outline

- Announcements
- Review: Static, Ratioed, and Pass Gate CMOS Logic
- Dynamic Logic
- **Impact of Internal Circuit Nodes**
- Sizing
- Clocking Styles Overview
- Static Latches and Flip-Flops

Complex Gate Power Example

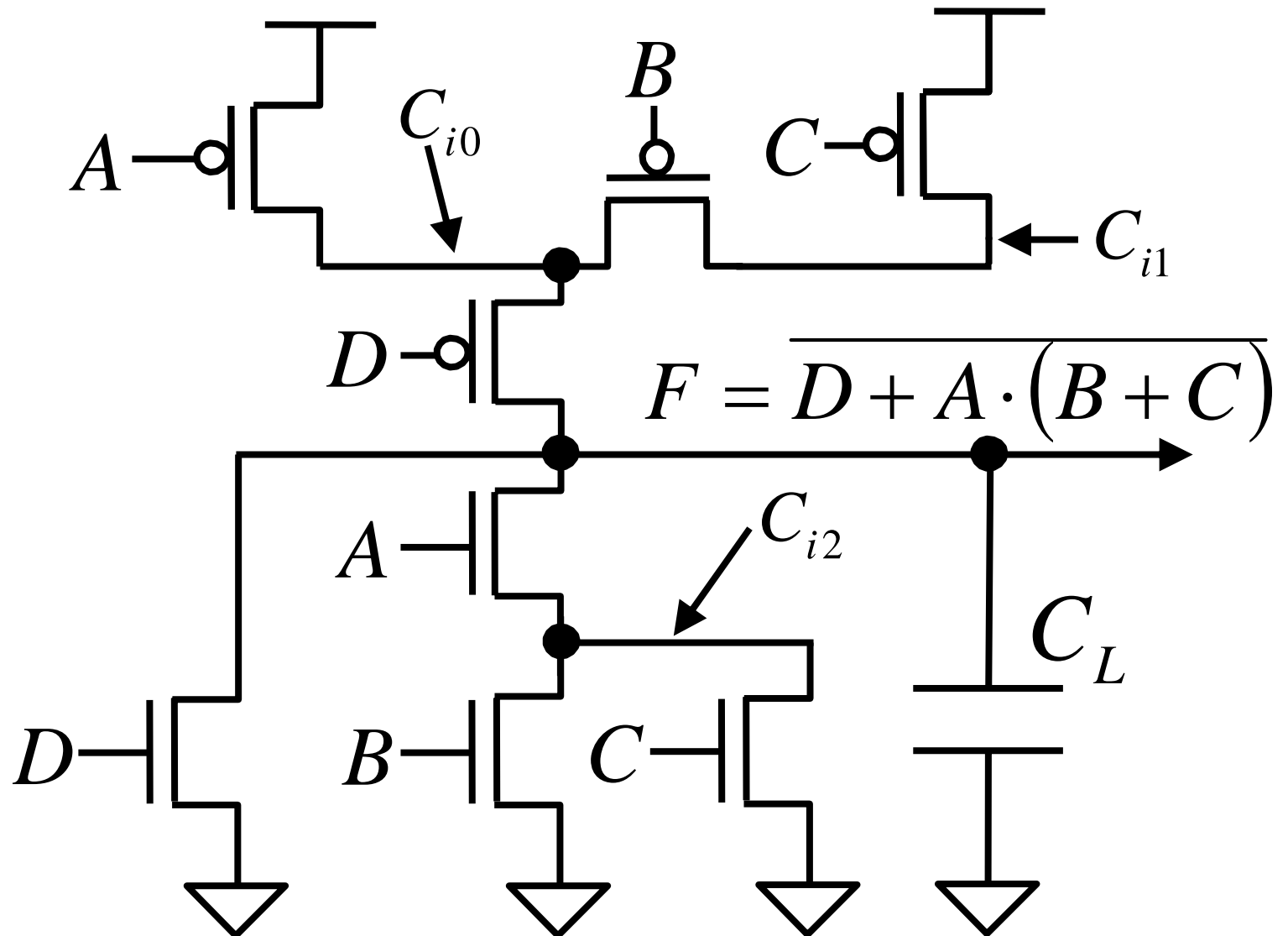

Internal Node Capacitance Example

1. Suppose in Cycle 0, $A = B = C = D = 0$, $F = 1$, then C_{i0} , C_{i1} charged to V_{DD} .
2. In Cycle 1, A and C transition high, other inputs stay low.
3. Capacitors C_{i0} and C_{i1} in addition to output load C_L must all be discharged.
4. Depending on the state of the inputs in cycles preceding Cycle 0, C_{i2} may need to be discharged as well (for example, if A was the last input to transition low).

Power Consumption With Internal Nodes

- **Gate represents a variable capacitance to power and ground rails**
 - Capacitance depends on current state and history of input signals
- **Optimal routing of equivalent inputs is to put signal with highest activity factor closest to output**
 - Reduces the amount of switched capacitance and power for the gate
 - Similar to optimizing gate inputs for speed, but not necessarily the same
- **Can incorporate internal node capacitances into power estimation methodology**

Power Estimation With Internal Nodes

- Incorporate into internal node capacitances into dynamic power estimation:

$$P = V_{DD}^2 f \left(C_L \alpha_L + \sum_{n_i} C_{n_i} \alpha_{n_i} \right)$$

- Where C_{n_i} are normalized internal node capacitances
 - Many internal nodes may typically charge only to $V_{DD} - V_{Tn}$
 - Can fold this voltage factor into either capacitance or activity, but capacitance makes more sense since it corresponds to charge
- Because input history affects internal nodes, computing activity is NP-hard (usually just estimate)

Final Words on Internal Nodes

- **Data dependent capacitance affects speed as well as power**
 - Try to minimize through layout: share sources and drains by implementing in the same diffusion whenever possible
- **In addition to data dependence, source / drain depletion region capacitances depend on voltage also**
- **Consider both effects in extreme high performance and extreme low power designs**
 - Late generation Alpha processors from Compaq considered data and voltage dependence in delay models for cells
 - Must have a lot of confidence in simulation and process characterization to optimize this way


Outline

- Announcements
- Review: Static, Ratioed, and Pass Gate CMOS Logic
- Dynamic Logic
- Impact of Internal Circuit Nodes
- **Sizing**
- Clocking Styles Overview
- Static Latches and Flip-Flops


Sizing for Speed and Low Power

- **Lowest level of design optimization**
 - Explore sizing for minimum delay and energy and compare optimal points
- **Will see that device sizing combined with voltage reduction is very effective approach to reducing energy consumption**
- **Still an ongoing area of research**
 - Optimal points can change quantitatively as device characteristics change (for example, due to velocity saturation)
 - Choice of metric to optimize (PDP vs. EDP) important
 - Increased leakage affects shifts optimal point to smaller devices

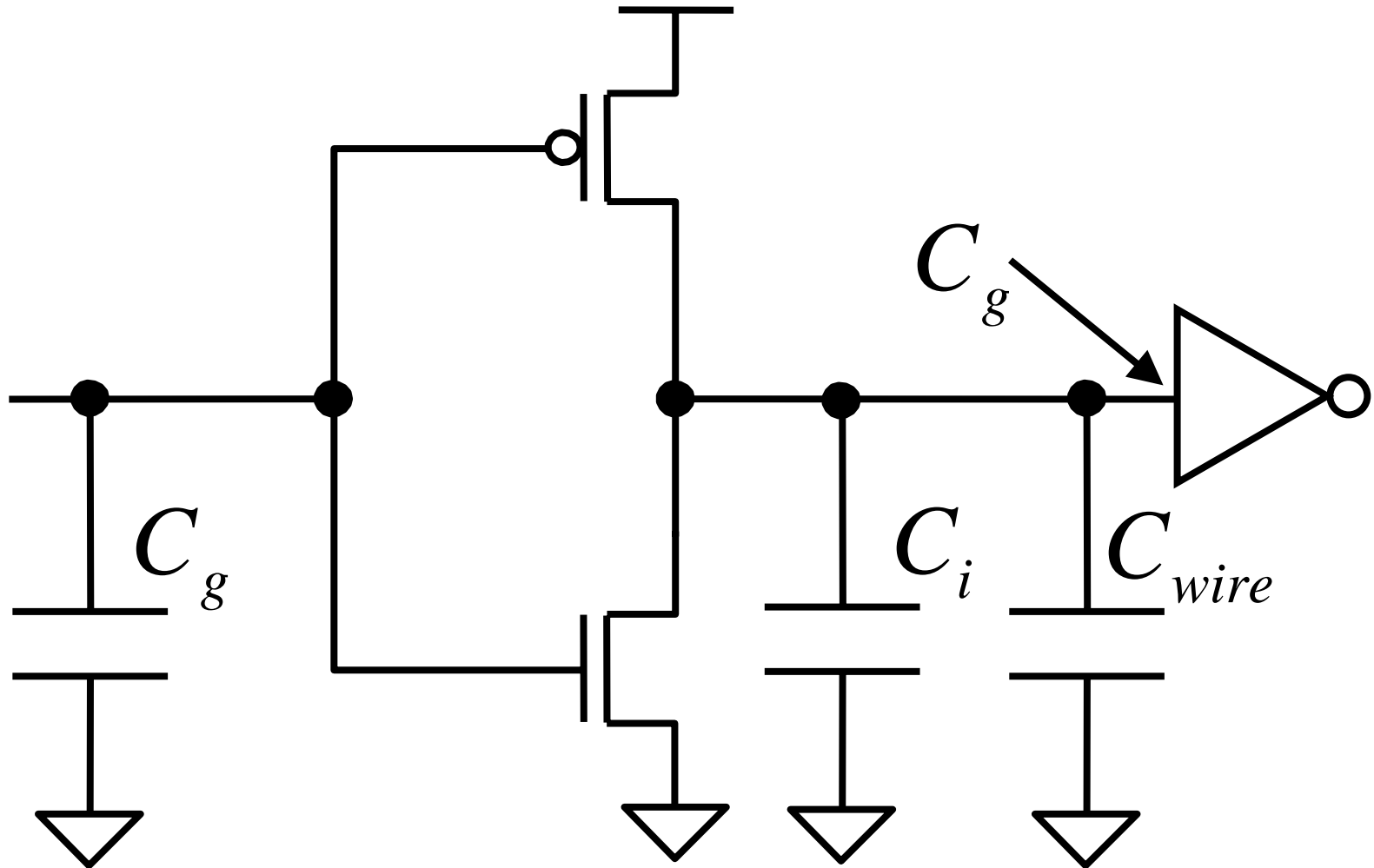Intrinsic (Self-Load) and Extrinsic Capacitance



RC Switch Model for Inverter Sizing

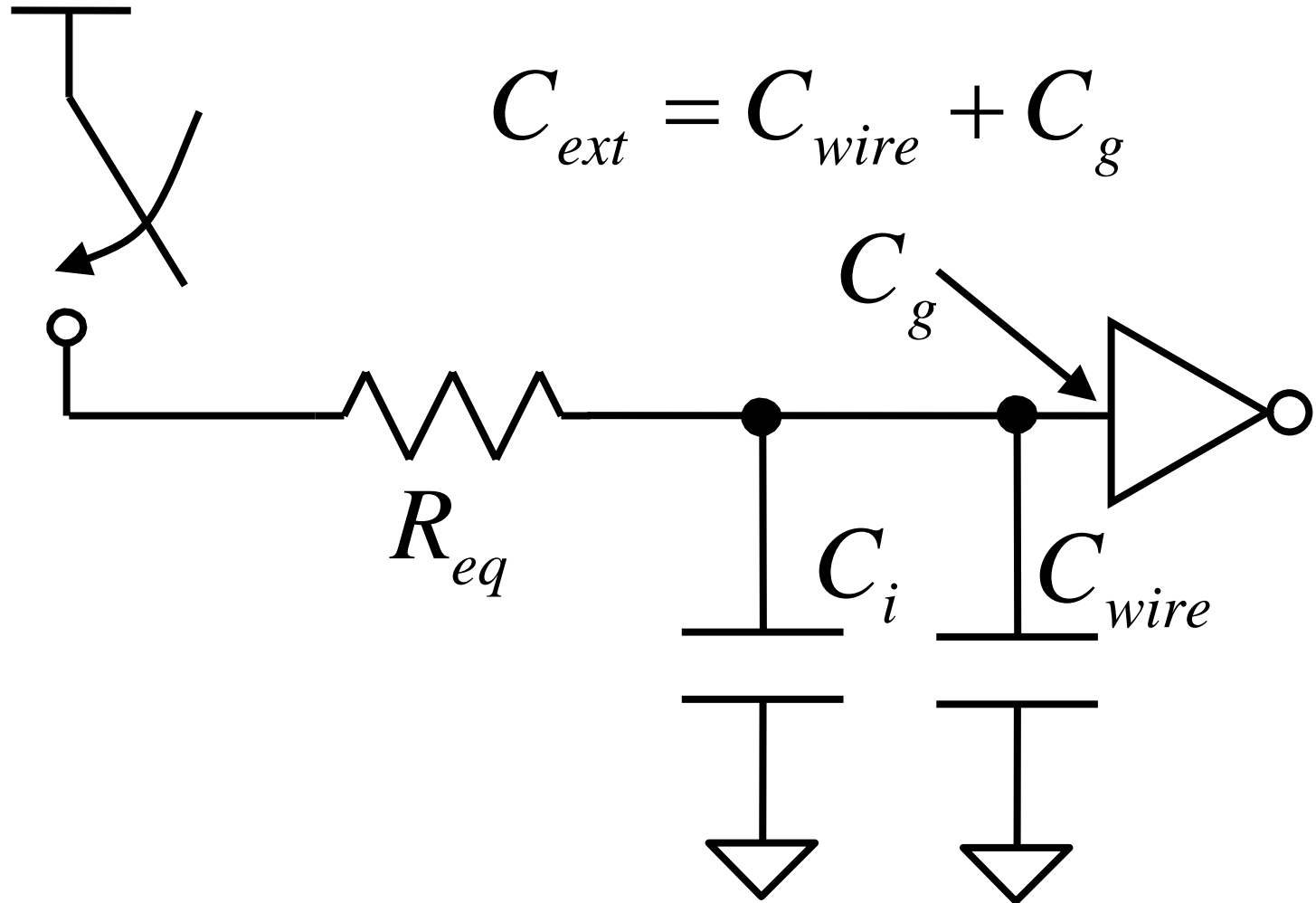

- **Model delay using ideal switch and resistor for MOSFET**

Unloaded Inverter Delay

- **Estimate delay using ideal switch and resistor model (RC time constant):**

$$t_{pd} \propto R_{eq} (C_i + C_{ext})$$

$$\propto R_{eq} C_i (1 + C_{ext} / C_i)$$

$$\propto t_{p0} (1 + C_{ext} / C_i)$$

- **Define intrinsic inverter delay (with fudge factor):**

$$t_{p0} = 0.69 R_{eq} C_i$$

- **C_i consists of source / drain and overlap capacitance**

Fastest Loaded Inverter Sizing

- Decrease delay by enlarging transistor (increases current, decreases R_{eq}) by factor S :

$$t_{pd} = 0.69 \frac{R_{eq}}{S} SC_i \left(1 + \frac{C_{ext}}{SC_i} \right)$$

$$t_{pd} = t_{p0} \left(1 + \frac{C_{ext}}{SC_i} \right)$$

- Intrinsic delay independent of sizing
- Infinite S yields fastest gate (eliminates external load), reducing delay to intrinsic in the limit

Relating Self-Load to Gate Capacitance


- Increasing transistor sizing enlarges self-load and gate input capacitance
- Convenient to relate them by a constant factor γ (γ around 1 in submicron processes)

$$C_i = \gamma C_g$$

$$t_{pd} = t_{p0} \left(1 + \frac{C_{ext}}{\gamma C_g} \right) = t_{p0} (1 + k/\gamma)$$

- k is effective fanout of gate
- Delay depends only on ratio between external load capacitance and input capacitance

Inverter Chain Sizing for Minimum Delay

 

- Using inverter sizing, want to minimize delay of driving large load C_L
- Optimize using equivalent resistance delay equation derived in previous slides

Total Inverter Chain Delay

- Delay of the j th inverter stage is (ignoring wiring):

$$t_{pd,j} = t_{p0} \left(1 + \frac{C_{g,j+1}}{\gamma C_{g,j}} \right) = t_{p0} \left(1 + \frac{k_j}{\gamma} \right)$$

- Total delay is:

$$T_{pd} = \sum_{j=1}^N t_{pd,j} = t_{p0} \sum_{j=1}^N \left(1 + \frac{C_{g,j+1}}{\gamma C_{g,j}} \right)$$

where

$$C_{g,N+1} = C_L = KC_{g,1}$$

Optimal Inverter Sizing for Minimum Delay

- **Minimize delay by taking partial derivatives wrt $C_{g,j}$, set them equal to 0**
 - N-1 equations in N unknowns
 - Solution for jth inverter is geometric mean of its neighbors sizing:

$$C_{g,j} = \sqrt{C_{g,j-1} C_{g,j+1}}$$

- **Implies each inverter has constant scale-up factor k_j :**

$$k_j = k = \sqrt[N]{C_L / C_{g,1}} = \sqrt[N]{K}$$

- **Minimum delay:** $T_{pd} = N t_{p0} \left(1 + \sqrt[N]{K} / \gamma \right)$


Optimal Inverter Stages for Minimum Delay

- **Delay trade off in the number of stages N**
 - Too many stages, intrinsic delay term dominates
 - Too few stages, extrinsic delay term due to fanout ratio dominates
- **Taking derivative of T_{pd} wrt N and setting equal to zero yields scale up factor for optimal number of stages:**

$$k = e^{\left(1 + \frac{\gamma}{k}\right)}$$

- **Closed form solution when $\gamma = 0$, $N = \ln(K)$**
 $k = e = 2.71828$
- **For more typical case of $\gamma = 1$, $k = 3.6$**
- **Often choose $k = 4$**

Inverter Chain Sizing for Minimum Energy

 

- Using inverter sizing, want to minimize energy of driving large load C_L while maintaining fixed delay
- Again, optimize using equivalent resistance delay equation derived in previous slides

Optimal Inverter Sizing for Minimum Energy 1

- Write delay equation for chain with two stages:

$$T_{pd} = t_{p0} \left(\left(1 + \frac{k}{\gamma} \right) + \left(1 + \frac{K}{\gamma k} \right) \right)$$

- Delay for an individual stage (assuming velocity saturation):

$$t_{p0} \approx \frac{\alpha(C_i + C_{ext})V_{DD}}{V_{DD} - V_T - \frac{V_{DSAT}}{2}}$$

- Total energy dissipated depends on total capacitance:

$$E = V_{DD}^2 C_{g1} \left((1 + \gamma)(1 + k) + K \right)$$

Optimal Inverter Sizing for Minimum Energy 2

- Goal is to choose k factor to minimize energy
- Obvious approach is to choose k to minimize delay, then reduce voltage until delay constraint is met
 - In two stage example, this approach yields $k = \sqrt{K}$
- Suppose supply voltage for $k = 1$ is V_0 and delay is T_0
 - Assuming $\gamma = 1$, increase k and decrease V_{DD} until $T_{pd} = T_0$ again
- Ratio of total energy for reduced voltage case to energy for $V_{DD} = V_0$ is:
$$\frac{E}{E_0} = \frac{V_{DD}^2}{V_0^2} \frac{(2 + 2k + K)}{(4 + K)}$$
- Increasing k allows greater reduction in V_{DD} (1st term) at expense of increased capacitance (2nd term)

Energy vs. Transistor Sizing Factor

 


Fig. 6. Plot of energy versus transistor sizing factor for various parasitic contributions.

- From Chandrakasan92, “Low-Power CMOS Digital Design”

Summary of Sizing for Minimum Energy

- **Device sizing combined with voltage reduction is very effective approach to reducing energy consumption**
 - For large fanouts, a factor of 10 reduction can be gained
 - $K = 1$ case is exception; minimum-size device optimal
- **Overly large sizing can result in large power penalty**
 - Typical of designs today, especially standard cells since cells designed for worst case load conditions to guarantee design meets timing
- **Optimal sizing for minimum energy (at fixed delay) smaller than sizing for minimum delay**
 - Example: for fanout $K = 20$, $k_{opt}(energy) = 3.53$ vs. $k_{opt}(delay) = 4.47$
 - Further increasing sizes leads to minimal voltage reductions

Caveats

- **Leakage power ignored in analysis so far**
 - Increase pressure for smaller devices, shifting optimal point to smaller scaling factors
- **Sizing opportunities may be limited**
 - Synthesized design, cannot customize each cell very finely
 - Best approach is not to overdesign cells by assuming pessimistic loading conditions
 - Have many device sizes (INV_1X, INV_2X, NAND2_4X) so tool can pick cells to meet timing-driven synthesis, place, and route constraints

Extending Sizing Optimization to Logic

- So far only looked at sizing of inverter chains
- Can extend results to explore sizing of more complex logic gates
 - RC model leads to design concept of *logical effort*
 - Logical effort is systematic way of sizing arbitrary logic gates in a critical path to minimize delay
- Choose appropriate metric and constraints to optimize for low power design
 - Previous examples focused on minimizing power for a fixed delay constraint (corresponds to Power-Delay Product)
 - Can minimize Energy-Delay Product instead to count performance more heavily


Outline

- Announcements
- Review: Static, Ratioed, and Pass Gate CMOS Logic
- Dynamic Logic
- Impact of Internal Circuit Nodes
- Sizing
- **Clocking Styles Overview**
- Static Latches and Flip-Flops

High Level Clocking Styles


- **Timing classification of digital systems (Messerschmitt 1990) depends on relation to system clock**
 - *Synchronous*: same frequency, known fixed phase offset
 - *Mesochronous*: same frequency, unknown phase offset
 - *Plesiochronous*: nominally same frequency, but slightly different (difference causes phase offset to drift in time)
 - *Asynchronous*: signals transition at arbitrary times relative to system clock
- **Traditionally designed for synchronous operation**
- **As speeds get higher, clock skew and jitter increases, total synchronization less likely**
- **Mesochronous, Plesiochronous, Asynchronous styles more prevalent (for example, GALS)**

Synchronous System With Global Clock

 


- **Simple and convenient design style with minimal circuit overhead**
- **Challenge is creating and distributing clock with low skew and jitter (timing uncertainty) at high frequencies**

Critical Path Replica Self-Timed System

 

- **Similar to synchronous style except clock frequency directly correlated to circuit speed**
- **Robust to process, voltage, temperature variations**
- **Minimal circuit overhead for self-timing**

Handshaking Between Pipeline Stages

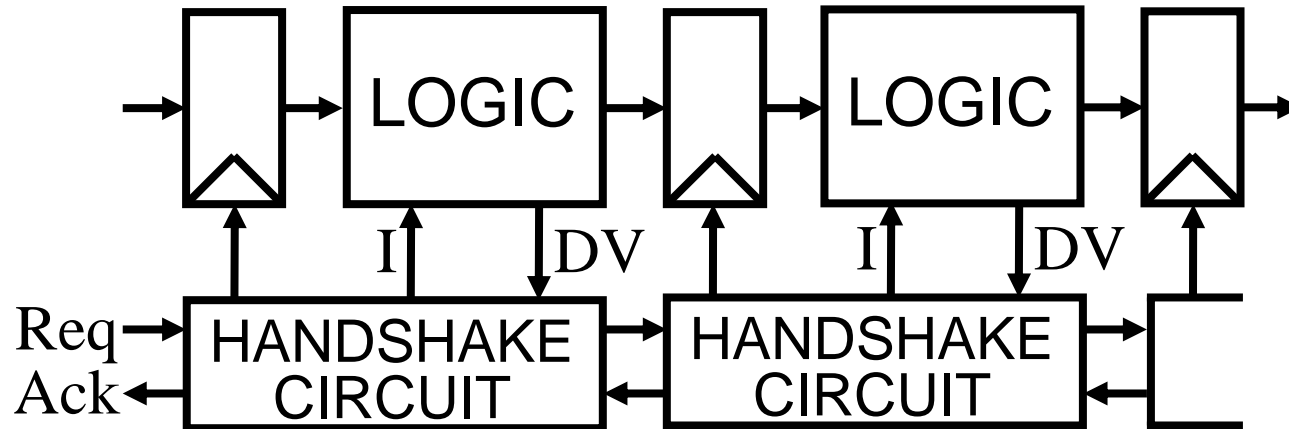

- **Truly asynchronous style with maximum performance**
 - Each stage computes as fast as possible on each datum
 - Overhead between stages to guarantee information flows correctly through pipeline
- **Also robust to process, voltage, temperature variations**
- **Circuit overhead implies more switched capacitance**

Clocking Styles for Low Power

- **No definitive conclusions on which is better ... yet**
- **Asynchronous styles offer highest speed and greatest voltage reductions**
 - Offset significantly by higher switched capacitance
 - Difficulty of designing circuits properly a barrier to widespread adoption
 - Functions reliably with respect to voltage variations, allows aggressive supply scaling and battery operation
- **Synchronous benefits include ease of design and minimum circuit overhead**
- **Combination of styles likely in future**
 - Globally Asynchronous, Locally Synchronous blocks
 - Mixed clocked and self-timed pipeline stages

Outline

- Announcements
- Review: Static, Ratioed, and Pass Gate CMOS Logic
- Dynamic Logic
- Impact of Internal Circuit Nodes
- Sizing
- Clocking Styles Overview
- **Static Latches and Flip-Flops**


Sequential Element Design for Low Power

- **Clock power is often large component of chip dynamic power**
 - Activity factor is high (charges every cycle)
 - Interconnect capacitance due to clock distribution wiring is very large
 - Clock inputs to latches and flip-flops can present significant capacitance
- **Sequential element design style must balance several competing demands**
 - Robustness wrt noise, timing uncertainty, leakage current
 - Speed since setup/hold times and clock-to-Q delays directly impact critical path delay
 - Power dissipation


Static vs. Dynamic Design Styles

- **Tradeoffs are similar to static and dynamic combinational logic styles**
- **Static designs rely on feedback to maintain state**
 - Internal nodes as well as outputs always driven to supply rails by low impedance path
 - Requires more devices, area, possibly power
 - Robust design style with wide noise margins, scales to lower frequencies and supply voltages
- **Dynamic designs store state on parasitic capacitances**
 - Very fast since fewer devices, no static current fights
 - Sensitive to noise, challenging to scale to lower frequencies / voltages
 - Power dissipation depends on specific circumstances


Static Latch Bistability

 

Multiplexer-Based Static Latches

 


Negative Latch

 


Positive Latch

- **Latches are transparent during half of clock cycle**

Transmission Gate Positive Latch

 


NMOS Pass Gate Positive Latch

 

- Fewer devices, less area, lower clock load
- Threshold drop on internal nodes implies more static power, less noise margin

Master-Slave Positive Edge-Triggered FF

 


- **Connect two opposite phase transparent latches**

Positive Edge-Triggered FF Clock Load


- **Latch choice clearly impacts flip-flop power**
- **Full transmission gate latch has high loading**
 - Requires 7 inverters (one extra to create local inverted clock, can be amortized over entire registers)
 - Clock touches 1 inverter and 8 transmission gate FETs
 - Transmission gate load less than inverter since PMOS can be sized same as NMOS (mobility ratio is overkill)
- **NMOS only pass gate latches reduce loading**
 - Requires 5 inverters including local clock inversion
 - Clock touches 1 inverter and 4 transmission gate FETs
 - Static power when storing 1 since internal nodes charged to $V_{DD} - V_{Tn}$
- **Specific circumstances dictate which is better**

Reduced Clock Load Static Positive FF

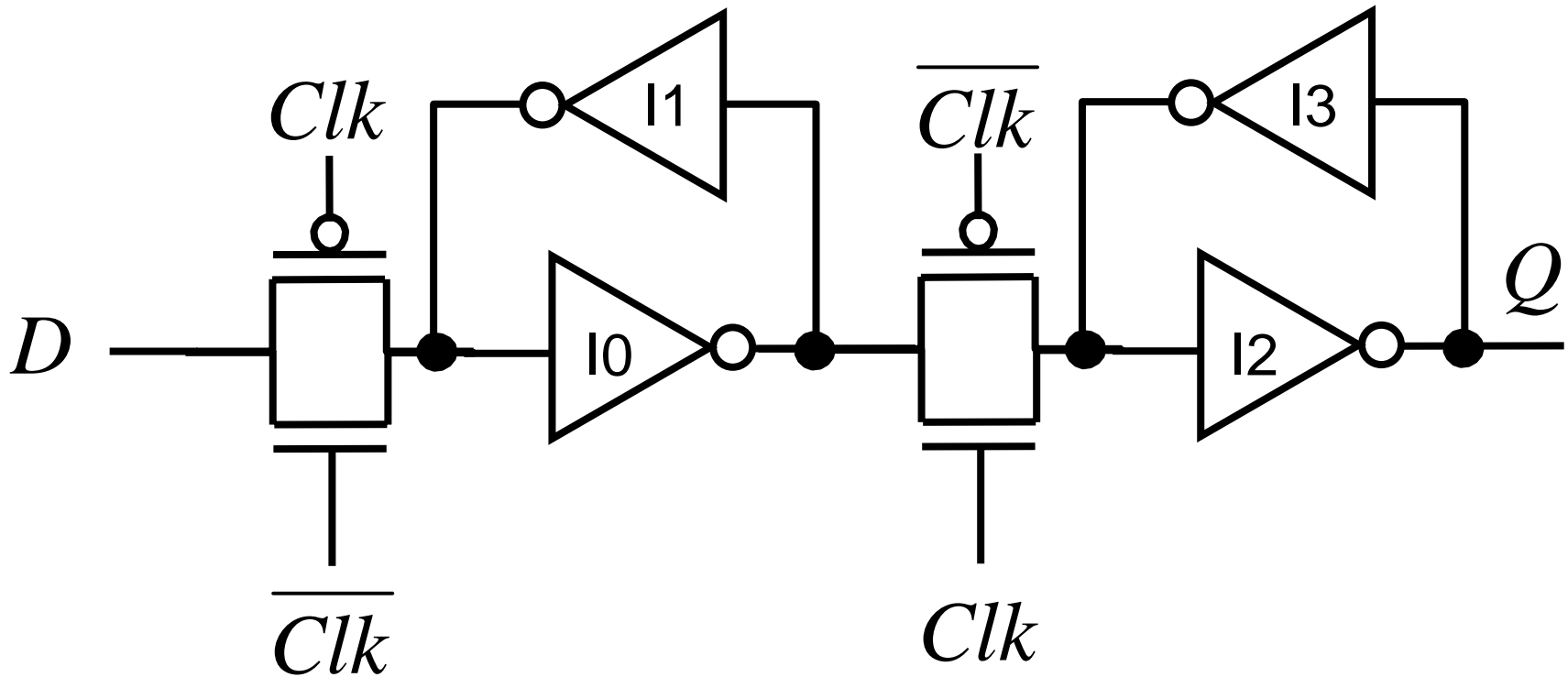


- Reduce clock load by directly cross-coupling inverters
- Ratioed circuit: must size transmission gate to overpower feedback inverters I_1 and I_3
 - Can make I_1 , I_3 intentionally weak ($>$ minimum length)

Reverse Conduction Problem

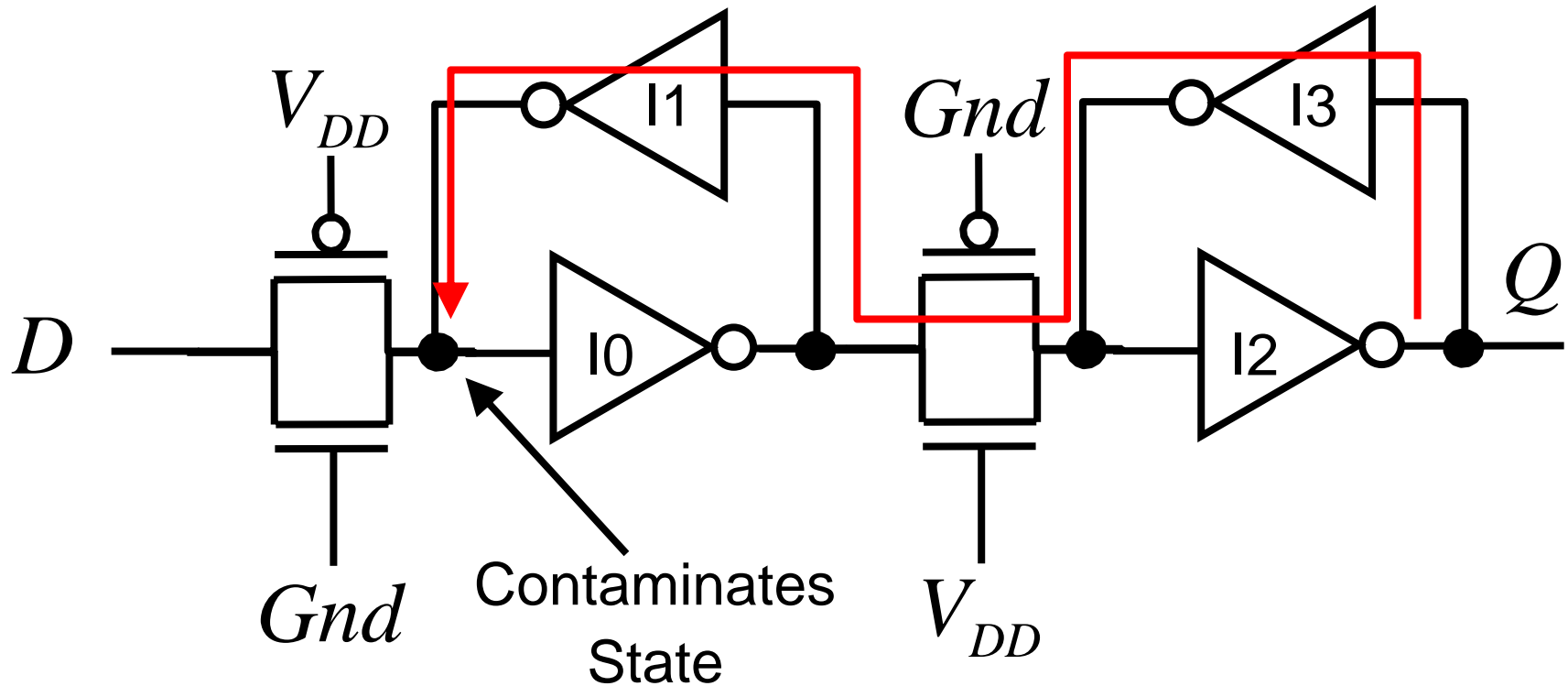


- Second stage output can affect first stage state
- Must size feedback inverter $I3$ to avoid contamination by making it weak enough

Clock Overlap Failures

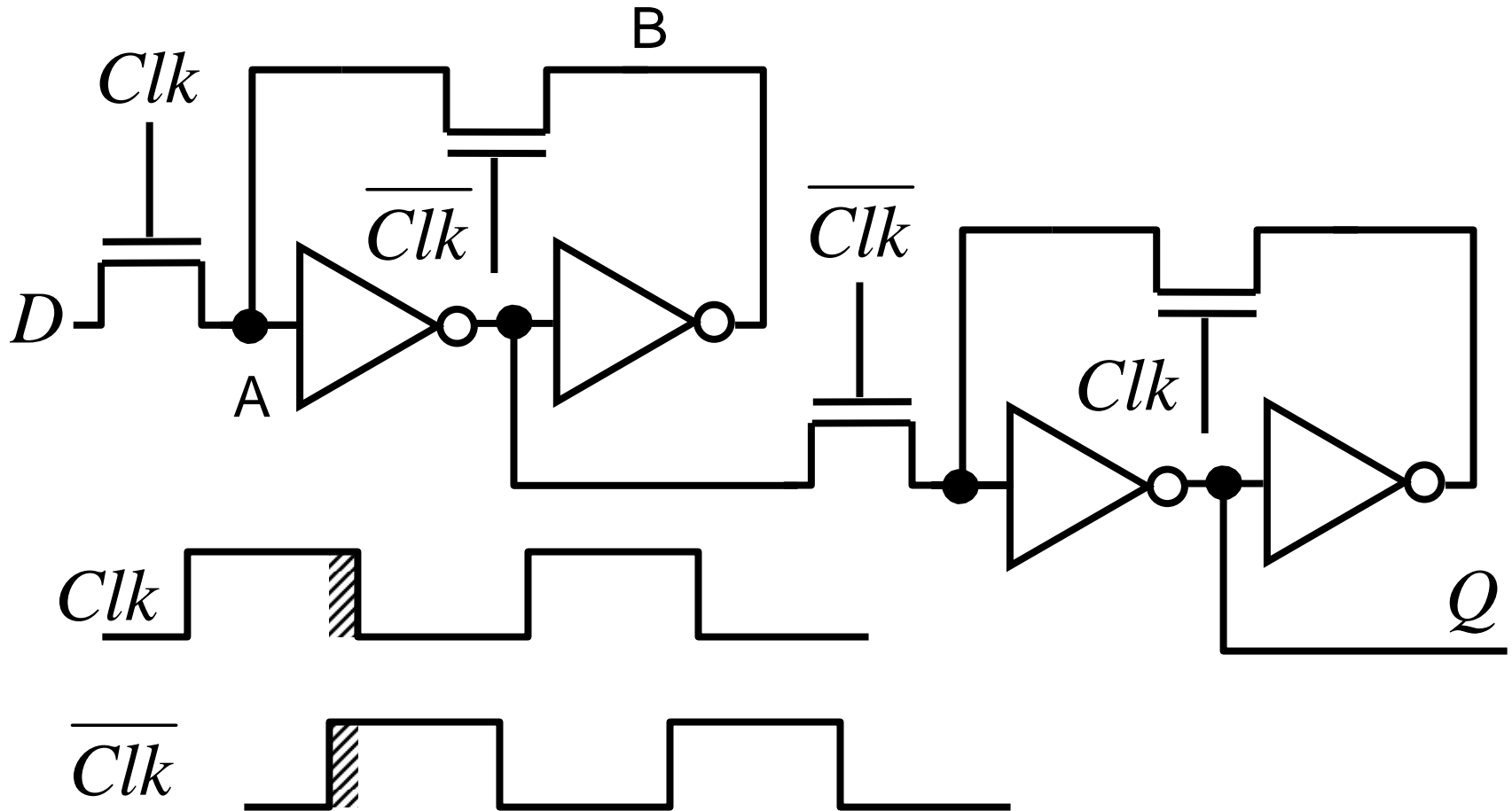


1. Both high simultaneously, race condition from D to Q
2. Node A can be driven simultaneously by D and B

Race Through and Feedback Paths

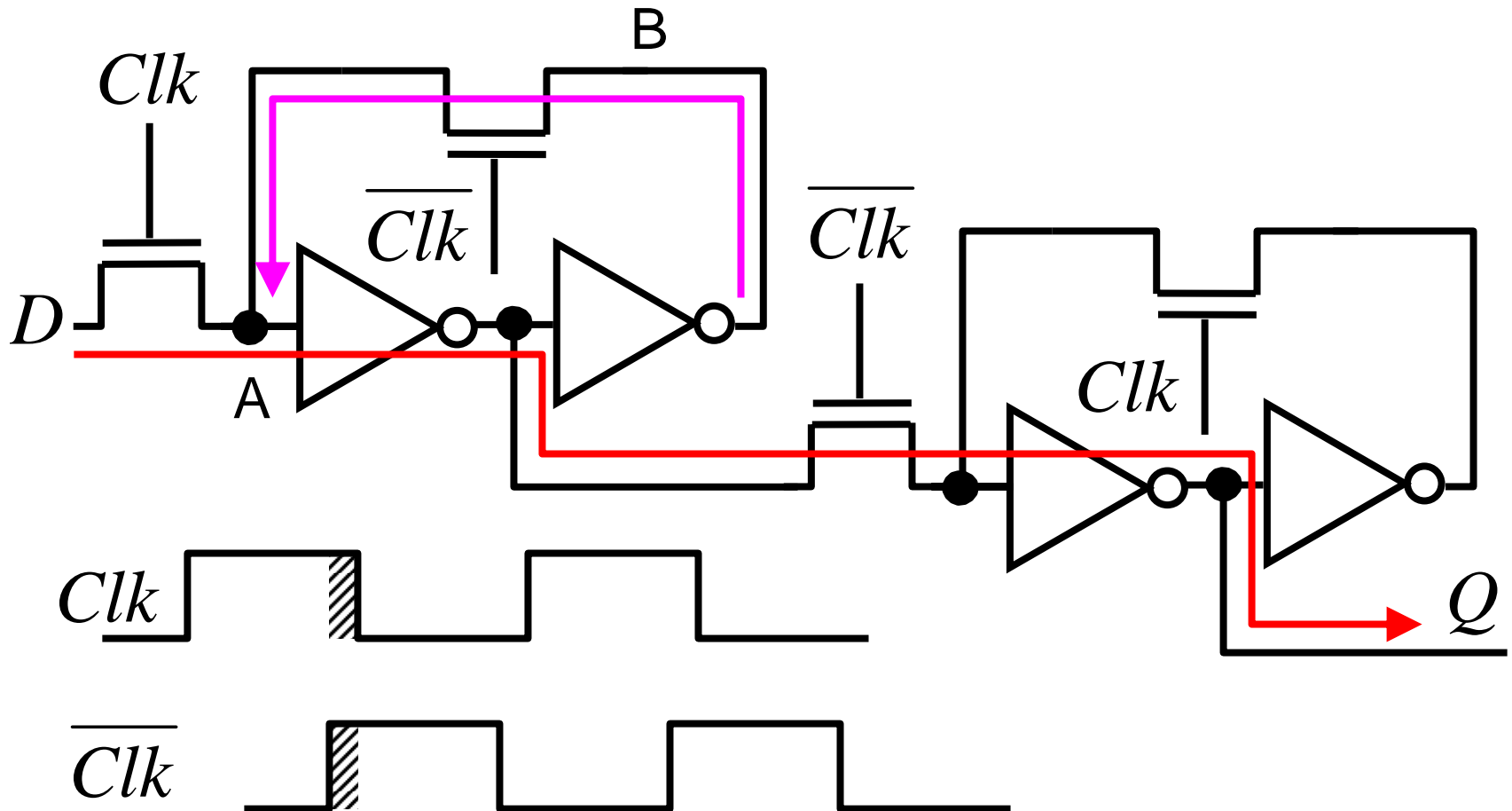

1. Both high simultaneously, race condition from D to Q
2. Node A can be driven simultaneously by D and B

Nonoverlapping Clocks Methodology

 

- **Guarantee nonoverlap period long enough**
- **Note: internal nodes left high Z during nonoverlap**

Closing Thoughts

- **Rich design space of circuit styles, sizing methodology, and clocking strategies**
 - Must balance large circuit capacitance (static CMOS) vs. higher activity factor (dynamic CMOS)
 - Dynamic logic is faster, so must be used if speed is priority
 - Can mitigate higher activity by sharing pulldown networks (multiple-output domino) or using complex static gates to eliminate dynamic gates and inverters (compound domino)
- **Next topic: dynamic latch styles, self-timed circuits**