

EEC 216 Lecture #8A: Subthreshold Circuit Design

**Rajeevan Amirtharajah
University of California, Davis**

Outline

- **Announcements**
- Review: Low Power Interconnect
- Finish Lecture 7
- Leakage Mechanisms
- Circuit Styles for Low Leakage
- Cache SRAM Design Examples
- Next Time: Energy Recovery Circuits

Announcements

- **Design Project 2 due February 29, 5 PM in 3173 Kemper Hall**

Extremely Brief MOSFET Review

Saturation:
$$I_D = \frac{\mu C_{ox}}{2} \frac{W}{L} (V_{GS} - V_T)^2 (1 + \lambda V_{DS})$$

Triode:
$$I_D = \mu C_{ox} \frac{W}{L} \left((V_{GS} - V_T) V_{DS} - \frac{V_{DS}^2}{2} \right)$$

Subthreshold:
$$I_D = I_S e^{\frac{V_{GS}}{n kT/q}} \left(1 - e^{-\frac{V_{DS}}{kT/q}} \right)$$

“Classical” MOSFET model, will discuss deep submicron modifications as necessary

Subthreshold Current Equation

$$I_D = I_S e^{\frac{V_{GS}}{n kT/q}} \left(1 - e^{-\frac{V_{DS}}{kT/q}} \right) (1 + \lambda V_{DS})$$

- I_S and n are empirical parameters
- Typically, $n \geq 1$ often ranging around $n \approx 1.5$
- Usually want small subthreshold leakage for digital designs
 - Define quality metric: inverse of rate of decline of current wrt V_{GS} below V_T
 - Subthreshold slope factor S : $S = n \frac{kT}{q} \ln(10)$


Detailed Subthreshold Current Equation

$$I_D = A \exp\left(\frac{q}{nkT}(V_{GS} - V_{T0} - \gamma V_S + \eta V_D)\right) \left(1 - \exp\left(\frac{-qV_{DS}}{kT}\right)\right)$$

$$A = \mu_0 C_{ox} \frac{W}{L} \left(\frac{kT}{q}\right)^2 e^{1.8}$$


- **V_{T0} = zero bias threshold voltage,**
- **μ_0 = zero bias mobility**
- **C_{ox} = gate oxide capacitance per unit area**
- **γ = linear body effect coefficient (small source voltage)**
- **η = DIBL coefficient**

Leakage Currents vs. Active Currents

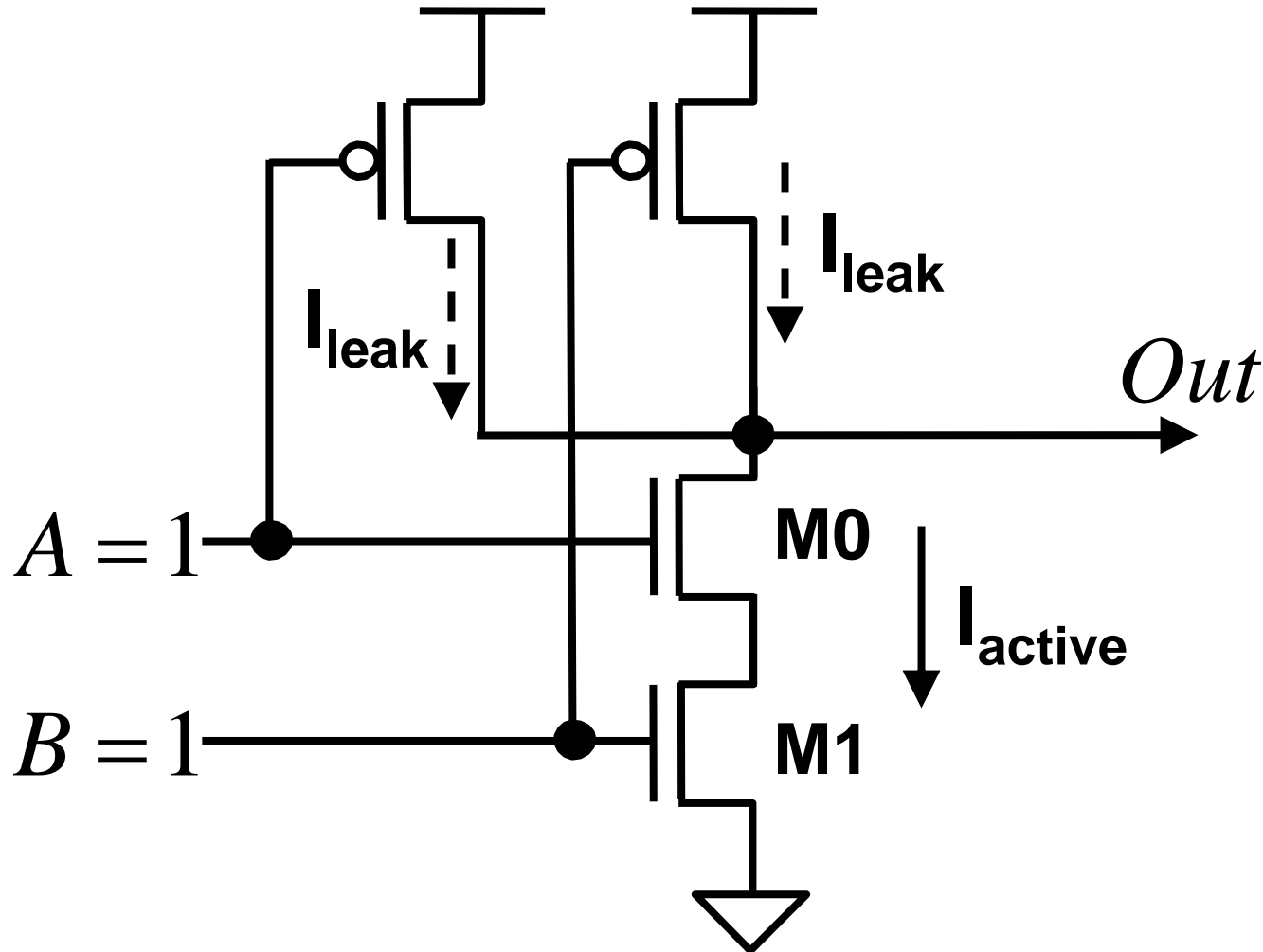


- I_{active}/I_{leak} (I_{on}/I_{off}) ratio can be small in subthreshold


Degraded Output Levels

 

 - **Balance current ratio through sizing, limiting fanin**



SRAM Cell Leakage Paths

 

- Leakage paths can degrade read and write noise margins

Conclusions

- **Subthreshold design similar to ratioed ckt design**
 - Must guarantee active currents sufficiently greater than leakage currents to maintain valid logic levels
 - Degraded logic levels can cause failure in combinational and sequential circuits
 - All circuits (esp. SRAMs) sensitive to V_{TH} variation
- **Be careful with subthreshold circuits**
 - Consider worst case leakage situations (data dependent) when analyzing I_{on}/I_{off} ratio problems
 - Use nonminimum channel lengths, limit fanin
 - Watch sneak leakage paths through pass gates
 - Interrupt pass gate chains with static logic