 


### 8.3 Gate Delays and Timing Diagrams




In "steady state" (after "enough" time), logic gate outputs will reach a fixed final value. However, it takes some time to get there.



About 15 ns max for 74LS04 parts for output to change after input changes  
 $\Rightarrow$  propagation delay


Propagation delay for fastest modern chips  $\sim 30\text{ps} - 40\text{ps}$  (trillionths of a second).

Show delay with a timing diagram

   

 
### 8.4 Hazards in Combinational Logic

Static 1 Hazard exists in a logic circuit if its output is 1, momentarily goes to 0, then returns to settle at 1 when a single input changes:



 Static 0 Hazard output momentarily transitions to 1 when initially 0 and finally settling at 0:



Ex: Static 1 Hazard

BC \ A	0	1
00		
01	1	
11	1	1
10		1



Labels:  $A'C$  (covering 01, 11),  $AB$  (covering 11, 10)

Transition  $A: 0 \rightarrow 1$

	A	B	C
0	1	1	
1	1	1	1

Time axis  $t$  with a downward arrow indicating the transition.


$$Z = A'C + AB$$

  

Solution: add redundant gates

AB \ A	0	1
00		
01	1	
11	1	1
10		1

 Labels:  $BC$  (covering 01, 11),  $AB$  (covering 11, 10),  $A'C$  (covering 01, 11)





Note: No longer a minimum solution.

Fix hazards by covering all adjacent 1's with their own group.

There will be no static 1 or 0 hazards within a group.

  Dynamic Hazards occur when an output makes additional (three or more) transitions when it is expected to transition from  $0 \rightarrow 1$  or  $1 \rightarrow 0$ .




Dynamic hazards occur with multi-level circuits where there are multiple paths from inputs to outputs.

Methods to fix static and dynamic hazards work only for single bit input transitions.

Fix dynamic hazards with static-hazard-free 2-level circuits.

Ex: Multiple input bit transitions.

 

Transition from  $abcd = 0101$  to  $abcd = 1111$

Case ①

a	b	c	d	f (output)
0	1	0	1	1
1	1	0	1	1
1	1	1	1	1

No hazard!

Case ②

a	b	c	d	f
0	1	0	1	1
0	1	1	1	0
1	1	1	1	1

Static 1 Hazard Unavoidable!

Some other names for possible bugs:

Glitch is an unnecessary (usually unwanted) pulse at the output of a combinational logic circuit (e.g., static 0, static 1 hazards)

Runt pulse is a brief transition that doesn't reach all the way to a valid logic level for 1 or 0

