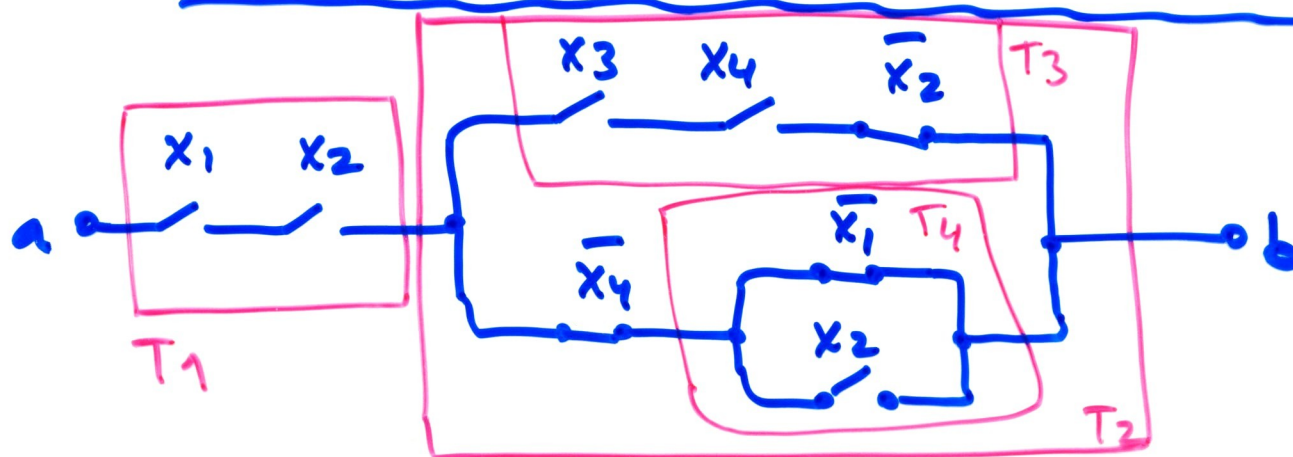


8.

Analysis of series-parallel networks :



$$f = T_1 \cdot T_2 = (x_1 \cdot x_2) \cdot T_2$$

$$T_2 = T_3 + \cancel{x_4} T_4 = x_3 \odot x_4 \odot \bar{x}_2 + \bar{x}_4 \cdot (\bar{x}_1 + x_2)$$

$$f = (x_1 \cdot x_2) [x_3 \odot x_4 \odot \bar{x}_2 + \bar{x}_4 (\bar{x}_1 + x_2)]$$

$$f = (x_1 \cdot x_2) (x_3 \odot \bar{x}_2 \odot \underline{x_4} + \bar{x}_1 \bar{x}_4 + \underline{x_2} \bar{x}_4)$$

$$f = (x_1 \cdot x_2) [x_3 \odot \bar{x}_2 \odot \cancel{x_4} + (\bar{x}_1 + x_2) \bar{x}_4]$$

$$f = (x_1 \cdot x_2) (\bar{x}_2 \cdot \cancel{x_3} \cdot \cancel{x_4} + \bar{x}_4 (\bar{x}_1 + x_2))$$

$$f = (x_1 \cdot x_2 \cdot \bar{x}_4) (\bar{x}_2 \cdot x_3 + \bar{x}_1 + x_2) = x_1 x_2 \bar{x}_4$$


9.

Analysis of Switching Networks

TIE SET : Connects a 2nd Lot a network) and no parts form a loop.

CUT SET :

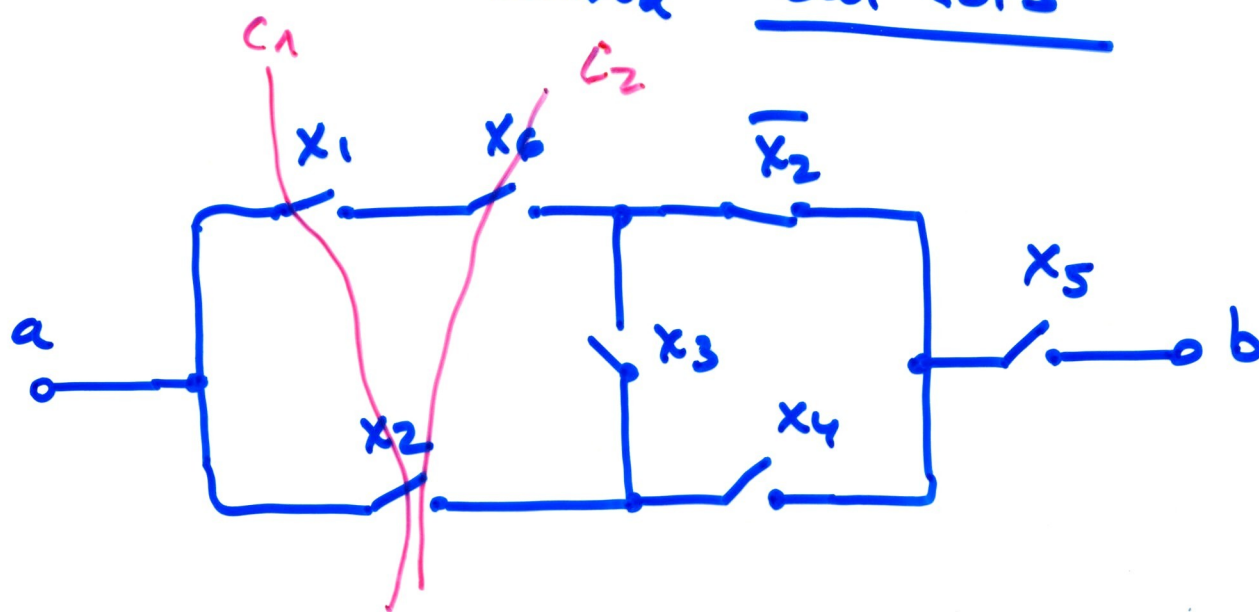- All contacts open simultaneously
- if two contacts connect two parts of the net they are called cut sets




Procedure :

FIND ALL cut-sets : form OR of all literals in each cut-set

⇒ The product (AND) of all OR's yields the function f .

10.

Analysis of Switching Networks

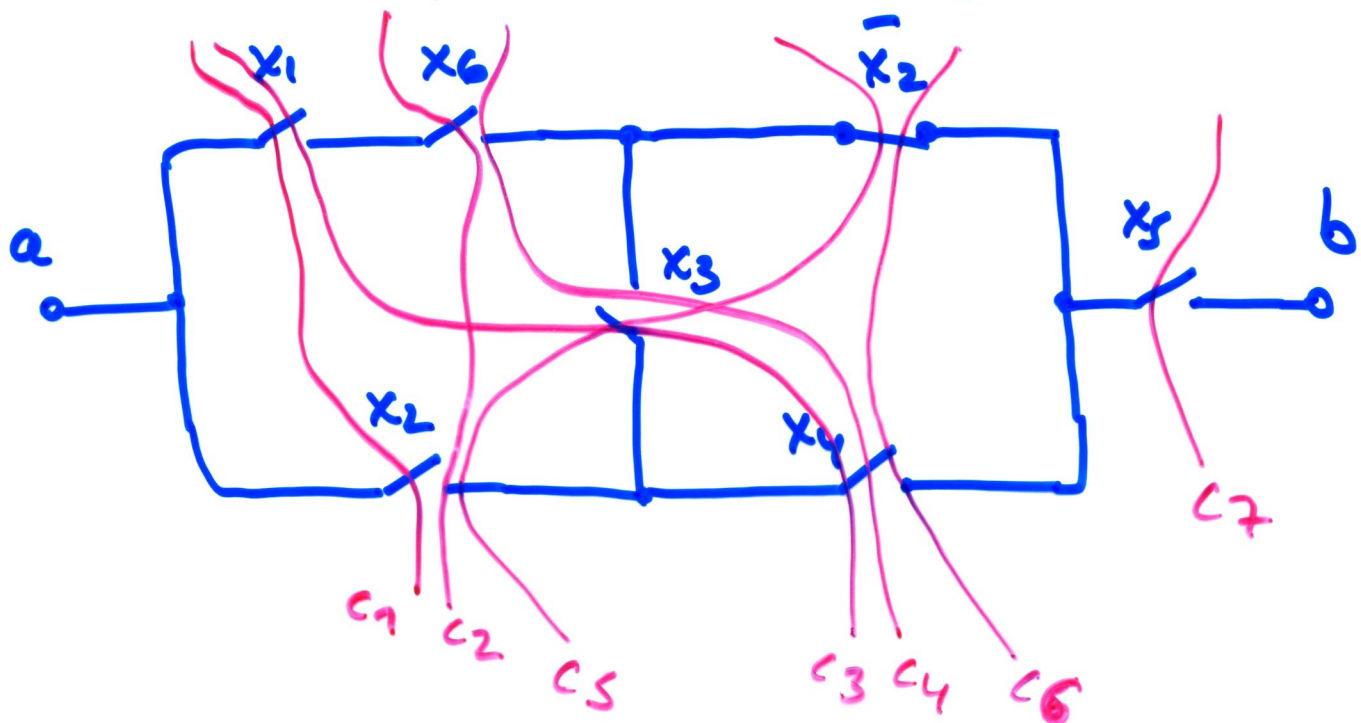

$$f = c_1 \cdot c_2 \cdot c_3 \cdot c_4 \cdot c_5 \cdot c_6 \cdot c_7$$

$$f = (x_1 + x_2)(x_2 + x_6)(\cancel{x_1} + \cancel{x_3} + \cancel{x_4})(x_6 + x_3 + x_4) \cdot (\cancel{\bar{x}_2} + \cancel{x_3} + \cancel{x_2})(\bar{x}_2 + x_4)(x_5)$$

$$f = (\cancel{x_1 + x_2})(\cancel{x_2 + x_6})(\cancel{x_6 + x_3 + x_4})(\cancel{\bar{x}_2 + x_4}) \cdot x_5$$

Consensus Theorem

If we have: $xy + \bar{x}z + yz$

$\overbrace{xy + \bar{x}z}^{\text{other two}}$

$\underbrace{xy + \bar{x}z}_{\text{complemented}}$

$\overline{\overline{xy + \bar{x}z}} =$

CONSENSUS TERM IS REDUNDANT CAN BE ELIMINATED!

Proof:

consensus

$$\begin{aligned} xy + \bar{x}z + yz &= xy + \bar{x}z + yz(x + \bar{x}) \\ &= xy + xyx + \bar{x}z + \bar{x}z\bar{y} \\ &= xy(1 + z) + \bar{x}z(1 + y) \\ &= xy + \bar{x}z \quad \therefore \end{aligned}$$

De Morgan Law:

$$\begin{array}{l} 1^0 \quad \overline{a+b} = \bar{a} \cdot \bar{b} \quad \checkmark \\ 2^0 \quad \overline{a \cdot b} = \bar{a} + \bar{b} \quad \checkmark \end{array} \quad \left. \vphantom{\begin{array}{l} 1^0 \\ 2^0 \end{array}} \right\} \text{Truth Table}$$

$$\boxed{\overline{(x_1 + x_2 \dots + x_k)} = \bar{x}_1 \cdot \bar{x}_2 \dots \bar{x}_k}$$

a	b	$\overline{a+b}$	$\bar{a} \cdot \bar{b}$
0	0	1	1
0	1	0	0
1	0	0	0
1	1	0	0

$$\overline{a+b+c} = \overline{(a+b) + c} = \overline{(a+b)} \cdot \bar{c} \quad \begin{array}{c} \textcircled{1} \quad \textcircled{2} \end{array}$$

$$= \bar{a} \cdot \bar{b} \cdot \bar{c}$$

$N \checkmark$ valid $\left\{ \begin{array}{l} \text{Induction} \end{array} \right.$ A.S $3 \leq k$

$$\overline{(x_1 + x_2 \dots + x_k + x_{k+1})} = \overline{(x_1 + x_2 \dots + x_k)} \cdot \bar{x}_{k+1} \quad \checkmark$$

$\textcircled{1}$
 $\textcircled{2}$
 $\textcircled{1}$
 $\textcircled{2}$


$$\overline{(x_1 \cdot x_2 \dots \cdot x_k)} = \bar{x}_1 + \bar{x}_2 + \dots + \bar{x}_k$$

$$f(x_1, x_2 \dots x_k, 0, 1, +, \cdot) = f(\bar{x}_1, \bar{x}_2 \dots \bar{x}_k, 1, 0, \cdot, +)$$



NAND




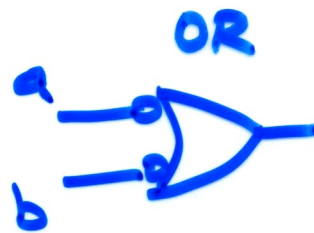
$$\overline{a \cdot b} = \bar{a} + \bar{b}$$


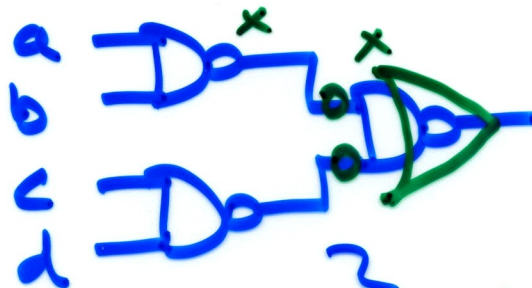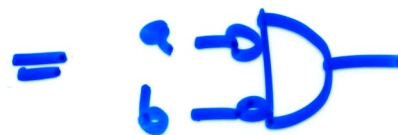
$$\overline{a + b} = \bar{a} \cdot \bar{b}$$



$$f = ab + cd$$

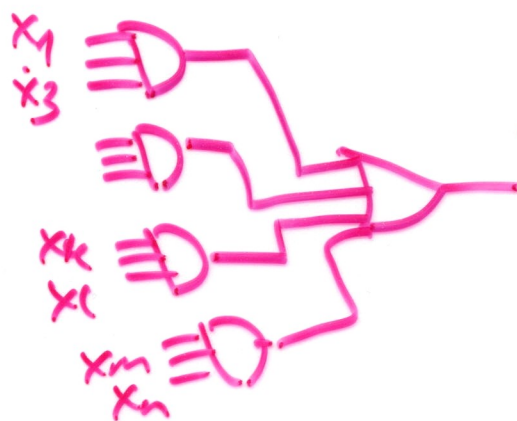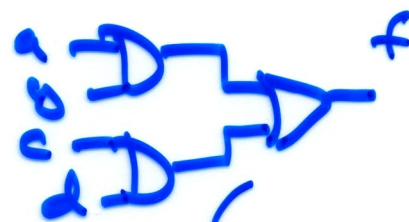

$$f = f(x_i)$$

SOP:

$$f = \text{---} + \text{---} + \text{---} + \text{---} + \text{---}$$

NAND-NAND

~~But...~~

$$[f(x_1, x_2, \dots, x_n), 0, 1, +, \cdot] =$$

$$= [f(\bar{x}_1, \bar{x}_2, \dots, \bar{x}_n), 1, 0, \cdot, +]$$

Example (De Morgan):

a	b	xor
0	0	0
0	1	1
1	0	1
1	1	0

$$f = \bar{a}b + a\bar{b} = a \oplus b : \text{XOR}$$

$$\begin{aligned} \bar{f} &= \overline{(\bar{a}b + a\bar{b})} = \overline{(\bar{a}b)} \cdot \overline{(a\bar{b})} = (a + \bar{b})(\bar{a} + b) \\ &= a\bar{a} + \bar{a}\bar{b} + ab + \bar{b}b = ab + \bar{a}\bar{b} : \text{XNOR} \end{aligned}$$

XOR Properties:

(1) Commutative:

$$a \oplus b = b \oplus a$$

(2) Associative:

$$(a \oplus b) \oplus c = a \oplus (b \oplus c)$$

(3) Distributive:

$$a \cdot (b \oplus c) = ab \oplus ac$$


(4) Identity Element:

$$a \oplus 0 = a$$


$$a \oplus 1 = \bar{a}$$


$$a \oplus a = 0$$

$$a \oplus \bar{a} = 1$$

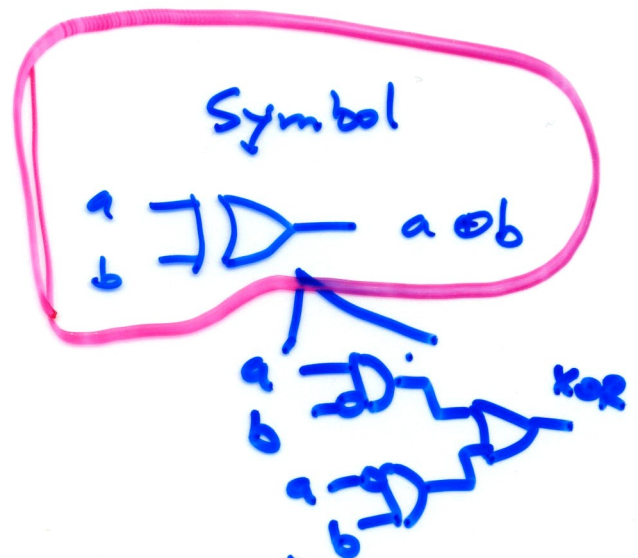

Inverter

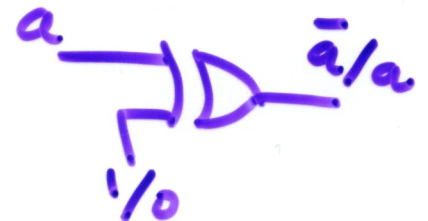

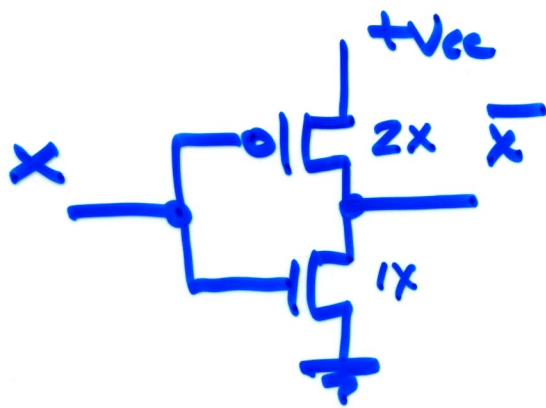

$$F = \bar{a}b + a\bar{b} = a \oplus b$$

$$\begin{aligned} \bar{F} &= \overline{\bar{a}b + a\bar{b}} = \\ &= (a + \bar{b}) \times (\bar{a} + b) \end{aligned}$$

$$\bar{F} = \bar{a}\bar{b} + ab$$

XOR			F
a	b		
0	0	0	1
0	1	1	0
1	0	1	0
1	1	0	1

XOR properties

$$a \oplus 0 = a \quad a \oplus 1 = \bar{a}$$

$$a \oplus 1 = \bar{a}$$

$$a \oplus a = 0$$

$$a \oplus \bar{a} = 1$$



2° Assoc :

$$(a \oplus b) \oplus c =$$

$$a \oplus (b \oplus c) =$$

$$= a \oplus b \oplus c$$

3° Distrib :

$$a \cdot (b \oplus c) = a \cdot b \oplus a \cdot c$$

$$1_{\text{def}} = \overline{a \oplus b} = \bar{a} \oplus b = a \oplus \bar{b}$$



Equivalence

$$x \equiv y$$

x	y	$x \equiv y$
0	0	1
0	1	0
1	0	0
1	1	1

$$Eq = \overline{x \oplus y}$$

$$x \equiv y \Rightarrow \text{XOR} \text{ gate} \text{ eq.}$$

Proof of Distributive property for XOR

$$\underline{x(y \oplus z) = xy \oplus xz = xy(\overline{xz}) + (\overline{xy}) \cdot xz}$$

$$= xy(\overline{x} + \overline{z}) + xz(\overline{x} + \overline{y})$$

$$= xy\overline{z} + x\overline{y}z = x(y\overline{z} + \overline{y}z)$$

$$= x(y \oplus z)$$

Duality Theorem :

$$[f(x_1 \dots x_k, 0, 1, +, \cdot)]^D = f(x_1 \dots x_k, 1, 0, \cdot, +)$$

Prove :

$$\overline{F} = \overline{G}$$

$$\text{if } F = G \\ F^D = G^D$$

$$f(\bar{x}_1 \dots \bar{x}_k, 0, 1, +, \cdot) = g(\bar{x}_1 \dots \bar{x}_k, 0, 1, +, \cdot) \\ y_i = \bar{x}_i$$

$$f(y_1, y_2 \dots y_k, 0, 1, +, \cdot) = g(y_1 \dots y_k, 0, 1, +, \cdot)$$

$$(x + \bar{y}) \cdot y = xy \quad \text{dual}$$

$$\boxed{x\bar{y} + y = x + y}$$

$$F = a\bar{b} + c + 0 \cdot \bar{d}(1 + e) = a\bar{b} + c \\ \downarrow d \quad \quad \quad \downarrow d \\ (a + \bar{b}) \cdot c \cdot (1 + \bar{d} + 0 \cdot e) = (a + \bar{b})c$$

Example Dual :

$$f = a\bar{b} + c + 0 \cdot \bar{d}(1+e) = a\bar{b} + c$$

$$f^D = (a+\bar{b})c \cdot (1+\bar{d}+0 \cdot e) = (a+\bar{b}) \cdot c$$

Proof by duality:

$$(x+\bar{y}) \cdot y = xy$$

↓

$$\boxed{x\bar{y} + y = x + y}$$

$$x\bar{y} + y = x + y$$

↓ dual

$$(x+\bar{y}) \cdot y = xy$$


Multiplying Out & Factoring

POS: $x \cdot (y + z) = xy + xz$: SOP


POS: $(x+y)(x+z) = x + yz$: SOP

$$(x+y)(\bar{x}+z) = xz + \bar{x}y$$
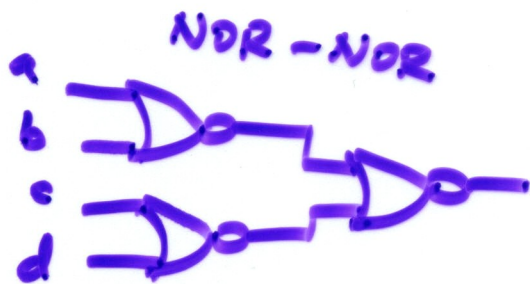
$$\begin{aligned} (x+y)(\bar{x}+z) &= x\bar{x} + y\bar{x} + xz + yz \\ &= xz + \bar{x}y + yz \quad (x+\bar{x}) \\ &= xz + xyz + \bar{x}y + \bar{x}yz \\ &= xz(1+y) + \bar{x}y(1+z) \\ &= xz + \bar{x}y \end{aligned}$$




$\Rightarrow$

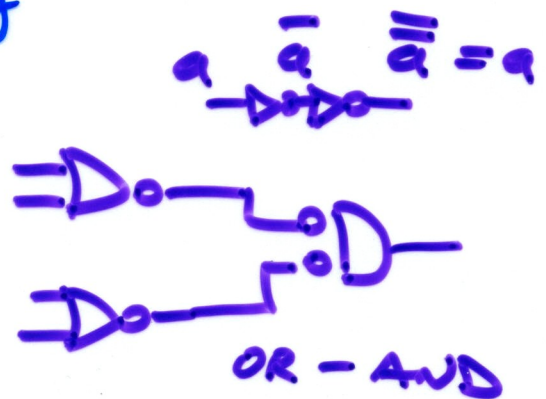



$$f = (x+y)(x+z)$$

Problem 3.15





Find F & G & Simplify:

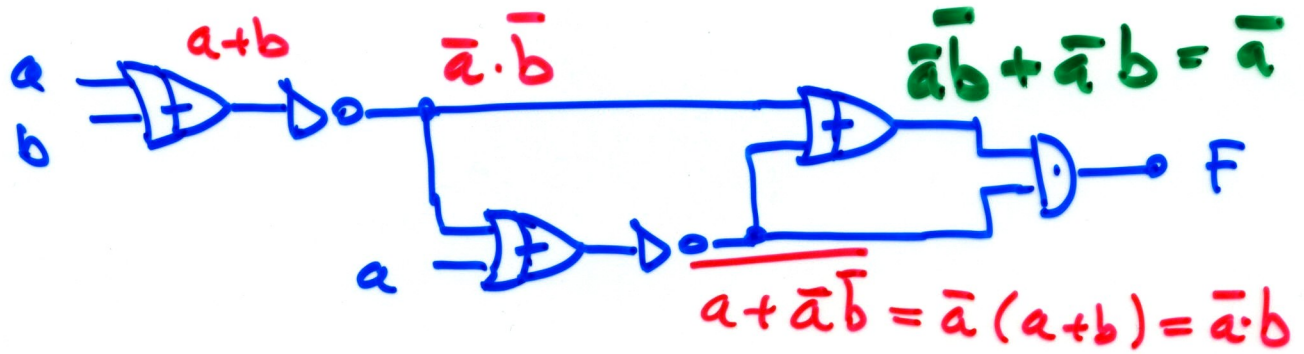
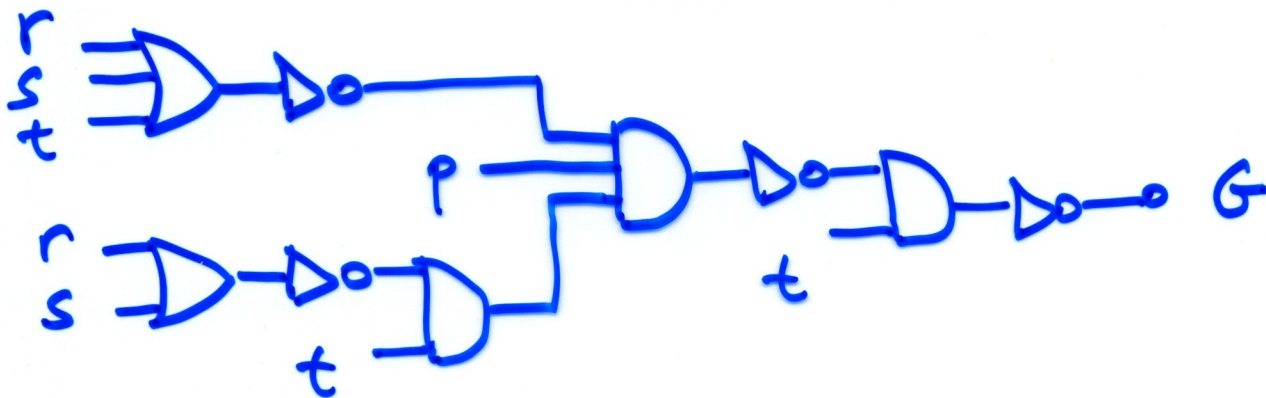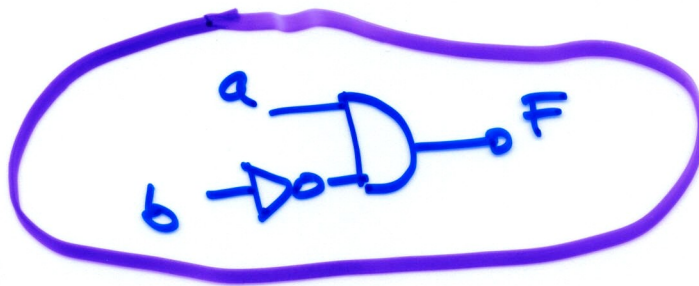
$$F = \bar{a} \cdot \bar{a}b = \bar{a}b$$



PMOS:

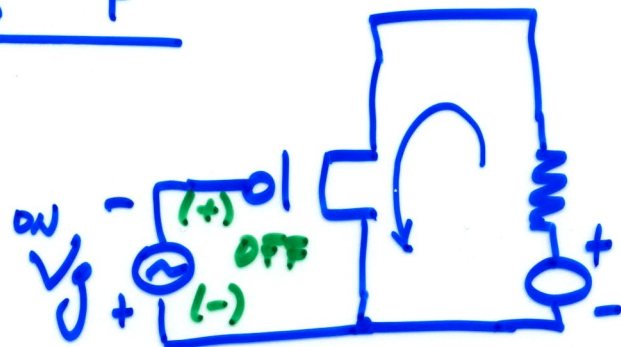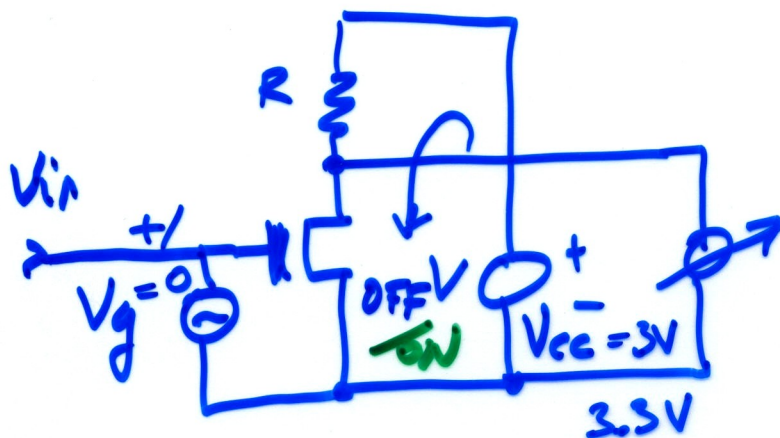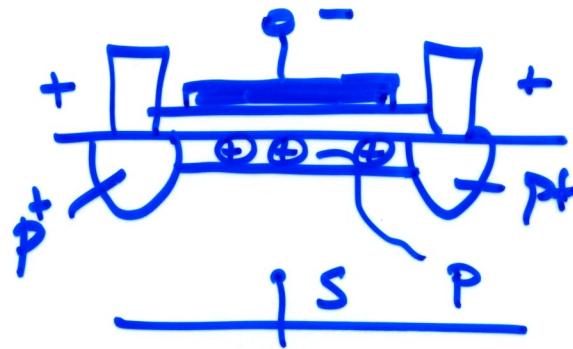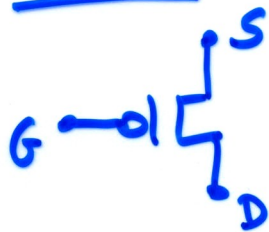


$V_i = V_{cc} ; V_g = 0 ; 1$
 $V_i = 0 ; V_g > V_t ; 0$

$$f = c + b \cdot (a + d) \quad r_c \ll R$$



V_{in}	V_{out}
1	0
0	1

inversion

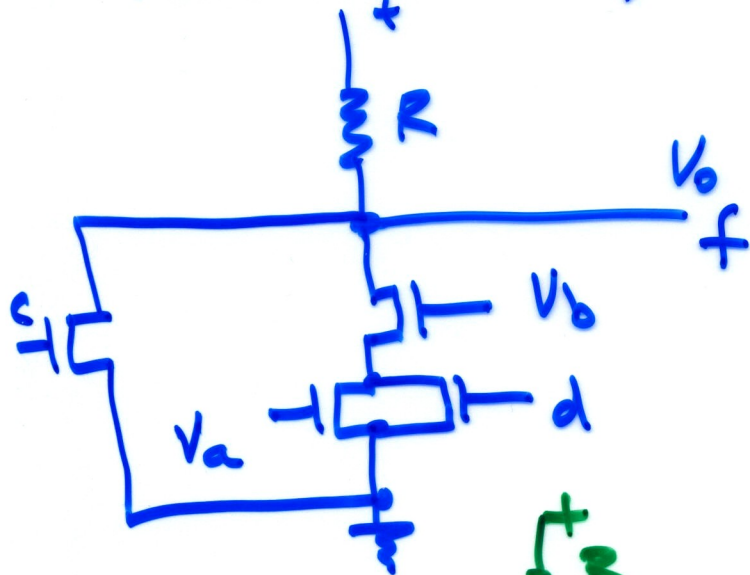


$V_a = 1, V_b = 1 \quad V_o = 0$

$$f = \overline{a \cdot b}$$

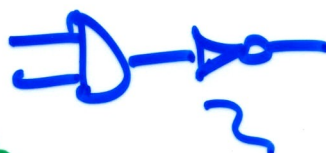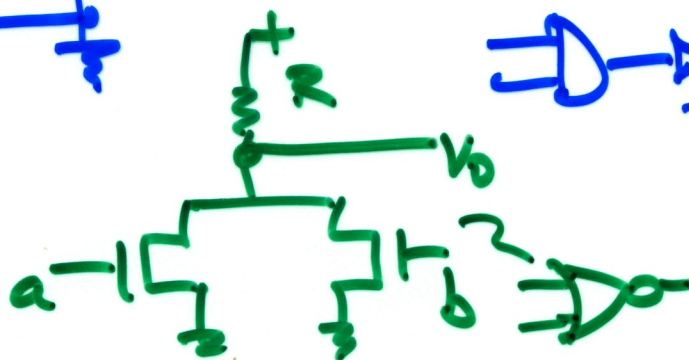


NAND

AND
OR

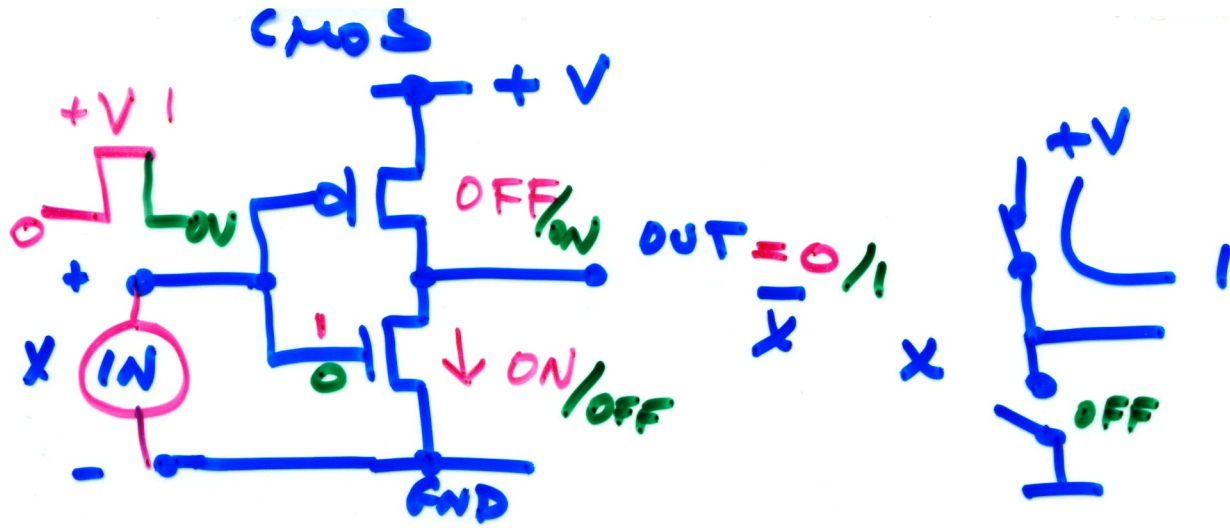

$X \rightarrow \text{Inverter} \rightarrow \bar{X}$: INVERT CMOS


nMOS :

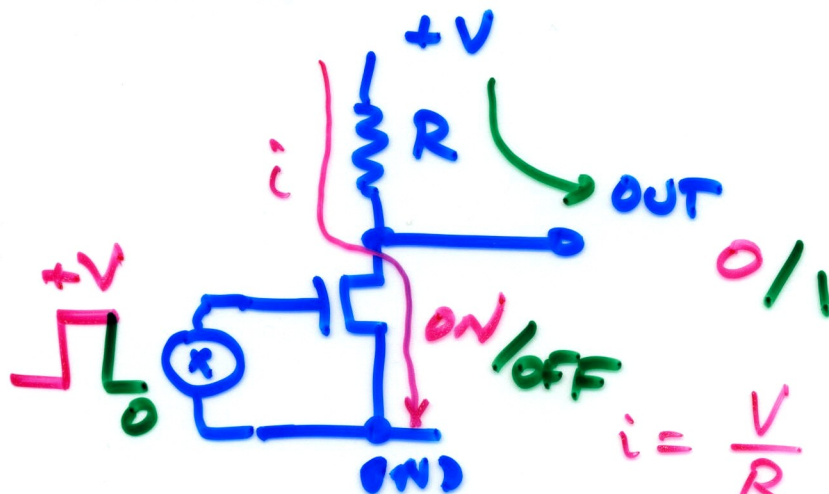




$$i = \frac{V}{R}$$

$$P = i \cdot V$$

$$P = \frac{V^2}{R}$$

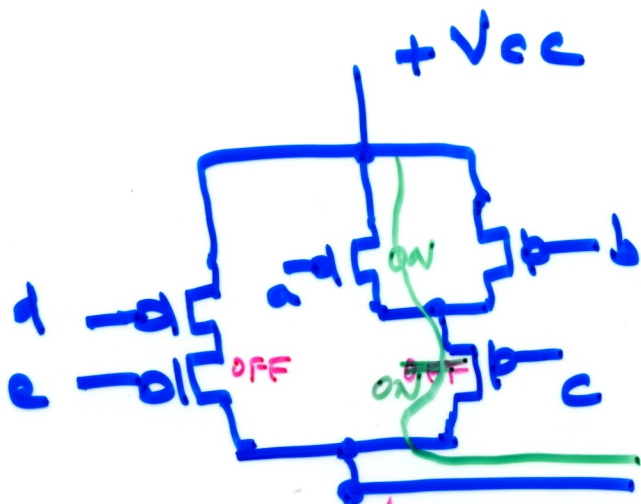

$$\bar{f} = (a \cdot b + c)(d + e)$$

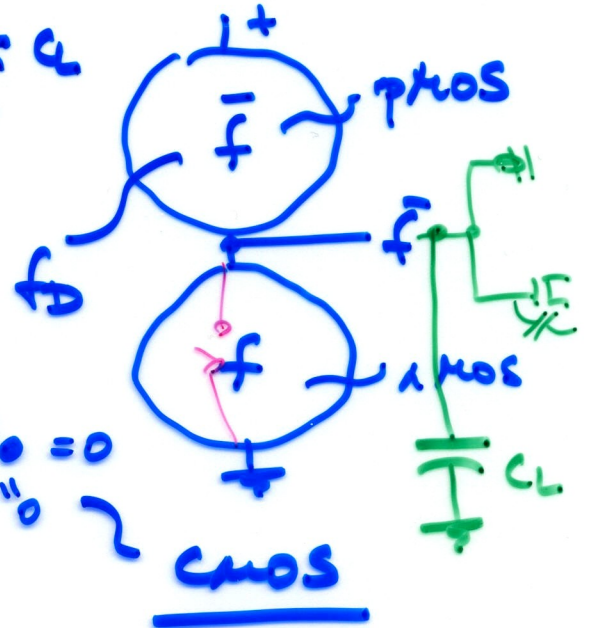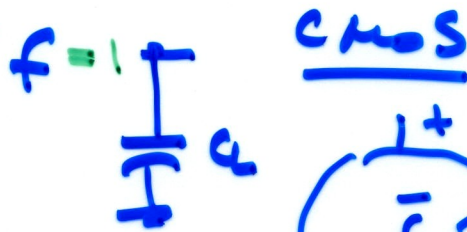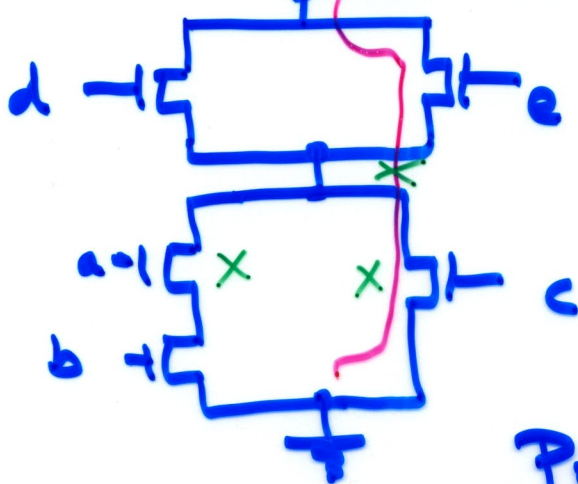

$$P = V_{cc} \cdot I_o = 0$$

