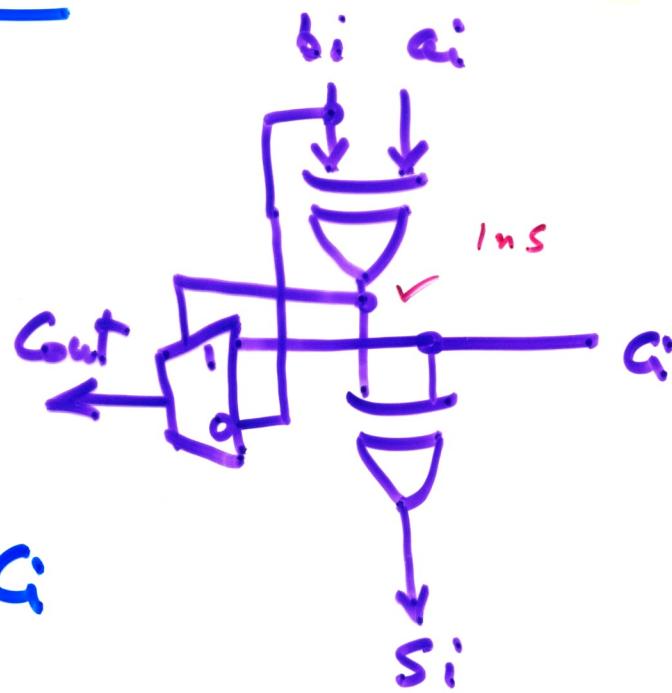



$$p_i = a_i \oplus b_i$$

$$g_i = a_i \cdot b_i$$





$$c_{out(i+1)} = g_i + p_i \cdot c_i$$

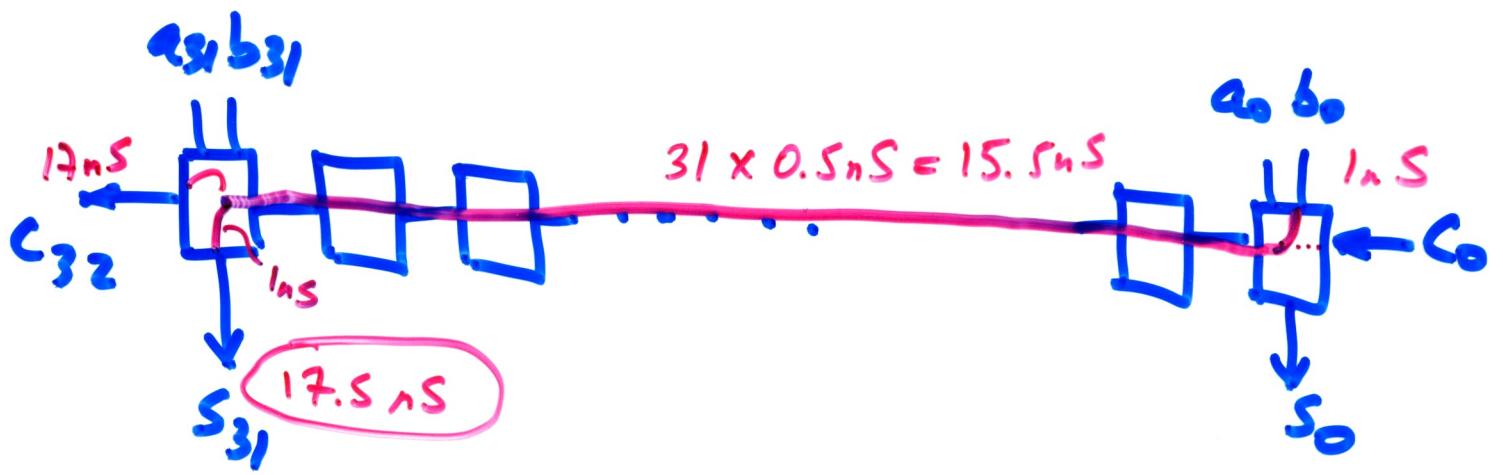
$$c_{i+1} = a_i b_i + a_i c_i + b_i c_i$$




$$\text{XOR} = 1\text{nS}$$

$$\text{Mux} = 0.5\text{nS}$$

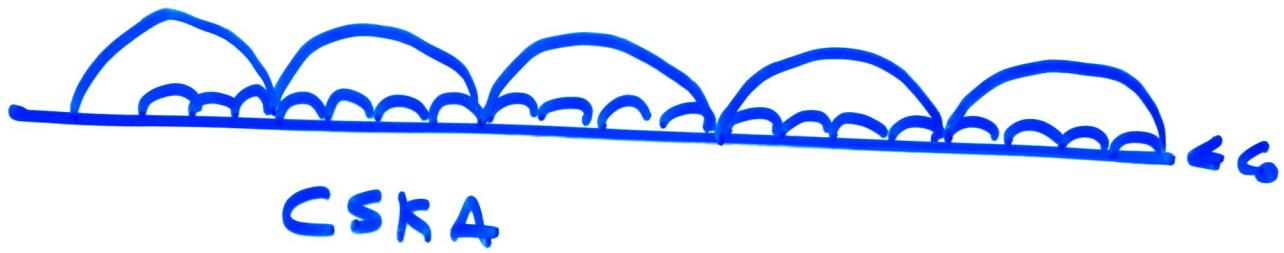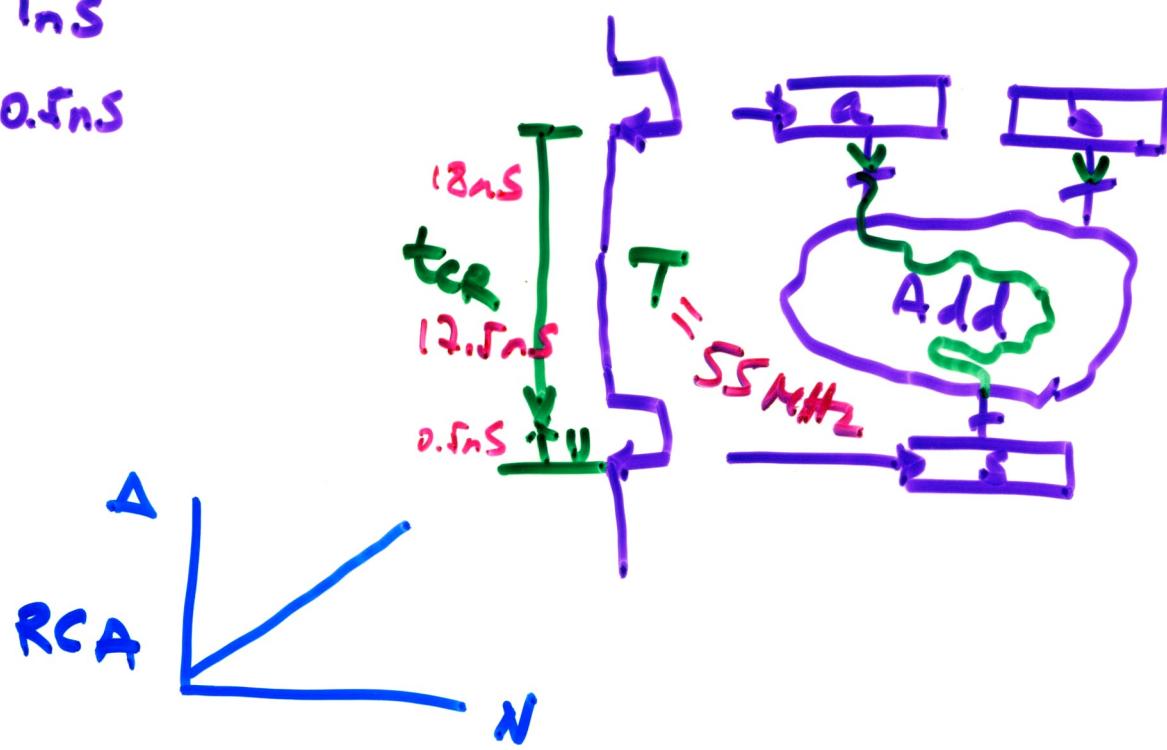

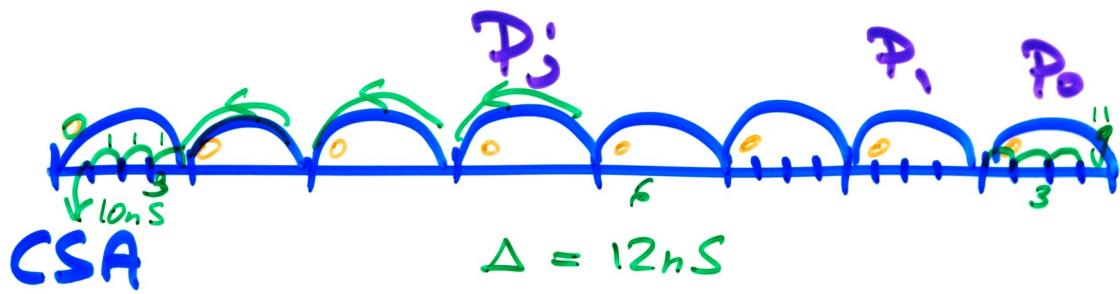

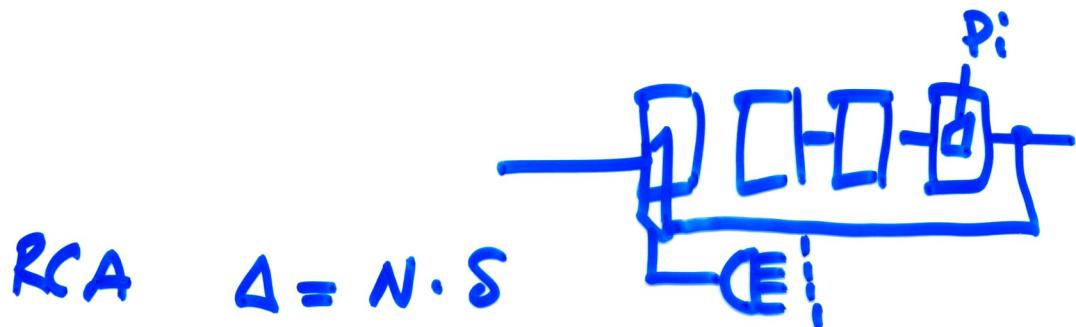
$$P_j = P_i P_{i+1} P_{i+2} P_{i+3} = 1 \quad \text{AND } P_j$$







CSK

$$\Delta = 2(k-1) + \left(\frac{N}{k} - 2\right)$$


$$\frac{N}{k} = \frac{32}{4} = 8$$

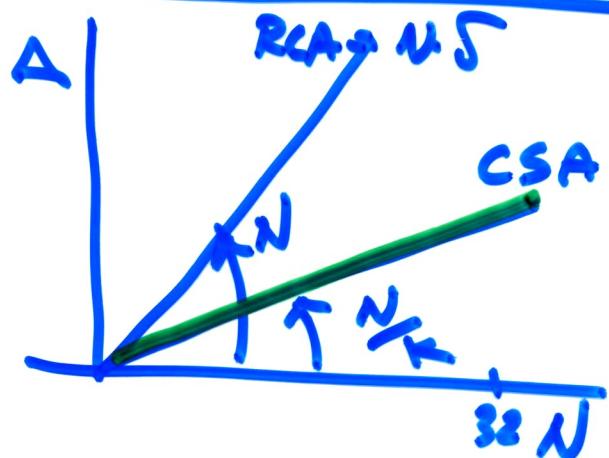

Circuits for Arithmetic <C-20>

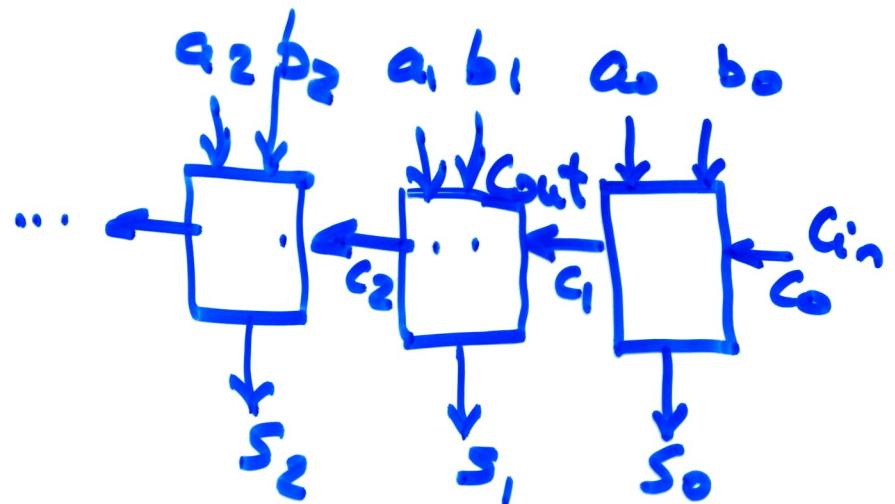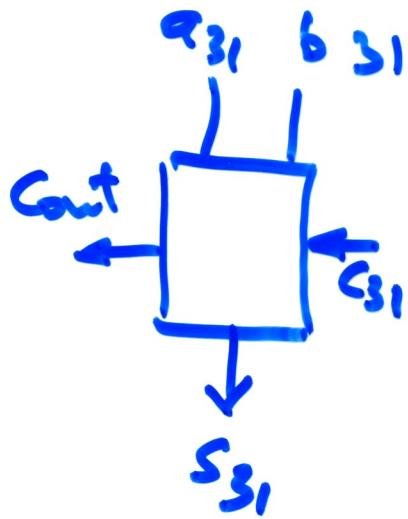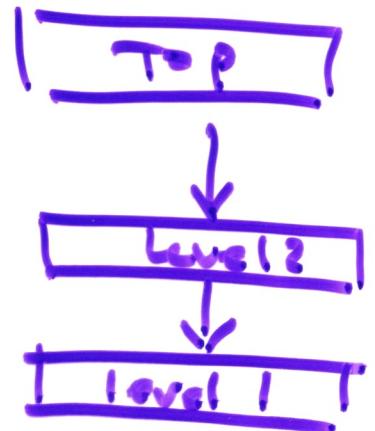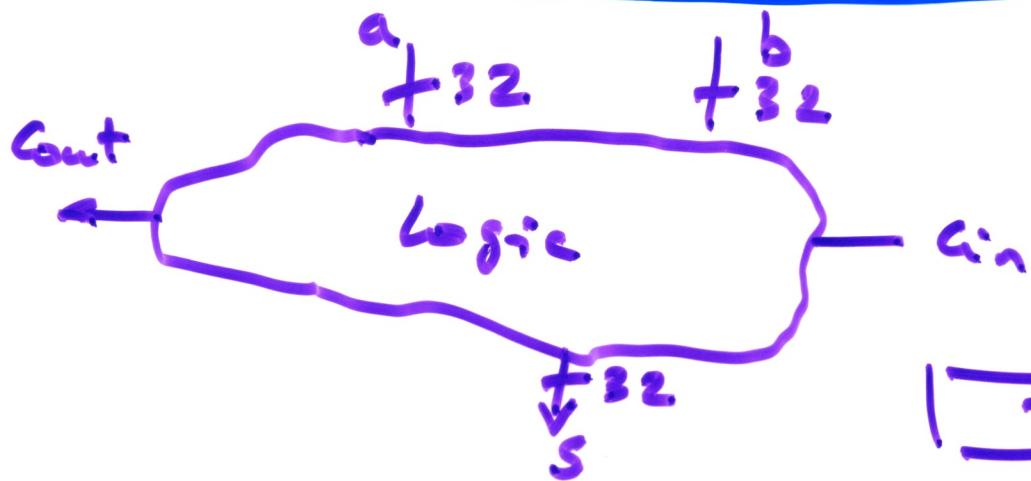

Adders (ALU)



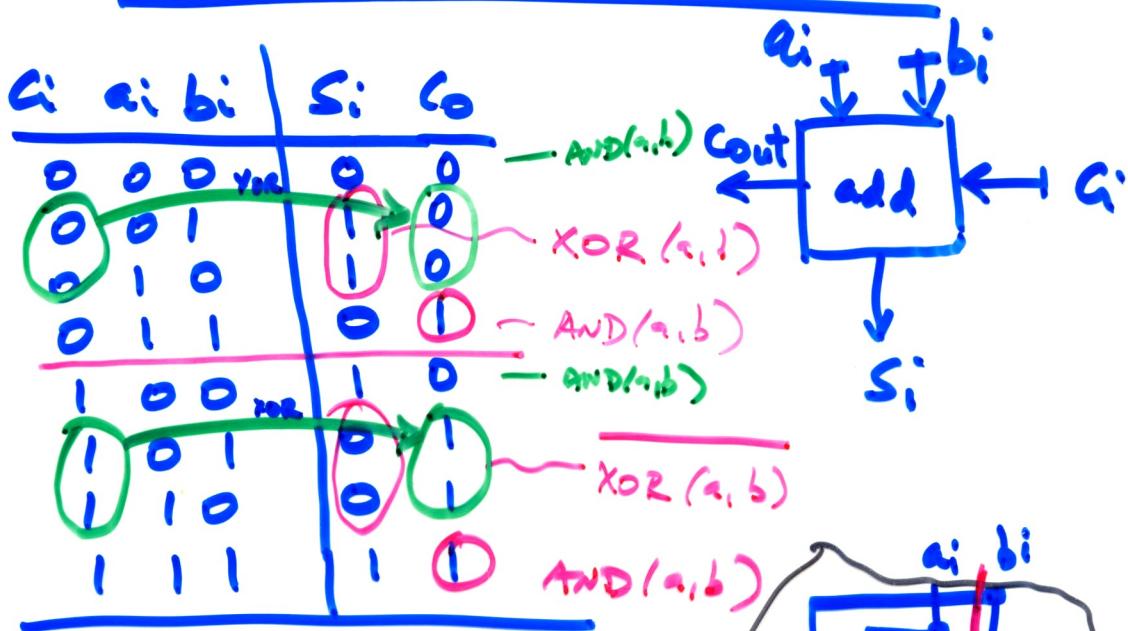


$$a = \sum D_i a_i$$


$$c_0 = g_i + p_i \cdot c_i$$

$$g_i = a_i \cdot b_i = D_i \bar{g}_i$$


$$p_i = a_i \oplus b_i$$

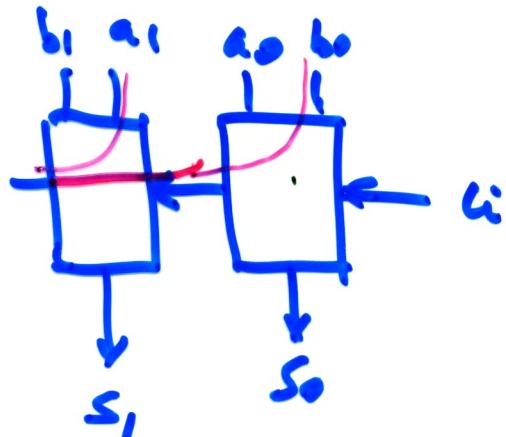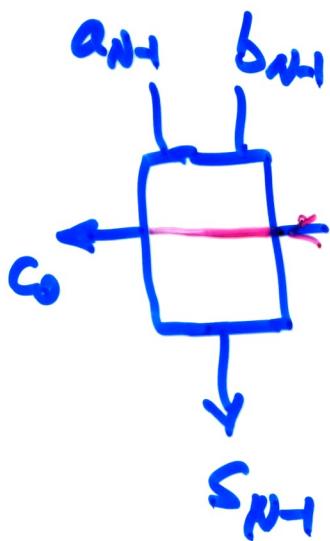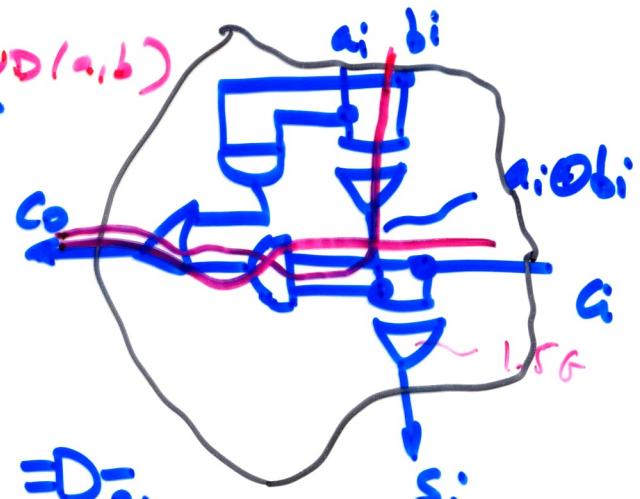
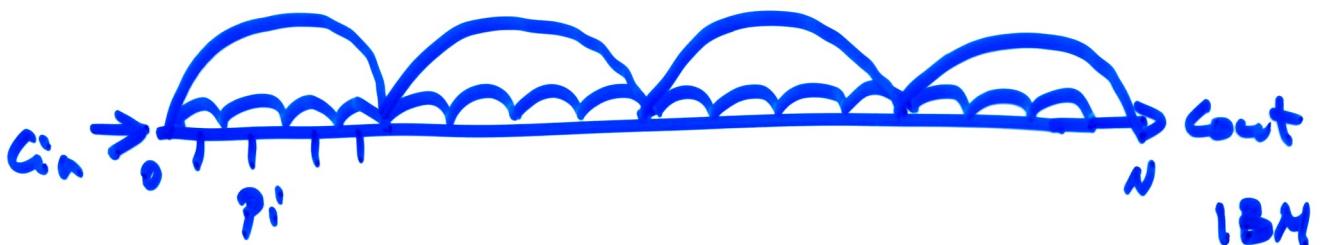
$$\underline{2\Delta(N \cancel{\oplus}) + \Delta_{XOR} = 6\Delta}$$




$$P_i = P_i P_{i+1} P_{i+2} P_{i+3}$$

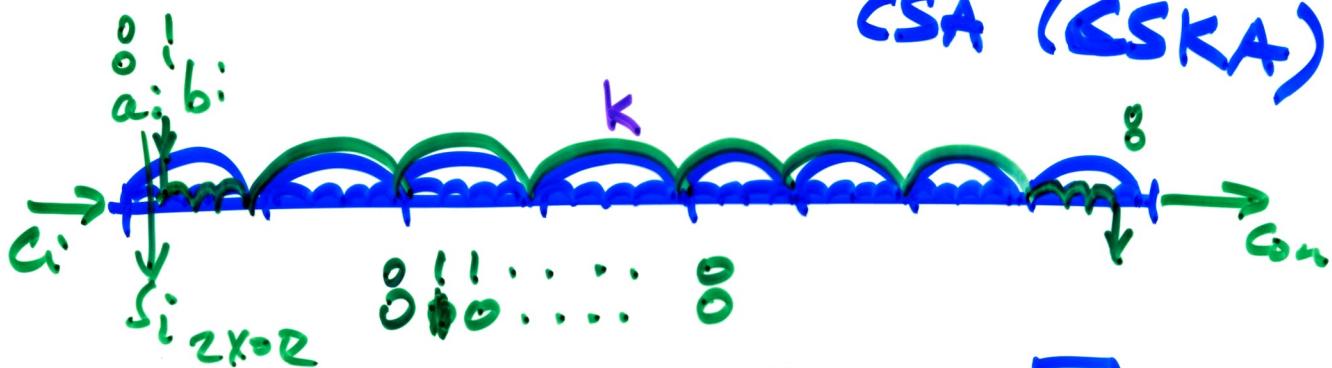

$$D = 8\Delta_s$$


$$D = \left[\left(\frac{N}{K} - 2 \right) + (K-1)2 \right] \Delta_s$$

CSKA

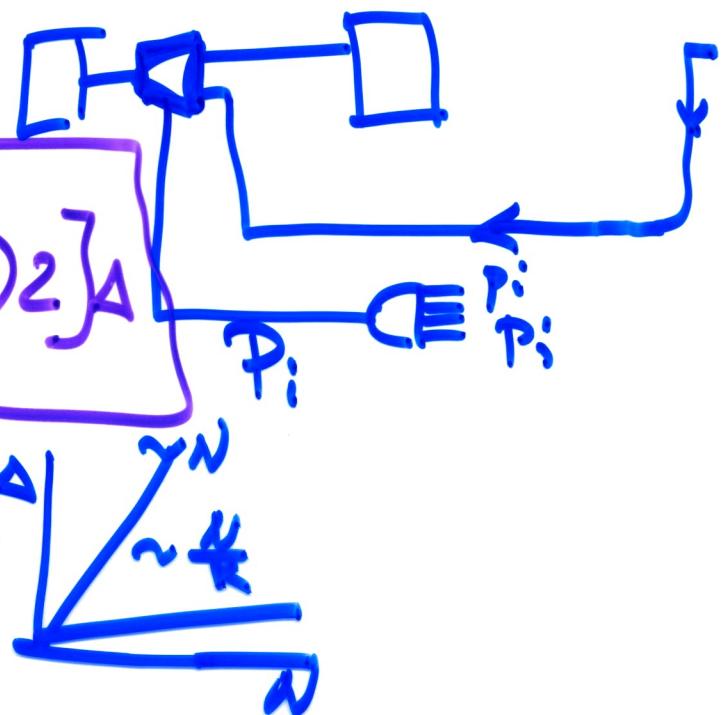


Earl Barnes $\langle FT \rangle$

ARITH '85 Urbana, IL

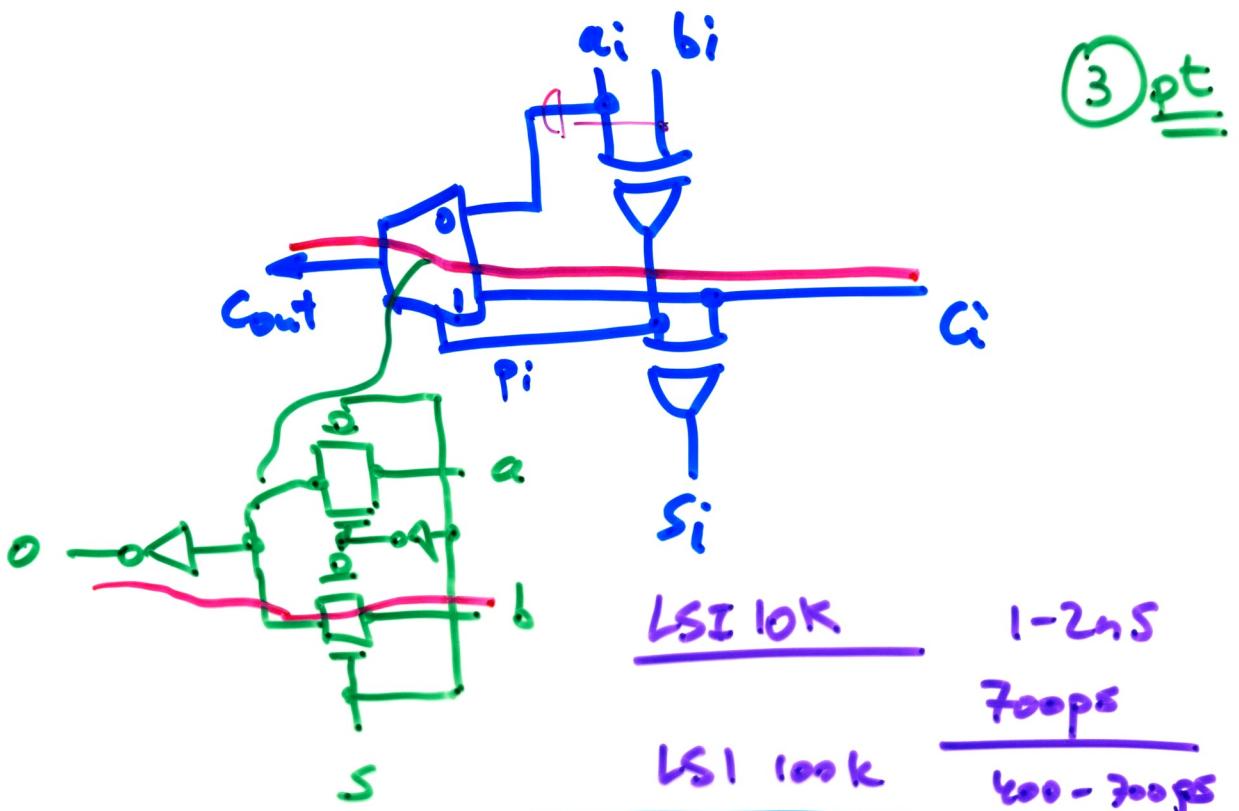


$$\text{Delay} = (n-1) \Delta_{\text{mux}} + \Delta_{\text{xor}}$$

RCA:

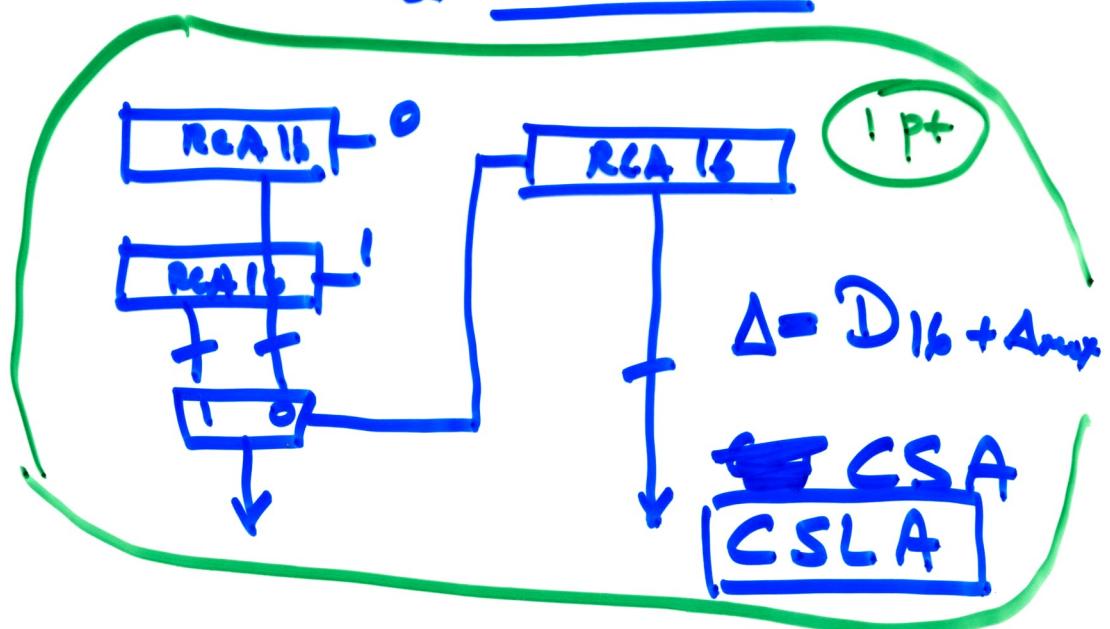

CLA < Arnold Weinberger 1959
 IBM NBS

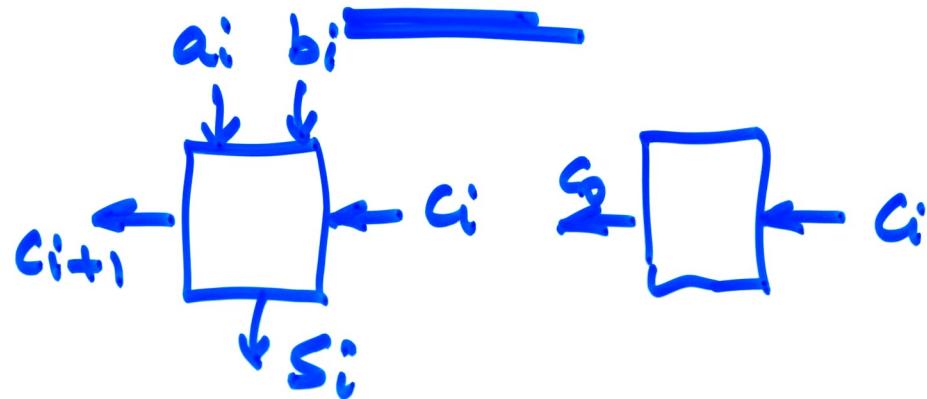


$$c_{i+1} = g_i + P \cdot c_i$$

$$g_i = g_0 + p \cdot c_{in}$$

$$c_1 = g_1 + p_1 (g_0 + p_0 c_{in})$$

$$= g_1 + p_1 g_0 + p_1 p_0 c_{in}$$

$$\vdots G$$

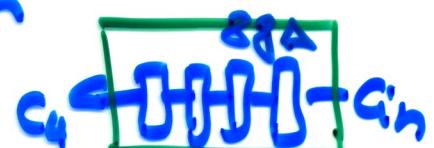


$$c_4 = \overbrace{g_3 + p_3 g_2 + p_3 p_2 g_1 + p_3 p_2 p_1 g_0}^G + \underbrace{p_3 p_2 p_1 p_0}_{P} \cdot c_{in}$$

$$c_{i+1} = g_i + p_i g_{i-1} + p_i p_{i-1} g_{i-2} \dots$$

$$c_4 = G + P \cdot c_{in}$$

$$D = 2\Delta + 2\Delta = 4\Delta$$

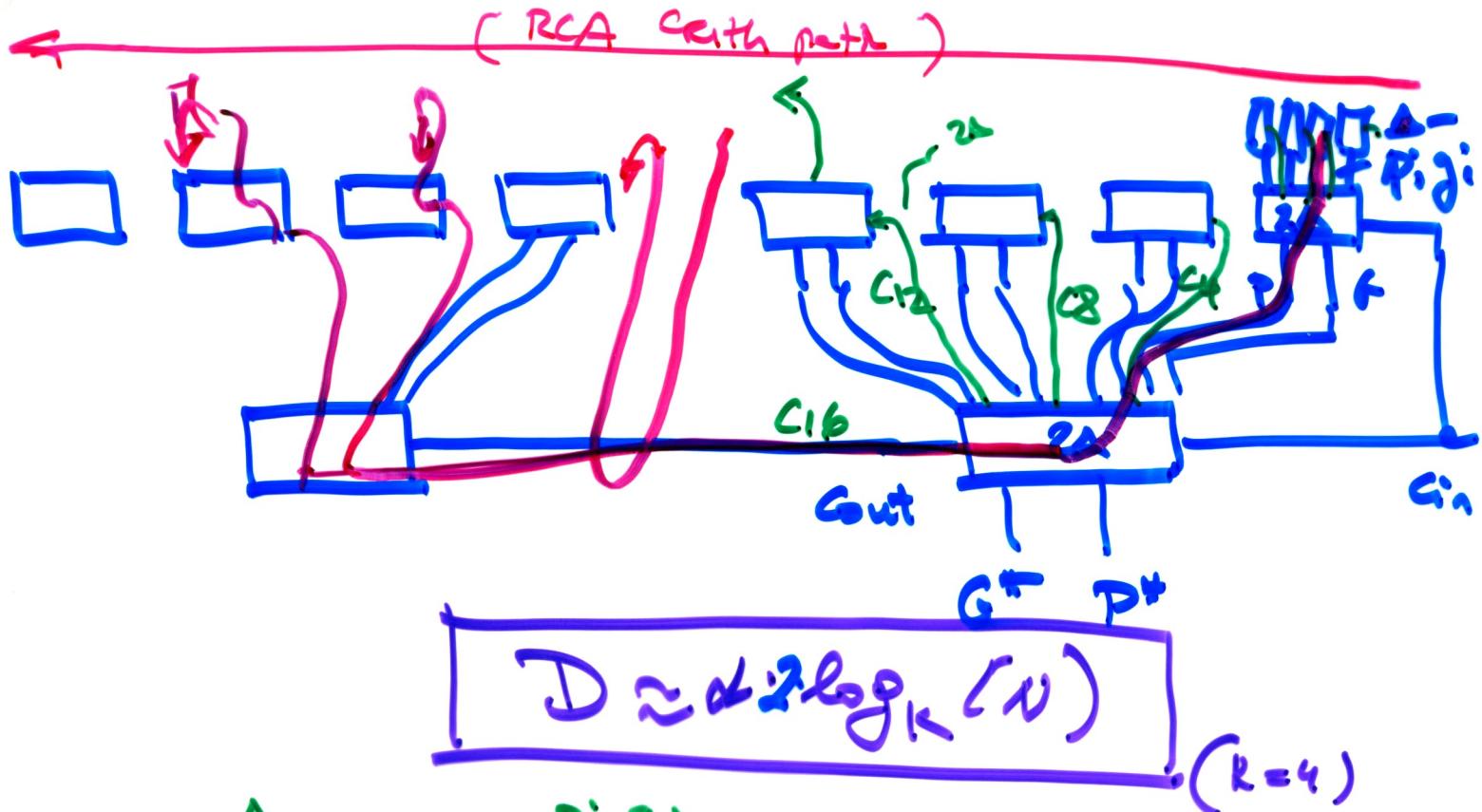

Δ ---- Pi \exists

$$z_A \dots P_1 G_1 c_1 c_2 c_3 \dots P^* = P_0 P_1 P_2 P_3$$

$z_A \dots p^*, G^*, c_{16} G^*$

$$2\Delta \dots c_4, c_8, c_{12}$$

2Δ \approx 1.5

A : - - - S :

10A CLA (65A RCA, 14A CSA)


CLA (1977, Weinberger, A.)
Carry Lookahead Smith

$$C_1 = g_0 + p_0 \cdot C_0$$

$$C_2 = g_1 + P_1 \cdot C_1$$

$$C_3 = g_2 + P_2 \cdot C_2$$


$$C_4 = g_3 + P_3 \cdot C_3$$

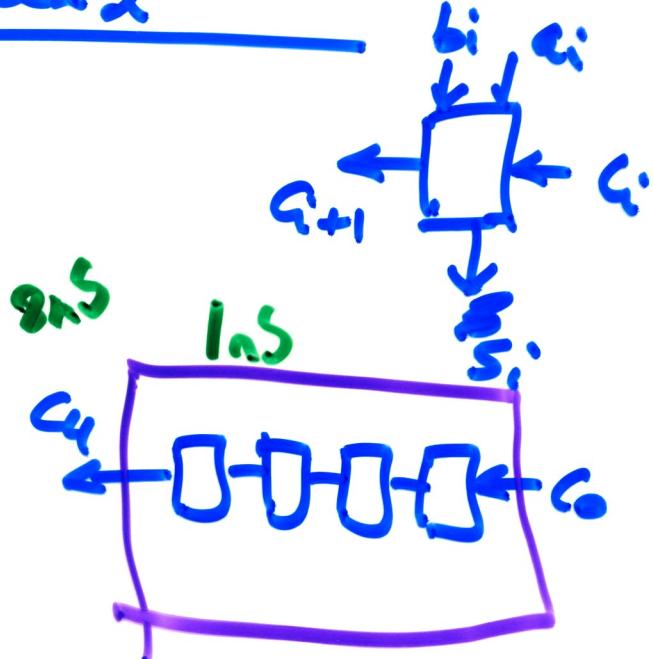



$$C_4 = \underbrace{g_3 + P_3 g_2 + P_3 P_2 g_1 + P_3 P_2 P_1 g_0}_{G} + \underbrace{P_3 P_2 P_1 P_0 \cdot C_0}_P$$

$$C_4 = G + P \cdot C_0$$

- | | | | |
|-----|------------|-----|-----|
| (1) | P_i, g_i | 1L6 | 1ns |
| (2) | P | 1L6 | 2ns |
| (3) | G | 2L | 3ns |
| (4) | C_4 | 2L | 5ns |

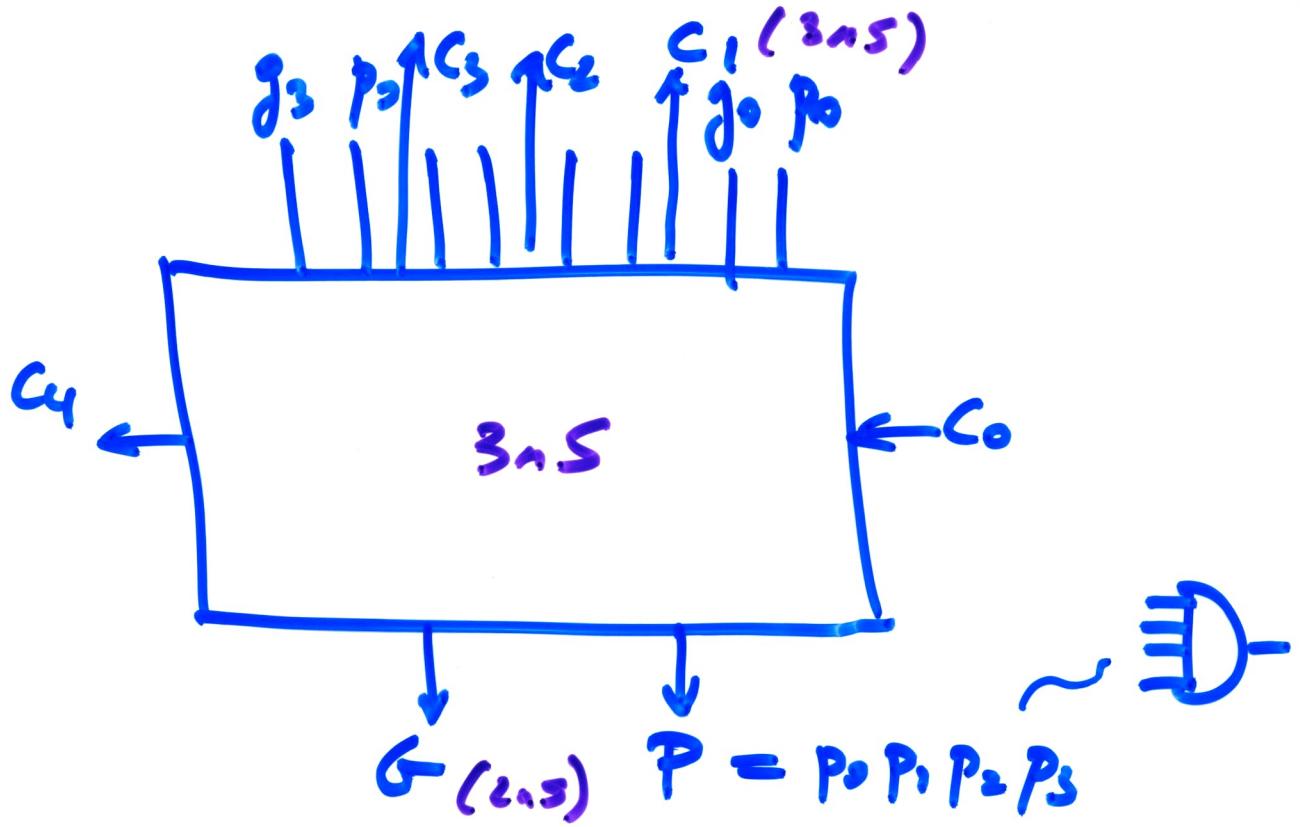
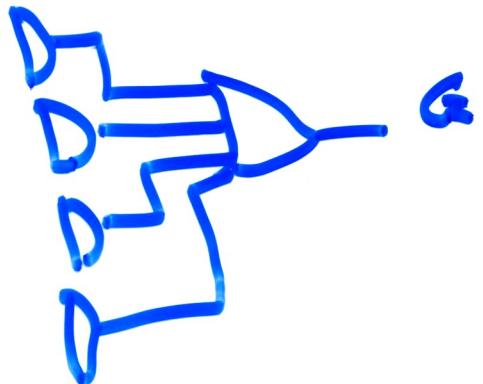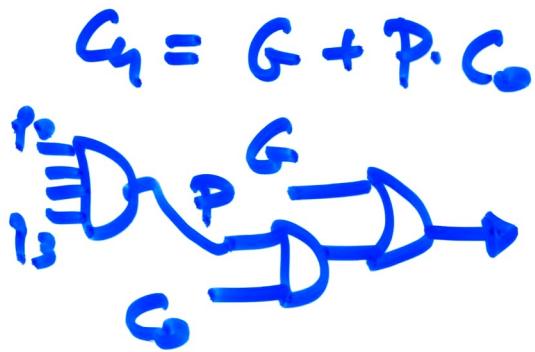
$$G = g_3 + g_2 p_3 + g_1 p_2 p_3 + g_0 p_1 p_2 p_3$$




$$C_0 = g_0 + p_0 C_0$$

$$C_1 = \dots$$

$$C_2 = \dots$$

32-bit CLA (Weinberger '69)

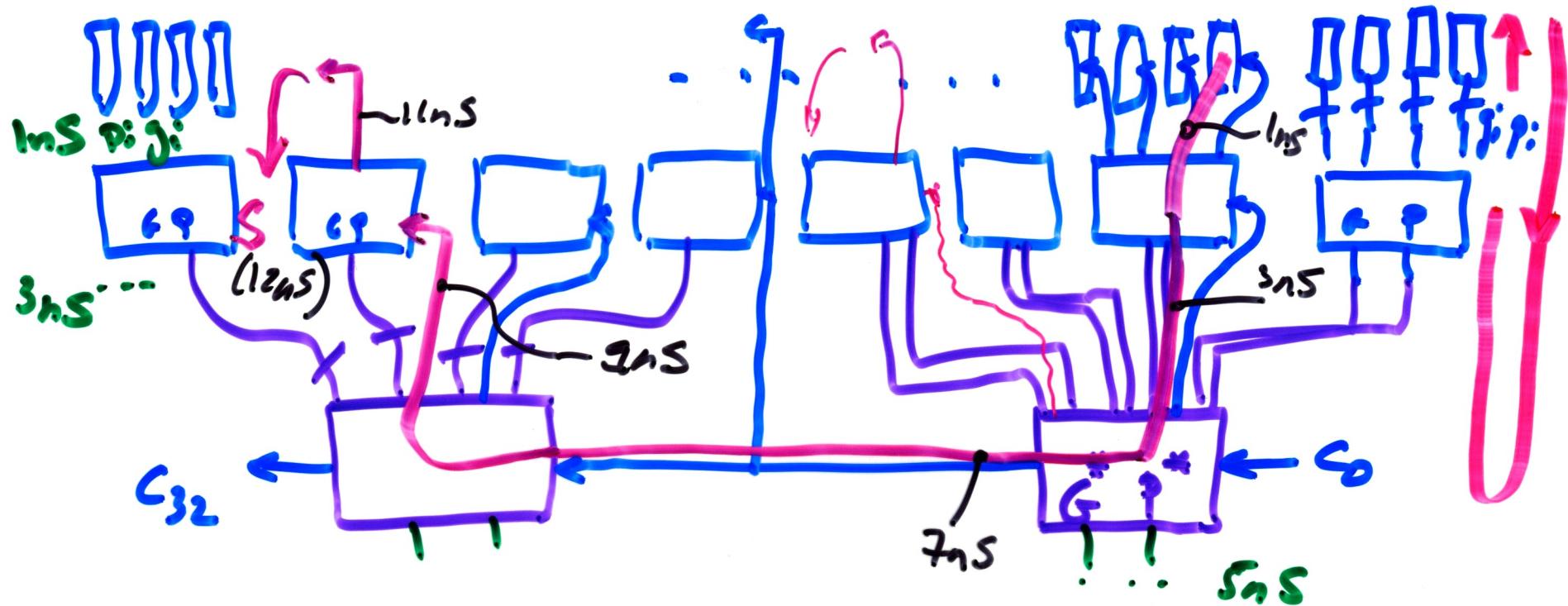


$$RCA \quad 32 \times 2 \times 1\text{ns} = 64\text{ns}$$


$$g_j = g^* + P^+ g_{j+1} \quad \text{2L } (2\text{ns})$$

$CLA = 12\text{ns}$	vs	$64\text{ns} (\text{RCA})$
---------------------	-------------	----------------------------

$24\text{ns} (\text{CSA})$

Depth $\sim \log_2 N \sim \Delta \sim k \log_2 N$

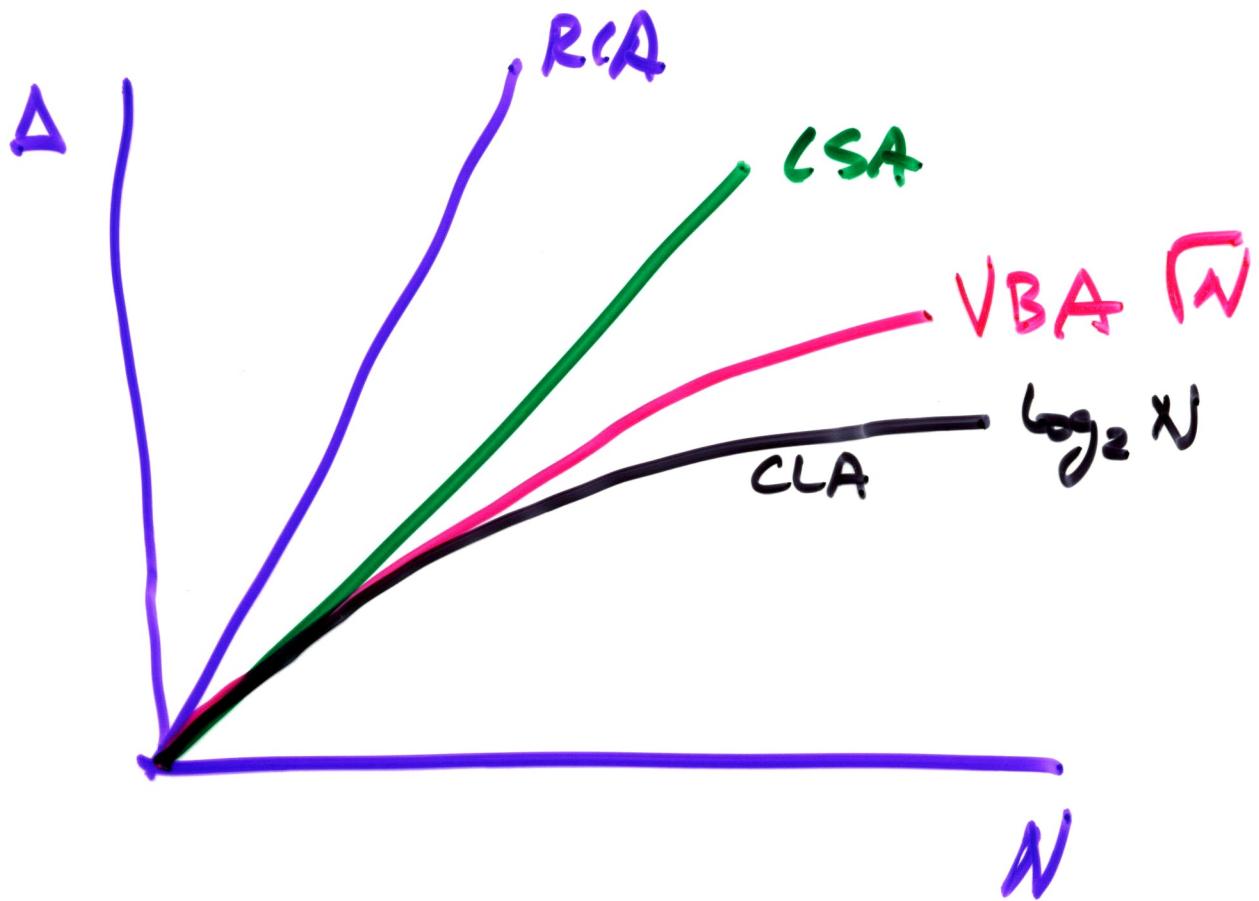

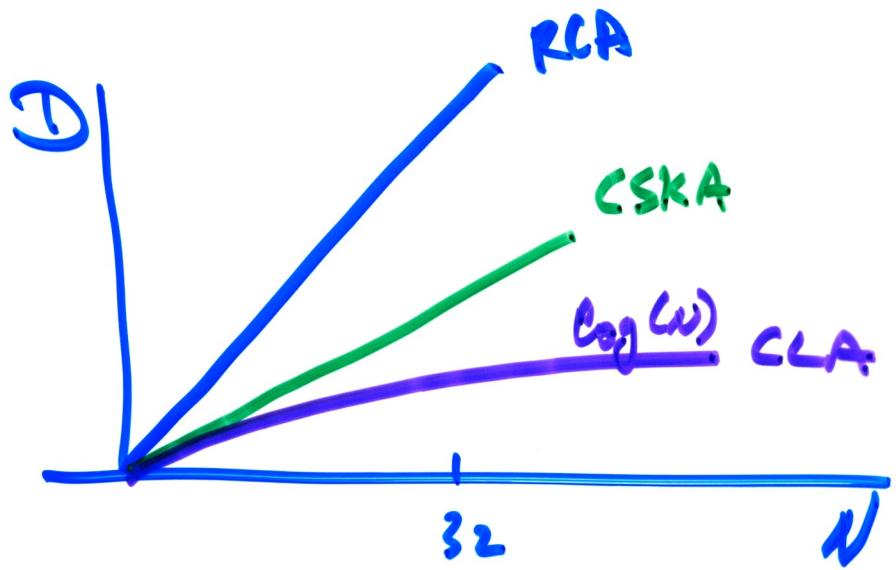


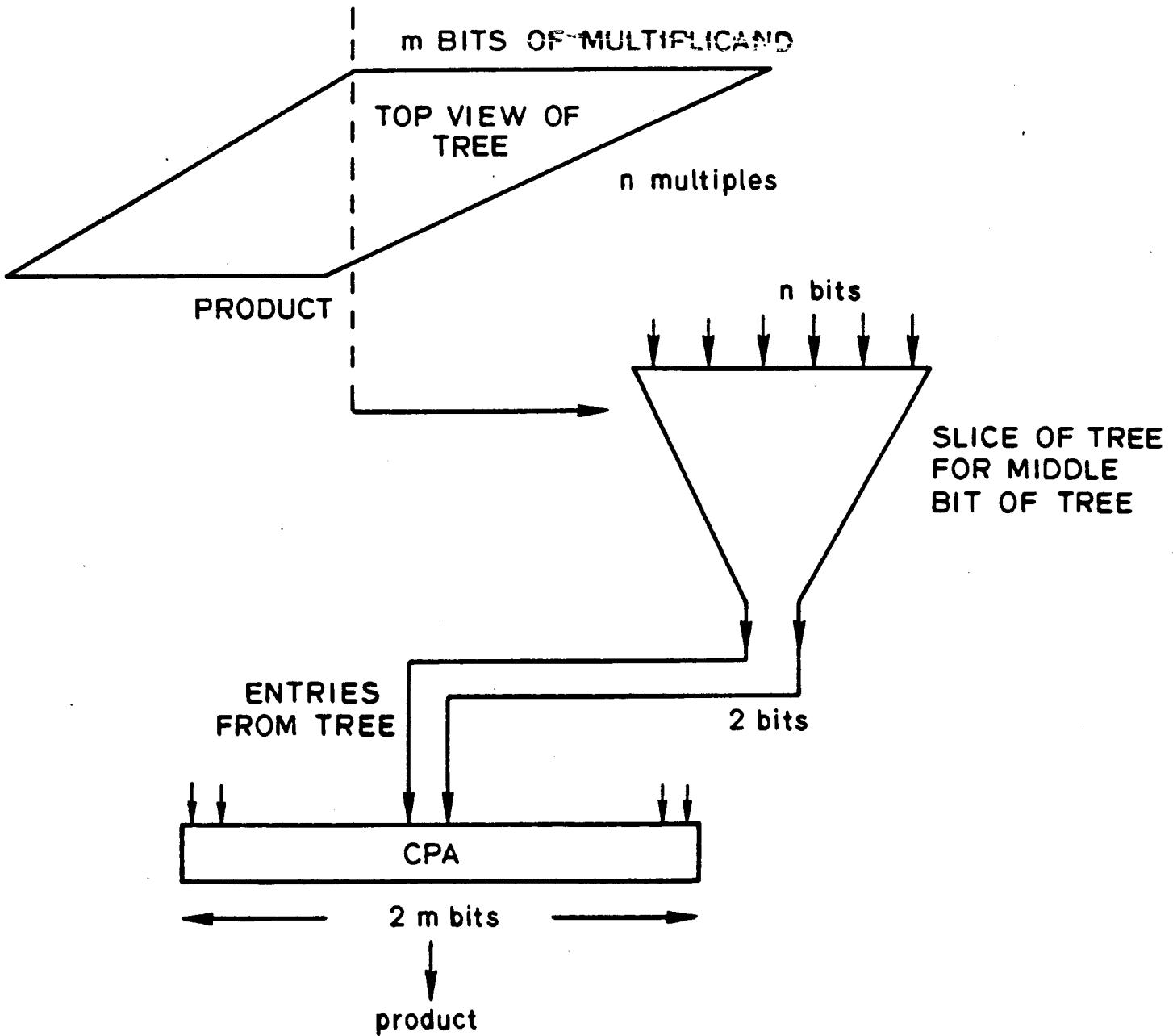


Figure 4-6. Wallace tree

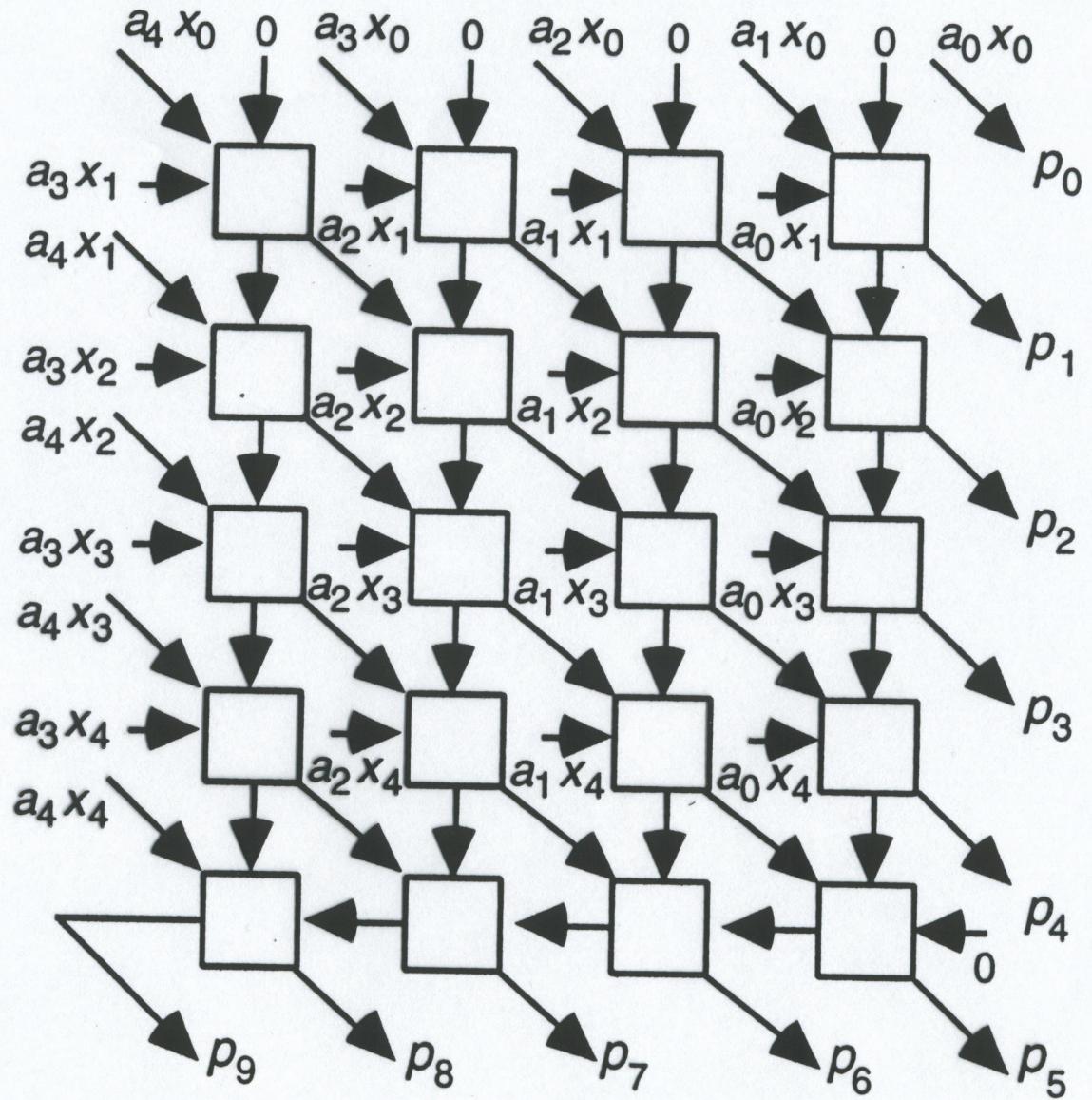

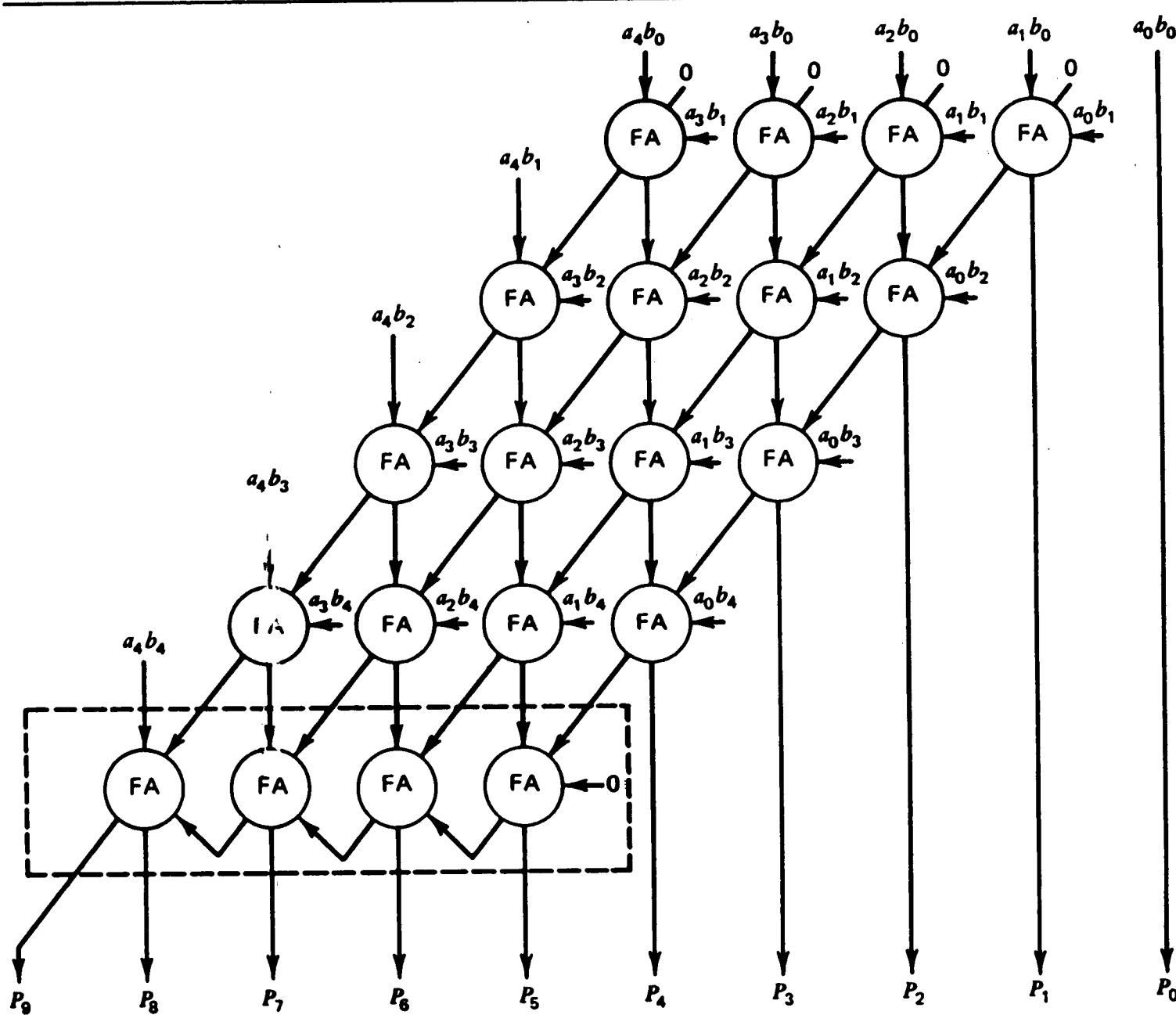


Figure 6.3 The schematic circuit diagram of a 5-by-5 unsigned array multiplier (Braun [5]).

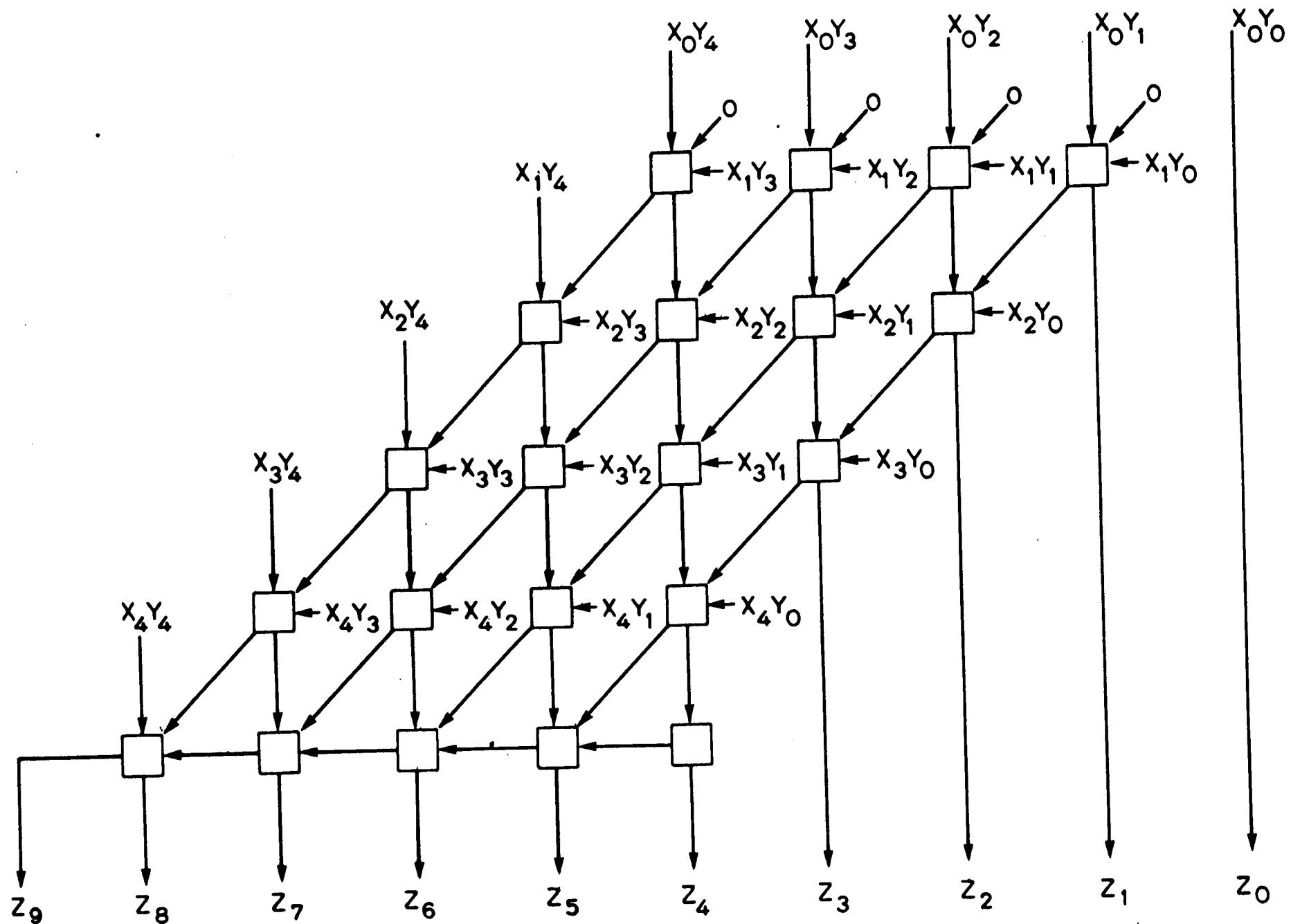


Figure 4-15a. 5×5 unsigned multiplication.

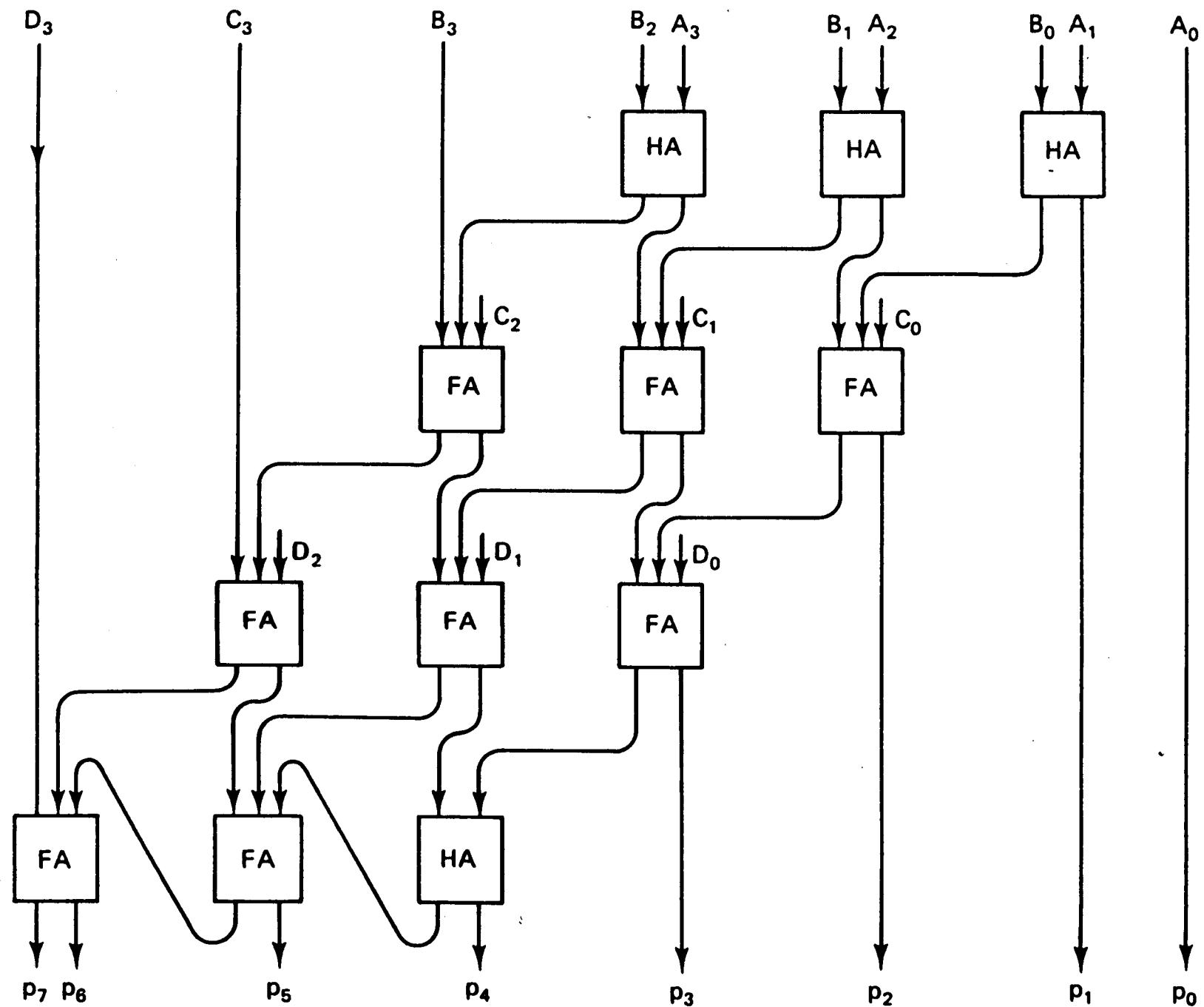


Figure 4.4 Array of half-adders and full-adders for 4-bit \times 4-bit multiplication.