 



VLSI Arithmetic

Adders & Multipliers




Prof. Vojin G. Oklobdzija
University of California

<http://www.ece.ucdavis.edu/acsel>

 

Addition of Binary Numbers

 Full Adder. The full adder is the fundamental building block of most arithmetic circuits:



The sum and carry outputs are described as:

$$s_i = a_i \bar{b}_i \bar{c}_i + \bar{a}_i b_i \bar{c}_i + \bar{a}_i \bar{b}_i c_i + a_i b_i c_i$$

$$c_{i+1} = \bar{a}_i \bar{b}_i c_i + a_i \bar{b}_i \bar{c}_i + a_i \bar{b}_i c_i + a_i b_i \bar{c}_i = a_i b_i + a_i c_i + b_i c_i$$

Addition of Binary Numbers

<i>Inputs</i>			<i>Outputs</i>	
c_i	a_i	b_i	s_i	c_{i+1}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Full-Adder Implementation


Full Adder operations is defined by equations:

$$s_i = a_i \bar{b}_i \bar{c}_i + \bar{a}_i b_i \bar{c}_i + \bar{a}_i \bar{b}_i c_i + a_i b_i c_i = a_i \oplus b_i \oplus c_i = p_i \oplus c_i$$

$$c_{i+1} = \bar{a}_i b_i c_i + a_i \bar{b}_i c_i + a_i b_i = g_i + p_i c_i$$

Carry-Propagate: $p_i = a_i \oplus b_i$
and Carry-Generate g_i


$$g_i = a_i \bullet b_i$$

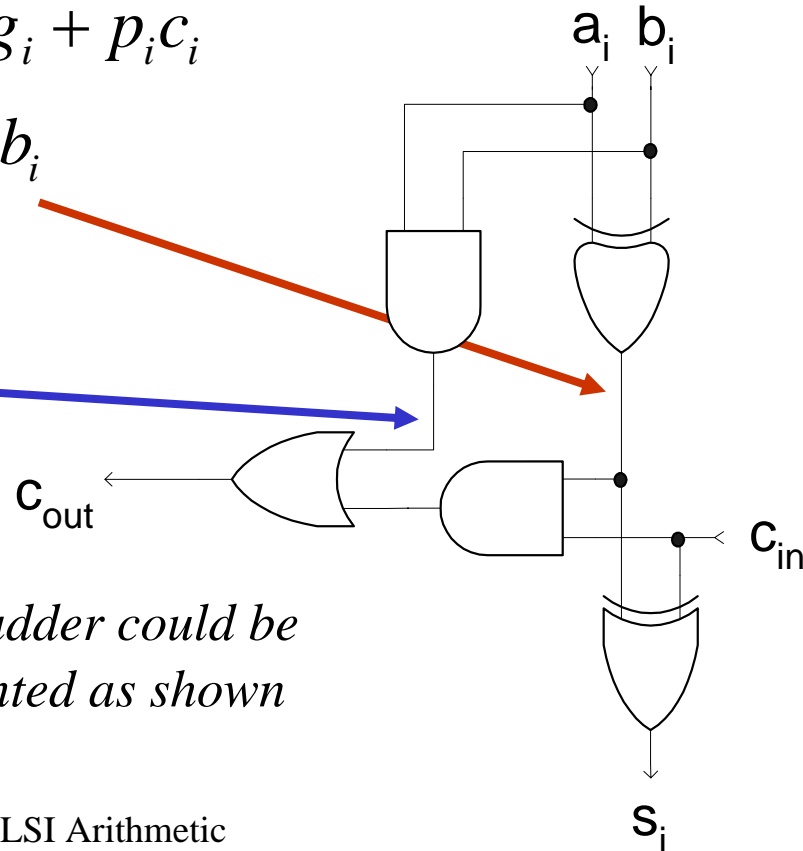

One-bit adder could be implemented as shown

High-Speed Addition


$$C_{i+1} = g_i + p_i C_i$$

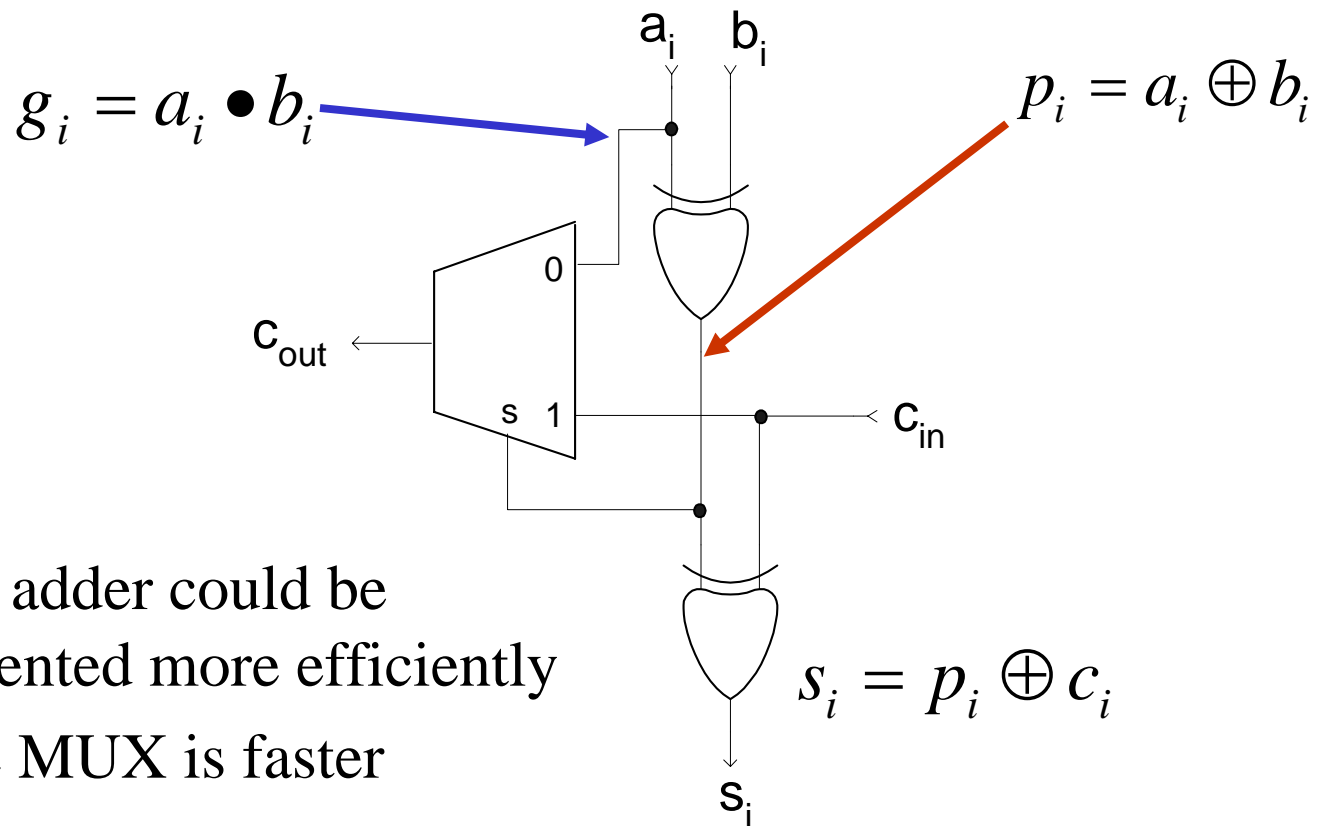

One-bit adder could be implemented more efficiently because MUX is faster

The Ripple-Carry Adder

The Ripple-Carry Adder

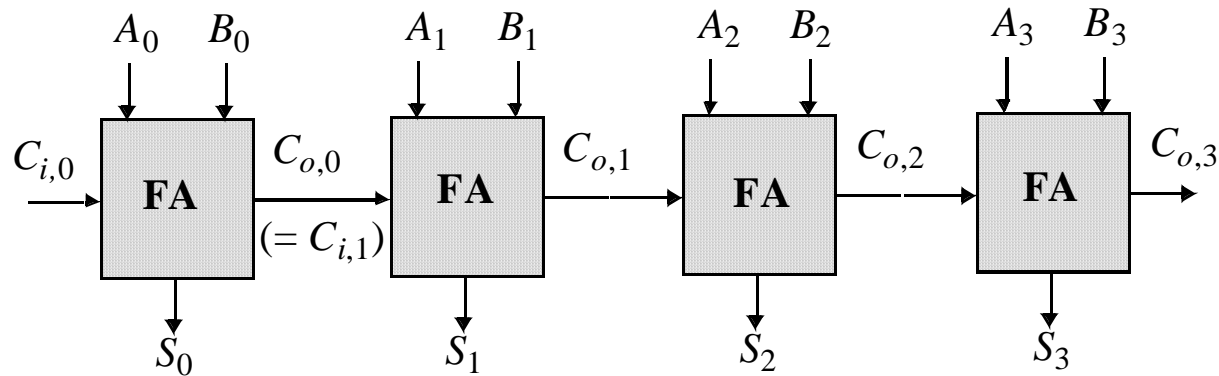

Worst case delay linear with the number of bits

$$t_d = O(N)$$

$$t_{\text{adder}} \approx (N - 1)t_{\text{carry}} + t_{\text{sum}}$$


Goal: Make the fastest possible carry path circuit

From Rabaey

Prof. V.G. Oklobdzija

VLSI Arithmetic

Inversion Property

 

$$\bar{S}(A, B, C_i) = S(\bar{A}, \bar{B}, \bar{C}_i)$$
$$\bar{C}_o(A, B, C_i) = C_o(\bar{A}, \bar{B}, \bar{C}_i)$$


From Rabaey

Prof. V.G. Oklobdzija

VLSI Arithmetic

8

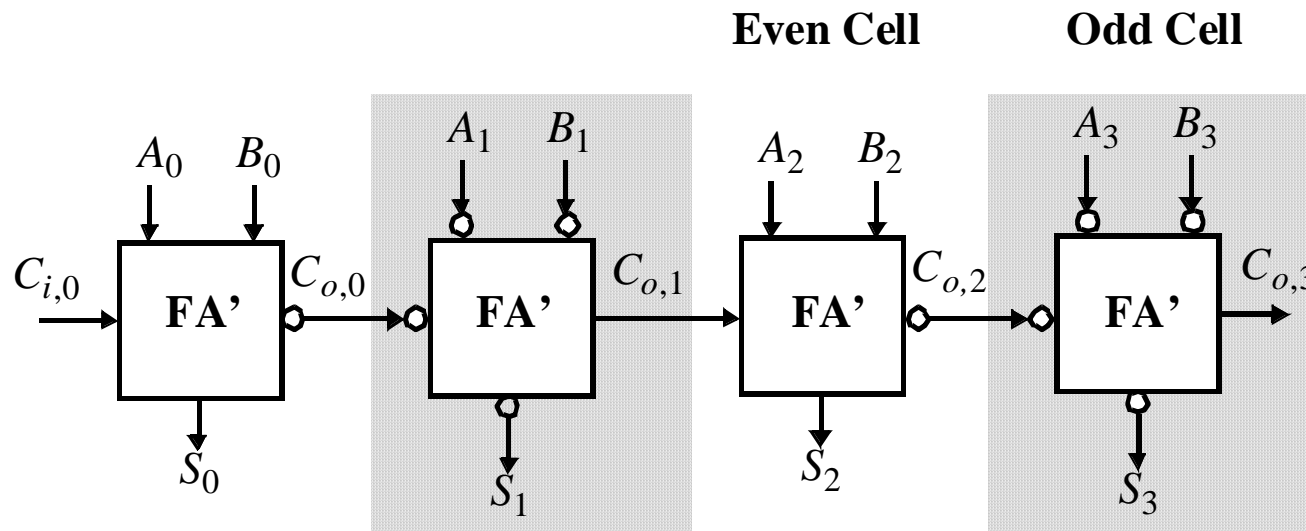Minimize Critical Path by Reducing Inverting Stages




Exploit Inversion Property

From Rabaey **Note: need 2 different types of cells**

Manchester Carry-Chain


Realization of the Carry Path

 - Simple and very popular scheme for implementation of carry signal path



Manchester Carry Chain

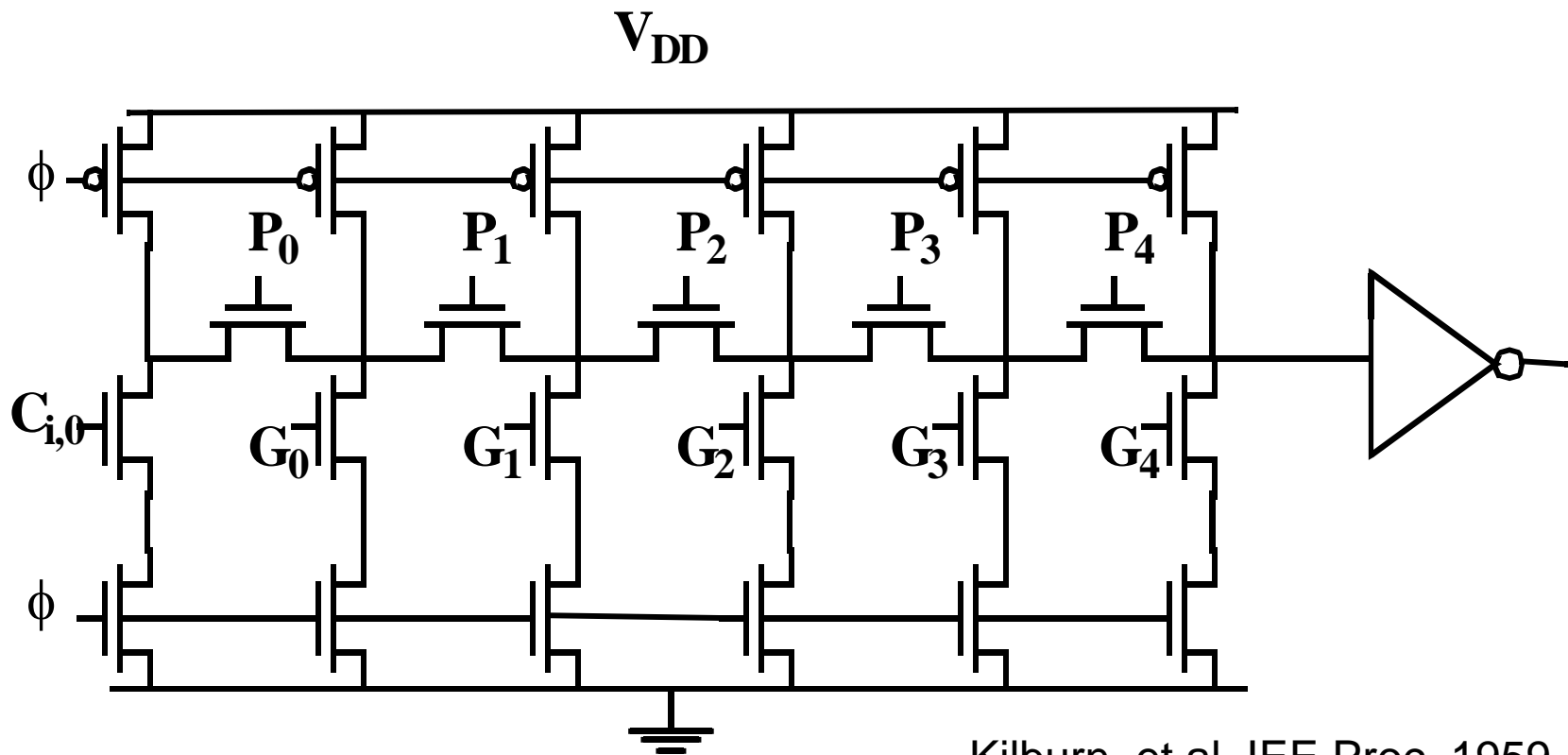
- Implement P with pass-transistors
- Implement G with pull-up, kill (delete) with pull-down
- Use dynamic logic to reduce the complexity and speed up



Kilburn, et al, IEE Proc, 1959.

Ripple Carry Adder

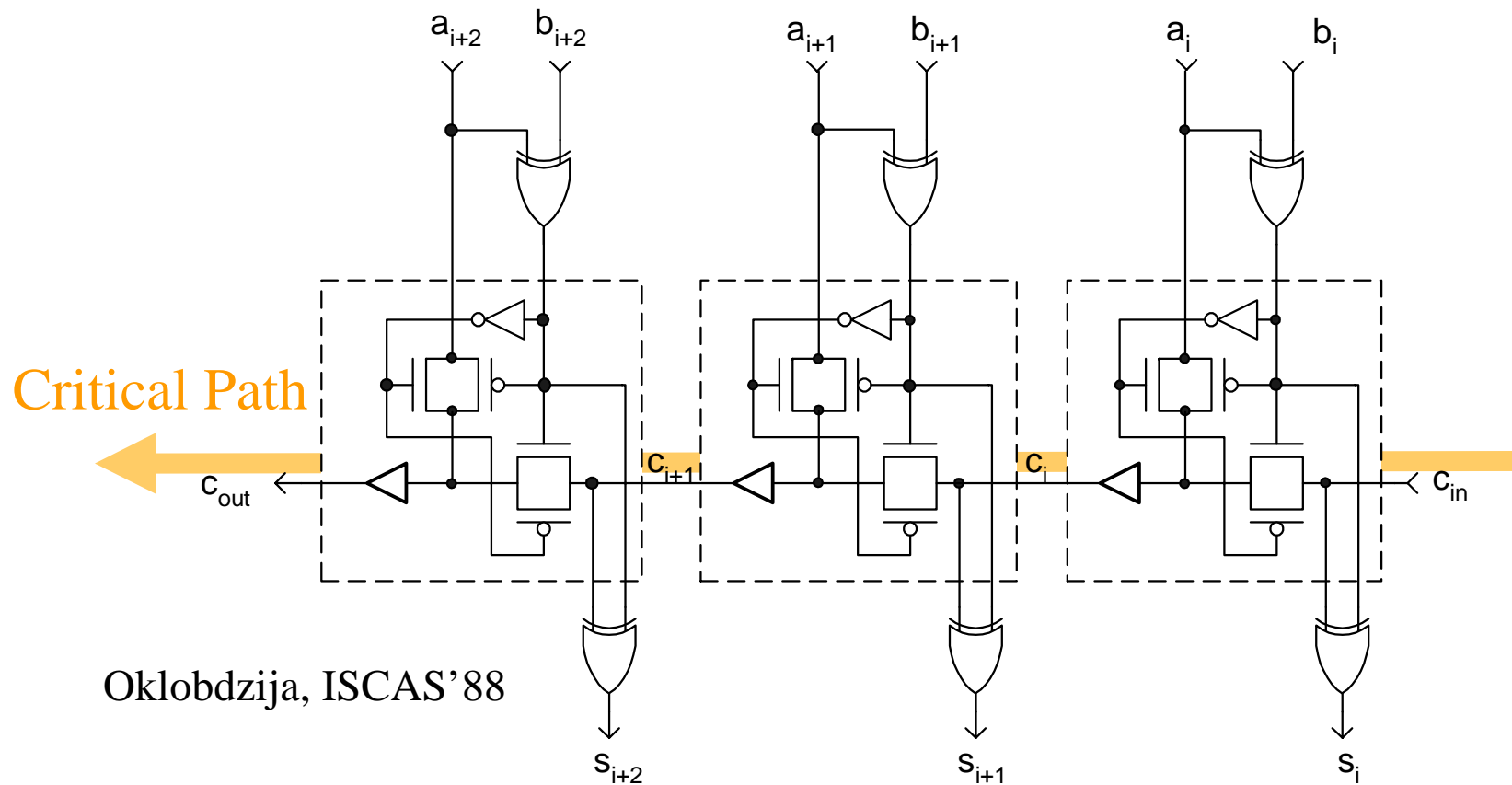Carry-Chain of an RCA implemented using multiplexer from the standard cell library:



Oklobdzija, ISCAS'88

Carry-Lookahead Adder

(Weinberger and Smith)

Weinberger and J. L. Smith, “A Logic for High-Speed Addition”,
National Bureau of Standards, Circ. 591, p.3-12, 1958.

Carry-Lookahead Adder

(Weinberger and Smith)

$$c_{i+1} = \bar{a}_i b_i c_i + a_i \bar{b}_i c_i + a_i b_i = g_i + p_i c_i$$

$$c_{i+2} = g_{i+1} + p_{i+1} c_{i+1}$$

$$= g_{i+1} + p_{i+1} (g_i + p_i c_i)$$

$$= g_{i+1} + p_{i+1} g_i + p_{i+1} p_i c_i$$

$$c_{i+3} = g_{i+2} + p_{i+2} c_{i+2}$$


$$= g_{i+2} + p_{i+2} (g_{i+1} + p_{i+1} g_i + p_{i+1} p_i c_i)$$

$$= g_{i+2} + p_{i+2} g_{i+1} + p_{i+2} p_{i+1} g_i + p_{i+2} p_{i+1} p_i c_i$$

Carry-Lookahead Adder

$$G_j = g_{i+3} + p_{i+3}g_{i+2} + p_{i+3}p_{i+2}g_{i+1} + p_{i+3}p_{i+2}p_{i+1}c_j$$

$$P_j = p_{i+3}p_{i+2}p_{i+1}p_i$$

 


$$c_{4(j+1)} = G_i + P_i c_{4j}$$

Compare that to 8 Δ in RCA !

Carry-Lookahead Adder (Weinberger and Smith)

$$G^*_j = G_{i+3} + P_{i+3}G_{i+2} + P_{i+3}P_{i+2}G_{i+1} + P_{i+3}P_{i+2}P_{i+1}G_i$$

$$P^*_j = P_{i+3}P_{i+2}P_{i+1}P_i$$

 


$$C_{4(j+1)} = G^*_k + P^*_k C_{4j}$$

Additional two gate delays

C_{16} will take a total of 5Δ vs. 32Δ for RCA !

32-bit Carry Lookahead Adder

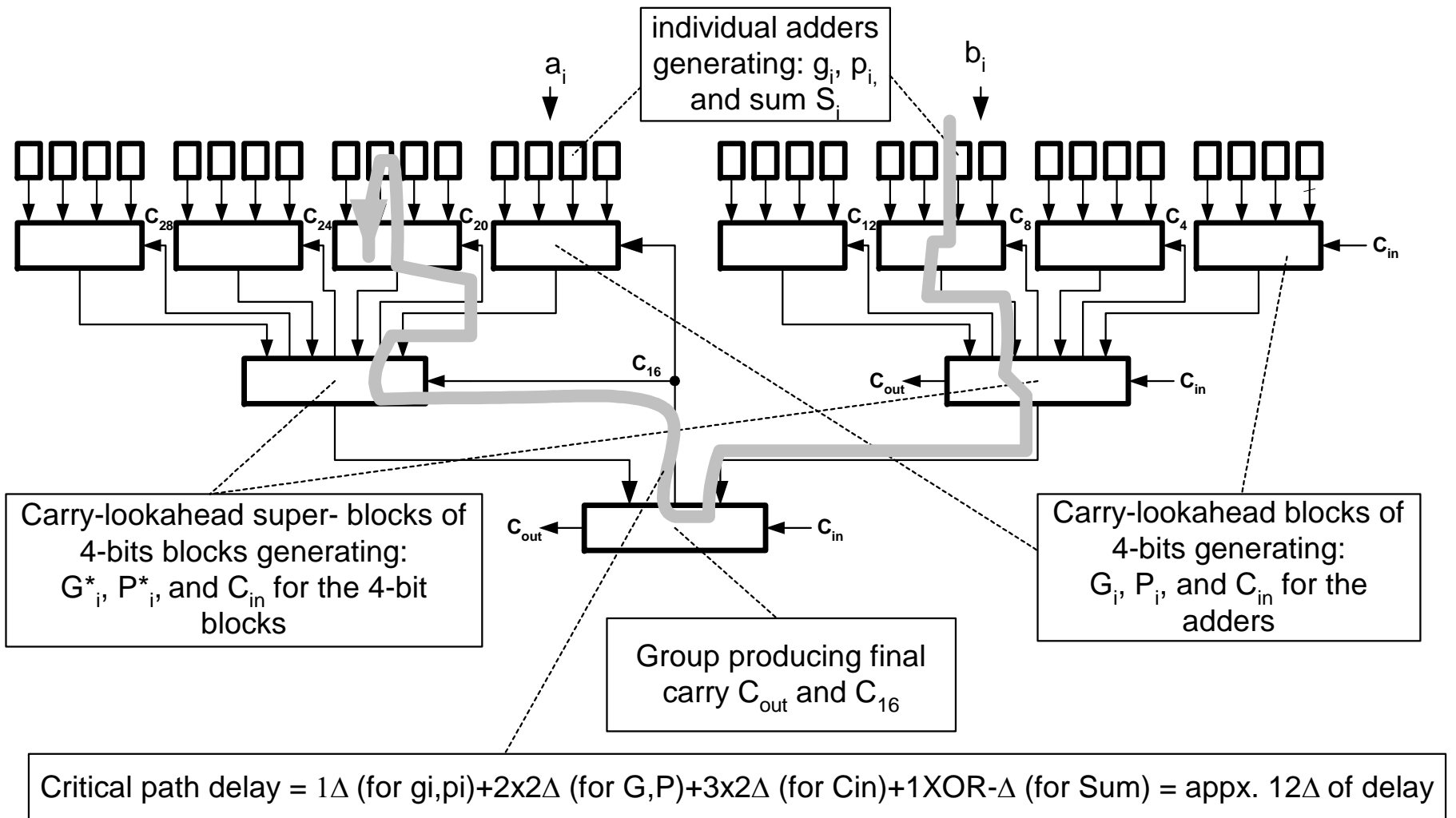

Carry-Lookahead Adder

(Weinberger and Smith: original derivation)

$$C_1 = A_1 B_1 \\ + (A_1 + B_1) C_0$$

$$C_2 = A_2 B_2 \quad = \quad A_2 B_2 \\ + (A_2 + B_2) C_1 \quad + (A_2 + B_2) A_1 B_1 \\ + (A_2 + B_2) (A_1 + B_1) C_0$$

$$C_3 = A_3 B_3 \quad = \quad A_3 B_3 \\ + (A_3 + B_3) C_2 \quad + (A_3 + B_3) A_2 B_2 \\ + (A_3 + B_3) (A_2 + B_2) A_1 B_1 \\ + (A_3 + B_3) (A_2 + B_2) (A_1 + B_1) C_0$$

Carry-Lookahead Adder

(Weinberger and Smith: original derivation)

$$\begin{aligned}
 C_4 &= A_4 B_4 &= A_4 B_4 \\
 &+ (A_4 + B_4) C_3 &+ (A_4 + B_4) A_3 B_3 \\
 &&+ (A_4 + B_4) (A_3 + B_3) A_2 B_2 \\
 &&+ (A_4 + B_4) (A_3 + B_3) (A_2 + B_2) A_1 B_1 \\
 &&+ (A_4 + B_4) (A_3 + B_3) (A_2 + B_2) (A_1 + B_1) C_0 \\
 &= A_4 B_4 &+ (A_4 + B_4) A_3 B_3 \\
 &&+ (A_4 + B_4) (A_3 + B_3) A_2 B_2 \\
 &&+ (A_4 + B_4) (A_3 + B_3) (A_2 + B_2) (A_1 + B_1) (A_1 + C_0) (B_1 + C_0).
 \end{aligned}$$

Carry-Lookahead Adder (Weinberger and Smith)

please notice the similarity with Parallel-Prefix Adders !

 


FIGURE 1.9. Twenty-one-bit parallel binary adder

Carry-Lookahead Adder (Weinberger and Smith)

please notice the similarity with Parallel-Prefix Adders !

 


FIGURE 1.10. Fifty-three-bit parallel binary adder.