

Your Name: _____

Problem #1:

Write decimal number 38 in:


(a.) binary: 100110

(b.) hexadecimal:

(c.) octal:

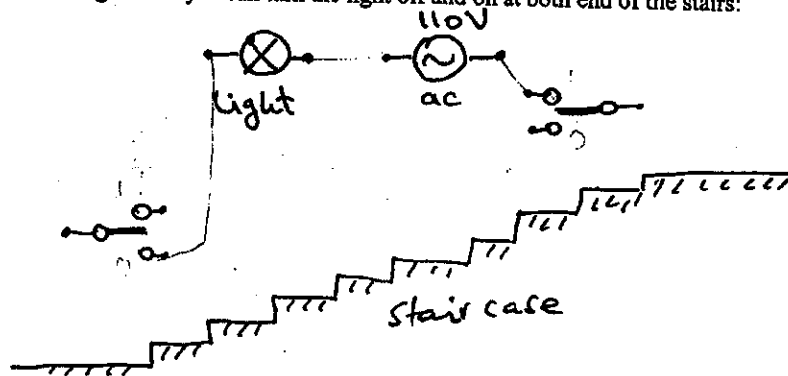
Problem #2:

Given are the light bulb, two double-throw switches and power source.
Finish the wiring so that you can turn the light off and on at both end of the stairs:



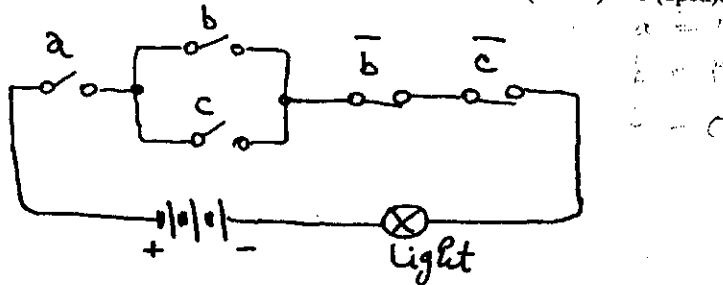Problem #3:

When is the light ON in the circuit shown? Note when $a=1$ (closed) $\bar{a}=0$ (open).



Your Name: _____

Problem #1:

Write decimal number 38 in:

$$2 \times 4 + 3 + 10 = 32$$

a = 0
b = 1
:
:
f = 15


(a.) binary: 0010 0110

(b.) hexadecimal:

(c.) octal:

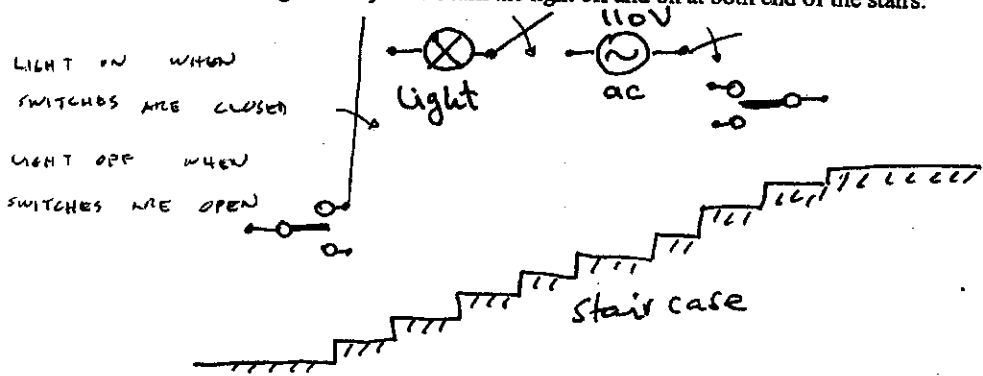
Problem #2:

Given are the light bulb, two double-throw switches and power source.
Finish the wiring so that you can turn the light off and on at both end of the stairs:



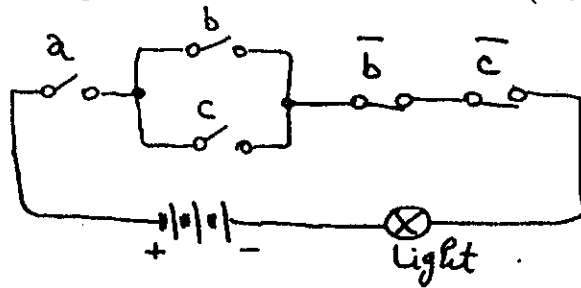Problem #3:

When is the light ON in the circuit shown? Note when a=1 (closed) a=0 (open).



WHEN a = 1 ALWAYS
AND
WHEN EITHER
b = 1
OR
c = 1

Your Name: _____


Problem #1:

Write decimal number 38 in:

- (a.) binary:
- (b.) hexadecimal:
- (c.) octal:

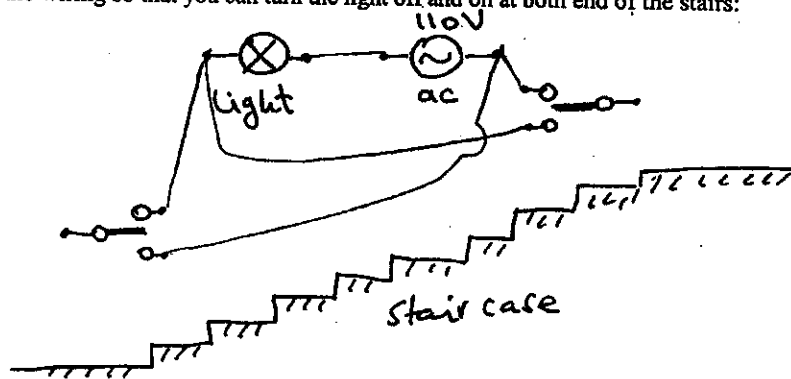
Problem #2:

Given are the light bulb, two double-throw switches and power source.
Finish the wiring so that you can turn the light off and on at both end of the stairs:



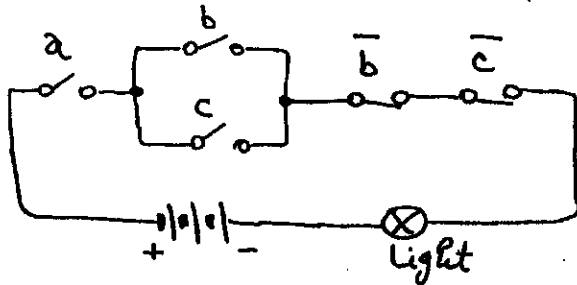Problem #3:

When is the light ON in the circuit shown? Note when $a=1$ (closed) $\bar{a}=0$ (open).



in this ckt,
the light will
never be on
whether $a=1$
or
 $a=0$

because of the contradictory nature of

how they are placed in the ckt

Your Name: _____

Problem #1:

Write decimal number 38 in:


(a.) binary: 0010 0110

(b.) hexadecimal:

(c.) octal:

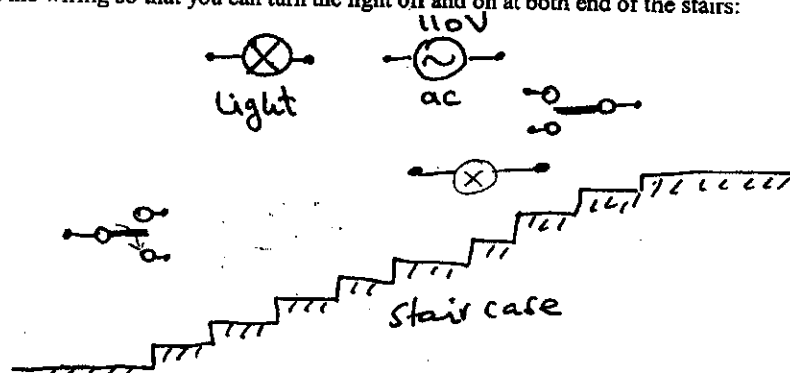
Problem #2:

Given are the light bulb, two double-throw switches and power source.
Finish the wiring so that you can turn the light off and on at both end of the stairs:



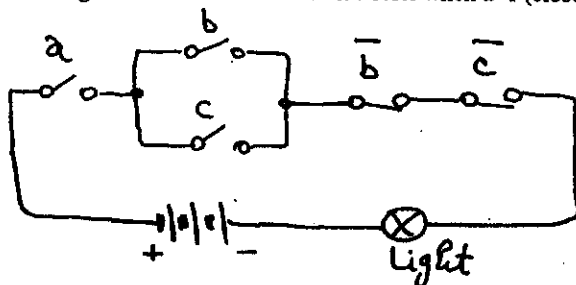Problem #3:

When is the light ON in the circuit shown? Note when $a=1$ (closed) $\bar{a}=0$ (open).



Your Name: _____

Problem #1:

Write decimal number 38 in:


(a.) binary: 100110

(b.) hexadecimal: 26

(c.) octal: 46

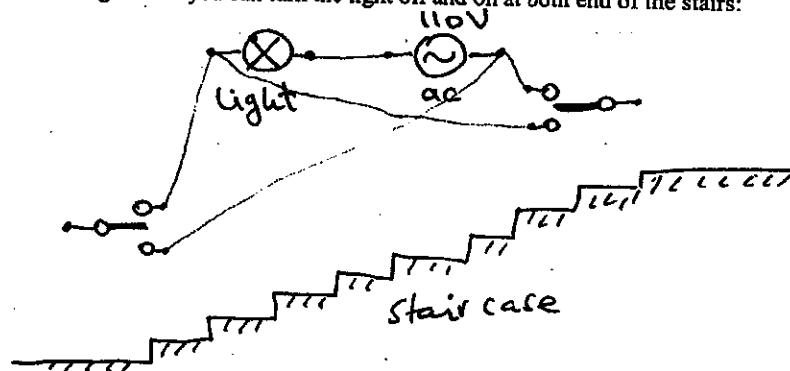
Problem #2:

Given are the light bulb, two double-throw switches and power source.
Finish the wiring so that you can turn the light off and on at both end of the stairs:



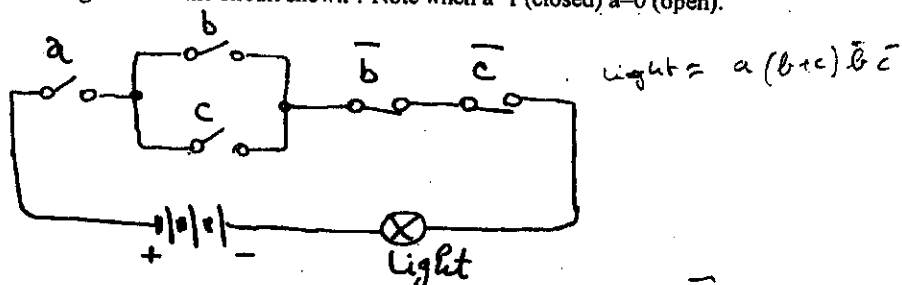Problem #3:

When is the light ON in the circuit shown? Note when $a=1$ (closed) $\bar{a}=0$ (open).



The light is on when a is closed and \bar{b} is closed and \bar{c} is closed and (either b or c is closed)

Your Name: _____

Problem #1:

Write decimal number 38 in:

(a.) binary: 011001


(b.) hexadecimal: 62

(c.) octal: 64

38	19	0	38
19	9	1	38 2 6
9	4	1	2 0 2
4	2	0	
2	1	0	
1	0	1	

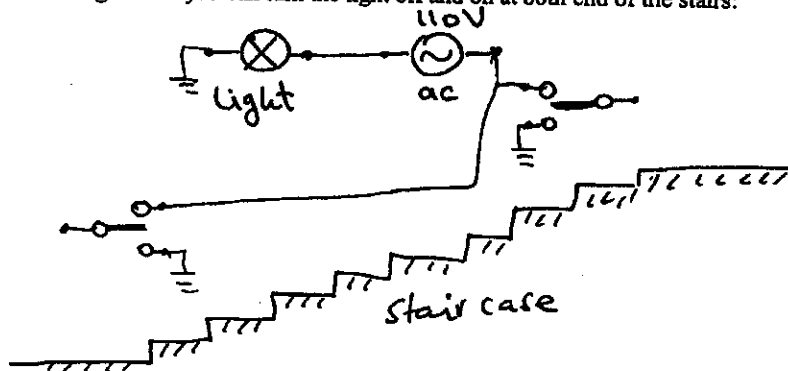
Problem #2:

Given are the light bulb, two double-throw switches and power source. Finish the wiring so that you can turn the light off and on at both end of the stairs:



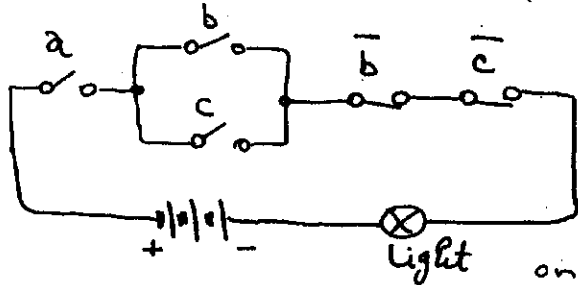Problem #3:

When is the light ON in the circuit shown? Note when $a=1$ (closed) $\bar{a}=0$ (open).



The light can't be on since if b is closed \bar{b} is open, & if c is closed \bar{c} is open, thus no current flows to the light

Your Name: _____

Problem #1:

Write decimal number 38 in:

(a.) binary: 101110

(b.) hexadecimal: 26

(c.) octal: 46


$$\begin{array}{r} 2 \overline{) 38} \quad 0 \\ \underline{20} \\ 18 \\ \underline{16} \\ 2 \\ \underline{2} \\ 0 \end{array}$$

$$\begin{array}{r} 16 \overline{) 38} \quad 6 \\ \underline{32} \\ 6 \end{array}$$

$$\begin{array}{r} 8 \overline{) 38} \quad 6 \\ \underline{48} \\ -4 \end{array}$$

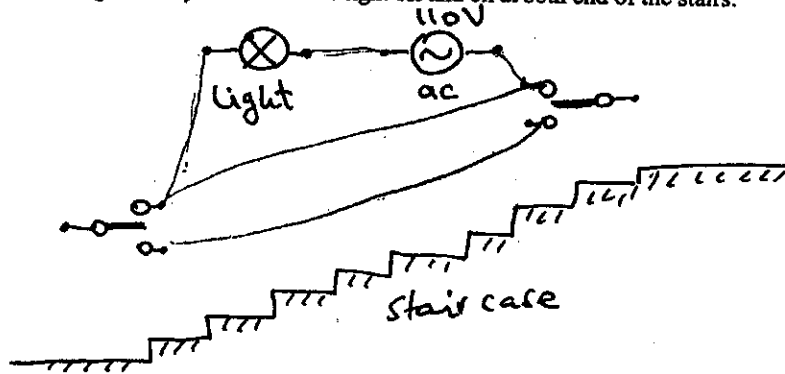
Problem #2:

Given are the light bulb, two double-throw switches and power source. Finish the wiring so that you can turn the light off and on at both end of the stairs:



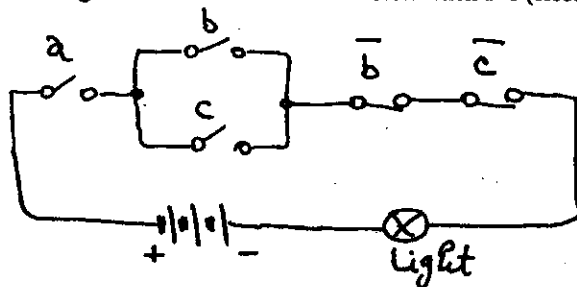Problem #3:

When is the light ON in the circuit shown? Note when $a=1$ (closed) $\bar{a}=0$ (open).



Light is ON:
when $a=1$ and c is closed
or when $a=1$, b is closed

Your Name: _____

Problem #1:

Write decimal number 38 in:

(a.) binary: 100110


(b.) hexadecimal: 26

(c.) octal: 46

$$\begin{aligned} \frac{38}{2} &= 19 \text{ r } 0 & \frac{19}{2} &= 9 \text{ r } 1 & \frac{9}{2} &= 4 \text{ r } 1 \\ \frac{4}{2} &= 2 \text{ r } 0 & \frac{2}{2} &= 1 \text{ r } 0 & \frac{1}{2} &= 0 \text{ r } 1 \\ \frac{38}{4} &= 6 \text{ r } 2 & \frac{6}{6} &= 1 \text{ r } 0 & \frac{1}{6} &= 0 \text{ r } 1 \\ \frac{38}{8} & & & & & \end{aligned}$$

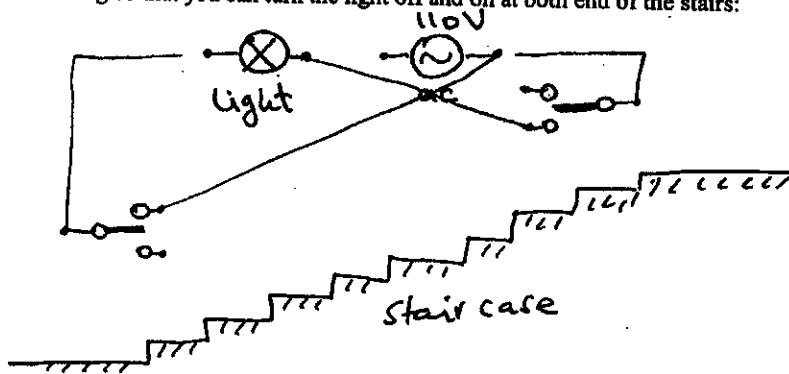
Problem #2:

Given are the light bulb, two double-throw switches and power source. Finish the wiring so that you can turn the light off and on at both end of the stairs:



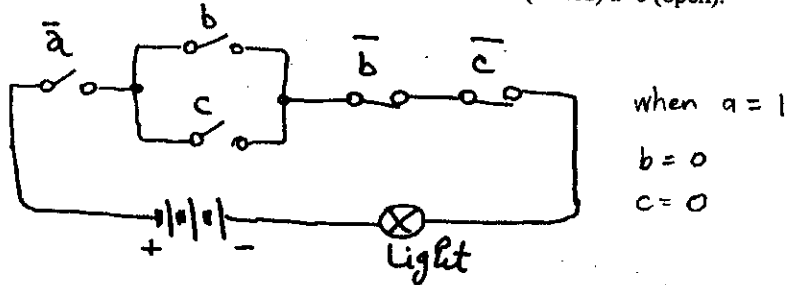Problem #3:

When is the light ON in the circuit shown? Note when $a=1$ (closed) $\bar{a}=0$ (open).



Your Name: _____

Problem #1:

Write decimal number 38 in:

(a.) binary: 100110


(b.) hexadecimal: 26

(c.) octal: 46

26
31 38

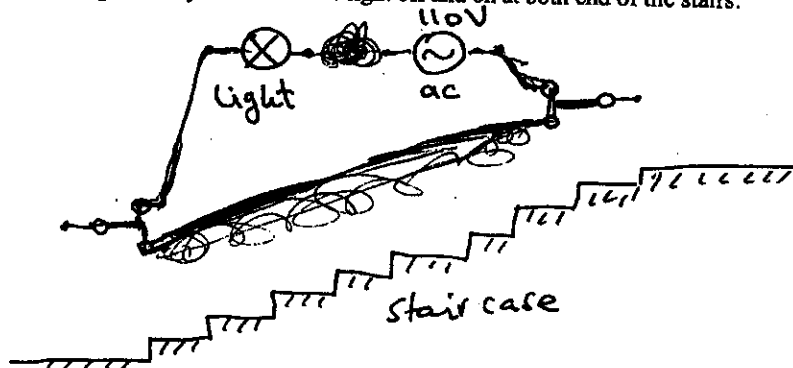
Problem #2:

Given are the light bulb, two double-throw switches and power source.
Finish the wiring so that you can turn the light off and on at both end of the stairs:



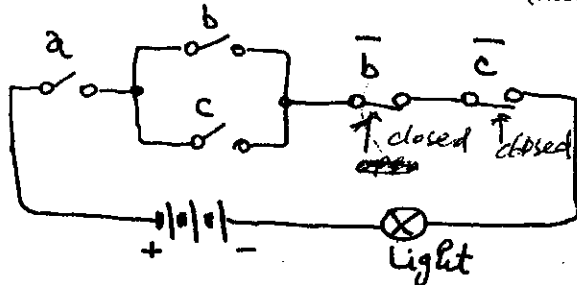Problem #3:

When is the light ON in the circuit shown? Note when $a=1$ (closed) $\bar{a}=0$ (open).



either b. or c can be open.

Your Name: _____

Problem #1:

Write decimal number 38 in:

2 (a.) binary:

100001

6 (b.) hexadecimal:


26

8 (c.) octal:

46

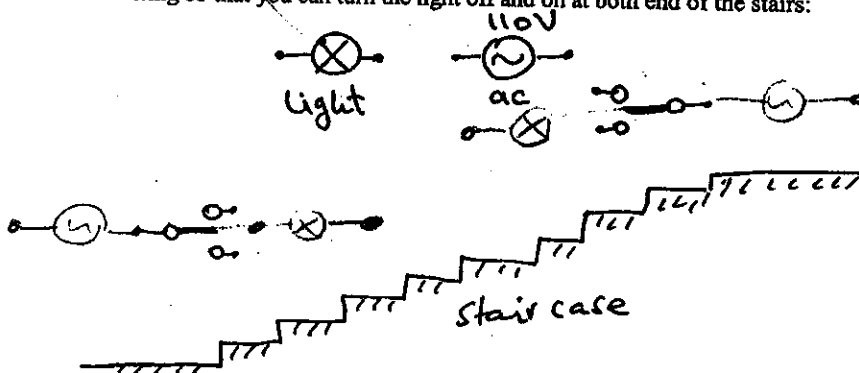
Problem #2:

Given are the light bulb, two double-throw switches and power source.
Finish the wiring so that you can turn the light off and on at both end of the stairs:



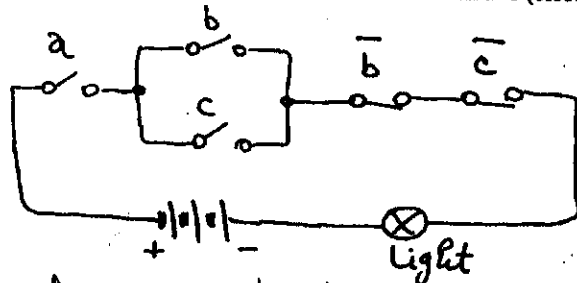Problem #3:

When is the light ON in the circuit shown? Note when $a=1$ (closed) $\bar{a}=0$ (open).



when $a=1, b=1, c=1$

Light bulb closed

Your Name: _____

Problem #1:

Write decimal number 38 in:


(a.) binary: ~~0000 0000 0000 0000~~ 10 10110

(b.) hexadecimal: 0000 0000 0000 0110

(c.) octal:

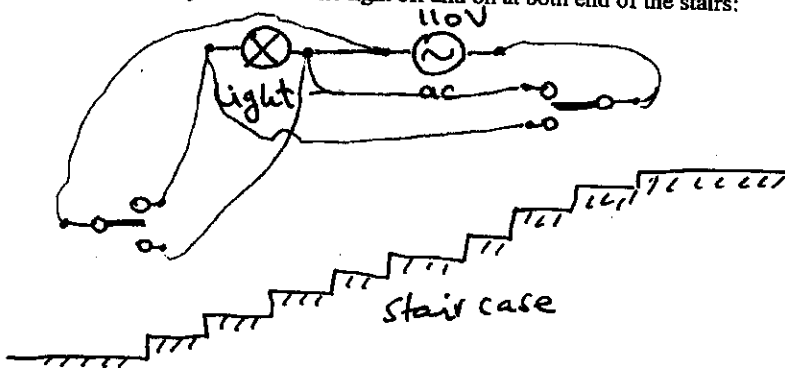
Problem #2:

Given are the light bulb, two double-throw switches and power source.
Finish the wiring so that you can turn the light off and on at both end of the stairs:



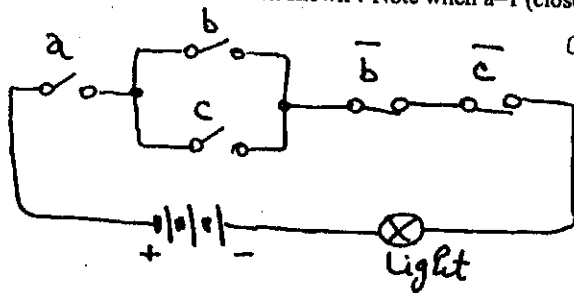Problem #3:

When is the light ON in the circuit shown? Note when $a=1$ (closed) $\bar{a}=0$ (open).



when all the switches are closed.

| | | |

Your Name: _____

Problem #1:

Write decimal number 38 in:

(a.) binary:

100110

 $1 \cdot 32 + 4 \cdot 1 + 1 \cdot 2 = 38$

(b.) hexadecimal:

26

 $2 \cdot 16 + 6 \cdot 1 = 38$


(c.) octal:

46

 $4 \cdot 8 + 6 \cdot 1 = 38$

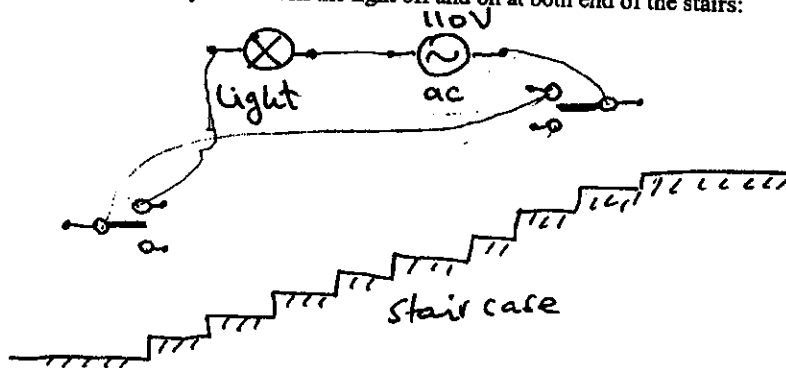
Problem #2:

Given are the light bulb, two double-throw switches and power source.
Finish the wiring so that you can turn the light off and on at both end of the stairs:



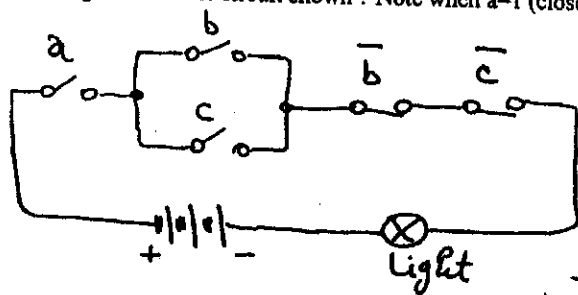Problem #3:

When is the light ON in the circuit shown? Note when $a=1$ (closed) $\bar{a}=0$ (open).



$A=1$
the light
won't be on
because by closing
b or c, \bar{b} or \bar{c}
opens the circuit

Your Name: _____

Problem #1:

Write decimal number 38 in:


(a.) binary: $38 = 2^5 + 2^2 + 2^1 \Rightarrow 100110$

(b.) hexadecimal: $0010\ 0110 \Rightarrow 26$

(c.) octal: $48^1 + 68^0 = 32 + 6 = 38$
 $\Rightarrow 0046$

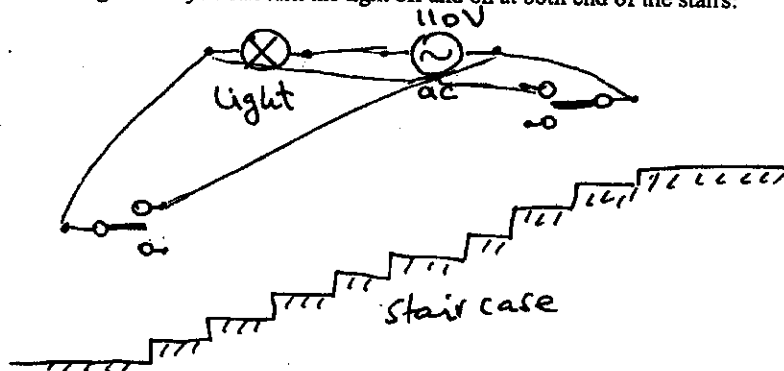
Problem #2:

Given are the light bulb, two double-throw switches and power source.
 Finish the wiring so that you can turn the light off and on at both end of the stairs:



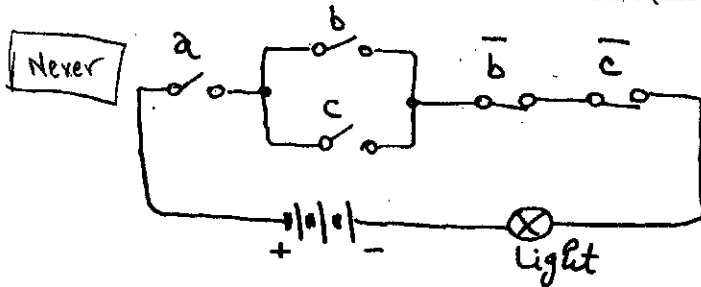Problem #3:

When is the light ON in the circuit shown? Note when $a=1$ (closed) $\bar{a}=0$ (open).



Your Name: _____

Problem #1:

Write decimal number 38 in:

(a.) binary:

$32 + 4 + 2$
100110

(b.) hexadecimal:


$16 \times 2 + 6$
26

(c.) octal:

$8 \times 4 + 6$
46

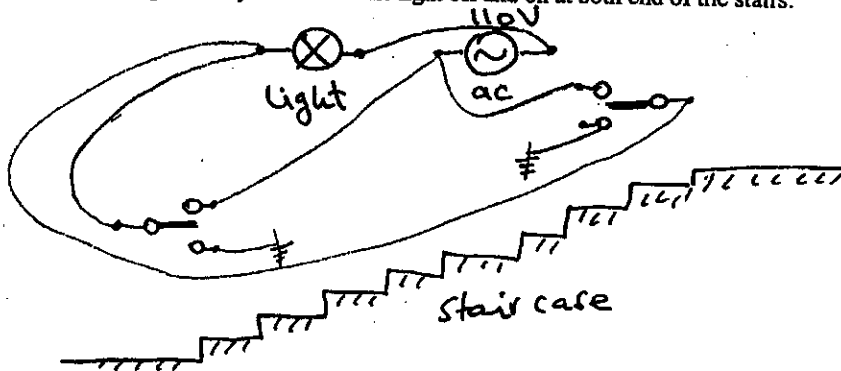
Problem #2:

Given are the light bulb, two double-throw switches and power source. Finish the wiring so that you can turn the light off and on at both end of the stairs:



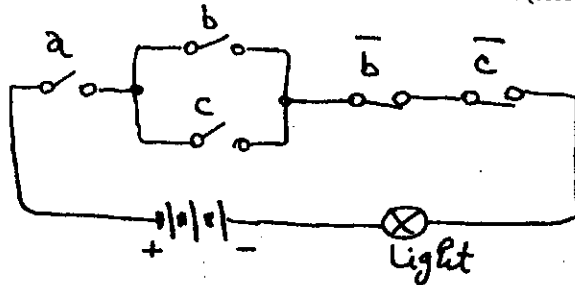Problem #3:

When is the light ON in the circuit shown? Note when $a=1$ (closed) $\bar{a}=0$ (open). Never



Your Name: _____

Problem #1:

$$38 \rightarrow 32 + 4 + 2$$

$$0010 \ 0110$$

$$16^3 \ 16^2 \ 16^1 \ 16^0$$

$$0 \ 0 \ 2 \ 6$$

Write decimal number 38 in:

(a.) binary: 0010 0110₍₂₎

(b.) hexadecimal: 0026₍₁₆₎

(c.) octal: 0046₍₈₎


$$8^3 \ 8^2 \ 8^1 \ 8^0$$

$$0 \ 0 \ 4 \ 6$$

38

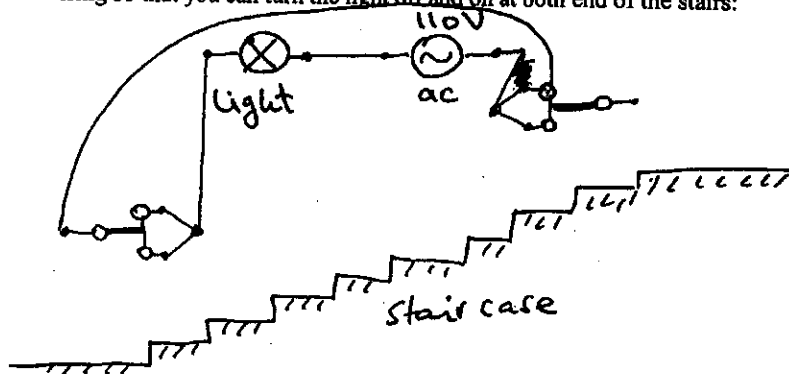
Problem #2:

Given are the light bulb, two double-throw switches and power source. Finish the wiring so that you can turn the light off and on at both end of the stairs:



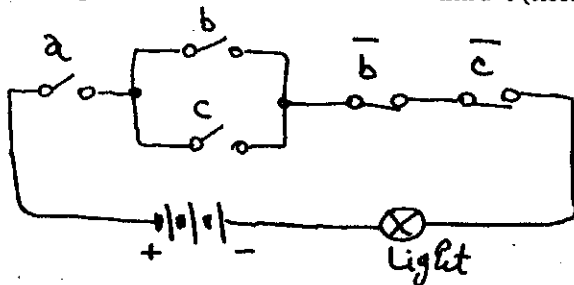Problem #3:

When is the light ON in the circuit shown? Note when $a=1$ (closed) $\bar{a}=0$ (open).



the light is on when $\bar{a} = 1$ or $\bar{c} = 1$

when $a=1$, $b=1$ then immediately $c=1$

Your Name: _____


Problem #1:

Write decimal number 38 in:

- (a.) binary: 38_2
 (b.) hexadecimal: 38_7
 (c.) octal: 38_8

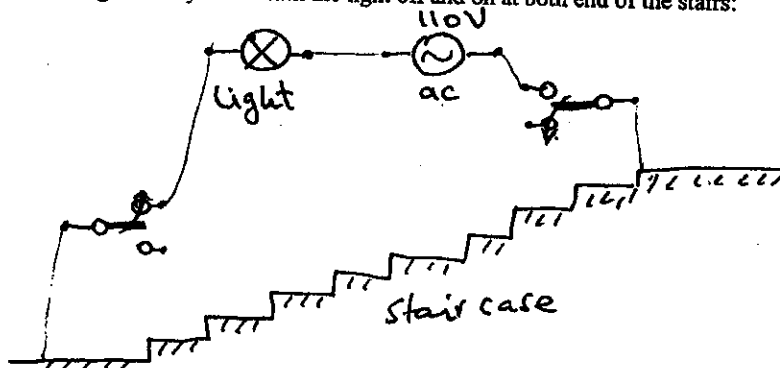
Problem #2:

Given are the light bulb, two double-throw switches and power source.
 Finish the wiring so that you can turn the light off and on at both end of the stairs:



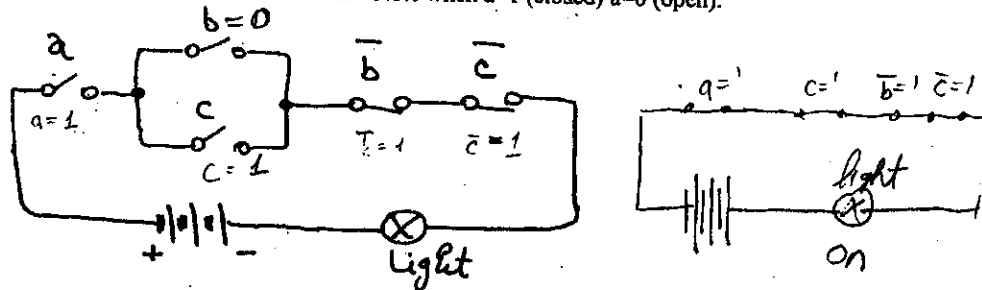Problem #3:

When is the light ON in the circuit shown? Note when $a=1$ (closed) $\bar{a}=0$ (open).



Your Name: Shreyas

Problem #1:


Write decimal number 38 in:

- (a.) binary: $38 = 32 + 4 + 2 =$ 100110
- (b.) hexadecimal: $32 + 6 =$ 26
- (c.) octal: $32 + 6 =$ 46

Problem #2:


Given are the light bulb, two double-throw switches and power source. Finish the wiring so that you can turn the light off and on at both end of the stairs:

0 on
1 off
1 on
0 off

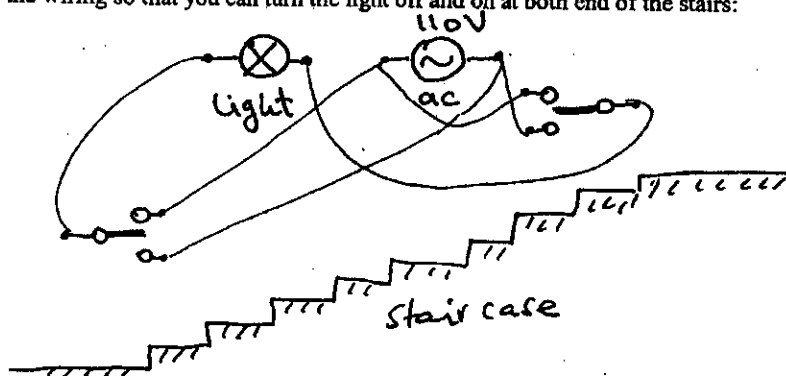

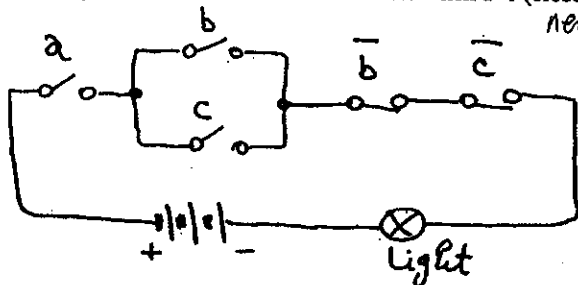Problem #3:

When is the light ON in the circuit shown? Note when $a=1$ (closed) $\bar{a}=0$ (open).



$\bar{b} = 1$ b or $c = 1$
 $\bar{c} = 1$
 $a = 1 \therefore$ impossible

It will Never goes on

~~$a=1$ $b=0$ $c=0$~~

Your Name: _____



Problem #1:

Write decimal number 38 in:

(a.) binary: 100110


(b.) hexadecimal: 26

(c.) octal: 46

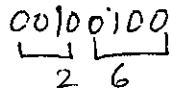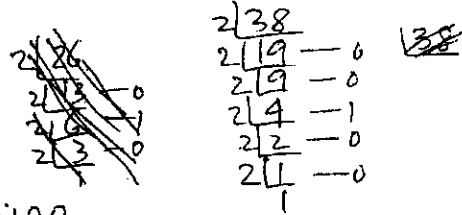

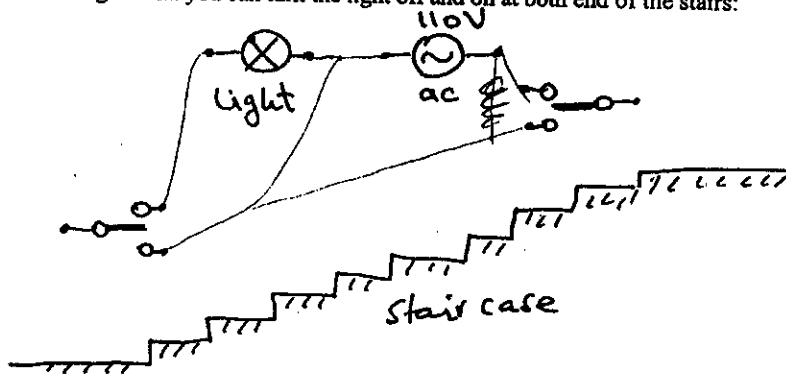
Problem #2:

Given are the light bulb, two double-throw switches and power source. Finish the wiring so that you can turn the light off and on at both end of the stairs:



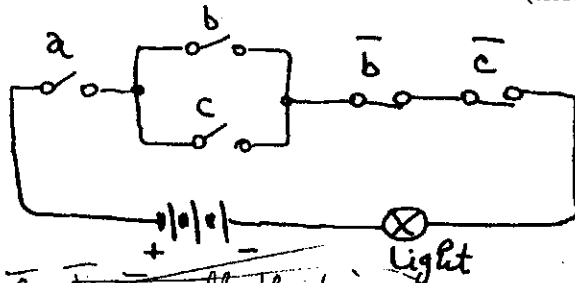
Problem #3:

When is the light ON in the circuit shown? Note when $a=1$ (closed) $\bar{a}=0$ (open).



~~a, b, c all the time.~~

The light is ON when

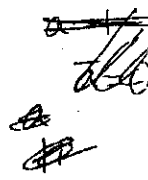

When $a=1$, c is closed,
 $a=1$, b is closed

Your Name: _____

Problem #1:

Write decimal number 38 in:


(a.) binary: 100110

(b.) hexadecimal: 0x16

(c.) octal: 100006

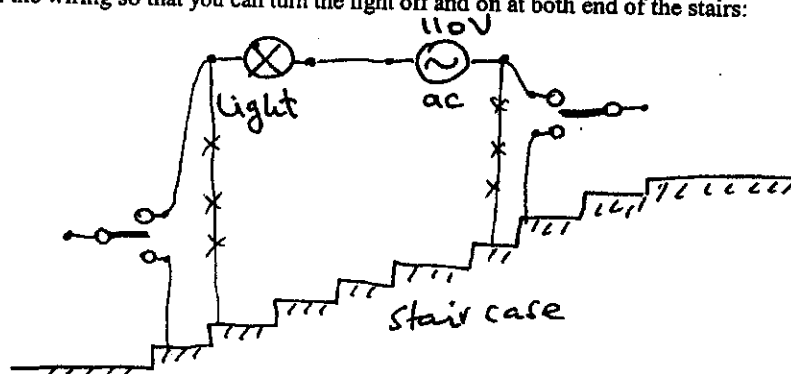
Problem #2:

Given are the light bulb, two double-throw switches and power source.
Finish the wiring so that you can turn the light off and on at both end of the stairs:



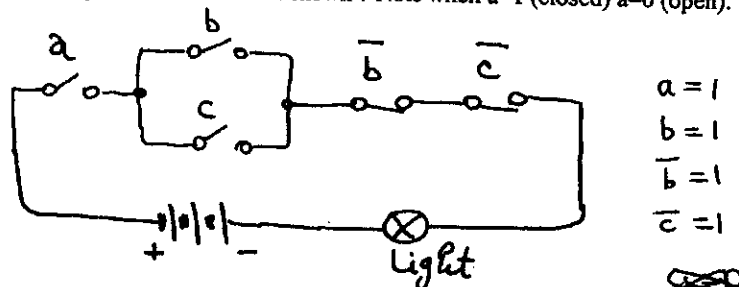Problem #3:

When is the light ON in the circuit shown? Note when $a=1$ (closed) $\bar{a}=0$ (open).



Your Name: Samir

Problem #1:

Write decimal number 38 in:

32 16 8 4 2 1
 2^5 2^4 2^3 2^2 2^1 2^0


(a.) binary: 0 0 1 0 0 1 1 0

(b.) hexadecimal: 0026

(c.) octal:

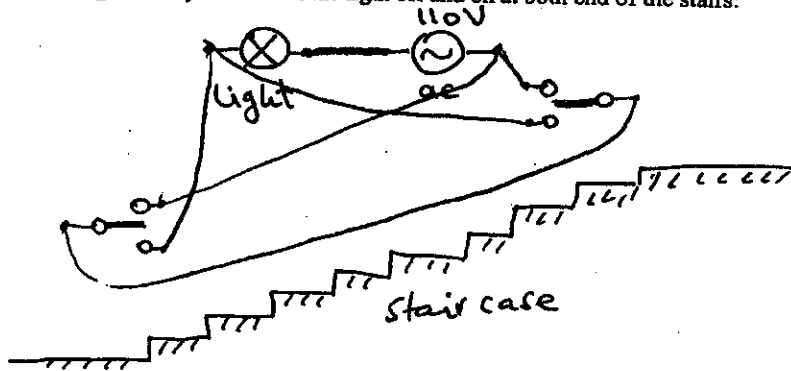
Problem #2:

Given are the light bulb, two double-throw switches and power source.
 Finish the wiring so that you can turn the light off and on at both end of the stairs:



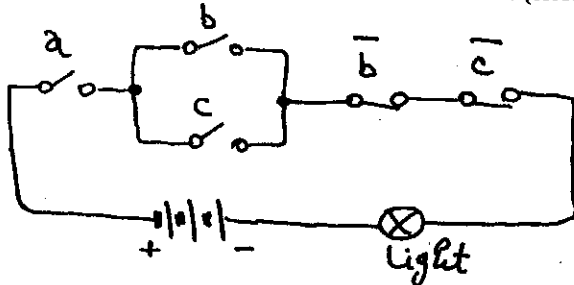Problem #3:

When is the light ON in the circuit shown? Note when $a=1$ (closed) $\bar{a}=0$ (open).



Never,
 the circuit is
 never completed

Your Name: _____

Problem #1:

$$\frac{38}{2} = \frac{19}{2} = \frac{9}{2} = \frac{4}{2} = 2$$

Write decimal number 38 in:

(a.) binary: 100110


001100110

(b.) hexadecimal: 26

(c.) octal: 46

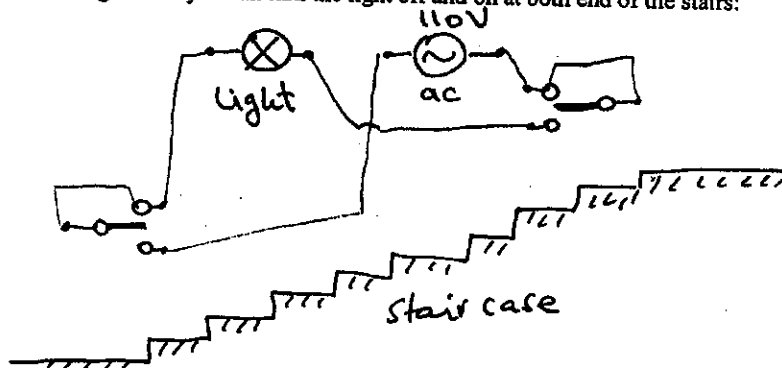
Problem #2:

Given are the light bulb, two double-throw switches and power source.
Finish the wiring so that you can turn the light off and on at both end of the stairs:



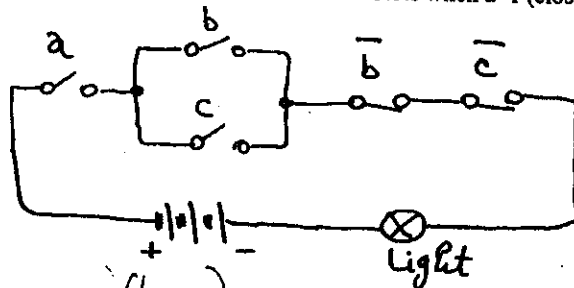Problem #3:

When is the light ON in the circuit shown? Note when $a=1$ (closed) $\bar{a}=0$ (open).



$$a \cdot (b + c)$$

Your Name: _____

Problem #1:

Write decimal number 38 in:


(a.) binary: 100110

(b.) hexadecimal: $0x0026$

(c.) octal: 46

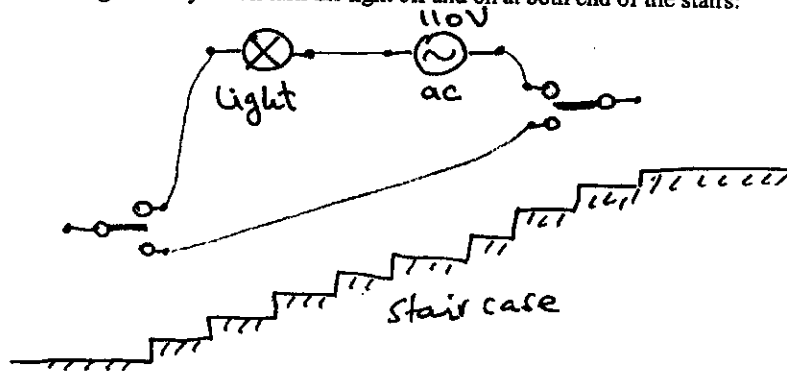
Problem #2:

Given are the light bulb, two double-throw switches and power source.
Finish the wiring so that you can turn the light off and on at both end of the stairs:



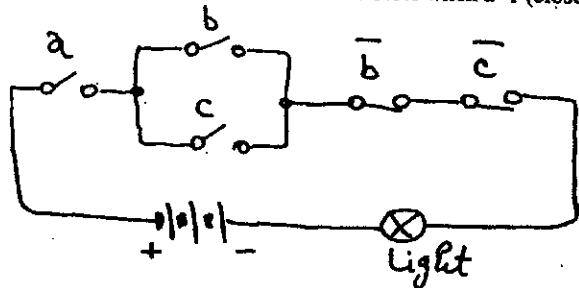Problem #3:

When is the light ON in the circuit shown? Note when $a=1$ (closed) $\bar{a}=0$ (open).



It never turns on

Your Name: _____

Problem #1:

Write decimal number 38 in:


(a.) binary: 100110

(b.) hexadecimal:

(c.) octal:

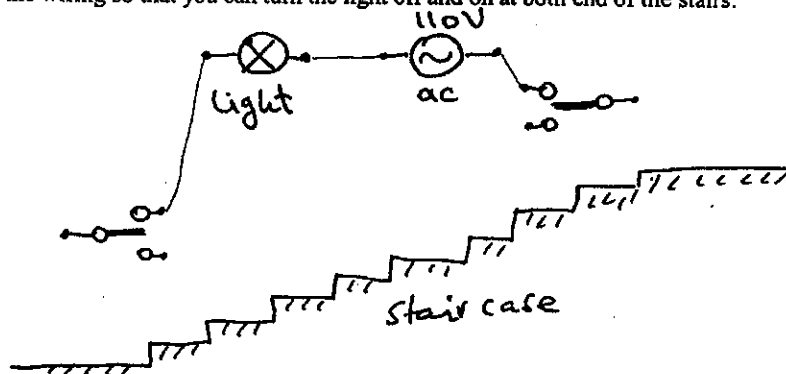
Problem #2:

Given are the light bulb, two double-throw switches and power source.
Finish the wiring so that you can turn the light off and on at both end of the stairs:



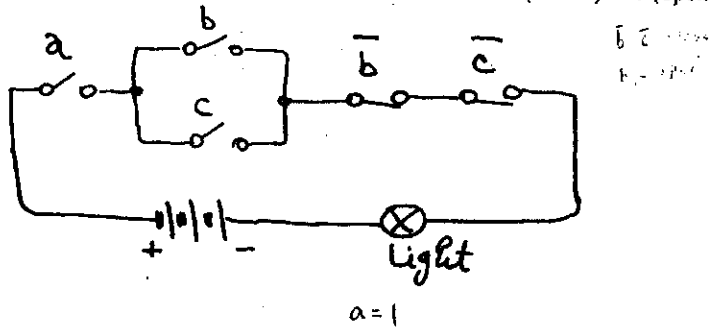Problem #3:

When is the light ON in the circuit shown? Note when $a=1$ (closed) $\bar{a}=0$ (open).



Your Name: _____

Problem #1:

Write decimal number 38 in:

2 (a.) binary: 100110

16 (b.) hexadecimal: 26

8 (c.) octal: 46


$$\begin{array}{r} 2 \overline{) 38} \\ \underline{19} \\ 2 \\ \underline{4} \\ 2 \\ \underline{2} \\ 2 \\ \underline{0} \end{array}$$

$$\begin{array}{r} 16 \overline{) 38} \\ \underline{32} \\ 6 \\ \underline{0} \end{array}$$

$$\begin{array}{r} 8 \overline{) 38} \\ \underline{32} \\ 6 \\ \underline{0} \end{array}$$

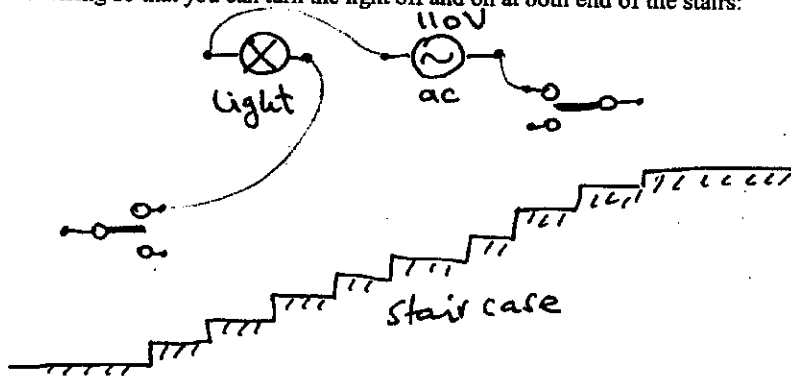
Problem #2:

Given are the light bulb, two double-throw switches and power source. Finish the wiring so that you can turn the light off and on at both end of the stairs:



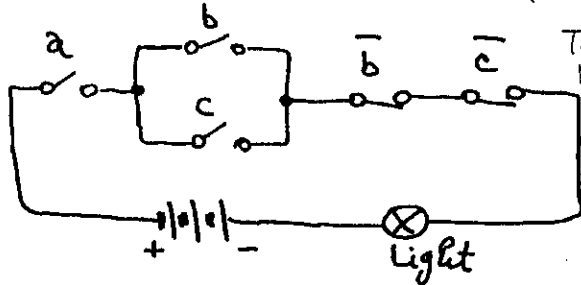Problem #3:

When is the light ON in the circuit shown? Note when $a=1$ (closed) $\bar{a}=0$ (open).



The light will never on because when b is closed, \bar{b} will open so about no current will go thru and so does c

Your Name: _____

Problem #1:

Write decimal number 38 in:


(a.) binary: 100110

(b.) hexadecimal: 26

(c.) octal: 46

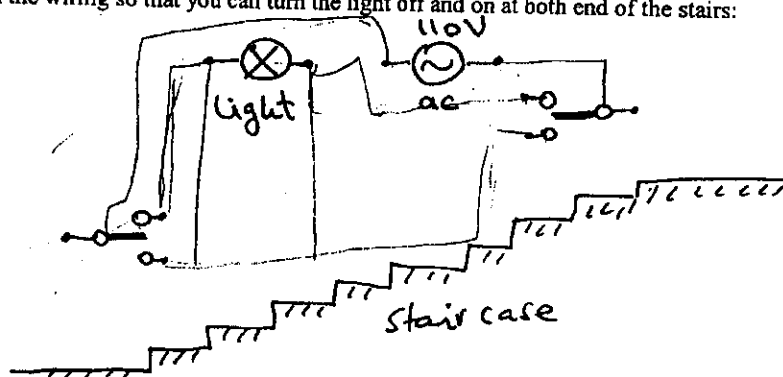
Problem #2:

Given are the light bulb, two double-throw switches and power source.
Finish the wiring so that you can turn the light off and on at both end of the stairs:



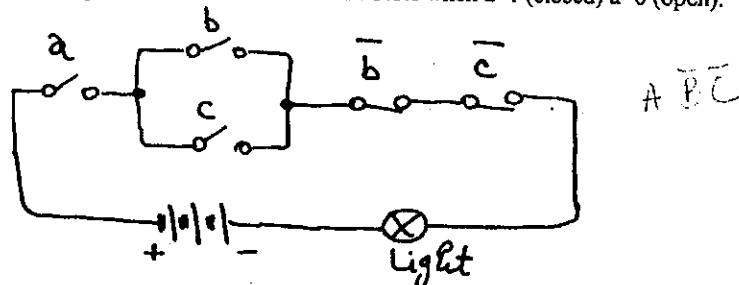Problem #3:

When is the light ON in the circuit shown? Note when $a=1$ (closed) $\bar{a}=0$ (open).



Your Name: _____

Problem #1:

Write decimal number 38 in:


(a.) binary: 100110_2

(b.) hexadecimal: $A5_{16}$

(c.) octal: 45_8

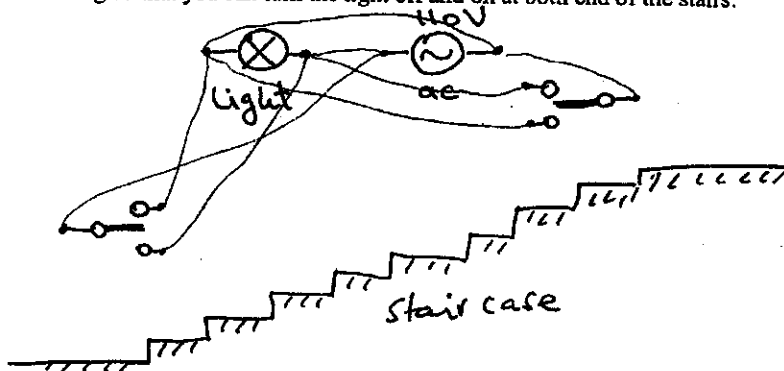
Problem #2:

Given are the light bulb, two double-throw switches and power source.
Finish the wiring so that you can turn the light off and on at both end of the stairs:



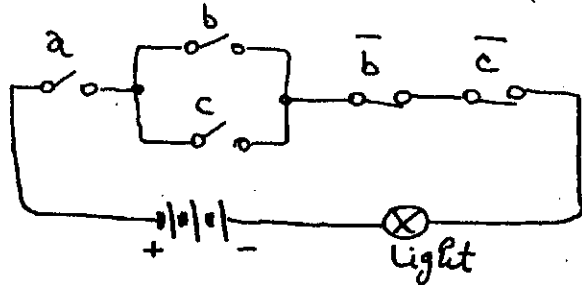Problem #3:

When is the light ON in the circuit shown? Note when $a=1$ (closed) $\bar{a}=0$ (open).



$a=1$

$a=1$ and $b=1$

$a=1$ and $c=1$

Your Name: _____

Problem #1:

Write decimal number 38 in:


(a.) binary: 10110

(b.) hexadecimal: 26

(c.) octal: 46

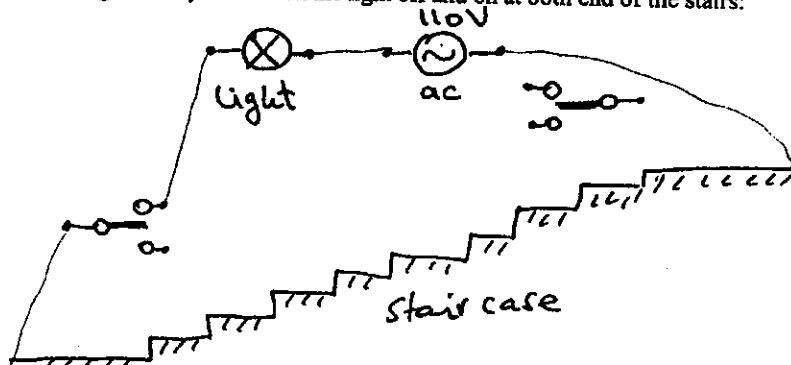
Problem #2:

Given are the light bulb, two double-throw switches and power source.
Finish the wiring so that you can turn the light off and on at both end of the stairs:



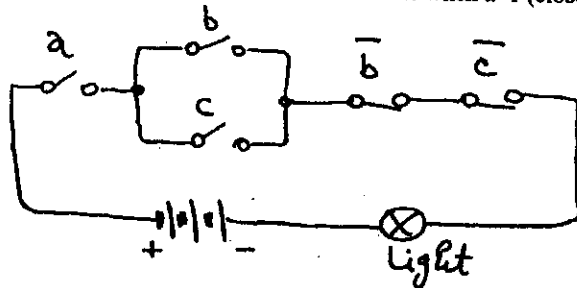Problem #3:

When is the light ON in the circuit shown? Note when $a=1$ (closed) $\bar{a}=0$ (open).



~~never~~
never because
 $b \rightarrow \bar{b}$
 $c \rightarrow \bar{c}$


Your Name: Amir Amir

$2 \times 2 \times 2 \times 2$
 8×16
 8×32
 8
 $+16$
 24
 $2 \times 2 \times 2 \times 2 \times 2$
 16×2
 32
 100110
 42

Problem #1:

Write decimal number 38 in:

(a.) binary:

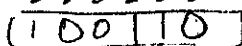


(b.) hexadecimal: 26

(c.) octal: 48

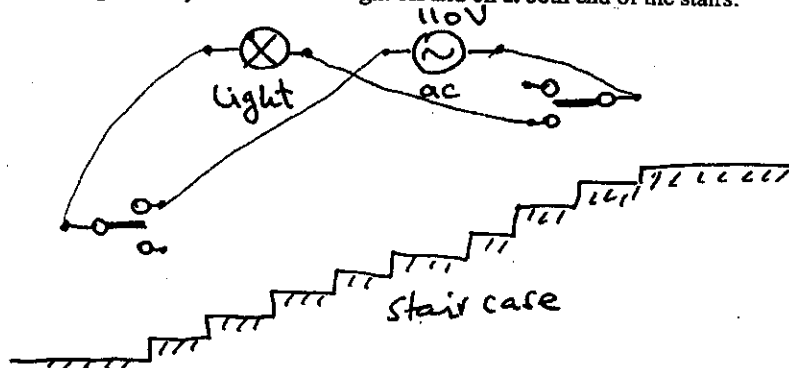
Problem #2:

Given are the light bulb, two double-throw switches and power source. Finish the wiring so that you can turn the light off and on at both end of the stairs:



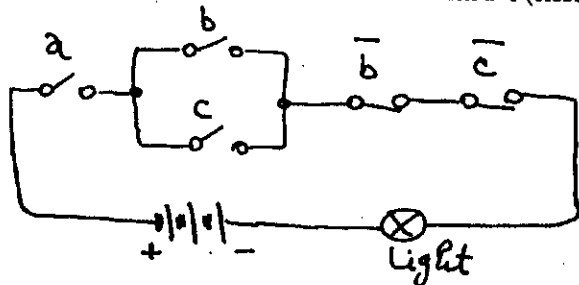Problem #3:

When is the light ON in the circuit shown? Note when $a=1$ (closed) $\bar{a}=0$ (open).



a when a is open the light is off.
 when a is closed and both b and c are closed then the light is on.

Your Name: _____

Problem #1:

Write decimal number 38 in:

(a.) binary: $2^4 \ 2^3 \ 2^2 \ 2^1 \ 2^0$
1 0 0 1 1 0


(b.) hexadecimal: 26

(c.) octal: 46

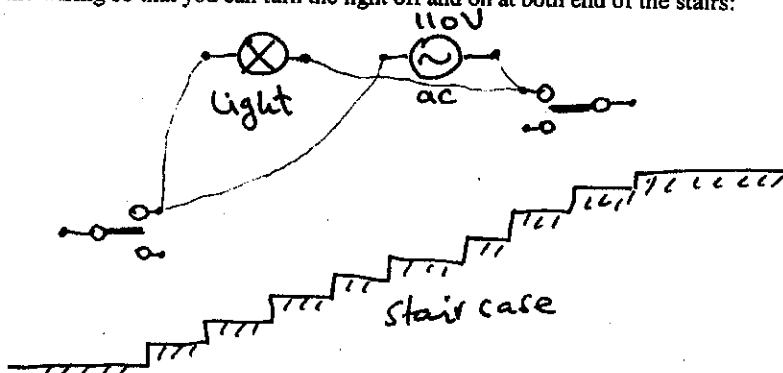Problem #2:


Given are the light bulb, two double-throw switches and power source.

Finish the wiring so that you can turn the light off and on at both end of the stairs:



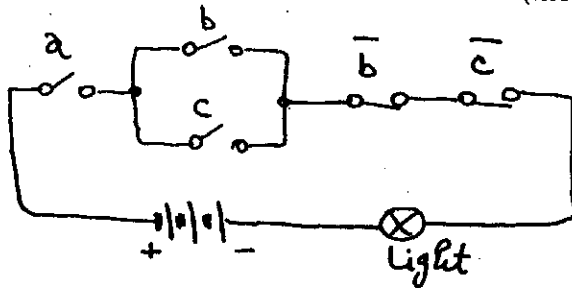Problem #3:

When is the light ON in the circuit shown? Note when $a=1$ (closed) $\bar{a}=0$ (open).



b open
and
c closed

or
c open
and
b closed

Your Name: _____

Problem #1:

Write decimal number 38 in:


(a.) binary: $0,38 \times 10^2$

(b.) hexadecimal:

(c.) octal:

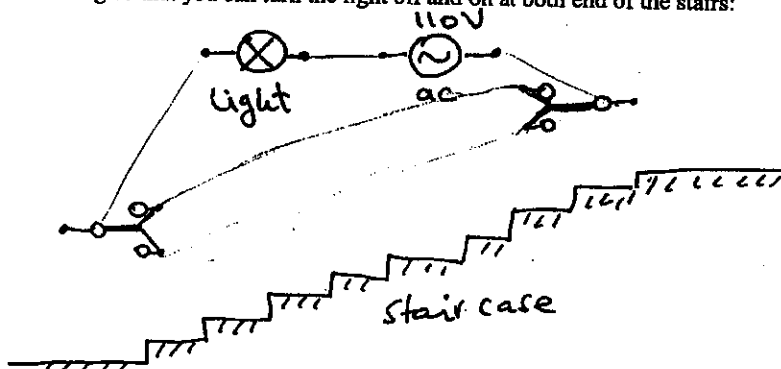
Problem #2:

Given are the light bulb, two double-throw switches and power source.
Finish the wiring so that you can turn the light off and on at both end of the stairs:



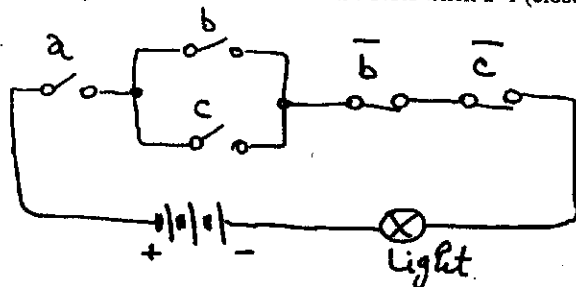Problem #3:

When is the light ON in the circuit shown? Note when $a=1$ (closed) $\bar{a}=0$ (open).



The light is on
either $a=1$ or $\bar{a}=0$