
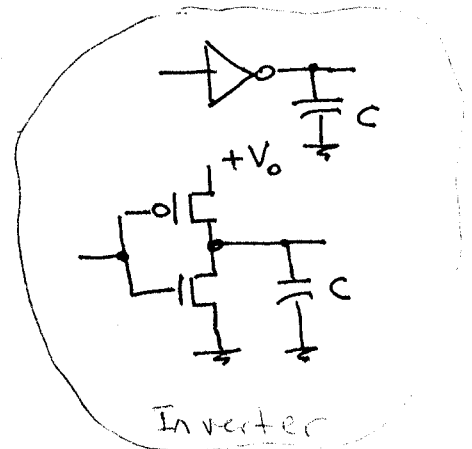


Your Name: _____

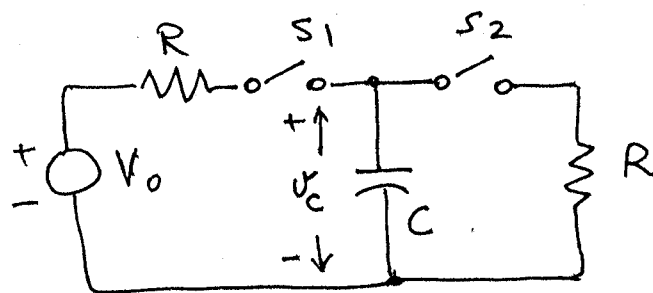Problem #1: Digital CMOS inverter can be approximated as a circuit given in the figure.

- (a.) find the expression for the voltage V_c (as a function of time t) when switch S_1 is ON and S_2 is off. Assume that the capacitor C was completely discharged before S_1 was turned ON. *Draw a graph of $V_c(t)$*
- (b.) find the expression for the voltage V_c (as a function of time t) when (after sufficient time has elapsed to charge the capacitor C fully) the switch S_1 is turned off and switch S_2 is turned on. *Draw a graph: $V_c(t)$*

Note: this is the first grade college physics (Sears & Zemansky) problem (for some of you perhaps a high-school problem). (12th grade)



Problems: