
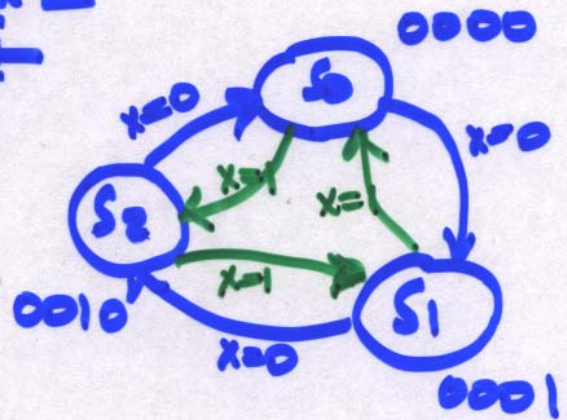
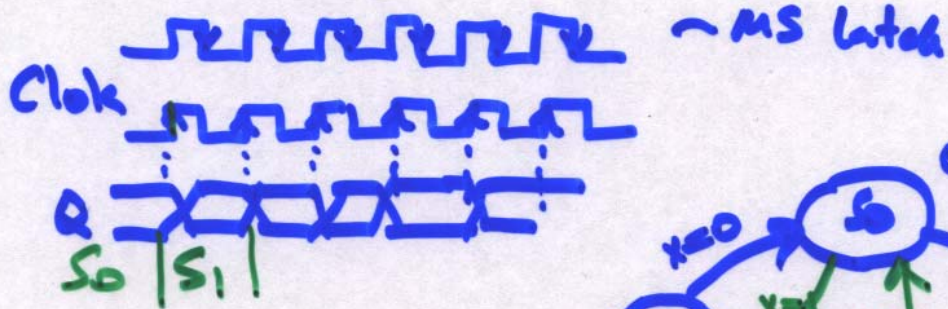



FSM

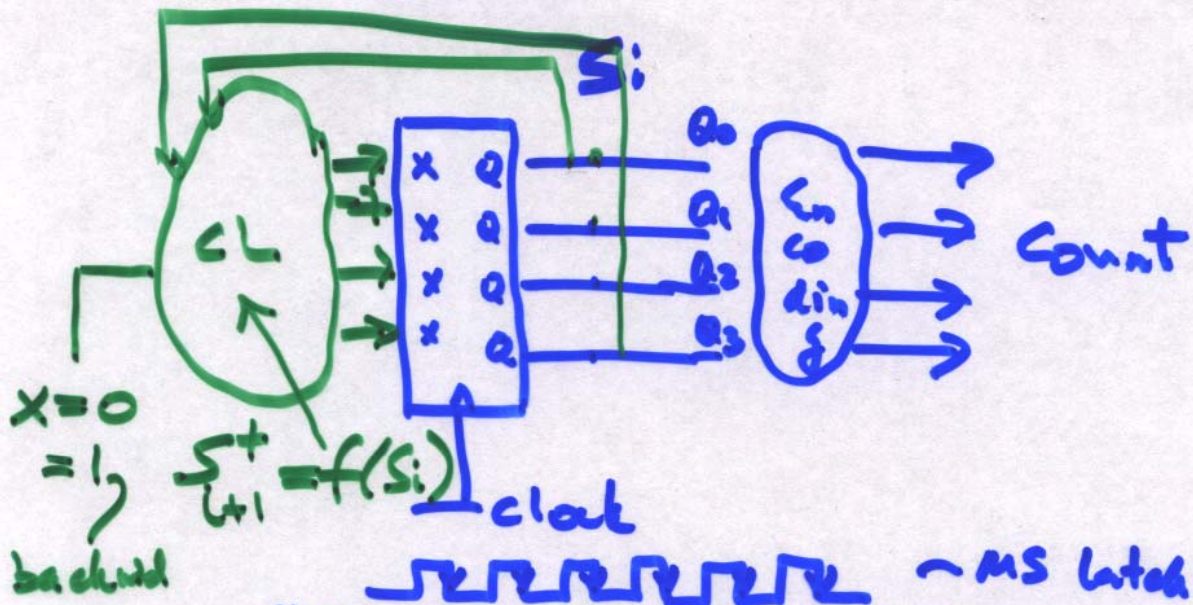

$$S_{i+1} = f(S_i, x)$$

x	S_i	S_{i+1}	S_i	R_i	S_0	S_1	S_2	S_3	$R_i = \psi(x, S_i)$
0	0	0	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	1
0	1	0	0	0	0	0	0	0	0
0	1	0	1	0	0	0	0	0	0
1	0	0	0	0	0	0	0	0	0
1	0	1	0	1	0	0	0	0	1
1	1	0	0	0	0	0	0	0	0
1	1	0	1	0	0	0	0	0	0

FSM

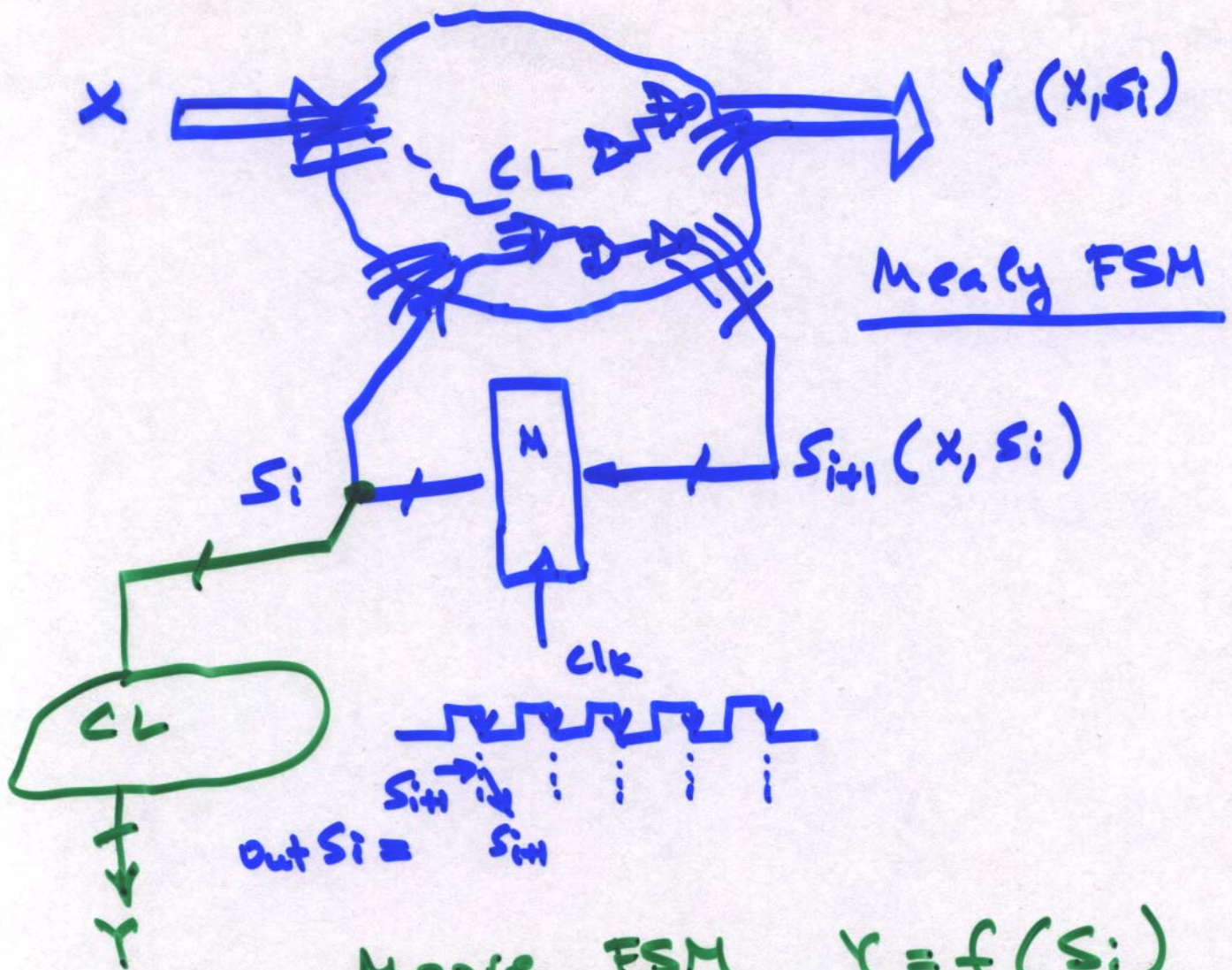


Mealy FSM


Moore FSM $Y = f(S_i)$

FSM


Mealy:

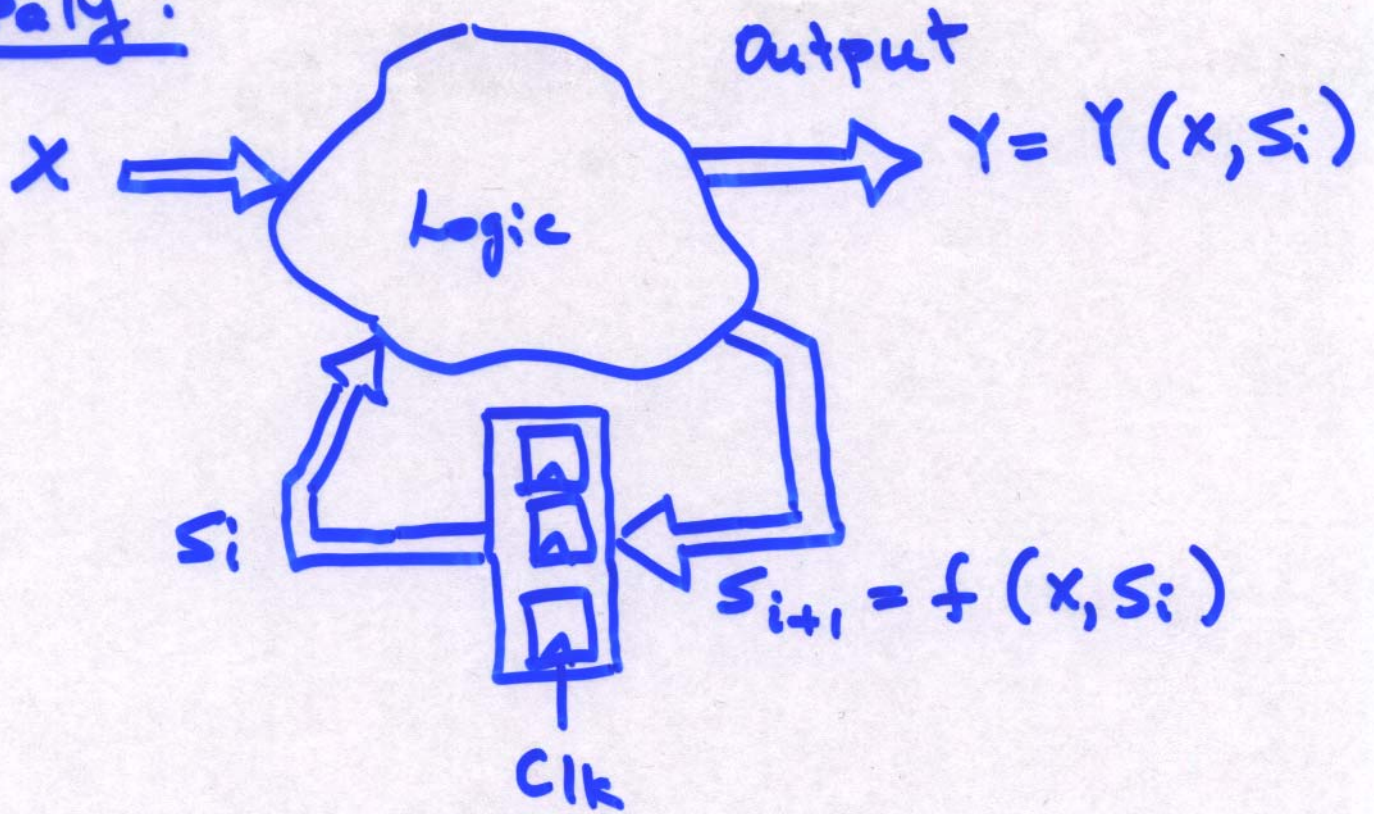


Moore FSM:

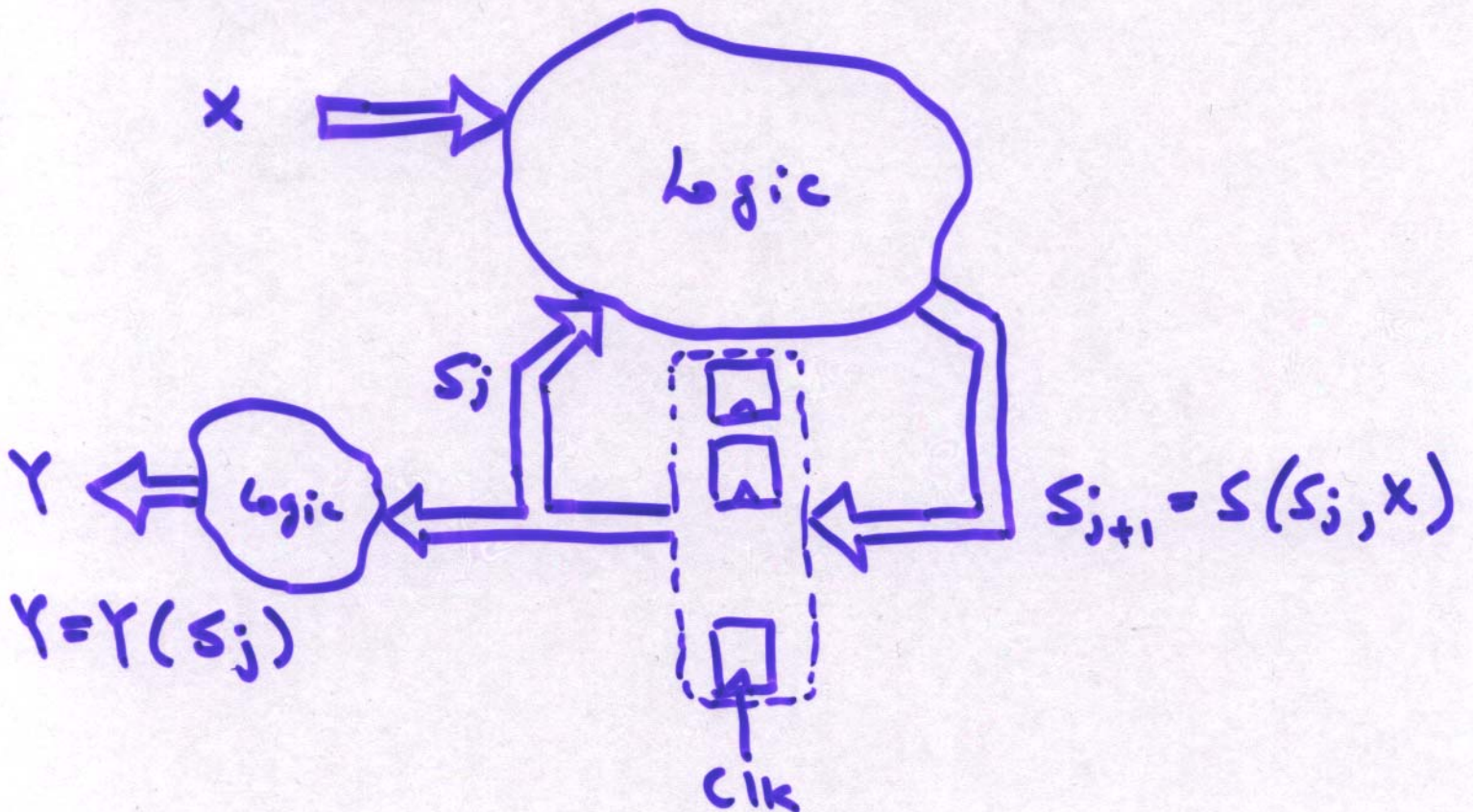


Mealy FSM:



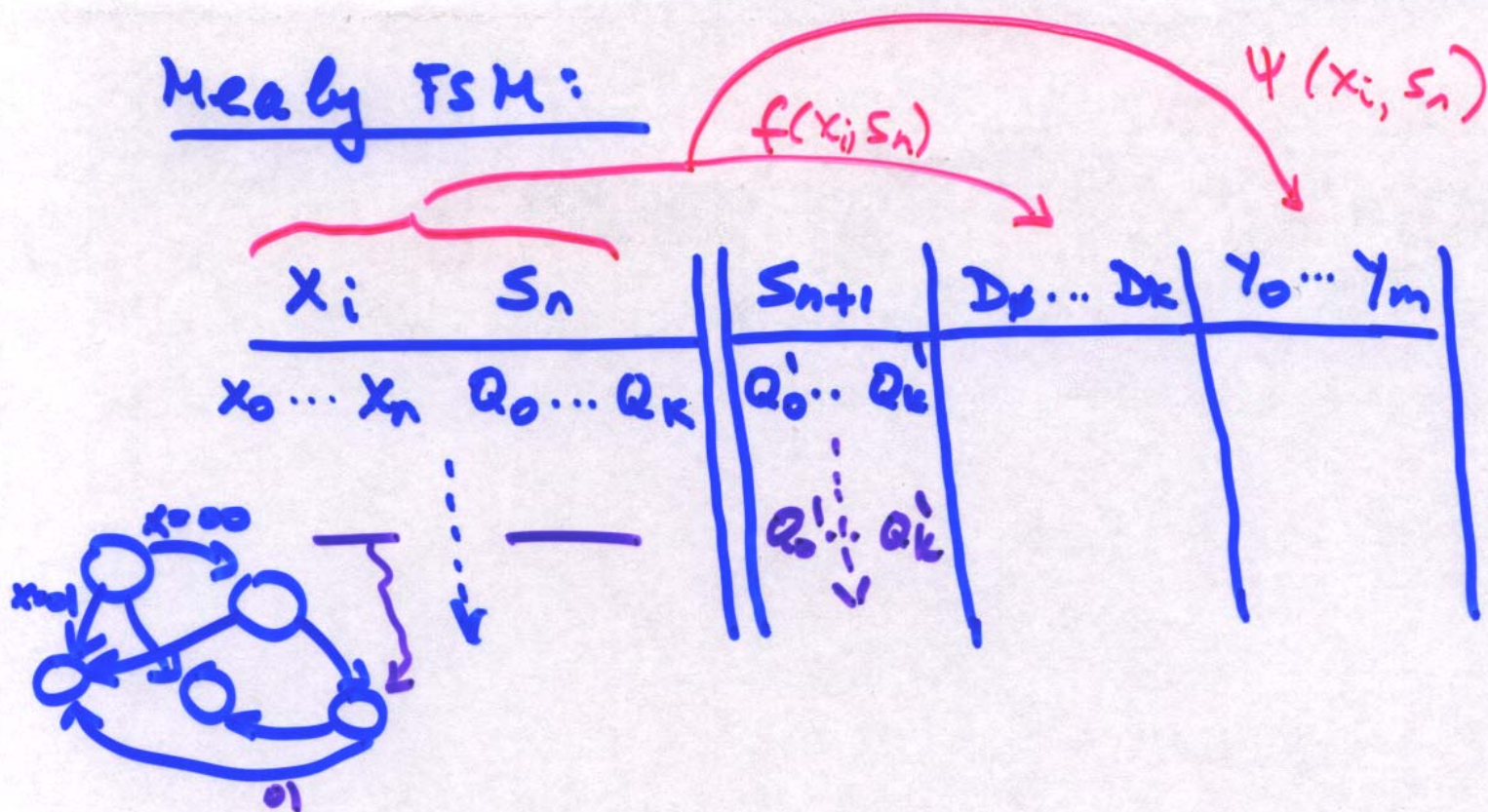


Moore FSM:

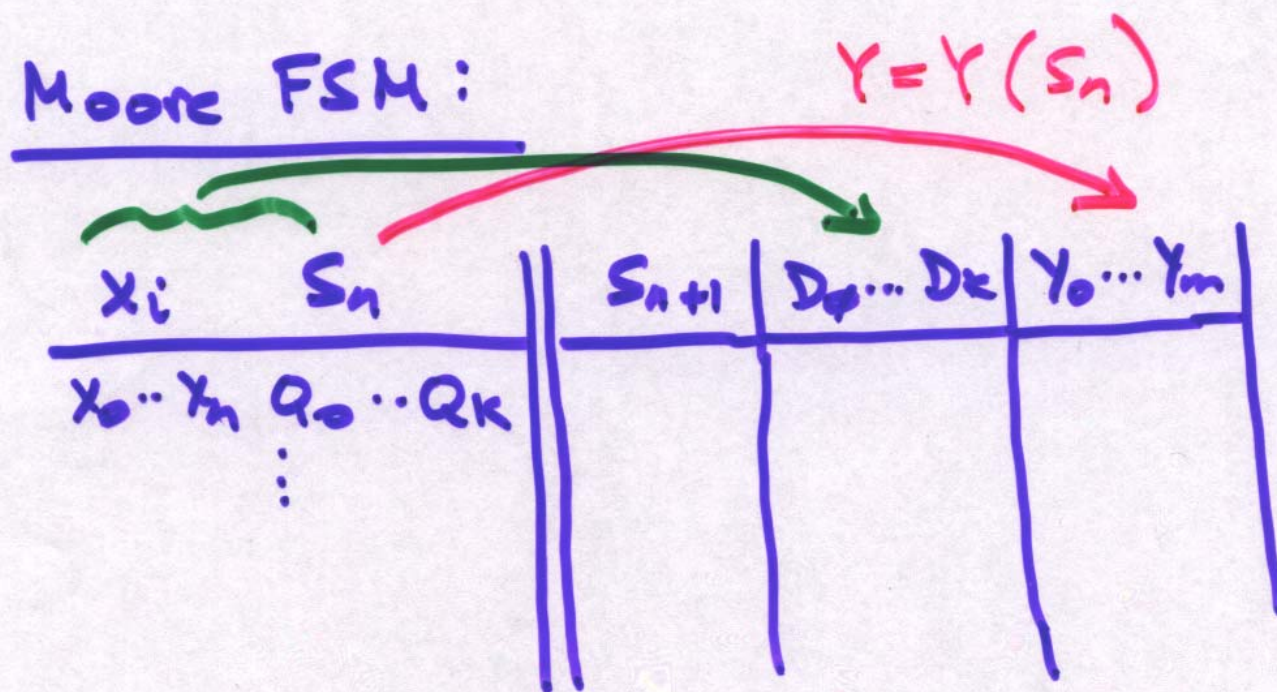

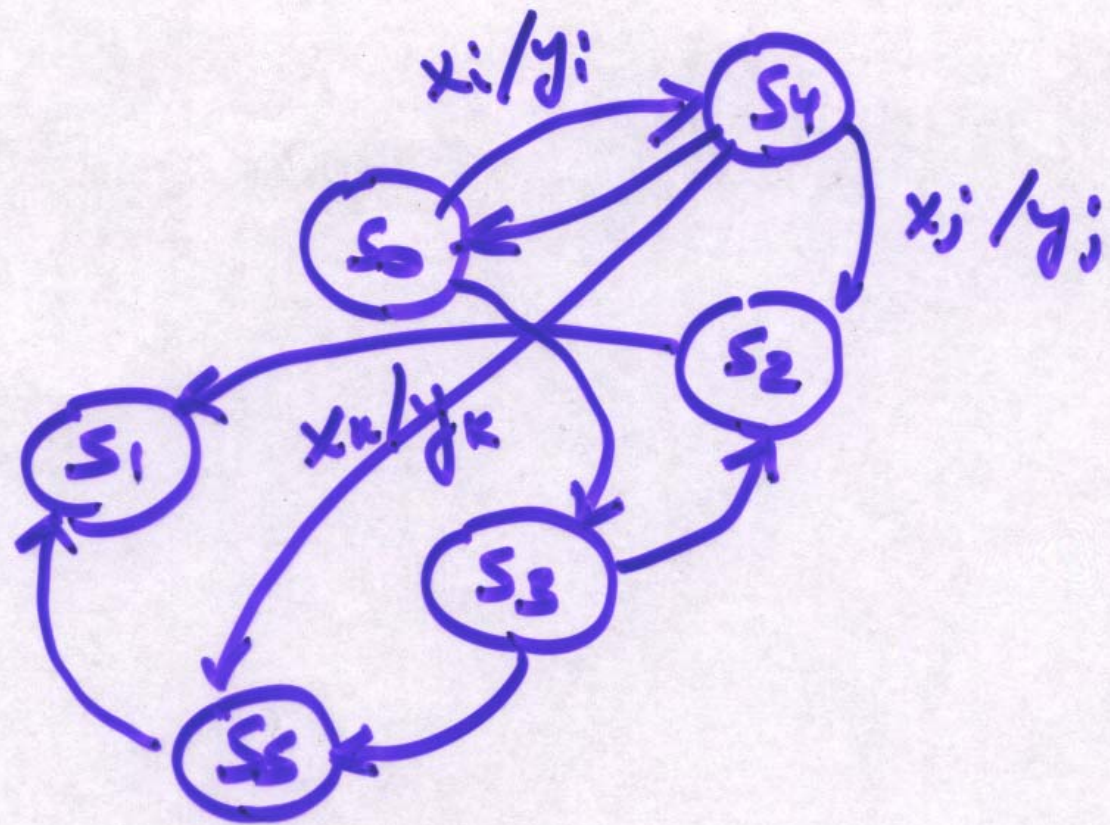


Up / Down Counter

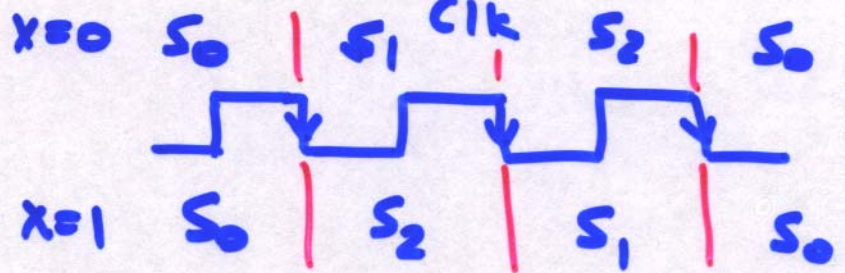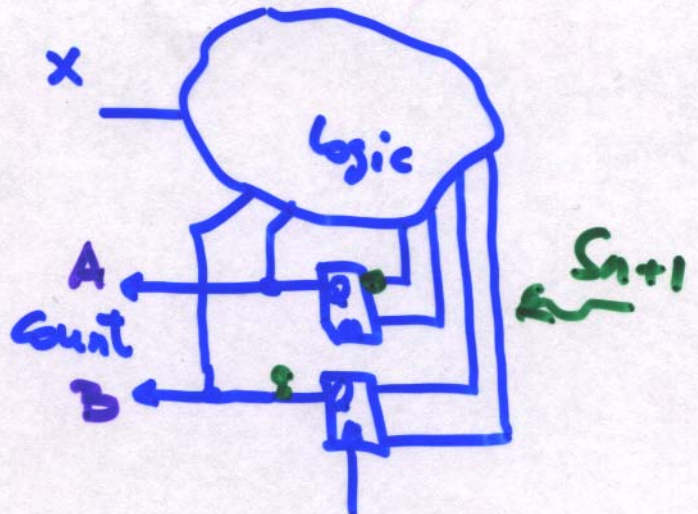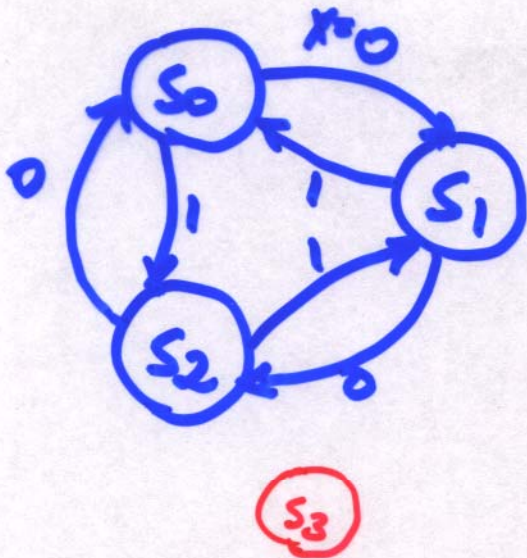

X	S_n		S_{n+1}		S_A	R_A	S_B	R_B
	Q_A	Q_B	Q_A	Q_B				
0	0	0	0	1	0	-	1	0
0	0	1	1	0	1	0	0	1
0	1	0	0	1	0	1	0	-
0	1	1	1	0	1	0	0	-
1	0	0	0	0	0	0	1	0
1	0	0	1	1	0	1	0	1
1	0	1	0	0	0	0	1	0
1	0	1	1	1	0	1	0	1




↑
"0" bar

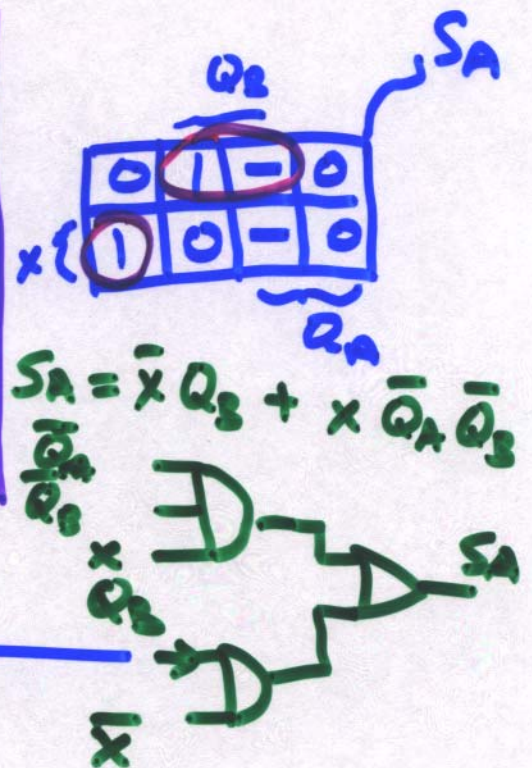

FSM

x/y

$x_1/y_1 \sim 110111$

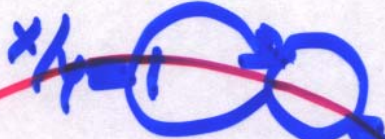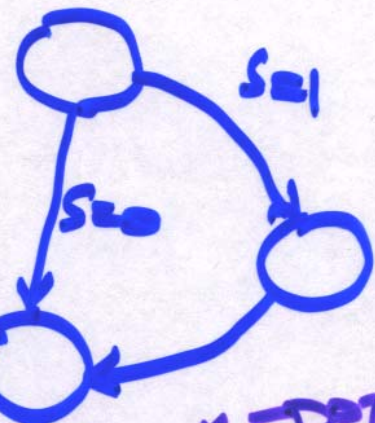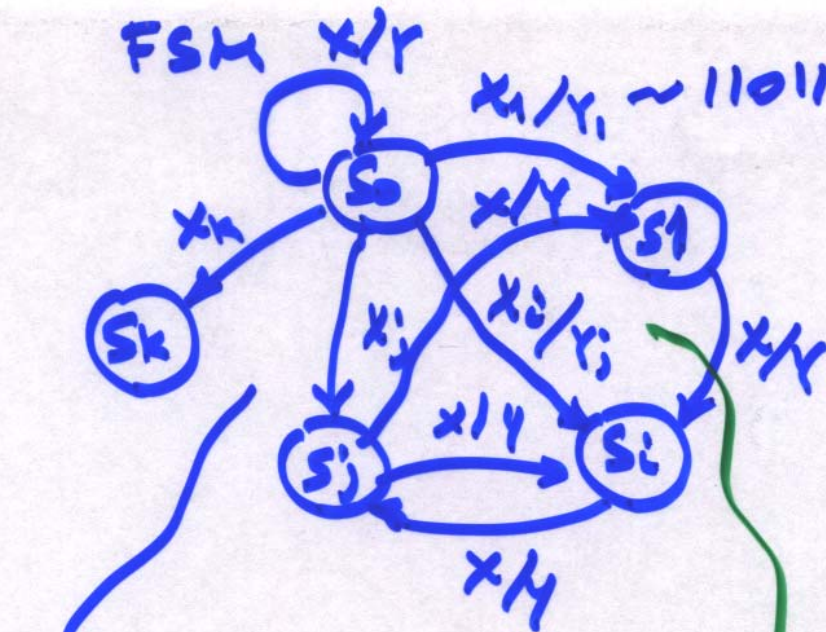

$$S_{i+1} = f(x, S_i)$$

x	S_i	S_{i+1}	SR	SR	SR	Y
000	000	010	0	1	0	010
000	001	010	0	1	0	010
...	010	...	...	...	...	...
001	000	011	x	x	x	111
...	...	...	...	...	...	...
111	111	...	...	...	...	...

$x = 110111$
 $S_1 = \dots$
 $S_2 = \dots$

$S_i = \dots$

$R_2 = \dots$

$\log_2 N$

$N = \# \text{ of states}$

$\{D, SR, JK, T\}$

$$S_{i+1} = f(x, S_i)$$

$$R_i = f(x, S_i)$$

$$Y = f(x, S_i)$$




Reduction of State Tables (15.x)

If input $X = 0101$ or 1001 , $Z = 1$
 Network resets every fourth input

X	S_n	S_{n+1}		Z	
		$X=0$	$X=1$	$X=0$	$X=1$
RESET	A	B	C	0	0
0	B	D	E	0	0
1	C	FE	DG	0	0
00	D	H	H	0	0
01	E	J	H	0	0
10	F	J	H	0	0
11	G	N	H	0	0
000	H	A	A	0	0
001	I	A	A	0	0
010	J	A	A	0	1
011	K	A	A	0	0
100	L	A	A	0	1
101	M	A	A	0	0
110	N	A	A	0	0
111	P	A	A	0	0


Elimination of Redundant States

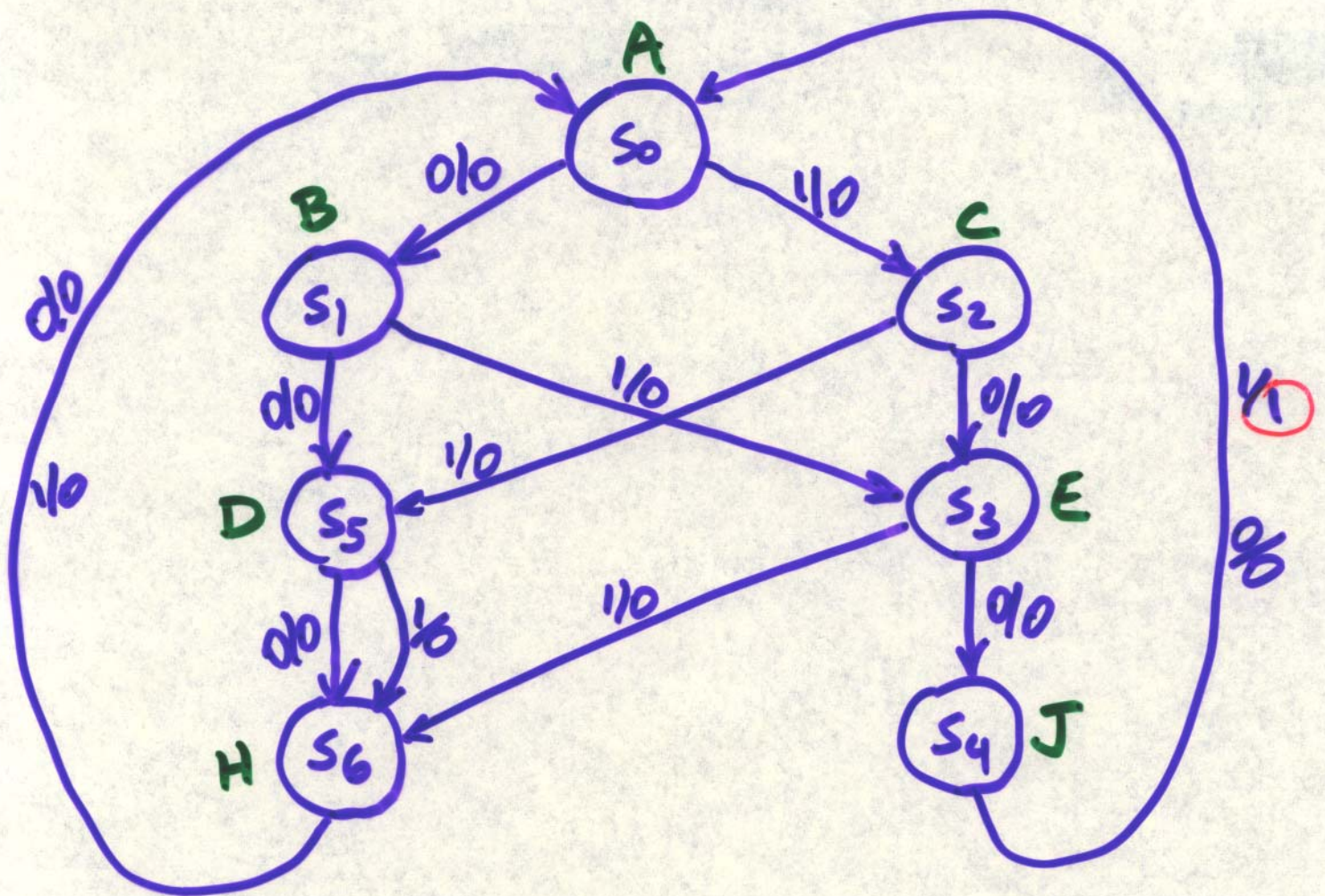

	S_n	S_{n+1} $x=0$	$x=1$	Z $x=0$	$x=1$
S_0	A	B	C	0	0
S_1	B	D	E	0	0
S_2	C	E	D	0	0
S_3	D	H	H	0	0
	E	A	A	0	0
	F	A	A	0	1

Equivalent States

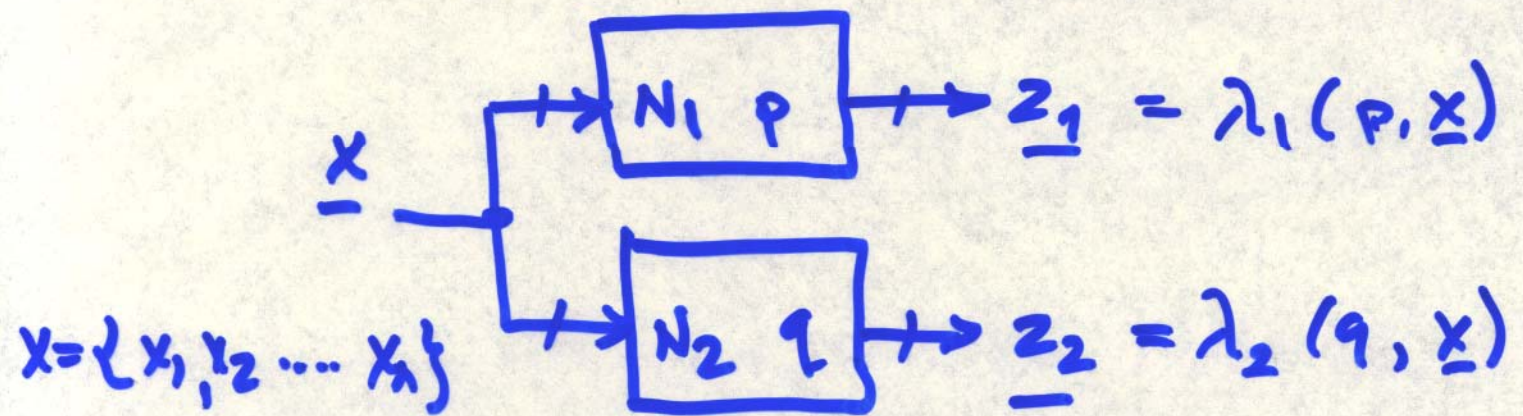Theorem : Two states are equivalent if there is no way of telling them apart from observation of network inputs & outputs



$$\underline{z}_1 = \underline{z}_2 \quad \forall X \Rightarrow \text{then } p \equiv q$$

Theorem 1a : Two states p & q are equivalent if $\forall X$ the outputs are the same and the next states are equivalent

$$\text{If } \lambda_1(p, \underline{X}) = \lambda_2(q, \underline{X})$$

$$\text{2 } \delta_1(p, \underline{X}) = \delta_2(q, \underline{X})$$

Then

$$p \equiv q$$

Implication Table

S_n	$x=0$	$x=1$	Z
a	d a	c	0
b	f	h	0
c	e c	d a	1
d	a	ce	0
e	c	a	1
f	f	b	1
g	b	h	0
h	c	g	1

Implication Chart

a							
b	a-b						
c	x	x					
d	a-d c-e	b-f	x				
e	x	x	c-e d-a	x			
f	x	x	a-b	x	d-a		
g	a-b c-e	b-f	x	a-b	x	x	
h	x	x	a-b	x	a-b	c-e	x
	a	b	c	d	e	f	g

h

$d \equiv a$
 $c \equiv e$