
 


VLSI Arithmetic

Lecture 10: Multipliers

Prof. Vojin G. Oklobdzija
University of California

<http://www.ece.ucdavis.edu/acsel>

 

Multiplication

Algorithm:

$$P = XY = X \times \sum_{i=0}^{n-1} y^i r^i = \sum_{i=0}^{n-1} X \times y^i r^i$$

$$p^{(0)} = 0 \quad \text{initially}$$

$$p^{(j+1)} = \frac{1}{r} (p^j + r^n X y_j) \quad \text{for } j=0, \dots, n-1$$

$$p(n) = XY \quad \text{after } n \text{ steps}$$

Multiplication Algorithm*

Notation for our discussion of multiplication algorithms:

a	Multiplicand	$a_{k-1}a_{k-2} \cdots a_1a_0$
x	Multiplier	$x_{k-1}x_{k-2} \cdots x_1x_0$
p	Product ($a \times x$)	$p_{2k-1}p_{2k-2} \cdots p_1p_0$

Initially, we assume unsigned operands

 


Fig. 9.1 Multiplication of two 4-bit unsigned binary numbers in dot notation.

**from Parhami*

Multiplication Algorithm*

Multiplication with right shifts: top-to-bottom accumulation

$$p^{(j+1)} = (p^{(j)} + x_j a 2^k) 2^{-1} \quad \text{with } p^{(0)} = 0 \quad \text{and}$$

$$p^{(k)} = p = ax + p^{(0)} 2^{-k}$$

|——add——|

|——shift right——|

Multiplication with left shifts: bottom-to-top accumulation

$$p^{(j+1)} = 2p^{(j)} + x_{k-j-1} a \quad \text{with } p^{(0)} = 0 \quad \text{and}$$

$$p^{(k)} = p = ax + p^{(0)} 2^k$$

|shift|

|——add——|

**from Parhami*

Multiplication Algorithm*

Right-shift algorithm


Left-shift algorithm

=====							
a	1	0	1	0			
x	1	0	1	1			
=====							
$p^{(0)}$	0	0	0	0			
$+x_0a$	1	0	1	0			
<hr/>							
$2p^{(1)}$	0	1	0	1	0		
$p^{(1)}$	0	1	0	1	0		
$+x_1a$	1	0	1	0			
<hr/>							
$2p^{(2)}$	0	1	1	1	0		
$p^{(2)}$	0	1	1	1	0		
$+x_2a$	0	0	0	0			
<hr/>							
$2p^{(3)}$	0	0	1	1	1	0	
$p^{(3)}$	0	0	1	1	1	0	
$+x_3a$	1	0	1	0			
<hr/>							
$2p^{(4)}$	0	1	1	0	1	1	0
$p^{(4)}$	0	1	1	0	1	1	0
=====							

=====								
a	1	0	1	0				
x	1	0	1	1				
=====								
$p^{(0)}$	0	0	0	0				
$2p^{(0)}$	0	0	0	0	0			
$+x_3a$	1	0	1	0				
<hr/>								
$p^{(1)}$	0	1	0	1	0			
$2p^{(1)}$	0	1	0	1	0	0		
$+x_2a$	0	0	0	0				
<hr/>								
$p^{(2)}$	0	1	0	1	0	0		
$2p^{(2)}$	0	1	0	1	0	0		
$+x_1a$	1	0	1	0				
<hr/>								
$p^{(3)}$	0	1	1	0	0	1	0	
$2p^{(3)}$	0	1	1	0	0	1	0	
$+x_0a$	1	0	1	0				
<hr/>								
$p^{(4)}$	0	1	1	0	1	1	1	0
=====								

**from Parhami*


Basic Hardware Multipliers

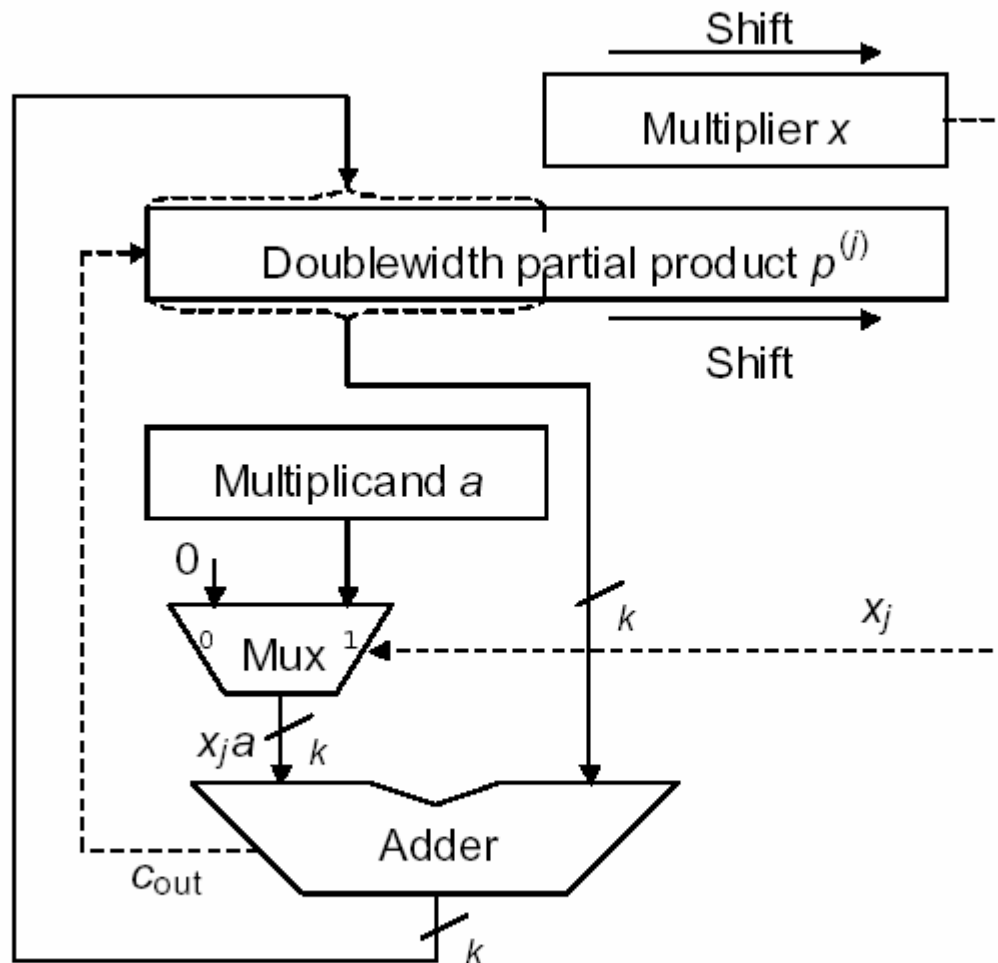

Hardware realization of the sequential multiplication algorithm with additions and right shifts.


**from Parhami*

Multiplication*

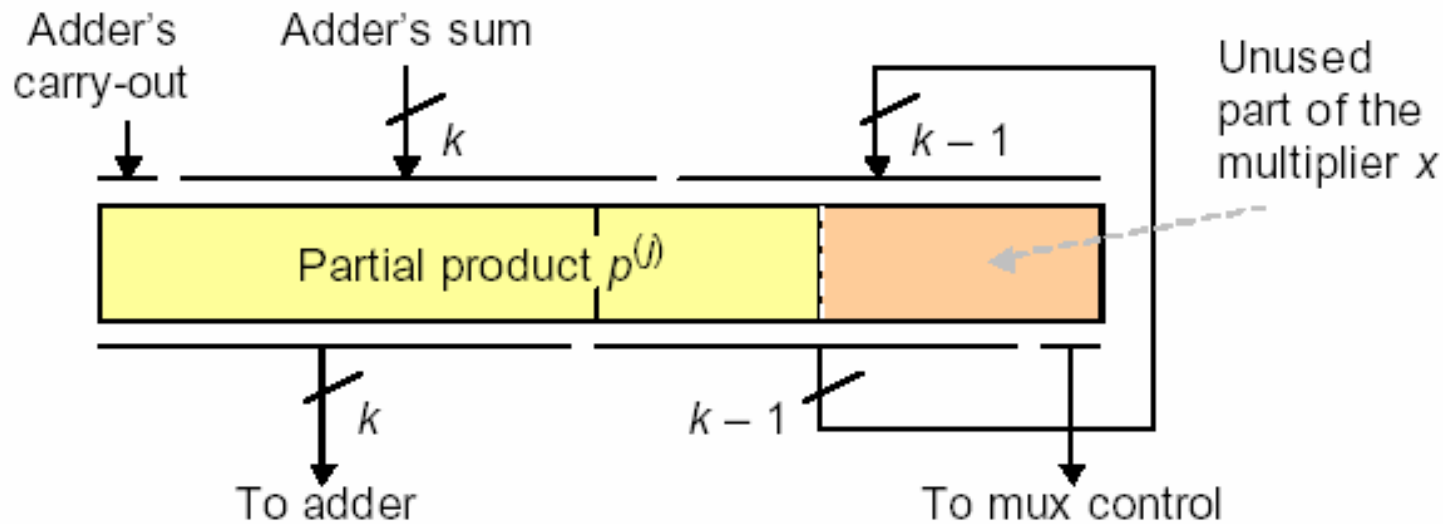

Combining the loading and shifting of the double-width register holding the partial product and the partially used multiplier.

Multiplication*

 

Hardware realization of the sequential multiplication algorithm with left shifts and additions.

**from Parhami*

$$\begin{array}{r}
 \text{Multiplicand : } \quad \circ \quad \circ \quad \circ \quad \circ \quad \circ \quad \circ \\
 \text{Multiplier : } \quad X \quad \circ \quad \circ \quad \circ \quad \circ \quad \circ \\
 \hline
 \quad \quad \quad \quad \quad \circ \quad \circ \quad \circ \quad \circ \quad \circ \quad \circ \\
 \text{Partial Products : } \quad \circ \quad \circ \quad \circ \quad \circ \quad \circ \quad \circ \\
 \quad \quad \quad \quad \quad \circ \quad \circ \quad \circ \quad \circ \quad \circ \quad \circ \\
 \quad \quad \quad \quad \quad \circ \quad \circ \quad \circ \quad \circ \quad \circ \quad \circ \\
 \quad \quad \quad \quad \quad \circ \quad \circ \quad \circ \quad \circ \quad \circ \quad \circ \\
 \hline
 \text{Result : } \quad \circ \quad \circ \quad \circ \quad \circ \quad \circ \quad \circ \quad \circ \quad \circ \quad \circ \quad \circ \quad \circ \quad \circ
 \end{array}$$

6 Bit Multiplication

 


Figure 6.3 The schematic circuit diagram of a 5-by-5 unsigned array multiplier (Braun [5]).

 


Figure 4-15a. 5×5 unsigned multiplication.


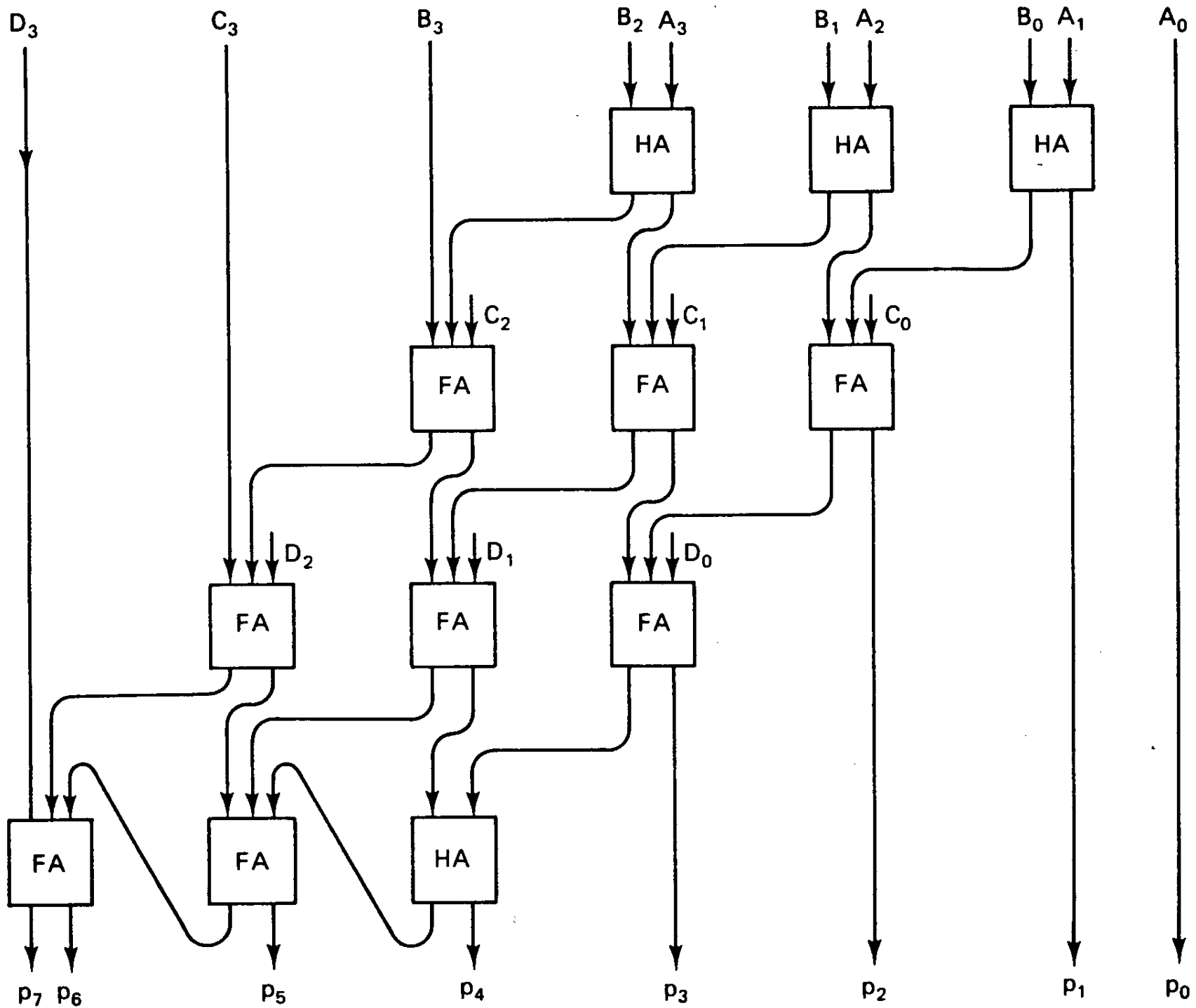


Figure 4.4 Array of half-adders and full-adders for 4-bit \times 4-bit multiplication.

Generating Partial Products


**from G. Bewick*

 
Multiplier = $63669_{10} = 1111100010110101$
 Multiplicand (M) = $40119_{10} = 1001110010110111$



10011000010000000001010101100011 = 2554336611_{10} = Product

Generating Partial Products

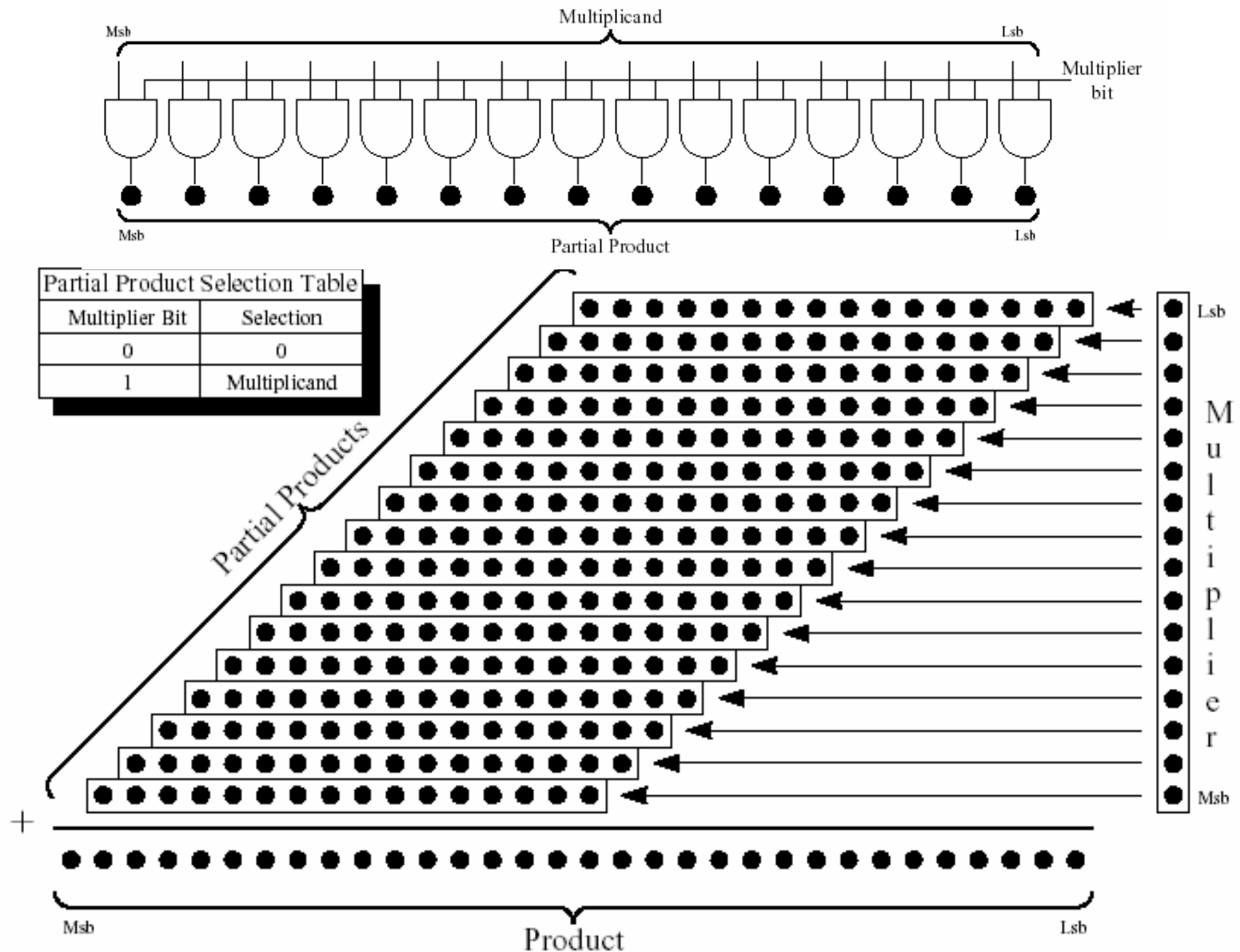

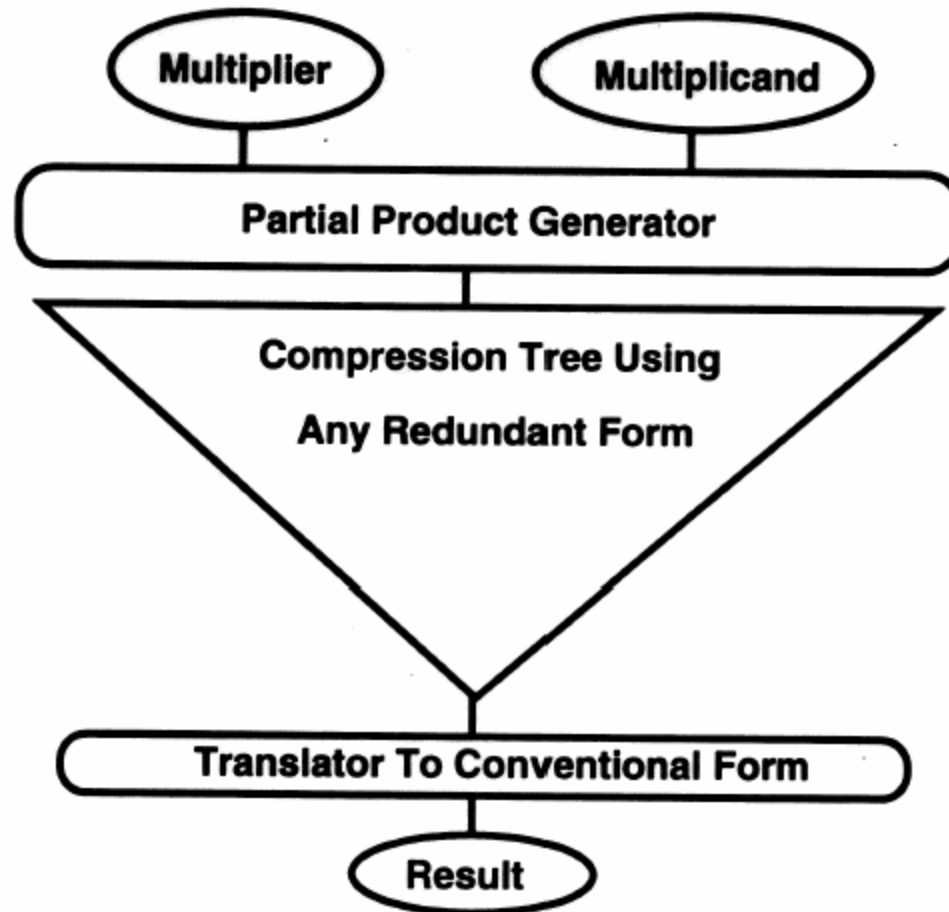


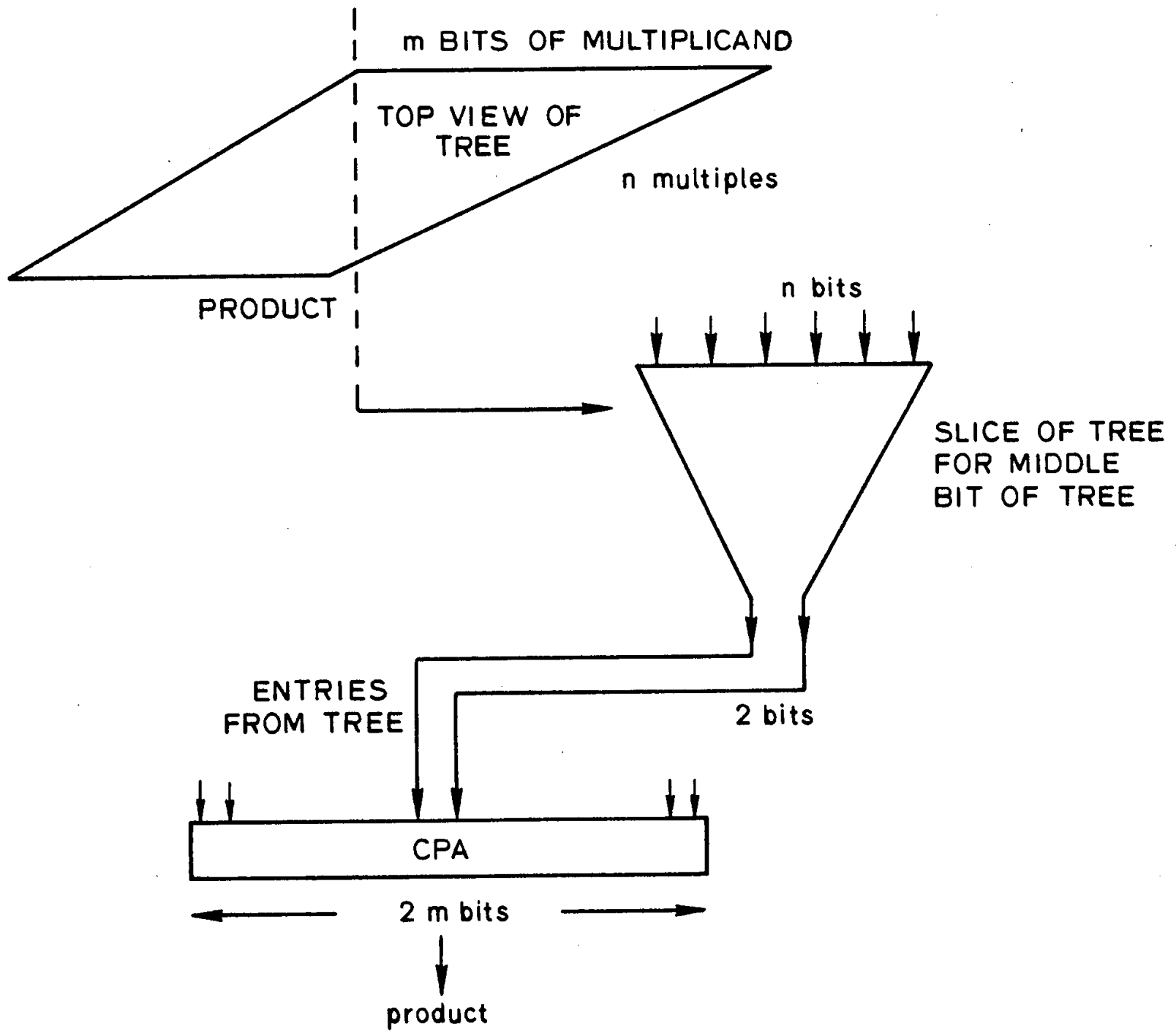


Figure 4-6. Wallace tree

Fast Parallel Multipliers


Wallace:

 

Prof. Vojin G. Oklobdzija


Advanced Logic Design

Parallel Multipliers

 


Fast Parallel Multipliers

Wallace:

 

Bit Reduction Using "Dadda" Counters

 

Minimum Number of Stages (Dada's Rule)


Number of bits in the multiplier	Minimum number of stages
3	1
4	2
$4 < n \leq 6$	3
$6 < n \leq 9$	4
$9 < n \leq 13$	5
$13 < n \leq 19$	6
$19 < n \leq 28$	7
$28 < n \leq 42$	8
$42 < n \leq 63$	9

Use of 4:2 Compressors

A. Weinberger 1981


M. Santoro 1988

4:2 Compressor

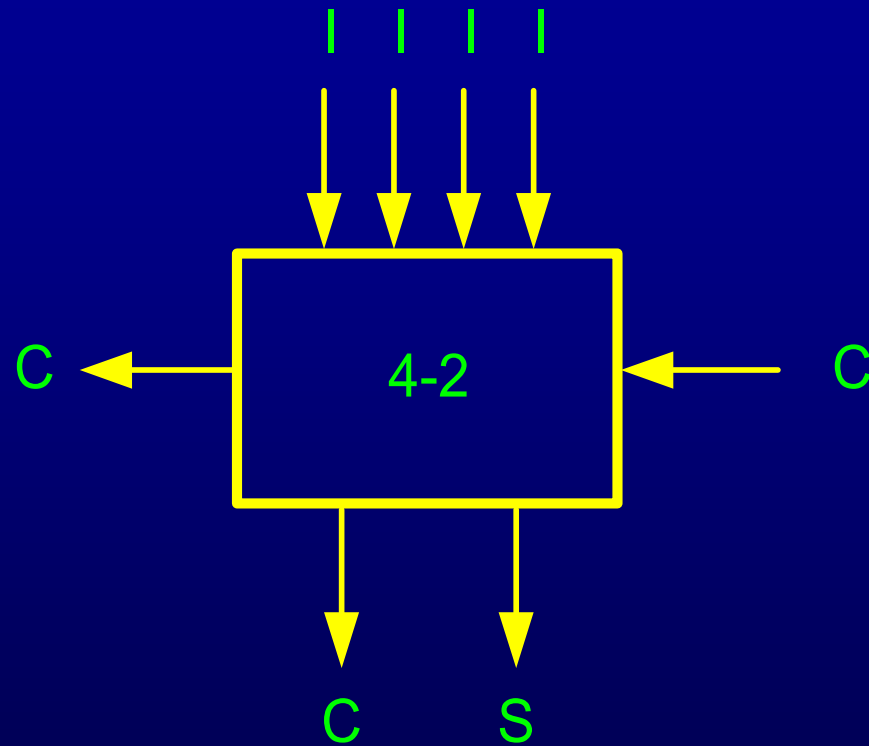


4

 
Re-designed 4:2 Compressor with 3 XOR Delay (Nagamatsu, Toshiba)



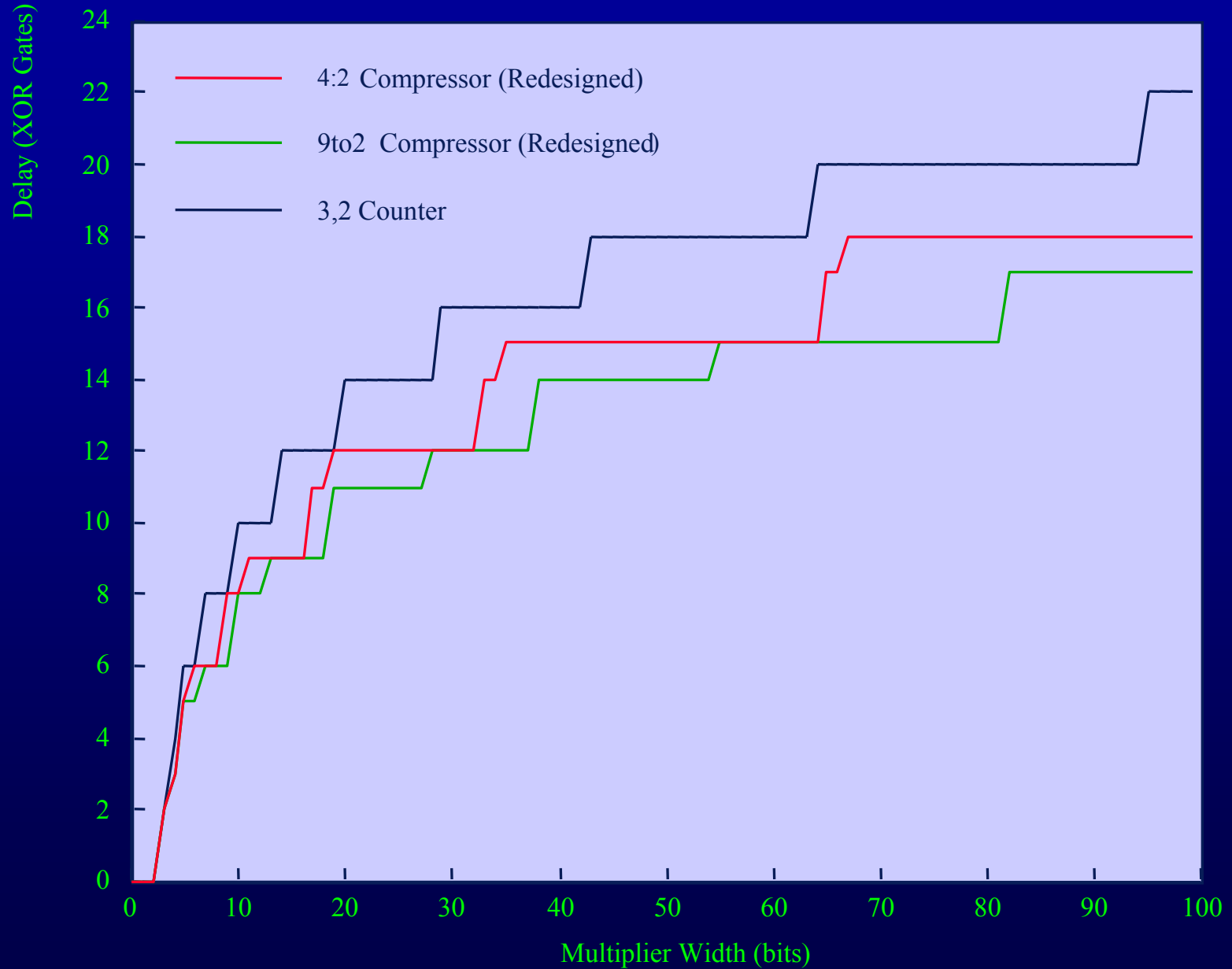Critical Path: (Equivalent XOR Gate Delays)




Tree Multipliers

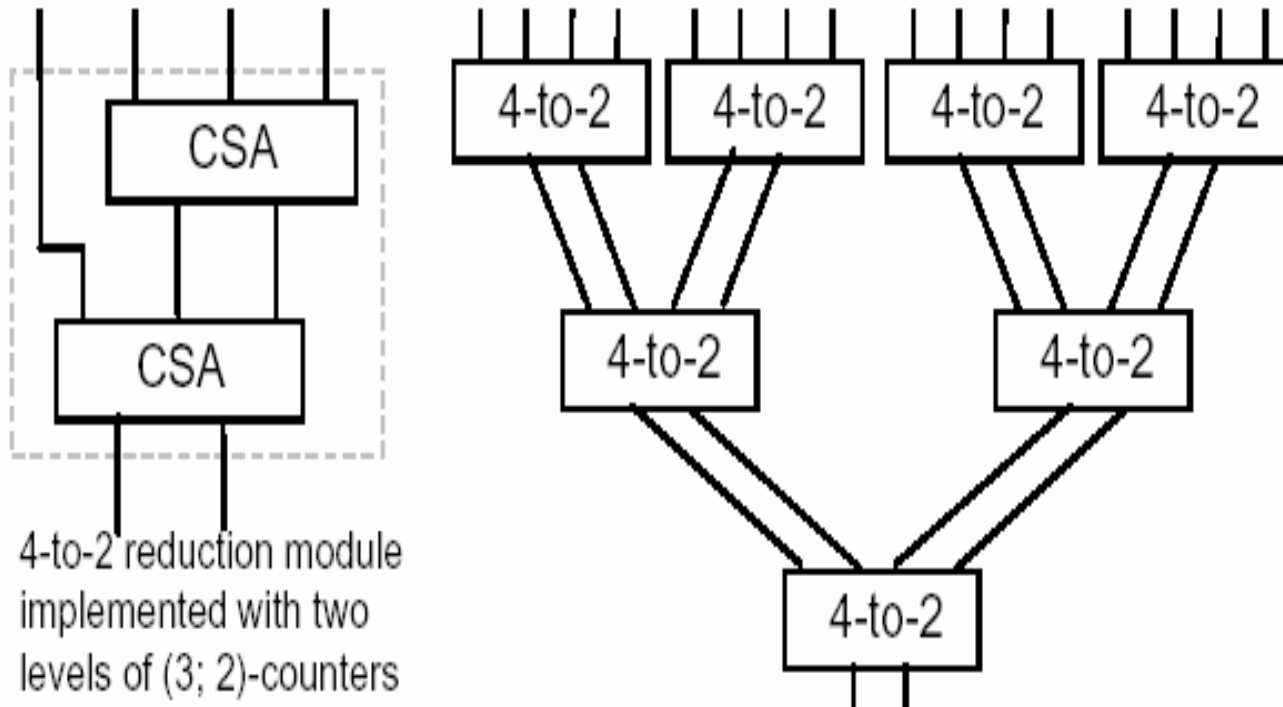

Tree multiplier with a more regular structure based on 4-to-2 reduction modules.


Reduction using 4:2 Compressors

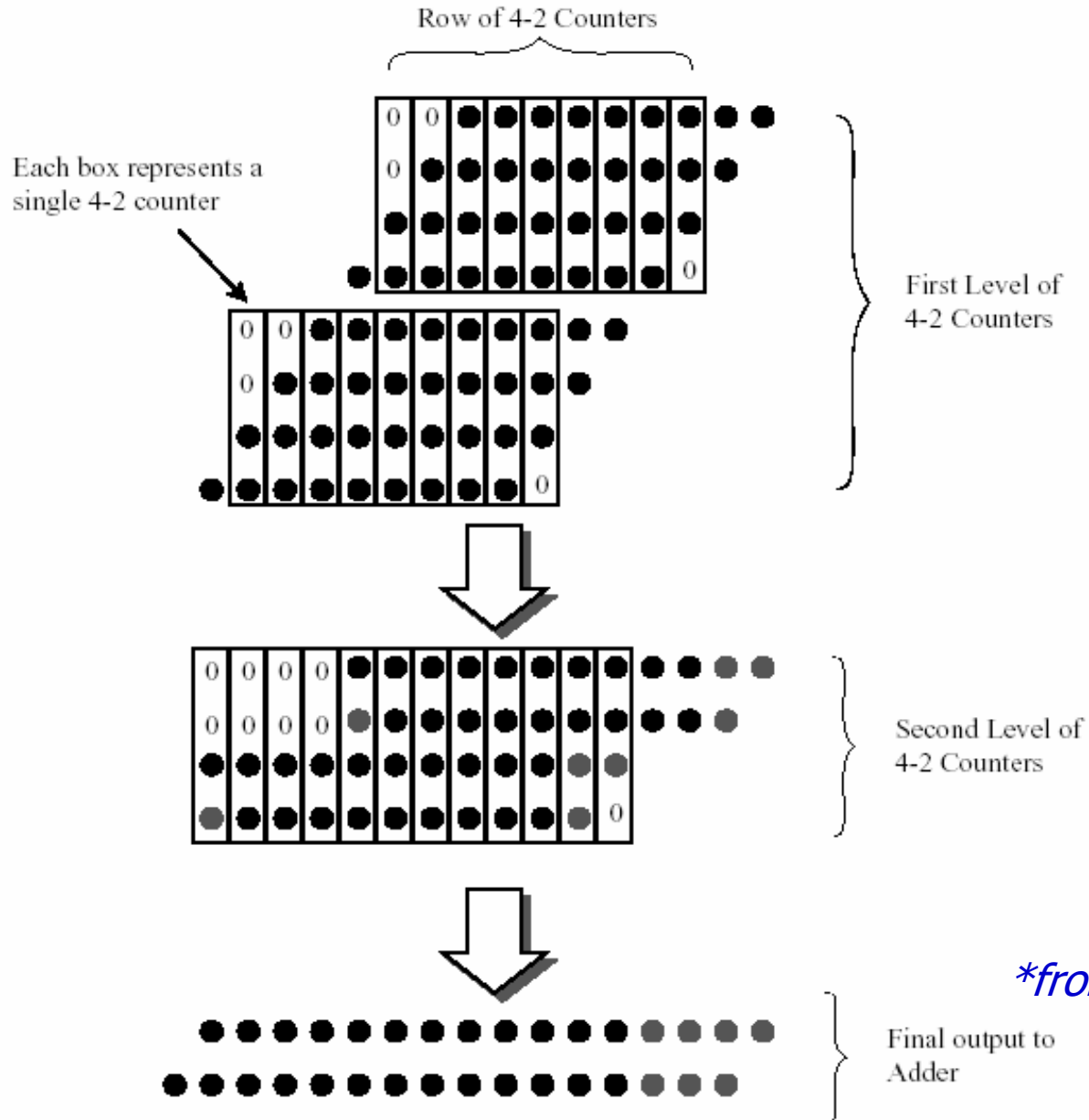

Use of Higher-Order Compressors

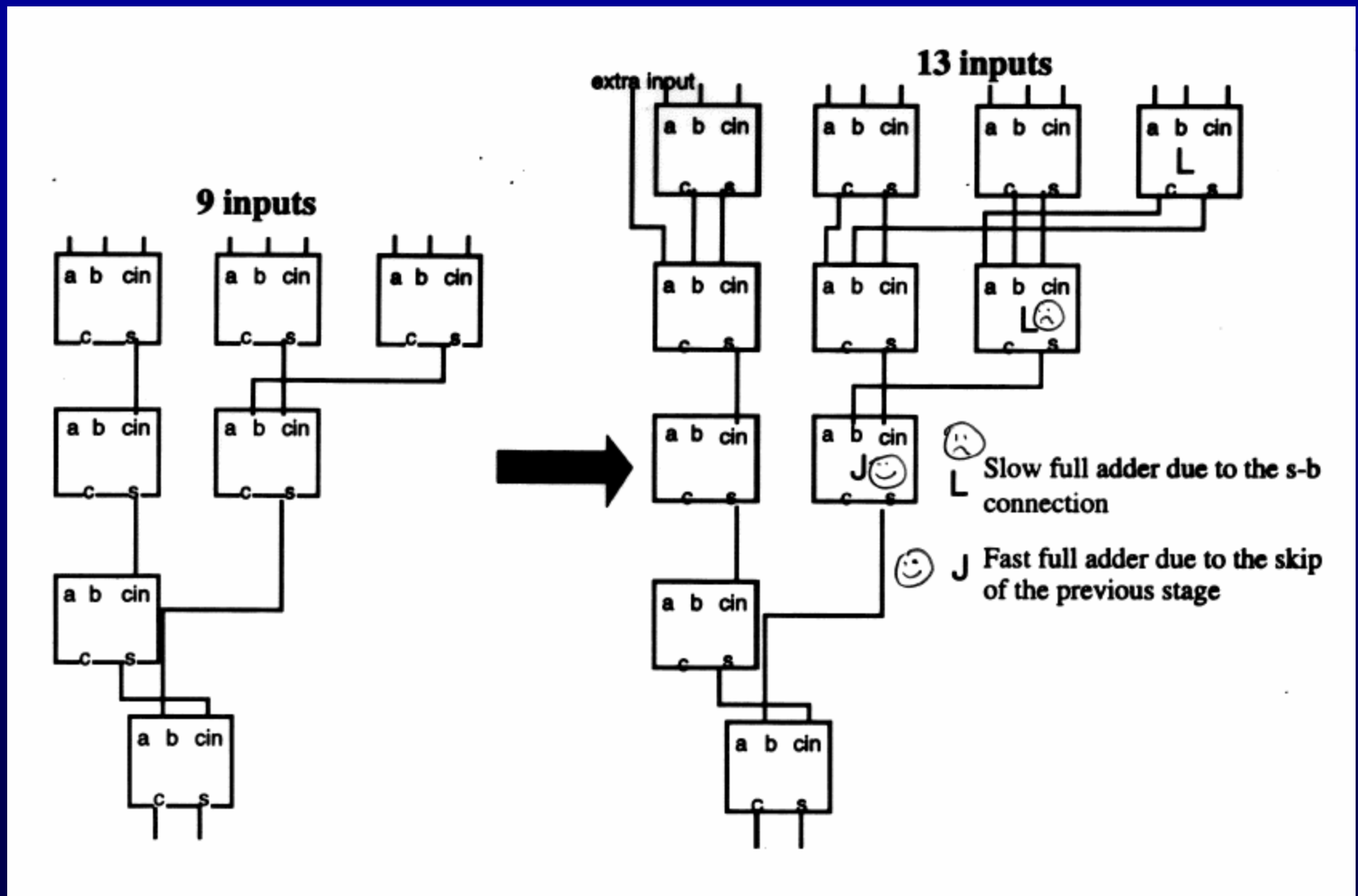D. Villeger, V.G. Oklobdzija 1993

Design of a 13:2 Compressor from a 9:2 Compressor




Compressor Family Characteristics

Compressor Counters	No of Full Adder Levels	No XOR Gates
4-2	2	3
6-2	3	5
9-2	4	6
13-2	5	8
18-2	6	9
24-2	7	11
53-2	9	14


Idea !!!!!



 
Partial Product Matrix Divided into Vertical Compressor Slices



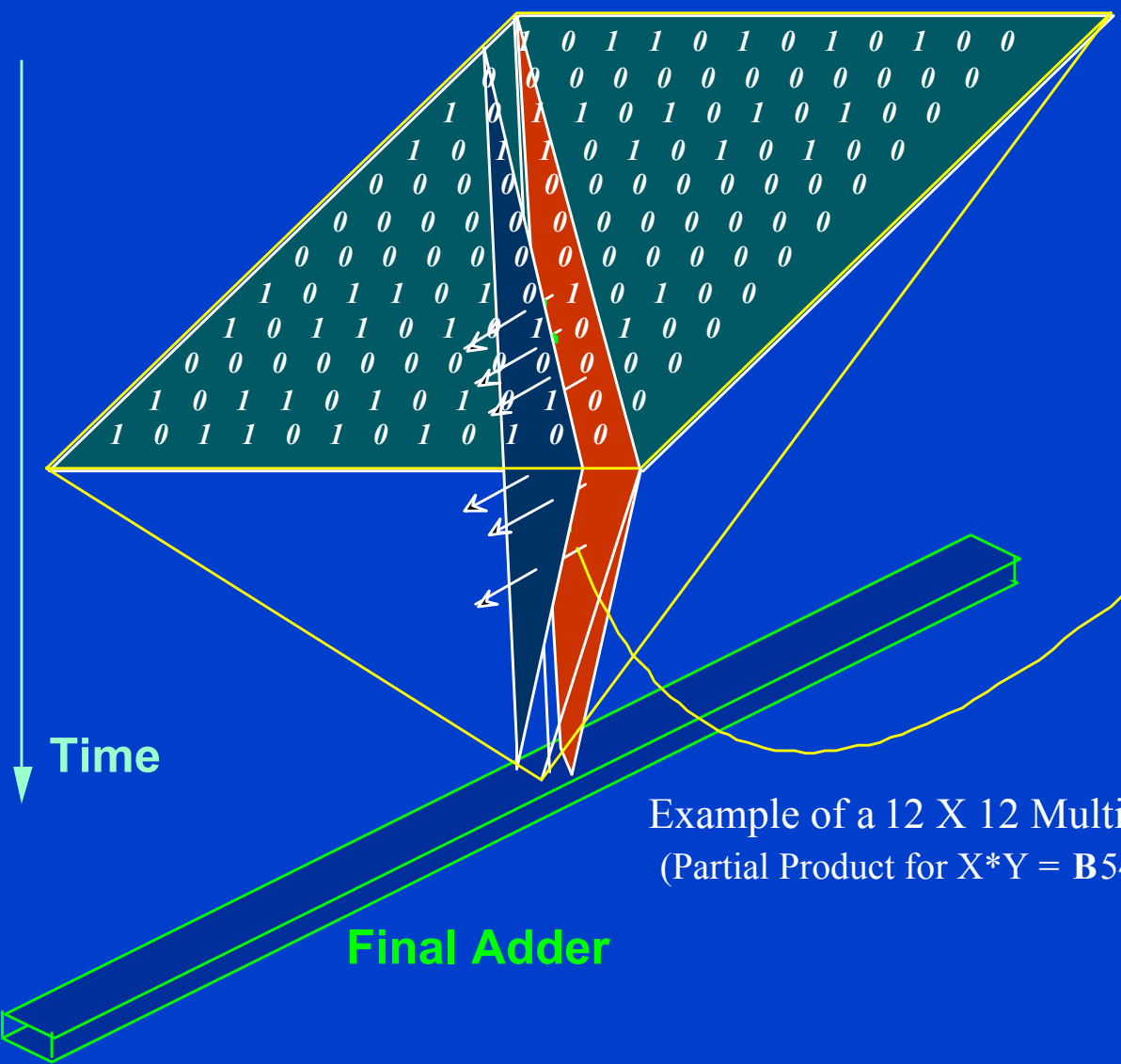3-Dimensional View of Partial Product Reduction



 
Example of a 12 X 12 Multiplication
(Partial Product for $X*Y = B54 * B1B$)




Final Adder

Signal Delays in a Full Adder

(3,2) Counter

 

 Three-Dimensional optimization Method: TDM (Oklobdzija, Villeger, Liu, 1996)




I1

I2


A
Multiplier Design

Method






 


Worst Case

 

TDM Arrangement

   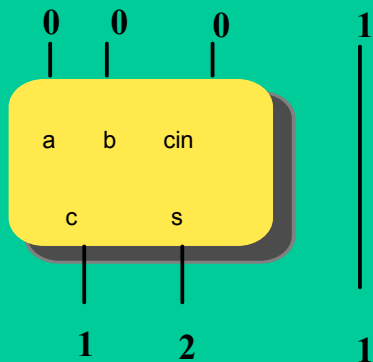Two cases of signals passing through the next level




Best Balanced Case

Average Case


Example of Delay Optimization




Example of a Optimized Interconnection

 


 Example of a not Optimized Interconnection



 The 9th Vertical Compressor Slice of a Multiplier



 


Computer Tools

Competing Approaches




Their Schemes



 

Tree Multipliers

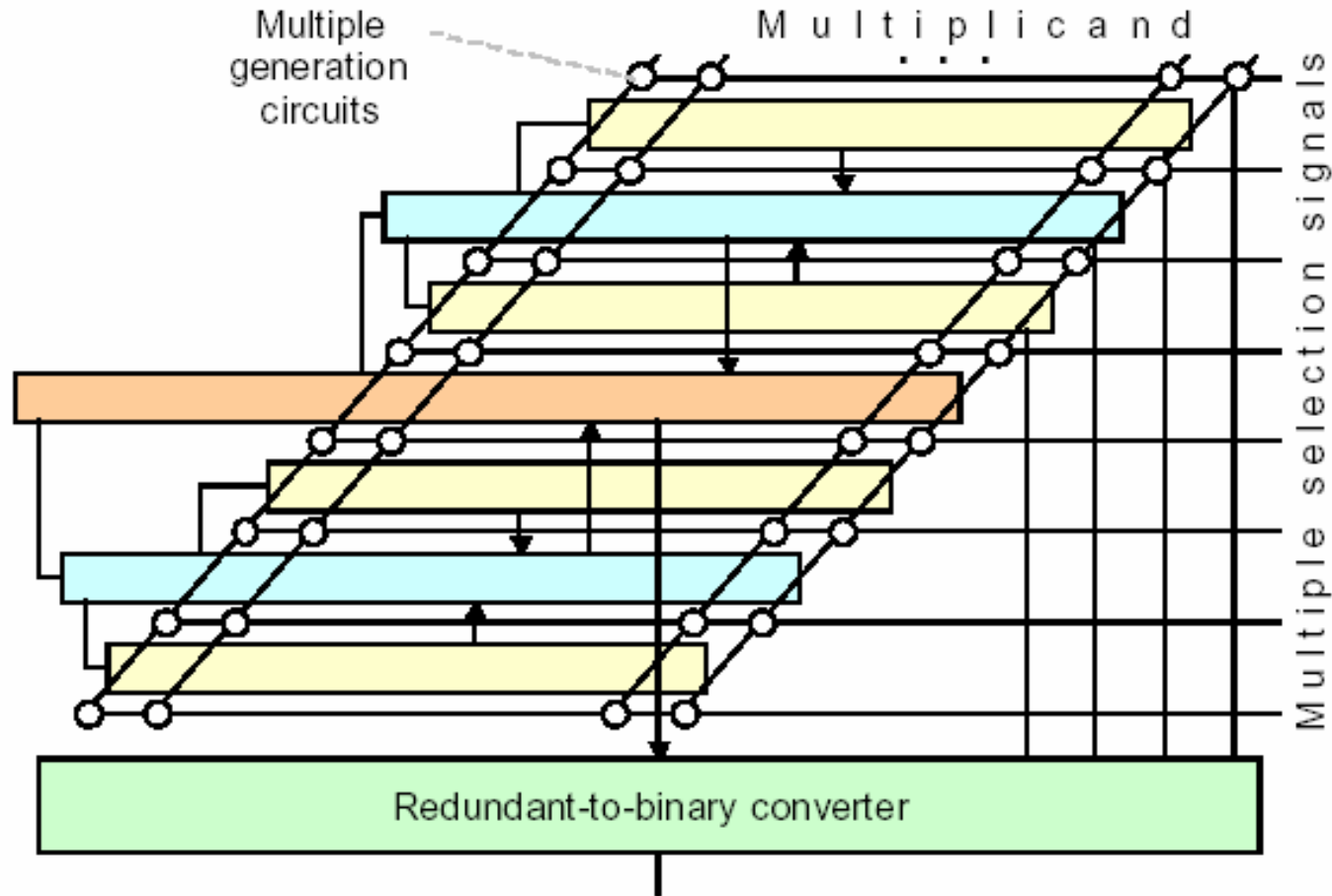

Layout of a partial-products reduction tree composed of 4-to-2 reduction modules. Each solid arrow represents two numbers.

**from Parhami*

Floor Plan of a Multiplier



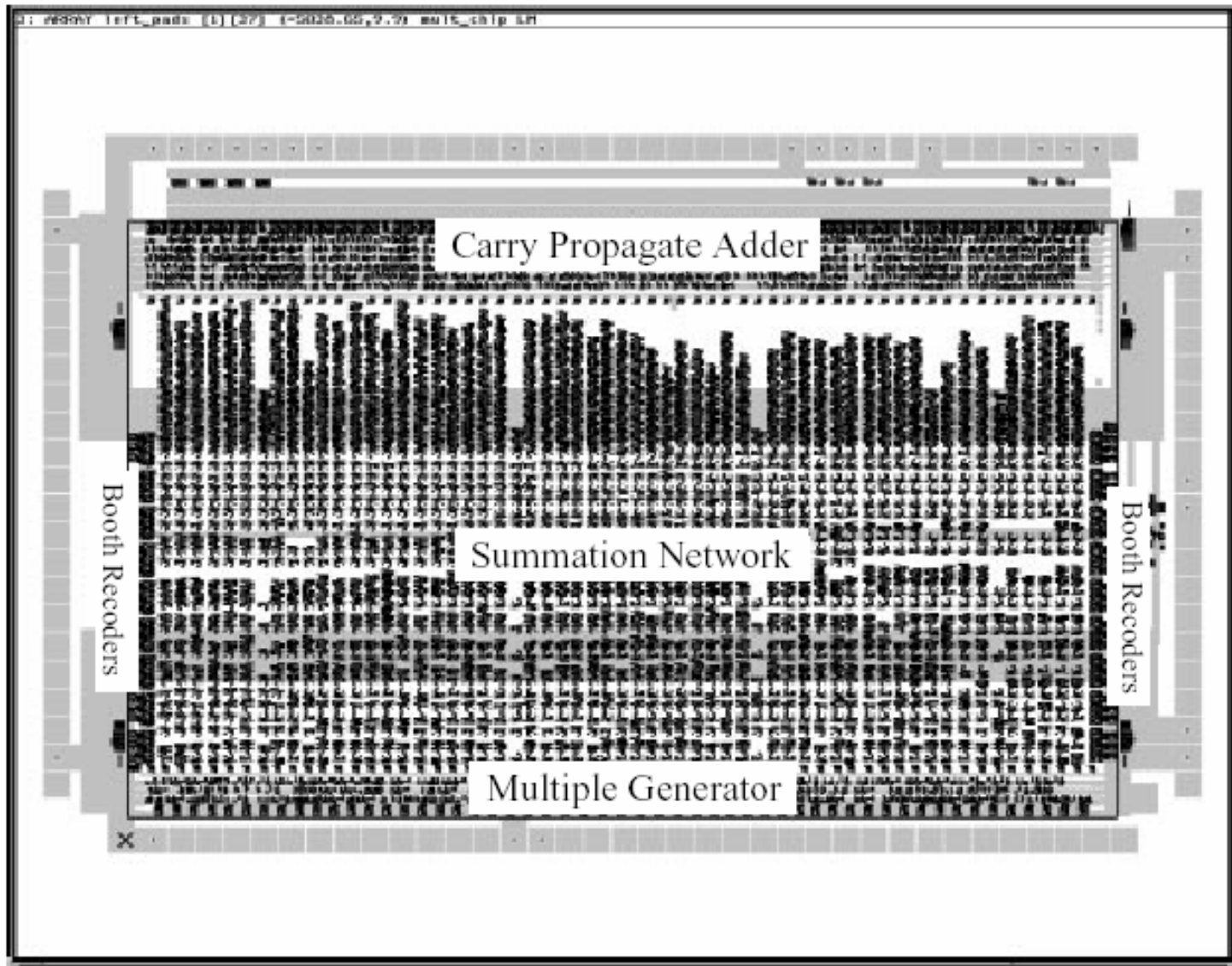


Figure 5.20: Floor plan of multiplier chip

**from G. Bewick*

 

RECOMENDATIONS

 



Holland

