
 


 

(a) A switch with the opposite behavior of Figure 3.2(a)



(b) PMOS transistor




(c) Simplified symbol for an PMOS transistor


**Figure 3.3** PMOS transistor as a switch.

McGraw, Hamacher, Zaky

### 3.2 NMOS LOGIC GATES

 


(a) NMOS transistor

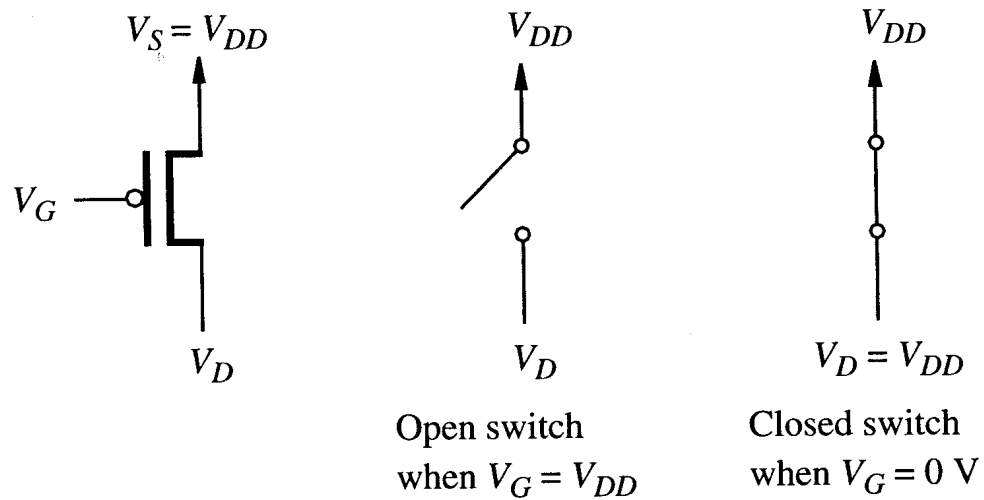


(b) PMOS transistor



**Figure 3.4** NMOS and PMOS transistors in logic circuits.

 

(a) Circuit diagram

 


(b) Simplified circuit diagram

  

(c) Graphical symbols


**Figure 3.5** A NOT gate built using NMOS technology.

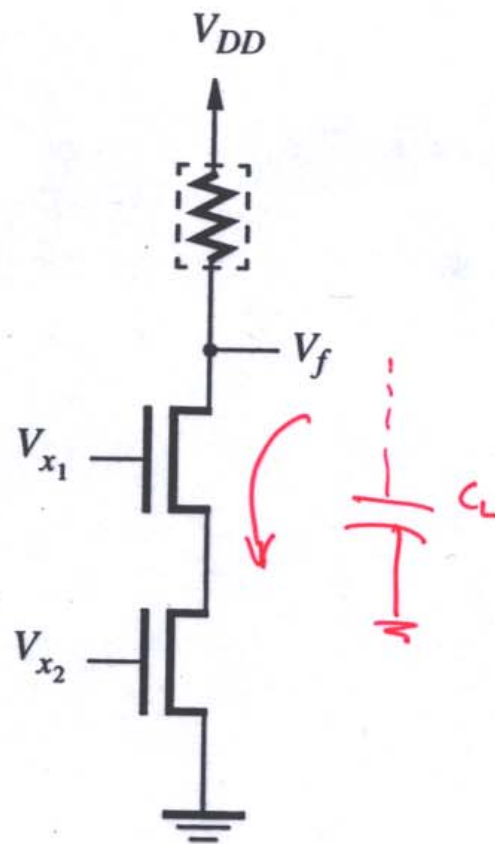

$x_1$	$x_2$	$f$
0	0	1
0	1	1
1	0	1
1	1	0

(a) Circuit


(b) Truth table

 

(c) Graphical symbols

**Figure 3.6** NMOS realization of a NAND gate.


## CHAPTER 3 • IMPLEMENTATION TECHNOLOGY

 

(a) Circuit

$x_1$	$x_2$	$f$
0	0	1
0	1	0
1	0	0
1	1	0


(b) Truth table

 

(c) Graphical symbols

**Figure 3.7** NMOS realization of a NOR gate.


### 3.3 CMOS LOGIC GATES

 

(a) Circuit


$x_1$	$x_2$	$f$
0	0	0
0	1	0
1	0	0
1	1	1

(b) Truth table

 


(c) Graphical symbols


**Figure 3.8** NMOS realization of an AND gate.

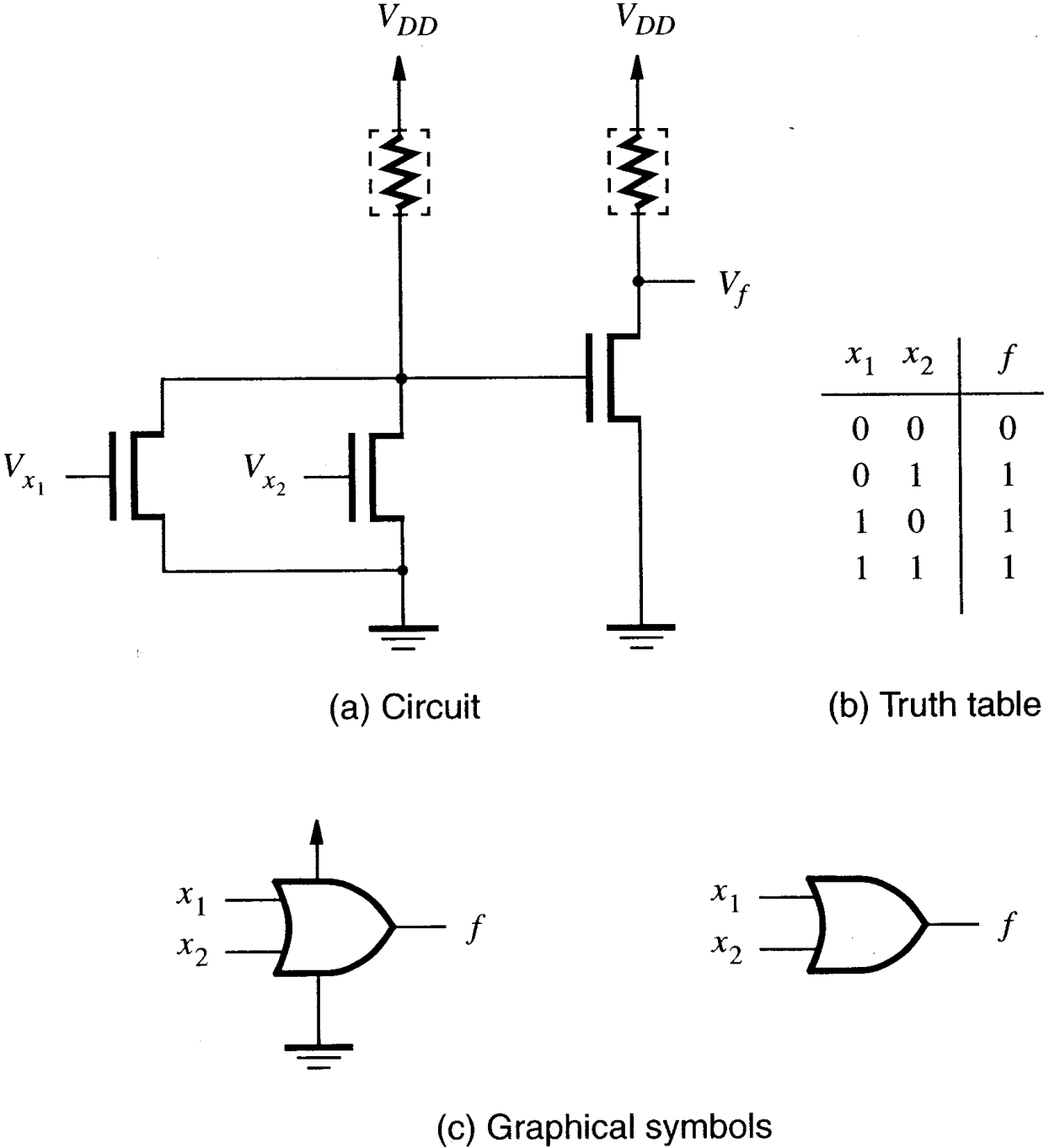

 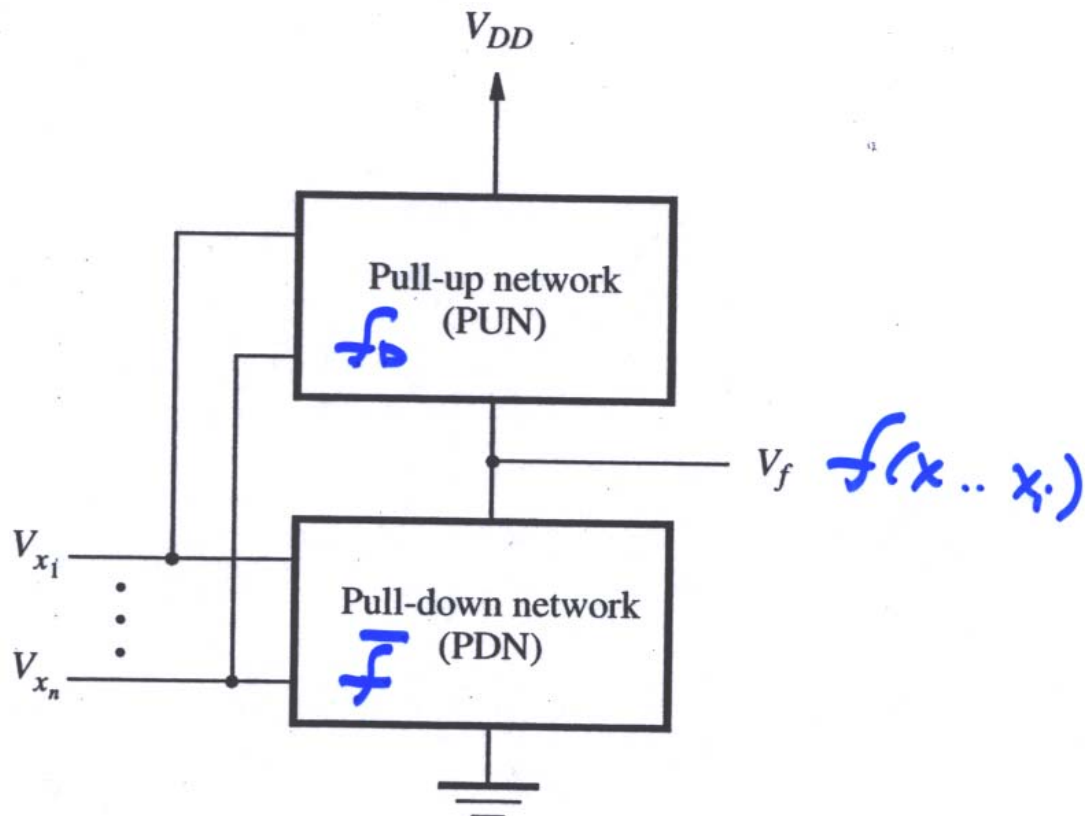**Figure 3.9** NMOS realization of an OR gate.

 


**Figure 3.10** Structure of an NMOS circuit.

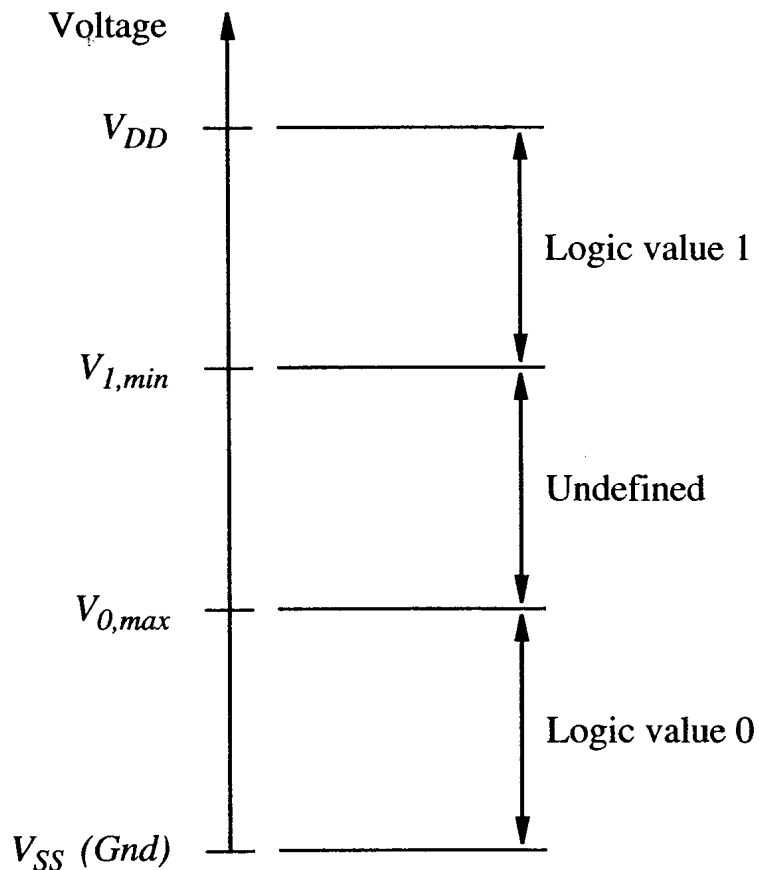


**Figure 3.11** Structure of a CMOS circuit.

 




**Figure 3.12** CMOS realization of a NOT gate.




**Figure 3.1** Representation of logic values by voltage levels.



(a) Circuit

$x_1$	$x_2$	$T_1$	$T_2$	$T_3$	$T_4$	$f$
0	0	on	on	off	off	1
0	1	on	off	off	on	0
1	0	off	on	on	off	0
1	1	off	off	on	on	0

(b) Truth table and transistor states

 
**Figure 3.14** CMOS realization of a NOR gate.

(a) Circuit


$x_1$	$x_2$	$T_1$	$T_2$	$T_3$	$T_4$	$f$
0	0	on	on	off	off	1
0	1	on	off	off	on	1
1	0	off	on	on	off	1
1	1	off	off	on	on	0

(b) Truth table and transistor states


**Figure 3.13** CMOS realization of a NAND gate.

 

**Figure 3.17** The circuit for Example 3.2.

 


 (a) When  $V_{GS} = 0\text{ V}$ , the transistor is off




(b) When  $V_{GS} = 5\text{ V}$ , the transistor is on

**Figure 3.43** Physical structure of an NMOS transistor.

 

**Figure 3.44** The current-voltage relationship in the NMOS transistor.

 


define the low *noise margin* as


$$NM_L = V_{IL} - V_{OL}$$

A similar situation exists when  $N_1$  produces its high output voltage  $V_{OH}$ . Any existing noise in the circuit may alter the voltage level, but it will be interpreted correctly by  $N_2$  as long as the voltage is greater than  $V_{IH}$ . The high noise margin is defined as

$$NM_H = V_{OH} - V_{IH}$$

 


(a) A NOT gate driving another NOT gate

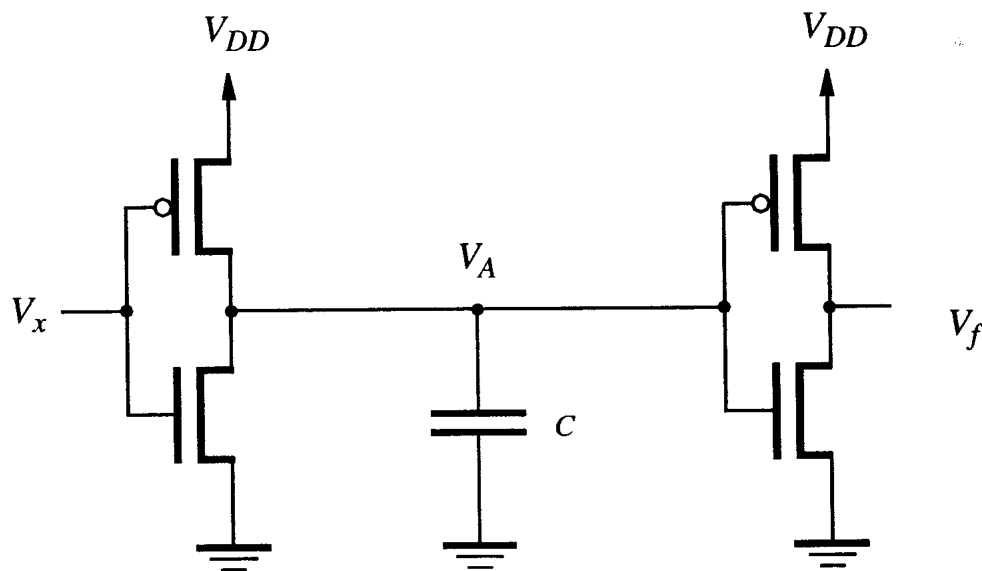


(b) The capacitive load at node A

**Figure 3.47** Parasitic capacitance in integrated circuits.

 


**Figure 3.53** High fan-in NMOS NAND gate.

  
### 3.8 PRACTICAL ASPECTS



(a) Inverter that drives  $n$  other inverters



 
(b) Equivalent circuit for timing purposes




(c) Propagation times for different values of  $n$

**Figure 3.55** The effect of fan-out on propagation delay.



 


 


(a) Circuit

$s$	$f$
0	Z
1	$x$

(b) Truth table

 

(c) Equivalent circuit

 


(d) Graphical symbol

**Figure 3.60** A transmission gate.


### 3.10 IMPLEMENTATION DETAILS FOR SPLDs, CPLDs, AND FPGAs

129

 

**Figure 3.62** A 2-to-1 multiplexer built using transmission gates.

$x_1$	$x_2$	$f = x_1 \oplus x_2$
0	0	0
0	1	1
1	0	1
1	1	0


(a) Truth table

  

(b) Graphical symbol




(c) Sum-of-products implementation

 

(d) CMOS implementation

**Figure 3.61** Exclusive-OR gate.

 

**Figure 3.62** A 2-to-1 multiplexer built using transmission gates.