

## OVERVIEW

This tutorial illustrates several advanced topics which were not covered in Lab 1. These topics include creating symbols for use in a hierarchical design, using Altera parameterized modules, such as ROM, and initializing ROM contents.

## USING PARAMETERIZED MODULES

Altera's Library of Parameterized Modules (LPM) contains many high-level components which can be configured to meet specific design goals. You will probably find the LPM components very convenient and easy to use.

In this tutorial, you will design a circuit which computes the Fibonacci sequence using an adder and registers. (The Fibonacci sequence is 0, 1, 1, 2, 3, 5, 8, ...) The data path will be 8-bits wide so that the circuit can be easily tested using the Altera Education Board.

- Recall that there are many ways to execute commands in the Altera environment. You can use the pull-down menus, a pop-up menu which is available when you click the right-mouse button, keyboard shortcut commands, or the toolbar buttons. To see the definition of a toolbar button, move the mouse so that the cursor is on top of the button. The button's function will be described at the lower-left corner of your window.
- Open a new schematic and enter the symbol **lpm\_add\_sub** from the mega\_lpm library. A dialog box should come up to allow you to configure the parameters and ports. Click on each parameter from the list and use the pull-down arrow in the dialog box to select the desired value for the parameter. Enter the following values for the parameters:

```
LPM_DIRECTION = "ADD"  
LPM_REPRESENTATION = "UNSIGNED"  
LPM_WIDTH = 8
```

Any other parameters, such as LPM\_PIPELINE or ONE\_INPUT\_IS\_CONSTANT, should be left unassigned. For an explanation on how the lpm\_add\_sub component works and how each of the parameters can be used, select the **Help on LPM\_ADD\_SUB** button in the dialog box.

Configure the ports so that **cin**, **cout**, **dataa[]**, **datab[]** and **result[]** are *Used* and all other ports are *Unused*. (Select each port name from the list and click on the *Used* or *Unused* button.) When you have configured all ports and parameters, press the OK button.

If you need to change any parameters or port declarations after you have closed the dialog box, click on the lpm\_add\_sub component on your schematic and select **Edit Ports/Parameters...** (Symbol menu). This will re-open the dialog box so that you can make corrections. Another way to re-open the dialog box is to double-click the left-mouse button (LMB) on the parameters box.

The adder will be used to add the last two numbers in the sequence to produce the next number. We will also need two 8-bit registers in order to store the last two numbers in the sequence. We could use a standard D flip-flop and let the Altera software create a "primitive array". However, the standard D flip-flop only has an asynchronous reset and in our design we would like to

synchronously clear the registers when a carry-out is generated by the adder. We can use another LPM component to design a D flip-flop with both asynchronous and synchronous clear inputs.

- Enter the symbol **lpm\_dff** from the mega\_lpm library. Set the parameters such that LPM\_WIDTH = 8 and the other parameters are unassigned. Configure ports **aclr**, **clock**, **data[]**, **q[]** and **sclr** as *Used* and all other ports as *Unused*.
- Make a copy of the **lpm\_dff** that you just configured and place the components as shown in Figure 1. Also, add the components **not**, **dff**, **input** and **output** and complete the schematic as shown in Figure 1. Note that buses are shown with a thick line and are labeled as NAME[MSB..LSB].
- Label the output bus with your first name. i.e. FRANK[7..0]. Also, label the output of the lpm\_add\_sub component with your initials followed by \_SUM[7..0]. Note that wires which have the same name on the same level of hierarchy are connected. *Remember to keep the wire labels close to wires which they label.* Otherwise, the Altera Compiler may not interpret the text as a valid net label.
- Save & Check your file to make sure that there are no errors. The Check command opens up the Compiler tool and performs the first part of a circuit compilation. With the Compiler tool still open, select the following options from the Processing menu: **Functional SNF Extractor** and **Preserve All Node Name Synonyms**. (You will have to turn *off* the **Timing SNF Extractor** before you can select the **Functional SNF Extractor**.) Once the options are selected, click on the **Start** button to compile your circuit. You must fix any compile errors before proceeding to the next step.
- Open the Waveform Editor and select the Nodes to watch during simulation. You can use **Enter Nodes from SNF...** (Node menu) to select nodes such as RESET, CLK and the output signal with your name. Some other nodes are difficult to find in the SNF list. Instead, you can select **Insert Node** (Node menu) and type the name of a node. Try this for entering nodes A[7..0], CIN, COUT and the output of the lpm\_add\_sub which has your initials in the name.
- Set the **Grid Size**(Options menu) to 20 ns.
- Select the CLK node with the left-mouse button so that it is highlighted. Then select **Overwrite > Clock** from the Edit pull-down menu. Specify a clock period of 40 ns.
- Assert the RESET node high for the first clock cycle. (Note that the RESET is active-high in this design.) Run a functional simulation and compare your results with Figure 2.

## CREATING A SYMBOL

You will now create a symbol for the circuit you have just designed so that it can be used as a component in a more complex design.

- Open the graphic design file (.gdf) for your circuit. Select **Create Default Symbol** (File menu). This will create a symbol file with the same name as your design and the .sym extension.

## CREATING A HIERARCHICAL DESIGN

You will now design a top-level schematic which uses the component you just created.

- Close any open windows such as the Graphics Editor, Simulator, Waveform Editor, etc. Create a new schematic file (.gdf) for your top-level design. Name the file and save it in your working directory. Change the project to this new name.

- Place an instance of your component in your top-level schematic. Your symbol should have RESET and CLK input ports and an output port named after you.

## USING ROM

In this design, we will use ROM to implement a combinational logic circuit which converts a 4-bit hex number to the corresponding 7-segment display driver signals. (This is a useful circuit which you may want to use in Lab 8&9!) We will illustrate how the ROM can be initialized using a Memory Initialization File (.mif) which can be created using a simple text editor.

- Select an **lpm\_rom** component from the mega\_lpm library. Select **address[]** and **q[]** as the only ports to be *Used*. Also, configure the parameters as shown below.

```
LPM_ADDRESS_CONTROL = "UNREGISTERED"
LPM_OUTDATA = "UNREGISTERED"
LPM_FILE = "hex7seg.mif"
LPM_WIDTH = 8
LPM_WIDTHHAD = 4
```

Note that you must type the quotes around the file name and the case of the name must match the file which you create. Once the ports and parameters are configured, press OK.

- Using Copy and Paste, place a second, identical ROM component on your schematic.

Next we will create the .mif file. The format of the MIF file is quite simple and is explained in Altera's on-line HELP documentation. The default radix is hexadecimal. Our ROM will be 16-bytes deep and 8-bits wide. The data represents active-low 7-segment display drivers where the MSB corresponds to signal a, MSB-1 corresponds to b, etc. and the LSB corresponds to the decimal point which should always be off. For example, when the value 0 is the address value, we would like to display the symbol 0 on the 7-segment display. This requires all segments to be on (low) except for g and the decimal point, giving a hex value of 03.

```
----- hex7seg.mif -----
DEPTH = 16;
WIDTH = 8;
CONTENT
BEGIN
0 : 03;
1 : 9F;
2 : 25;
3 : 0D;
4 : 99;
5 : 49;
6 : 41;
7 : 1F;
8 : 01;
9 : 19;
A : 11;
B : C1;
C : 63;
D : 85;
E : 61;
F : 71;
END;
-----
```

## CLOCK GENERATION

The Altera UP1 Education Board has a 25.175 MHz crystal oscillator which drives global clock input **pin 83** of the EPM7128S device and global clock input **pin 91** of the EPF10K20 device. Since the EPM7128S device does not support memory devices such as ROM we will use the EPF10K20 for this design. We will need to divide the clock signal down to a frequency on the order of 1 Hz so that we can observe the Fibonacci sequence on the 7-segment displays. We can use a counter from the LPM library to accomplish this.

- Select **lpm\_counter** (mega\_lpm library). Configure two ports, **clk** and **q[]**, as *Used* and all other ports as *Unused*. Set the LPM\_DIRECTION parameter to "UP" and the LPM\_WIDTH to 24. Then press the OK button.

You will use the most significant bit of the counter as the clock signal for the Fibonacci subcircuit. The frequency should be approximately  $(25 \text{ MHz} / 2^{24}) = 1.5 \text{ Hz}$ . After the design has been compiled with the **Timing SNF Extractor**, we will use the Timing Analysis tool to verify that the counter can operate with a clock frequency of 25 MHz.

## TRI-STATES

Based on the state of a push-button switch input, this design will display on the 7-segment displays either the value of eight input switches or the Fibonacci sequence. We will use tri-state buffers in order to multiplex these different output functions.

- Select **tri** from the primitive library. Although this primitive represents a single tri-state buffer, it can be connected to a bus and the Altera compiler will automatically generate a "primitive array" of the same width as the bus. Place a tri buffer at the output of the Fibonacci subcircuit and another connected to an **input** primitive, as shown in Figure 3.

There are some very important guidelines for designing with tri-state buffers using Altera tools. **Altera devices do not have tri-state buffers for driving internal logic.** When tri-state buffers are used to multiplex signals, as in our current design, MAX+PLUSII will convert the logic to a combinatorial multiplexer. However, bidirectional signals cannot be implemented in the internal Altera logic. Altera devices do have tri-state buffers in the I/O Elements so that bidirectional I/O pins with tri-state output capability can be implemented. For more information on using tri-state buses in Altera devices, check the documentation available on the Altera Web page:

<http://www.altera.com/html/atlas/examples/ged>

Within this directory, there are several examples relating to tri-state buffers such as tri\_state.html, g\_tri\_bb.html, g\_prim.html, g\_tri2mux.html, etc.

## PIN AND DEVICE ASSIGNMENTS

- Add the remaining components and connect the circuit as shown in Figure 3. Select **Line Style** (Options menu) to draw a bus between the input switches, SW[7..0], and the tri component.
- Label the output of the Fibonacci circuit with *your* name and the output of the tri-state multiplexer with *your* initials. An example is given in Figure 3.

We will now assign the device type and pin locations which correspond to the Altera Education Board.

- From the Graphics Editor, select **Device...** (Assign menu). Choose FLEX10K as the Device Family. Make sure that the option "Show Only Fastest Speed Grades" is not selected and select device **EPF10K20RC240-4**.

The pushbutton switches are active low and are each pulled-up through a 10 K ohm resistor. The pushbutton switches have the following pin assignments.

<u>Pushbutton switch</u>	<u>Pin number</u>
PB1	28
PB2	29

The pin assignments for the eight dip-switch inputs are:

<u>Switch</u>	<u>Pin number</u>
SW-1	41
SW-2	40
SW-3	39
SW-4	38
SW-5	36
SW-6	35
SW-7	34
SW-8	33

The pin assignments for the 7-segment display driver signals are shown below. **Note that these are different from the pin assignments for the EPM7128S.**

<u>Display segment</u>	<u>MS Digit pin number</u>	<u>LS Digit pin number</u>
a	6	17
b	7	18
c	8	19
d	9	20
e	11	21
f	12	23
g	13	24
decimal point	14	25

- Select **Pin/Location/Chip** (Assign menu) and, using the tables given above, assign pin numbers to all input and output ports in your design. For example,

```

OSC = 91
/RESET = 28
PB = 29
SW7 = 41 ... SW0 = 33
MSB7 = 6 ... MSB0 = 14
LSB7 = 17 ... LSB0 = 25

```

- Save and Check your design. (The project should be set to your top-level design.) When it checks without errors, compile the design using Timing SNF Extraction. If you receive warnings or errors, you can select the message and press the Help on Message button if you aren't sure how to fix the problem. You can also select the Locate button to locate the problem in your schematic.

## VERIFYING TIMING OF 24-BIT COUNTER

We should check that the 24-bit counter can actually operate with a clock frequency of 25 MHz.

- Select **Timing Analyzer** (MAX+plusII menu) and choose **Registered Performance** (Analysis menu). When the dialog box comes up, press the Start button. Since this design uses 2 clocks, OSC and Q23, the Timing Analyzer tools will calculate the maximum clock frequency for each clock. We only need to verify that the OSC signal can be  $\geq 25$  MHz.

After the Timing Analyzer has run, choose OSC from the Clock pull-down box. You should see a maximum clock frequency which is greater than 25 MHz.

## **VERIFYING THE FINAL DESIGN**

It is not necessary to do a complete simulation on the top-level design. The 24-bit counter would take excessive computer resources to simulate completely. If you desire to simulate your design, you should test the 24-bit counter and the remainder of the circuit separately.

Your TA will configure the Altera Education Board and help you download your circuit to the EPF10K20 device. The SRAM Object File (.sof) is used to program the FLEX10K family of devices rather than the Programmer Object File (.pof) which is used to program the MAX 7000S family of devices. Thus, you will need to transfer the .sof file to the lab PC for downloading.

## **LAB REPORT**

Each individual will be required to submit a lab report. Use the format specified in the "Lab Report Information" document available on the class web page. Include the following items in your lab report:

- Lab cover sheet with TA verification for circuit simulation and performance
- Altera schematic for your Fibonacci sub-circuit. (This will be similar to Figure 1.)
- Simulation waveforms showing the functional simulation of your Fibonacci sub-circuit, similar to Figure 2.
- Altera schematic for your top-level schematic, similar to Figure 3.

 


FIGURE 1

 


FIGURE 2



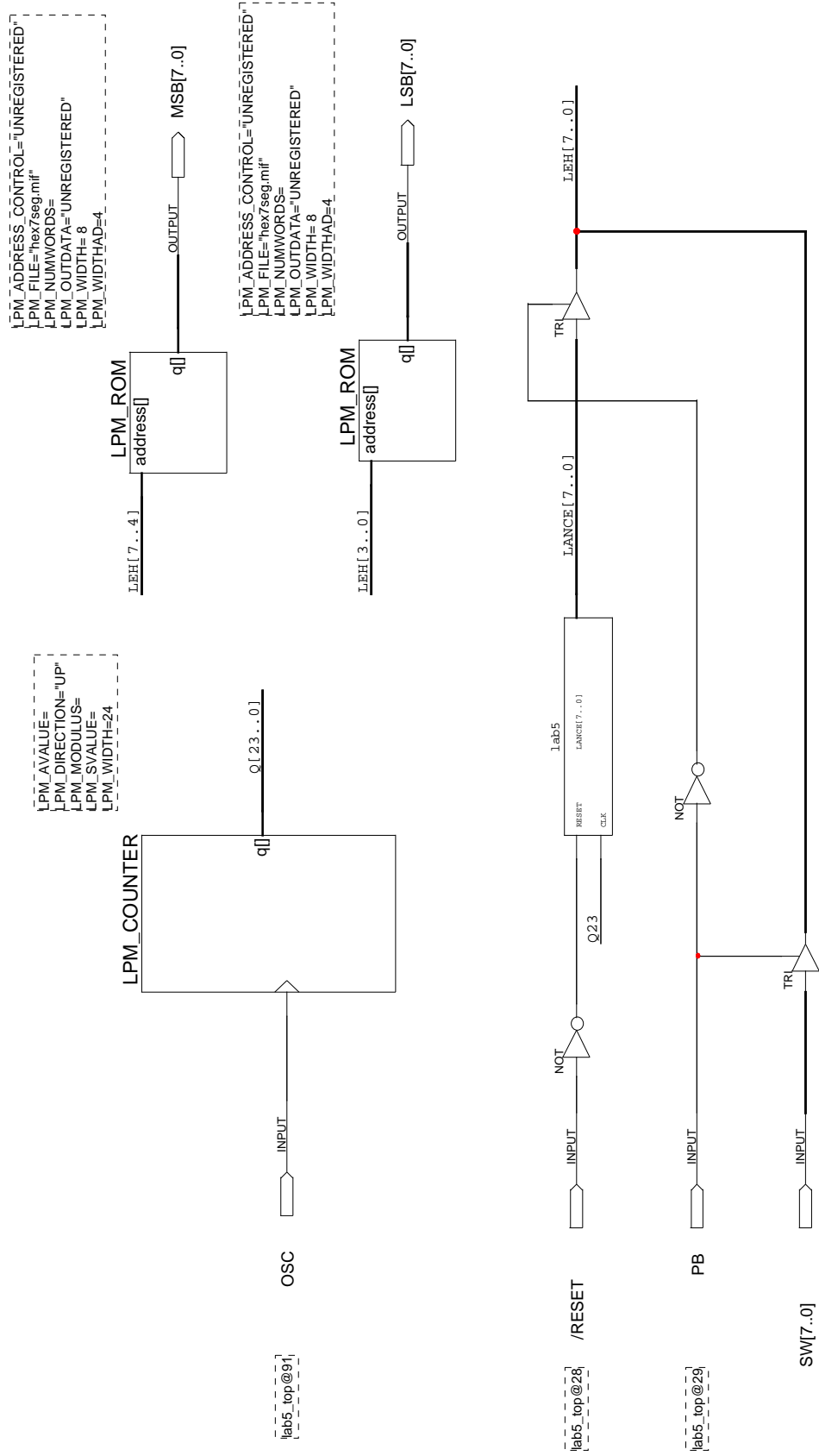


FIGURE 3