


Homework 3 Solutions

Problem 1:

The characterization of required gates is summarized below.


**** Inverter (a)! ****

| input | g[norm] | p[norm] | g[ps] | p[ps] |
|-------|---------|---------|--------|---------|
| a | 1.0000 | 1.4781 | 8.1413 | 12.0340 |

 


**** Nand2 (a*b)! ****

| input | g[norm] | p[norm] | g[ps] | p[ps] |
|-------|---------|---------|--------|---------|
| a | 1.1929 | 2.2218 | 9.7117 | 18.0880 |
| b | 1.1514 | 3.1414 | 9.3740 | 25.5750 |

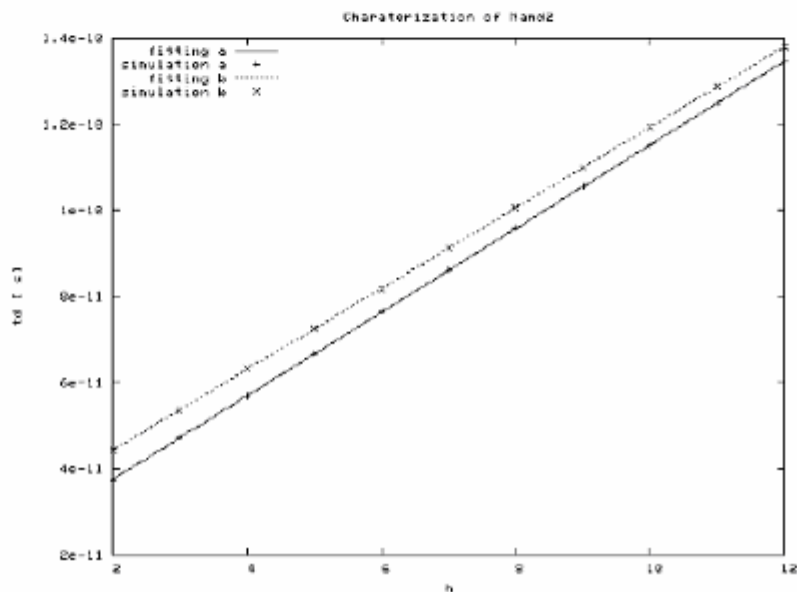


**** AOI [a+(b*c)]! ****

| input | g[norm] | p[norm] | g[ps] | p[ps] |
|-------|---------|---------|---------|---------|
| a | 1.5701 | 6.6493 | 12.7830 | 54.1340 |
| b | 1.6424 | 3.1206 | 13.3710 | 25.4060 |
| c | 1.5593 | 3.7645 | 12.6950 | 30.6480 |

 

**** OAI [a*(b+c)]! ****

| input | g[norm] | p[norm] | g[ps] | p[ps] |
|-------|---------|---------|---------|---------|
| a | 1.2089 | 3.9877 | 9.8419 | 32.4650 |
| b | 1.5611 | 3.3255 | 12.7090 | 27.0740 |
| c | 1.5732 | 4.4000 | 12.8080 | 35.8220 |

 

Problem 2:

Using the gate characterization of problem 1, the optimal stage effort, f_o can be computed.

$$f_o = (GBH)^{1/6} = [(g_{OAI}^3 g_{AOI}^2 g_{NAND2})(2^5)(64/1)]^{1/6} = 5.44$$

The corresponding gate sizes are (from the output to the input):

$$C_{OAI_6} = b C_{out} g / f_o = (2)(64C_{in})(1.57) / 5.44 = 36.9C_{in}$$

$$C_{AOI_5} = (2)(36.9C_{in})(1.66) / 5.44 = 22.5C_{in}$$

$$C_{OAI_4} = (2)(22.5C_{in})(1.57) / 5.44 = 13.0C_{in}$$

$$C_{AOI_3} = (2)(13.0C_{in})(1.66) / 5.44 = 7.93C_{in}$$

$$C_{OAI_2} = (2)(7.93C_{in})(1.57) / 5.44 = 4.57C_{in}$$

$$C_{NAND2_1} = (4.57C_{in})(1.19) / 5.44 = 1.0C_{in}$$

The total delay of the path:

$$\begin{aligned} D &= (6 f_o + 3p_{OAI} + 2p_{AOI} + p_{NAND2}) \tau = \\ &= [6 (5.44) + 3 (4.40) + 2 (3.67) + 2.22] (8.14ps) = 451ps \end{aligned}$$

Problem 3:

(a) With LE sizing, it is observed that all nodes at the same stage level have equal loading. Therefore, the branching factor at each node can be easily computed as:

$$b = (g_{AOI/OAI} + g_{INV}) / g_{AOI/OAI}$$

The detail spreadsheet is attached below. The computation of G , B , H and gate sizes are straight-forward. The computation of f_{opt} will lead to circular recurrence. To avoid that, f_{est} is used for sizing. The solution is reached when $f_{est} = f_{opt}$. It is indicated by *Error* cell.

| | NAND2 | AOI | OAI | INV | tau |
|----------|-------|------|------|------|------|
| g | 1.19 | 1.66 | 1.57 | 1 | 8.14 |
| p | 2.22 | 3.67 | 4.4 | 1.48 | |

| | | | |
|--------------|------|--------------|-------|
| f_est | 5.13 | Error | 0.000 |
| Cin | 1.00 | | |

| Stage | Off-path | On-path | Branch |
|-------------|--------------|---------------|--------|
| 1 | | NAND2 1.00 | 1.00 |
| 2 | INV 1.68 | OAI 2.63 | 1.64 |
| 3 | INV 3.24 | AOI 5.37 | 1.60 |
| 4 | INV 6.46 | OAI 10.15 | 1.64 |
| 5 | INV 12.47 | AOI 20.70 | 1.60 |
| Load | 64 | 64 | |

| | |
|------------------|------|
| G_calc | 8.08 |
| B_calc | 6.88 |
| H_calc | 64 |
| fopt_calc | 5.13 |

| | | |
|--------------------|-------|--------|
| | (tau) | (ps) |
| Total Delay | 44.02 | 358.37 |

(b) Using the netlist (included in the end), SPICE simulation data is obtained. Note that Cin is set to 1 μ m.

```
$DATA1 SOURCE='HSPICE' VERSION='U-2003.03-SP1 '
.TITLE '* takehome exam5'
tdf          tdr          tda          q          e
3.505e-10    3.535e-10    3.520e-10    -8.204e-13  8.204e-13
```

The worst-case delay goes through the bottom AOI of stage 5. The resulting delay is 353.5ps. It agrees very well to the estimation (358.4ps).