 


# VLSI Arithmetic


## Lecture 9: Carry-Save and Multi-Operand Addition




Prof. Vojin G. Oklobdzija  
University of California

<http://www.ece.ucdavis.edu/acsel>

 Motorola's PowerPC™ 603 RISC Microprocessor




# Carry-Save Addition\*

 


A ripple-carry adder turns into a carry-save adder if the carries are saved (stored) rather than propagated.

*\*from Parhami*

# Carry-Save Addition\*

 

 
Carry-propagate adder (CPA) and carry-save adder (CSA) functions in dot notation.



Specifying full- and half-adder blocks, with their inputs and outputs, in dot notation.

*\*from Parhami*

# Carry-Save Addition\*

 


Total cost = 7-bit adder + 28 FAs + 1 HA

*\*from Parhami*

**Addition of seven 6-bit numbers in dot notation.**

# Carry-Save Addition\*

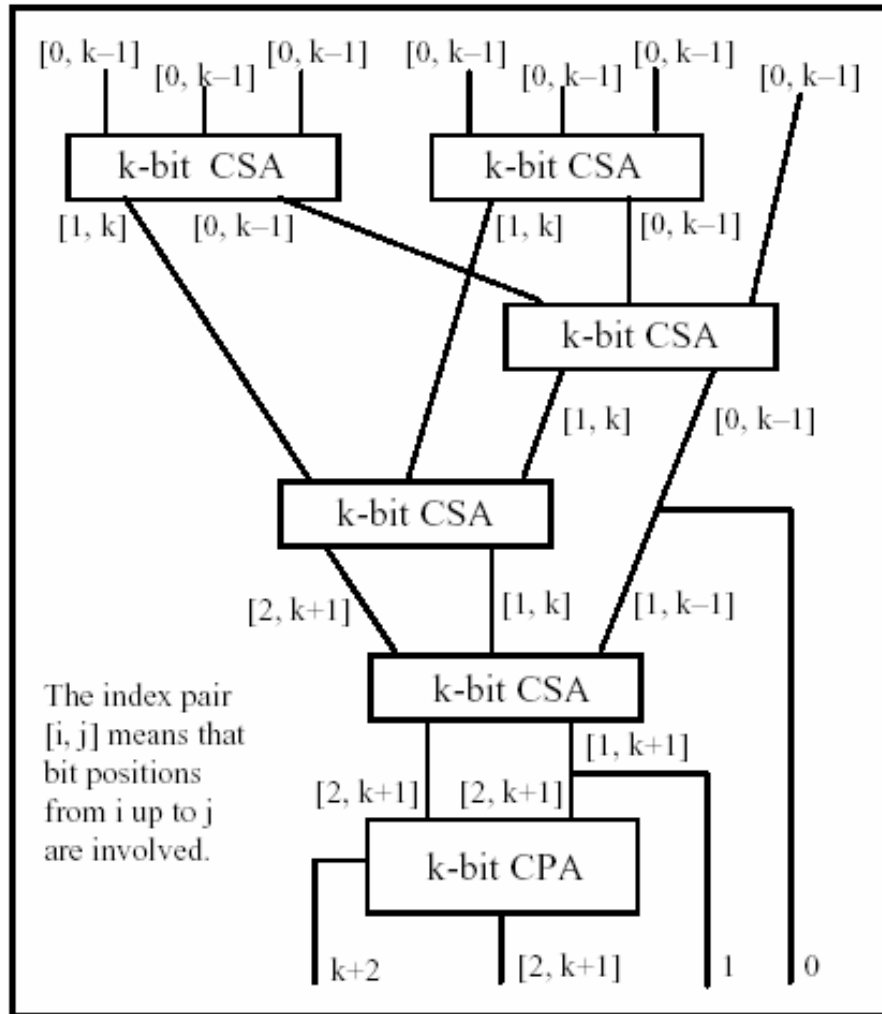


Adding seven  $k$ -bit numbers and the CSA/CPA widths required.

*\*from Parhami*

# Carry-Save Addition \*

## Wallace and Dadda Trees

 

$$h(n) = 1 + h(\lceil 2n/3 \rceil)$$

$$n(h) = \lfloor 3n(h-1)/2 \rfloor$$

$$2 \times 1.5^{h-1} < n(h) \leq 2 \times 1.5^h$$

*\*from Parhami*

# Carry-Save Addition \*

The maximum number  $n(h)$  of inputs for an  $h$ -level carry-save-adder tree

$h$	$n(h)$	$h$	$n(h)$	$h$	$n(h)$
0	2	7	28	14	474
1	3	8	42	15	711
2	4	9	63	16	1066
3	6	10	94	17	1599
4	9	11	141	18	2398
5	13	12	211	19	3597
6	19	13	316	20	5395

*\*from Parhami*

# Carry-Save Addition \*

In a Wallace tree, we reduce the number of operands at the earliest possible opportunity


In a Dadda tree, we reduce the number of operands at the latest possible opportunity that leads to no added delay (target the next smaller number in Table 8.1)

$h$	$n(h)$	$h$	$n(h)$	$h$	$n(h)$
0	2	7	28	14	474
1	3	8	42	15	711
2	4	9	63	16	1066
3	6	10	94	17	1599
4	9	11	141	18	2398
5	13	12	211	19	3597
6	19	13	316	20	5395

*\*from Parhami*



# Carry-Save Addition \*

 


Total cost = 7-bit adder + 28 FAs + 1 HA

*\*from Parhami*

Adding seven 6-bit numbers using Dadda's strategy.

# Carry-Save Addition \*

 

Total cost = 7-bit adder + 26 FAs + 3 HA

*\*from Parhami*


# Parallel Counters \*

Single-bit full-adder = (3; 2)-counter

Circuit reducing 7 bits to their 3-bit sum = (7; 3)-counter

Circuit reducing  $n$  bits to their  $\lceil \log_2(n + 1) \rceil$ -bit sum

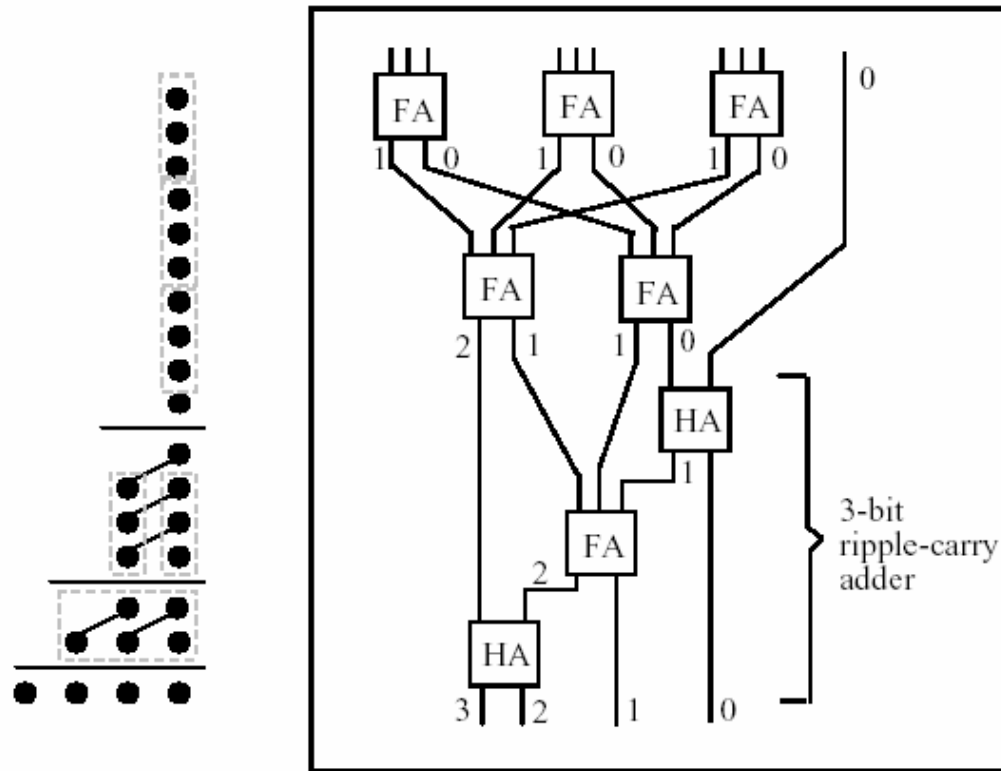=  $(n; \lceil \log_2(n + 1) \rceil)$ -counter



*\*from Parhami*

Fig. 8.16 A 10-input parallel counter also known as a (10; 4)-counter.

# Parallel Counters and Compressors \*


 


Fig. 8.17 Dot notation for a  $(5, 5; 4)$ -counter and the use of such counters for reducing five numbers to two numbers.

## $(n; 2)$ -counters

 

*\*from Parhami*

# Adding Multiple Signed Numbers \*

Extended positions	Sign	Magnitude positions							
$x_{k-1}$	$x_{k-1}$	$x_{k-1}$	$x_{k-1}$	$x_{k-1}$	$x_{k-1}$	$x_{k-2}$	$x_{k-3}$	$x_{k-4}$	$\dots$
$y_{k-1}$	$y_{k-1}$	$y_{k-1}$	$y_{k-1}$	$y_{k-1}$	$y_{k-1}$	$y_{k-2}$	$y_{k-3}$	$y_{k-4}$	$\dots$
$z_{k-1}$	$z_{k-1}$	$z_{k-1}$	$z_{k-1}$	$z_{k-1}$	$z_{k-1}$	$z_{k-2}$	$z_{k-3}$	$z_{k-4}$	$\dots$

(a)

Extended positions	Sign	Magnitude positions							
1	1	1	1	0	$\bar{x}_{k-1}$	$x_{k-2}$	$x_{k-3}$	$x_{k-4}$	$\dots$
					$\bar{y}_{k-1}$	$y_{k-2}$	$y_{k-3}$	$y_{k-4}$	$\dots$
					$\bar{z}_{k-1}$	$z_{k-2}$	$z_{k-3}$	$z_{k-4}$	$\dots$
	1								

(b)

*\*from Parhami*

**Fig. 8.18** Adding three 2's-complement numbers using sign extension (a) or by the method based on negatively weighted sign bits (b).

# Multi-Operand Addition

---

from

***Digital Arithmetic, Morgan-Kaufman Publishers, 2004***

**Miloš Ercegovic and Tomàs Lang**

- 
- Bit-arrays for unsigned and signed operands
    - simplification of sign extension
  - Reduction by rows and by columns
    - $[p:2]$  modules and  $[p:2]$  adders for reduction by rows
    - $(p:q)$  counters and multicolumn counters for reduction by columns
  - Sequential implementation
  - Combinational implementation
    - Reduction by rows: arrays of adders (linear arrays, adder trees)
    - Reduction by columns:  $(p:q)$  counters
    - systematic design method for reduction by columns with  $(3:2)$  and  $(2:2)$  counters
  - Pipelined adder arrays
  - Partially combinational implementation

## BIT ARRAYS FOR UNSIGNED AND SIGNED OPERANDS

---

2

$$\begin{array}{cccccccc} a_0 & a_0 & a_0 & a_0 & \cdot & a_1 & a_2 & \cdots & a_n \\ b_0 & b_0 & b_0 & b_0 & \cdot & b_1 & b_2 & \cdots & b_n \\ c_0 & c_0 & c_0 & c_0 & \cdot & c_1 & c_2 & \cdots & c_n \\ d_0 & d_0 & d_0 & d_0 & \cdot & d_1 & d_2 & \cdots & d_n \\ e_0 & e_0 & e_0 & e_0 & \cdot & e_1 & e_2 & \cdots & e_n \\ \underbrace{\hspace{1.5cm}} & & & & & & & & \end{array}$$

sign extension

Figure 3.1: SIGN-EXTENDED ARRAY FOR  $m = 5$ .



 


Figure 3.2: SIMPLIFYING SIGN-EXTENSION: (a) GENERAL CASE. (b) EXAMPLE OF SIMPLIFYING ARRAY WITH  $m = 5$ .

# REDUCTION

---

- By rows
- By columns

# $[p:2]$ ADDERS FOR REDUCTION BY ROWS

 


Figure 3.3: A  $[p:2]$  adder: (a) Input-output bit-matrix. (b)  $k$ -column  $[p:2]$  module decomposition.

# MODEL OF $[p:2]$ MODULE

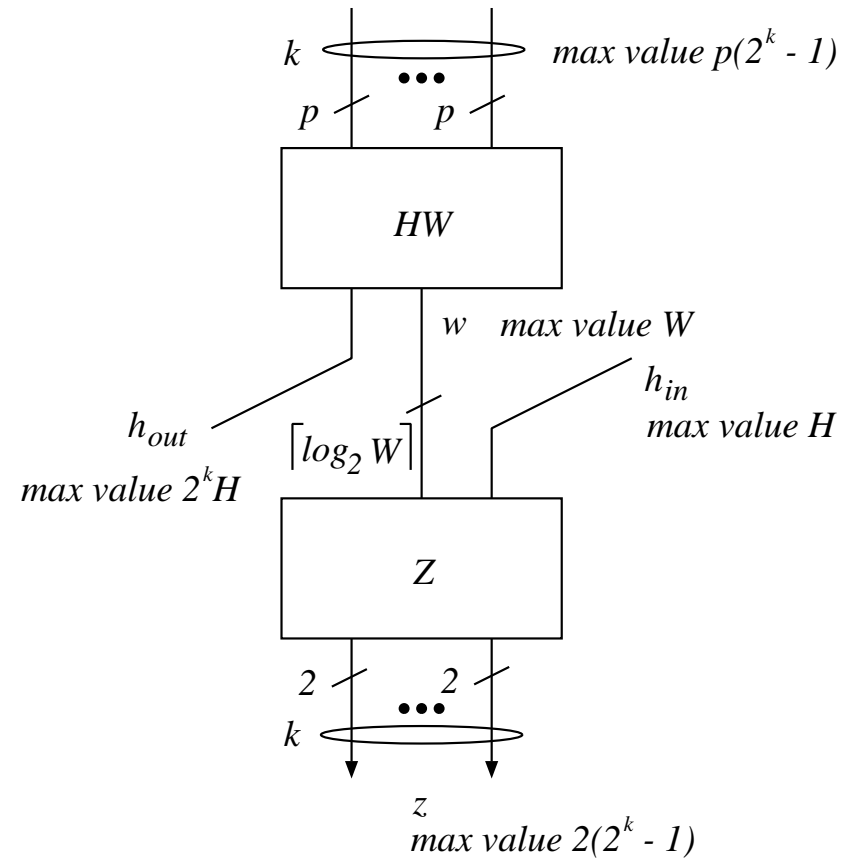


Figure 3.4: A model of a  $[p:2]$  module.

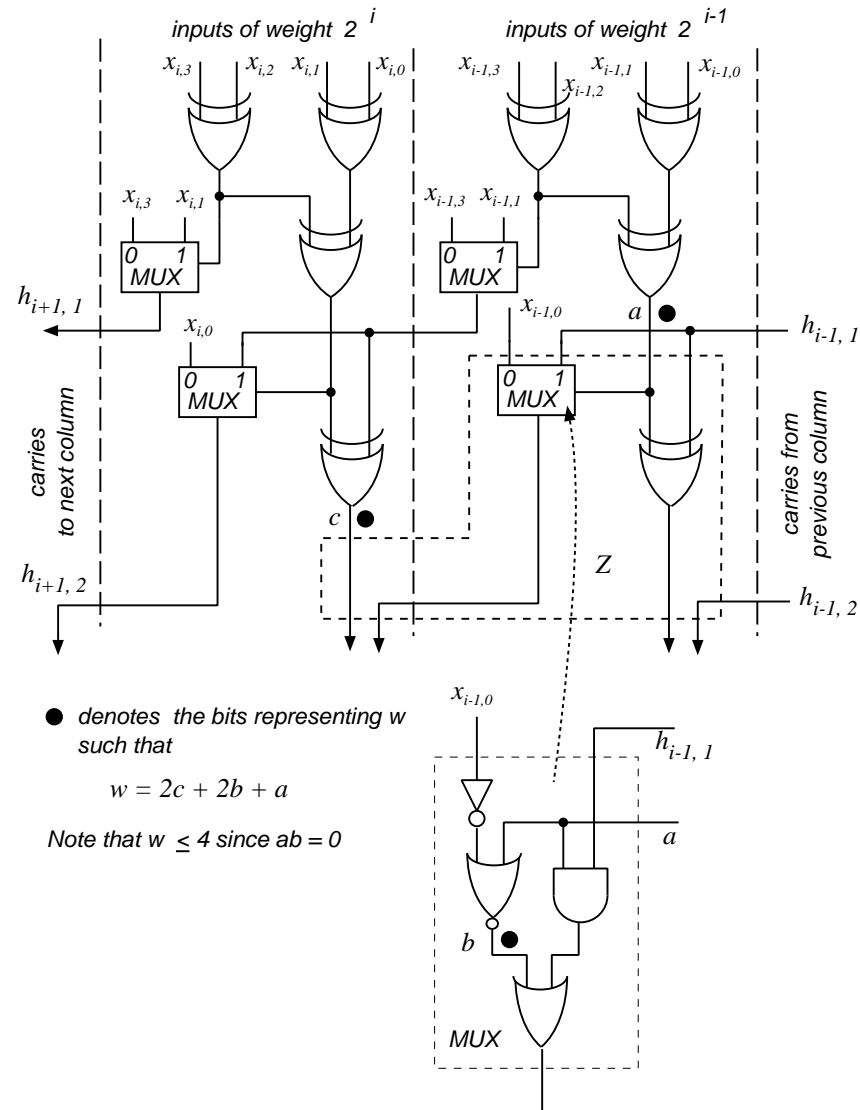


Figure 3.5: Gate network implementation of [4:2] module.

 


Figure 3.6: (a) [5:2] module. (b) [7:2] module.

# $(p:q]$ COUNTERS FOR REDUCTION BY COLUMNS

---

$$\sum_{i=0}^{p-1} x_i = \sum_{j=0}^{q-1} y_j 2^j$$

$$2^q - 1 \geq p, \text{ i.e., } q = \lceil \log_2(p + 1) \rceil$$

 


Figure 3.7: (a)  $(p:q]$  reduction. (b) Counter representation.

# IMPLEMENTATION OF $(p:q]$ COUNTERS

 


Figure 3.8: Implementation of  $(7:3]$  counter by an array of full adders.



 


Figure 3.9: Gate network of a (7:3] counter.

# MULTICOLUMN COUNTER

---

$$(p_{k-1}, p_{k-2}, \dots, p_0 : q]$$

$$v = \sum_{i=0}^{k-1} \sum_{j=1}^{p_i} a_{ij} 2^i \leq 2^q - 1$$

 


Figure 3.10: (a) (5,5:4] counter. (b) (1,2,3:4] counter.

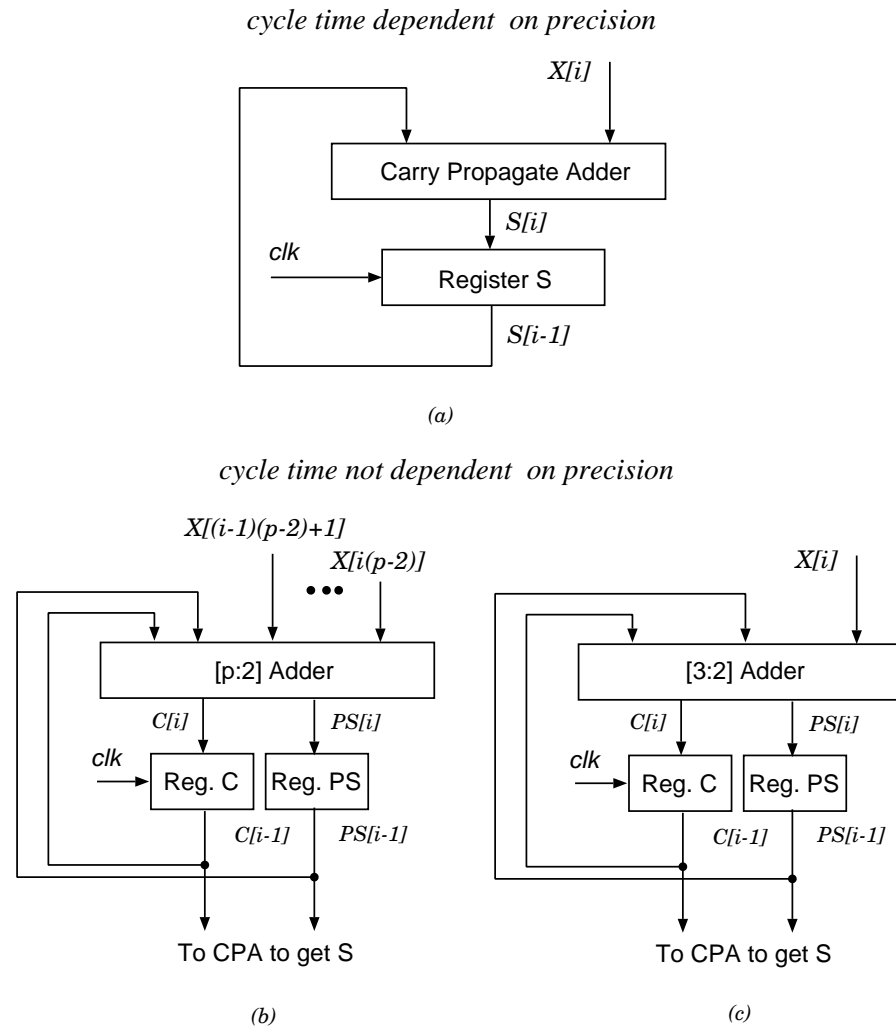


Figure 3.11: SEQUENTIAL MULTIOPERAND ADDITION: a) WITH CONVENTIONAL ADDER. b) WITH  $[p:2]$  ADDER. c) WITH  $[3:2]$  ADDER.

- Reduction by rows: array of adders
  - Linear array
  - Adder tree
- Reduction by columns with  $(p:q]$  counters

 


Figure 3.12: LINEAR ARRAY OF  $[p:2]$  ADDERS FOR MULTIOPERAND ADDITION.

# ADDER TREE

- $k$  - the number of  $[p:2]$  CS adders for  $m$  operands:

$$pk = m + 2(k - 1)$$

$$k = \left\lceil \frac{m - 2}{p - 2} \right\rceil \quad [p:2] \text{ carry-save adders}$$

- The number of adder levels

 


Figure 3.13: Construction of a  $[p:2]$  carry-save adder tree.

$$m_l = p \left\lfloor \frac{m_{l-1}}{2} \right\rfloor + m_{l-1} \bmod 2$$

## NUMBER OF LEVELS (cont.)

---

Table 3.1: [3:2] Reduction sequence.

$l$	1	2	3	4	5	6	7	8	9
$m_l$	3	4	6	9	13	19	28	42	63

$$m_l \approx \frac{p^l}{2^{l-1}}$$

$$l \approx \log_{p/2}(m_l/2)$$

 


Figure 3.14: [3:2] adder tree for 9 operands (magnitudes with  $n = 3$ ).



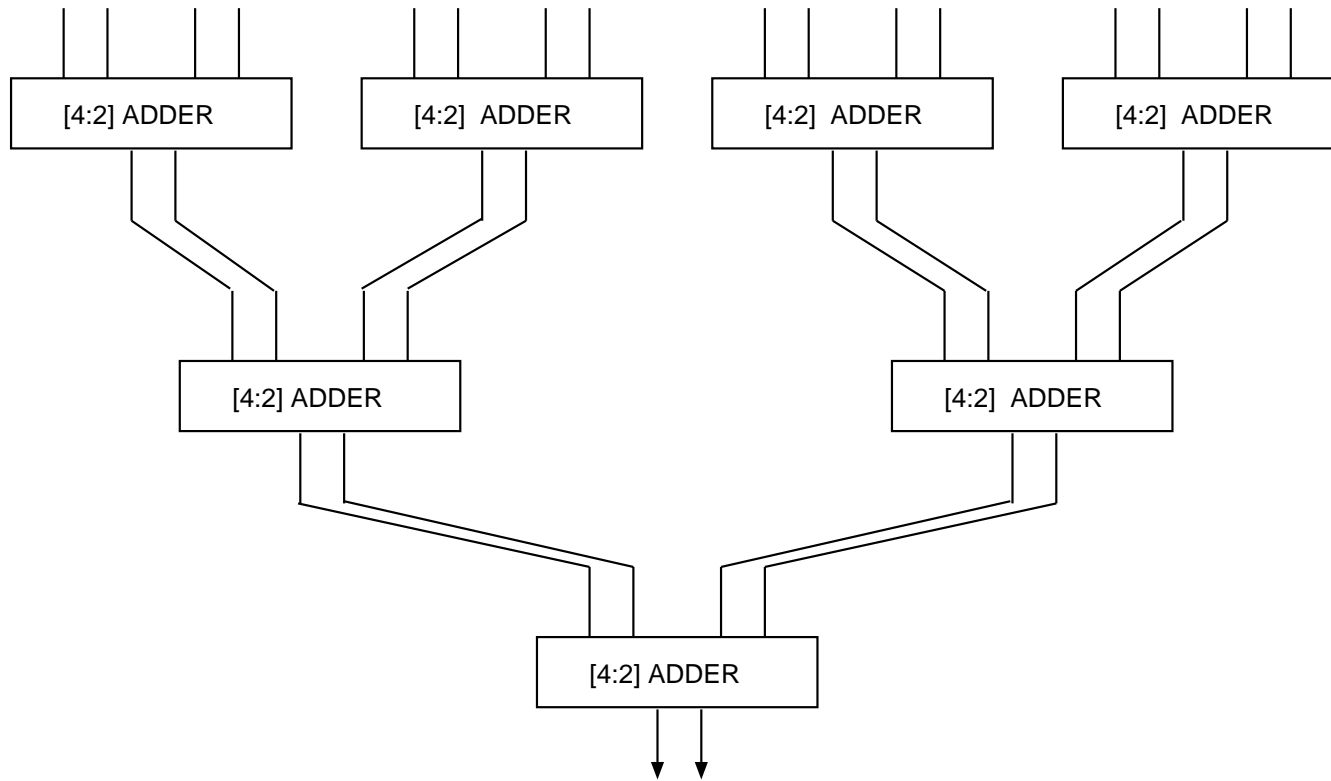


Figure 3.15: Tree of [4:2] adders for  $m = 16$ .

# REDUCTION BY COLUMNS WITH (p:q] COUNTERS

---

$$\begin{array}{rcccc}
 & 1 & 0 & 1 & 1 \\
 & 0 & 0 & 1 & 0 \\
 & 1 & 0 & 0 & 1 \\
 & 0 & 1 & 1 & 0 \\
 & 1 & 0 & 1 & 0 \\
 & 1 & 1 & 1 & 1 \\
 & 0 & 1 & 1 & 0 \\
 \hline
 & 0 & 1 & 0 & 1 \\
 & 0 & 1 & 1 & 1 \\
 1 & 0 & 1 & 0 &
 \end{array}$$

Figure 3.16: Example of reduction using (7:3] counters.

# NUMBER OF COUNTER LEVELS

$$m_1 = p$$

$$m_l = p \left\lfloor \frac{m_{l-1}}{q} \right\rfloor + m_{l-1} \bmod q$$

$$l \approx \log_{p/q}(m_l/q)$$

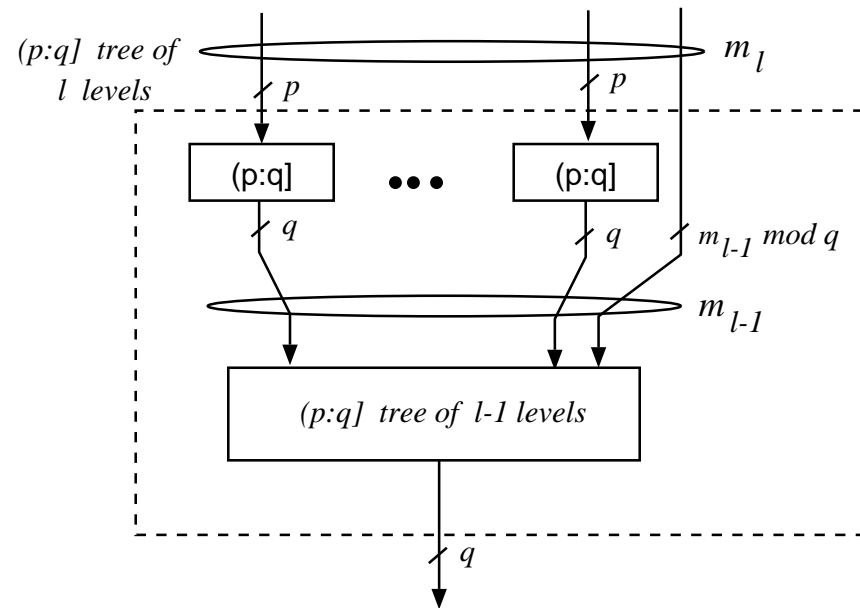


Figure 3.17: Construction of  $(p:q)$  reduction tree.

Table 3.2: Sequence for (7:3] counters

Number of levels	1	2	3	4	...
Max. number of rows	7	15	35	79	...

 


Figure 3.18: Multilevel reduction with  $(7:3]$  counters

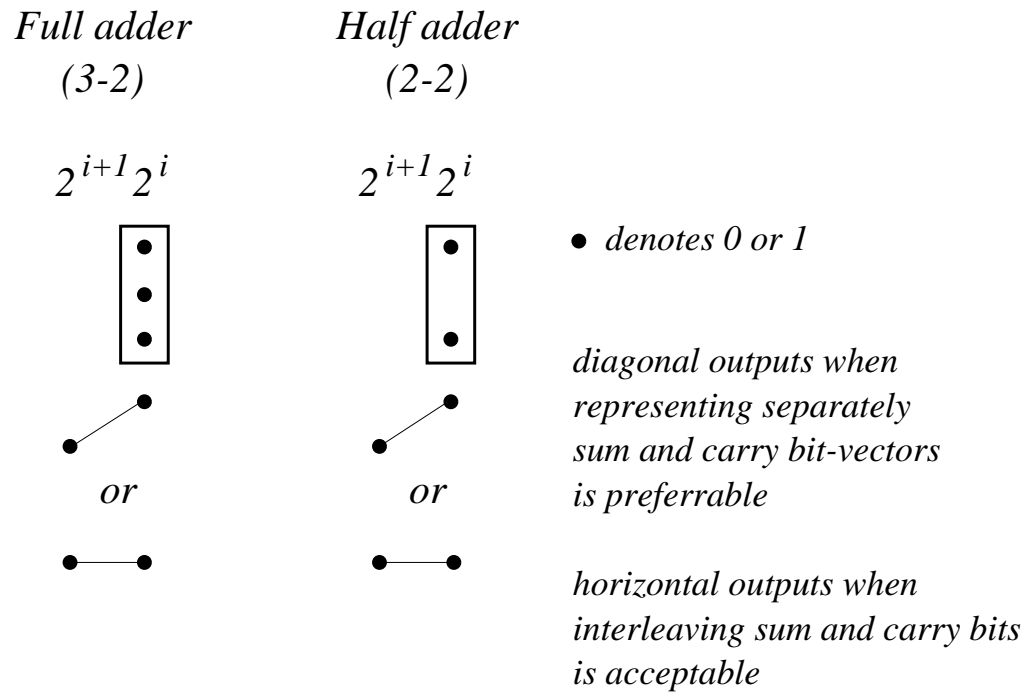


Figure 3.19: Full adder and half adder as (3:2] and (2:2] counters.

 


Figure 3.20: Reduction process.

## RELATION AT LEVEL $l$

---

$e_i$  – number of bits in column  $i$

$f_i$  – number of full adders in column  $i$

$h_i$  – number of half adders in column  $i$

$$e_i - 2f_i - h_i + f_{i-1} + h_{i-1} = m_{l-1}$$

resulting in

$$2f_i + h_i = e_i - m_{l-1} + f_{i-1} + h_{i-1} = p_i$$

Solution producing min number of carries:

$$f_i = \lfloor p_i/2 \rfloor \quad h_i = p_i \bmod 2$$



	$i$						
	6	5	4	3	2	1	0
$l = 4$							
$e_i$			8	8	8	8	8
$m_3$			6	6	6	6	6
$h_i$			0	0	0	1	0
$f_i$			2	2	2	1	1
$l = 3$							
$e_i$		2	6	6	6	6	6
$m_2$		4	4	4	4	4	4
$h_i$		0	0	0	0	1	0
$f_i$		0	2	2	2	1	1
$l = 2$							
$e_i$		4	4	4	4	4	4
$m_1$		3	3	3	3	3	3
$h_i$		0	0	0	0	0	1
$f_i$		1	1	1	1	1	0
$l = 1$							
$e_i$	1	3	3	3	3	3	3
$m_0$	2	2	2	2	2	2	2
$h_i$	0	0	0	0	0	0	1
$f_i$	0	1	1	1	1	1	0

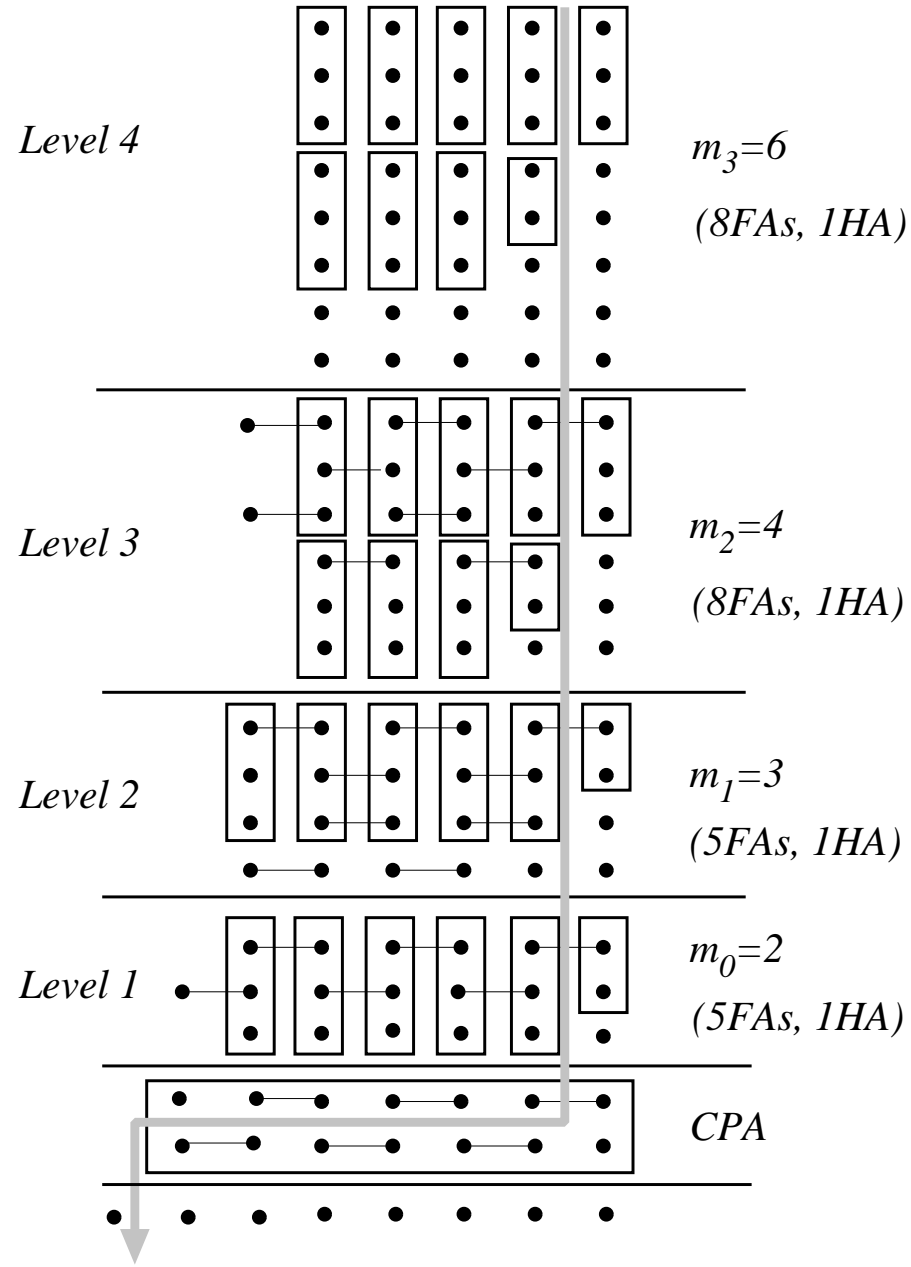


Figure 3.21: Reduction by columns of 8 5-bit magnitudes. Cost of reduction: 26 FAs and 4 HAs.

EXAMPLE: ARRAY FOR  $f = a + 3b + 3c + d$ 

---

Operands in  $[-4,3)$ . Result range:

$$-4 + (-12) + (-12) - 4 = -32 \leq f \leq 3 + 9 + 9 + 3 = 24$$

$$\begin{array}{r|llllll}
 a & a_2 & a_2 & a_2 & a_2 & a_1 & a_0 \\
 b & b_2 & b_2 & b_2 & b_2 & b_1 & b_0 \\
 2b & b_2 & b_2 & b_2 & b_1 & b_0 & 0 \\
 c & c_2 & c_2 & c_2 & c_2 & c_1 & c_0 \\
 2c & c_2 & c_2 & c_2 & c_1 & c_0 & 0 \\
 d & d_2 & d_2 & d_2 & d_2 & d_1 & d_0
 \end{array}$$

transformed into


$$\begin{array}{r|llll}
 a & & a'_2 & a_1 & a_0 \\
 & & -1 & & \\
 b & & b'_2 & b_1 & b_0 \\
 & & -1 & & \\
 2b & b'_2 & b_1 & b_0 & \\
 & -1 & & & \\
 c & & c'_2 & c_1 & c_0 \\
 & & -1 & & \\
 2c & c'_2 & c_1 & c_0 & \\
 & -1 & & & \\
 d & & d'_2 & d_1 & d_0 \\
 & & -1 & &
 \end{array}$$

FINAL BIT MATRIX

---

$$\begin{array}{cccccc} 1 & 0 & b'_2 & a'_2 & a_1 & a_0 \\ & & c'_2 & b'_2 & b_1 & b_0 \\ & & & b_1 & b_0 & \\ & & & c'_2 & c_1 & c_0 \\ & & & c_1 & c_0 & \\ & & & d'_2 & d_1 & d_0 \end{array}$$

	<i>i</i>					
	5	4	3	2	1	0
$l = 3$						
$e_i$	1	0	2	6	6	4
$m_2$	4	4	4	4	4	4
$h_i$	0	0	0	1	0	0
$f_i$	0	0	0	1	1	0
$l = 2$						
$e_i$	1	0	4	4	4	4
$m_1$	3	3	3	3	3	3
$h_i$	0	0	0	0	0	1
$f_i$	0	0	1	1	1	0
$l = 1$						
$e_i$	1	1	3	3	3	3
$m_0$	2	2	2	2	2	1*
$h_i$	0	0	0	0	0	0
$f_i$	0	0	1	1	1	1

 

Digital Arithmetic - Ercegovac/Lang 2003 Figure 3.22: Reduction array  $f = a + 3b + 3c + d$ .

# PIPELINED LINEAR ARRAY

 


Figure 3.23: Pipelined arrays with [4:2] adders for computing  $S[j] = \sum_{i=1}^8 X[i, j]$ ,  $j = 1, \dots, N$ : (a) Linear array. (b) Tree array.



# PARTIALLY COMBINATIONAL IMPLEMENTATION

 


Figure 3.24: Partially combinational scheme for summation of 4 operands per iteration: (a) Nonpipelined. (b) Pipelined.


 
 


Figure 3.25: Scheme for summation of  $q$  operands per iteration.

 


# VLSI Arithmetic

## Lecture 9b:


## Sign-Digit Arithmetic

**Prof. Vojin G. Oklobdzija**  
**University of California**

<http://www.ece.ucdavis.edu/acsel>

 

 Motorola's PowerPC™ 603 RISC Microprocessor



# Sign-Digit Addition

---

from

***Digital Arithmetic, Morgan-Kaufman Publishers, 2004***

**Miloš Ercegovic and Tomàs Lang**

## SIGNED-DIGIT ADDITION

---

- Uses signed-digit representation (redundant)

$$x = \sum_0^{n-1} x_i r^i$$

with digit set

$$D = \{-a, \dots, -1, 0, 1, \dots, a\}$$

- Limits carry propagation to next position
- Addition algorithm:

$$\begin{aligned} \text{Step 1: } x + y &= w + t \\ x_i + y_i &= w_i + r t_{i+1} \end{aligned}$$

$$\begin{aligned} \text{Step 2: } s &= w + t \\ s_i &= w_i + t_i \end{aligned}$$

- No carry produced in Step 2

## SD ADDER

 


Figure 2.34: Signed-digit addition.

## CASES CONSIDERED

---

**Case A** : two SD operands; result SD

Step 1:

$$(t_{i+1}, w_i) = \begin{cases} (0, x_i + y_i) & \mathbf{if} \ -a + 1 \leq x_i + y_i \leq a - 1 \\ (1, x_i + y_i - r) & \mathbf{if} \ x_i + y_i \geq a \\ (-1, x_i + y_i + r) & \mathbf{if} \ x_i + y_i \leq -a \end{cases}$$

- algorithm modified for  $r = 2$

**Case B** : two conventional operands; result SD

**Case C** : one conventional, one SD; result SD

RECODING 1:

$$\begin{aligned}x_i + y_i &= 2h_{i+1} + z_i \in \{-2, -1, 0, 1, 2\} \\h_i &\in \{0, 1\}, z_i \in \{-2, -1, 0\} \\q_i &= z_i + h_i \in \{-2, -1, 0, 1\}\end{aligned}$$

RECODING 2:

$$\begin{aligned}q_i = z_i + h_i &= 2t_{i+1} + w_i \in \{-2, -1, 0, 1\} \\t_i &\in \{-1, 0\}, w_i \in \{0, 1\}\end{aligned}$$

THE RESULT:  $s_i = w_i + t_i \in \{-1, 0, 1\}$



# METHOD 1 SD ADDER

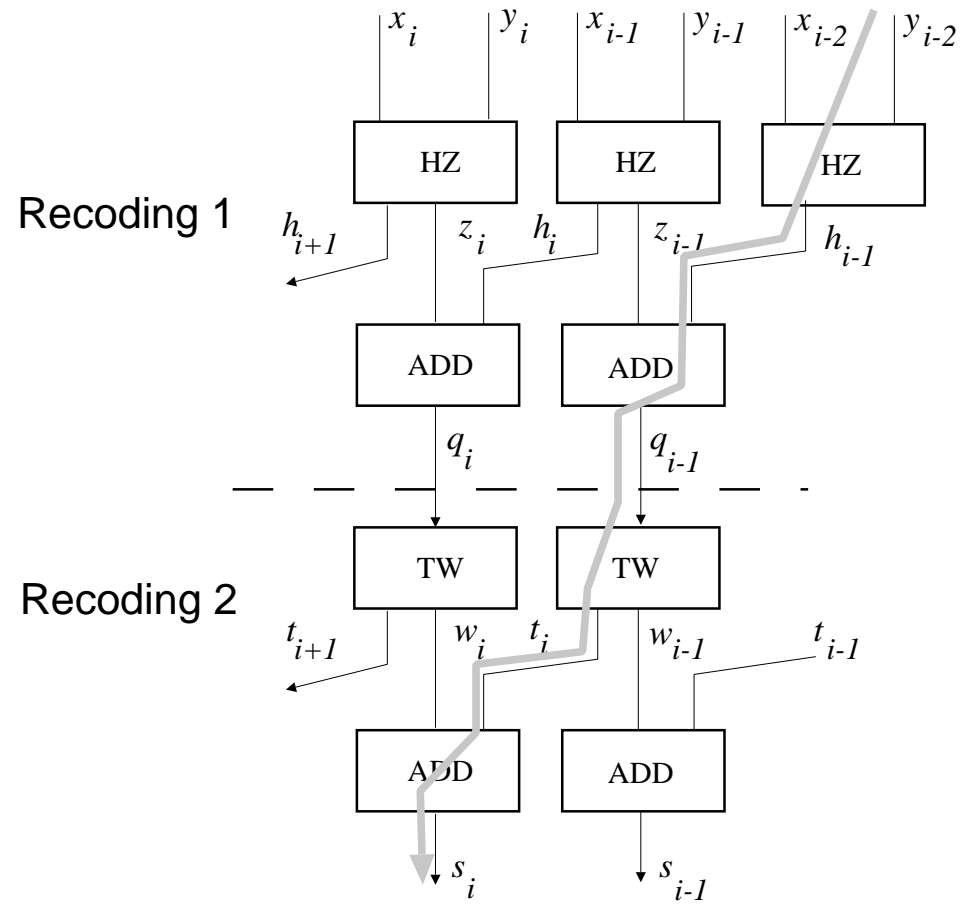


Figure 2.35: Double recoding method for signed-bit addition

# SIGNED BINARY ADDITION: METHOD 2 (Using Previous Digit)

---

$$P_i = \begin{cases} 0 & \text{if } (x_i, y_i) \text{ both nonnegative} \\ & \text{(which implies } t_{i+1} \geq 0) \\ 1 & \text{otherwise } (t_{i+1} \leq 0) \end{cases}$$

$x_i + y_i$	$P_{i-1}$	$t_{i+1}$	$w_i$
2	-	1	0
1	$0(t_i \geq 0)$	1	-1
1	$1(t_i \leq 0)$	0	1
0	-	0	0
-1	$0(t_i \geq 0)$	0	-1
-1	$1(t_i \leq 0)$	-1	1
-2	-	-1	0

# METHOD 2 SD ADDER

 


Figure 2.36: Signed-bit addition using the information from previous digit

## Example

---

X 0 1 1 1  $\bar{1}$  1 0  $\bar{1}$  1

Y 0 1 1 0  $\bar{1}$  0 1 0 1

P 0 0 0 0 1 0 0 1 0

W 0 0 0 1 0  $\bar{1}$  1  $\bar{1}$  0

T 0 1 1 0  $\bar{1}$  1 0 0 1 0

S 1 1 0 0 1  $\bar{1}$  1 0 0

- Case C:  $x_i \in \{0, 1\}$ ,  $y_i, s_i \in \{-1, 0, 1\}$
- Code: borrow-save  $y_i = y_i^+ - y_i^-$ ,  $y_i^+, y_i^- \in \{0, 1\}$ , sim. for  $s_i$
- $x_i + y_i \in \{-1, 0, 1, 2\}$ : recode to  $(t_{i+1}, w_i)$ ,  $t_{i+1} \in \{0, 1\}$ ,  $w_i \in \{-1, 0\}$

$$x_i + y_i^+ - y_i^- = 2t_{i+1} + w_i$$

$x_i + y_i$	-1	0	1	2
$w_i$	-1	0	-1	0
$t_{i+1}$	0	0	1	1

## SWITCHING FUNCTIONS FOR $t_{i+1}$ AND $w_i$

---

$x_i$	$y_i^+$	$y_i^-$	$x_i + y_i$	$t_{i+1}$	$-w_i$
0	0	0	0	0	0
0	0	1	-1	0	1
0	1	0	1	1	1
0	1	1	0	0	0
1	0	0	1	1	1
1	0	1	0	0	0
1	1	0	2	1	0
1	1	1	1	1	1

$$w_i = (x_i \oplus y_i^+ \oplus (y_i^-)')'$$

$$t_{i+1} = x_i y_i^+ + x_i (y_i^-)' + y_i^+ (y_i^-)'$$

$\implies$  implemented using a full-adder and inverters (for variables subtracted)

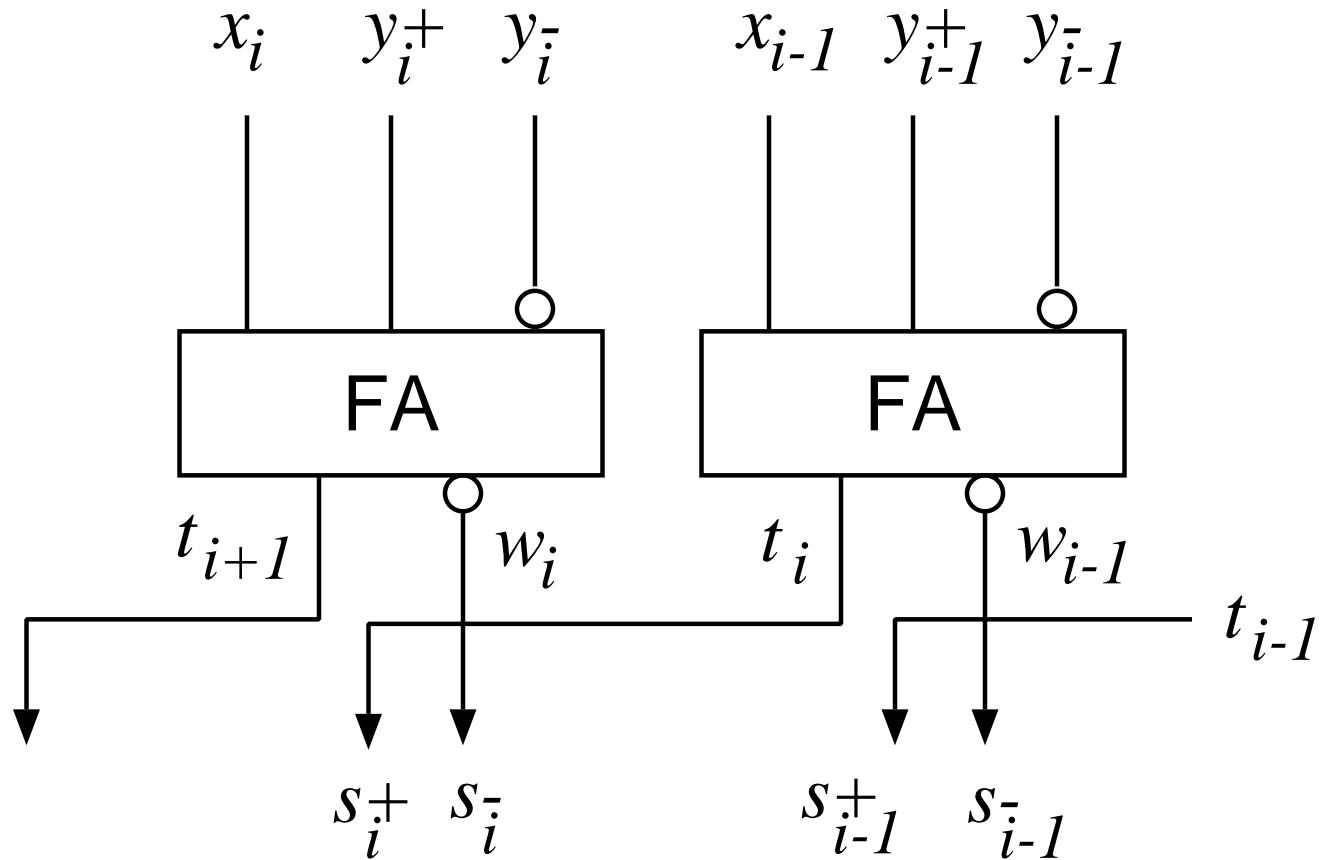


Figure 2.37: Redundant adder: one operand conventional, one operand redundant, result redundant.

- Apply double recoding



 


Figure 2.38: Redundant adder: operands and result redundant

 

 


# VLSI Arithmetic

## Lecture 9c:


## Sign-Digit Arithmetic

**Prof. Vojin G. Oklobdzija**  
**University of California**

<http://www.ece.ucdavis.edu/acsel>

 

 Motorola's PowerPC™ 603 RISC Microprocessor






# Example of Sign-Digit Arithmetic: Viterbi Detector

---

from

*A. K. Yeung, J. Rabaey, "A 210Mb/s Radix-4 Bit-Level Pipelined Viterbi Decoder", Proceedings of the International Solid-State Circuits Conference, San Francisco, California, 1995.*
 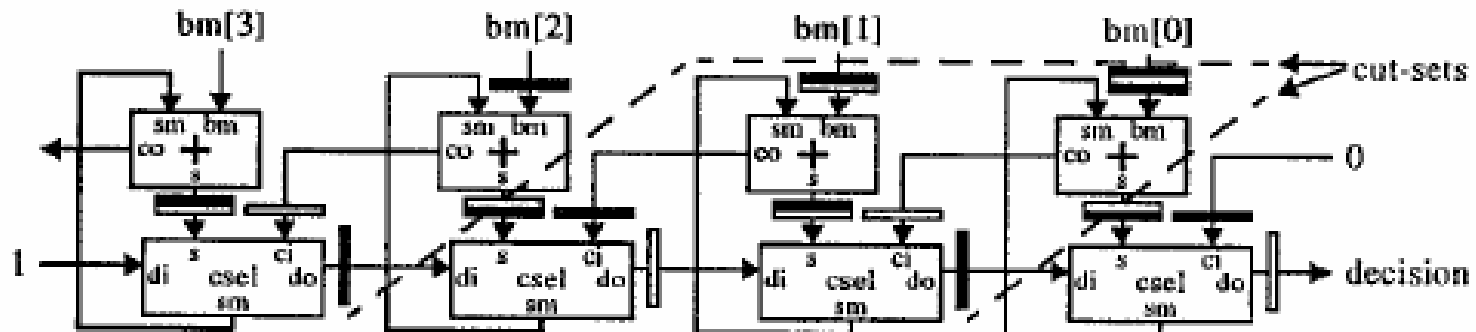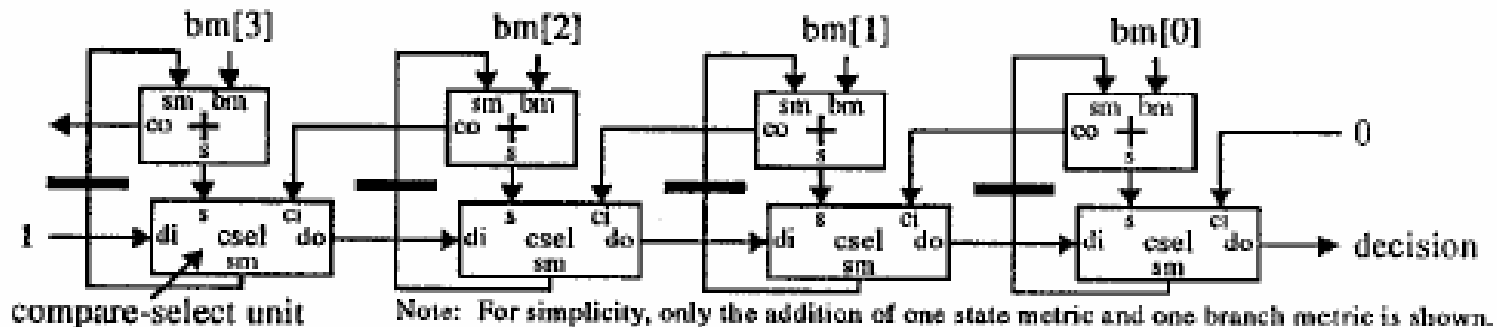
# 4-bit Add-Compare-Subtract Unit


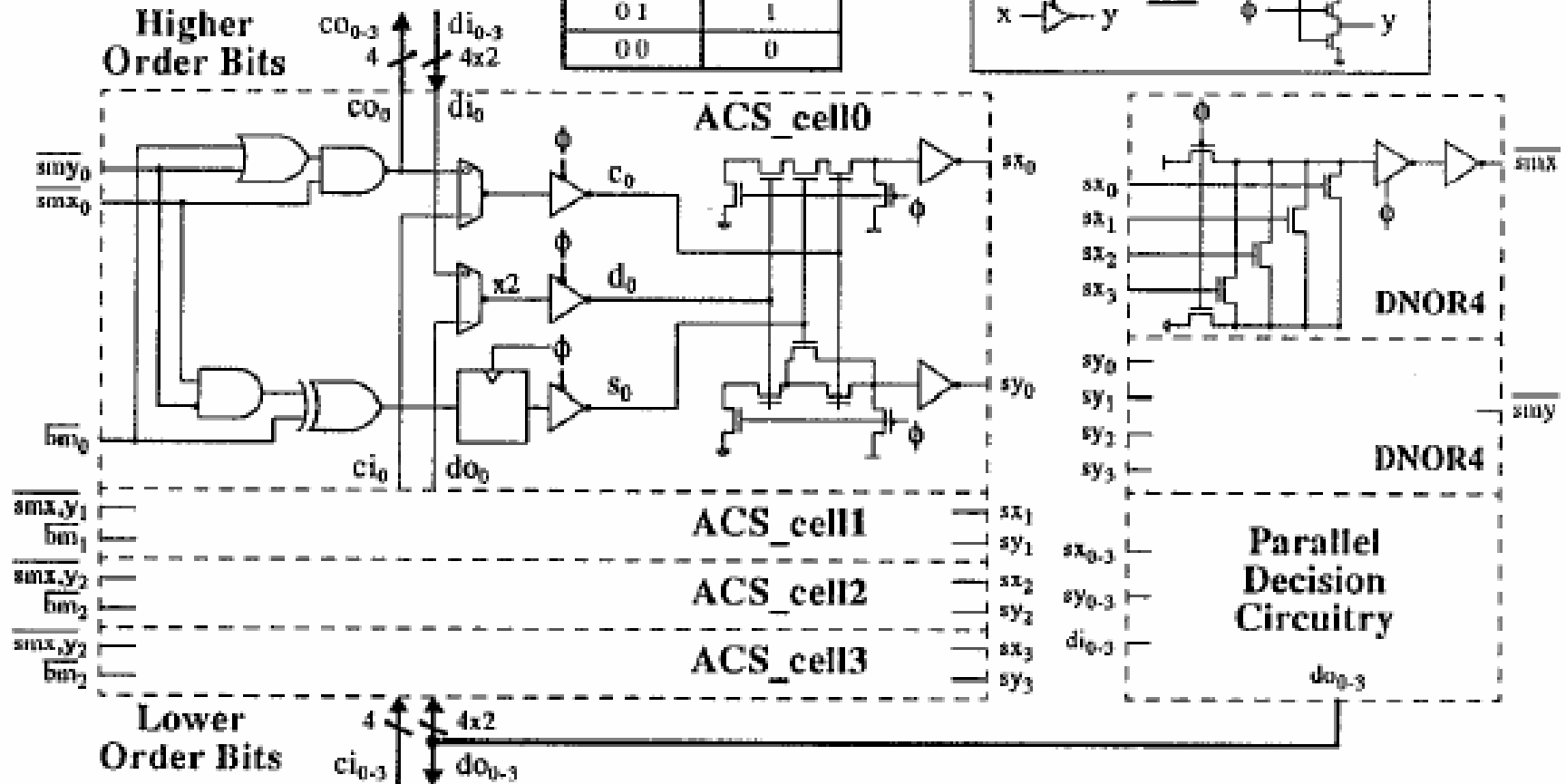


**Figure 1: (a) 4b ACS unit using carry-propagation-free addition. (b) Bit-level pipelined ACS (clock doubling, retiming). (c) Bit-level pipelined, time-multiplexed ACS unit.**

# Radix-4 ACS (one bit)

State metric Encoding:

smx	amy	Value
1	1	2
1	0	not used
0	1	1
0	0	0

 

**Figure 3: Radix-4 ACS bit-slice circuit.**