

BINARY MULTIPLICATION

Multipliers

- Multipliers are widely used in digital signal processing, generally more so than in general-purpose workloads
- Major categories of multiplier types
 - *Unsigned × Unsigned*
Also very useful for sign-magnitude data
 - *Signed 2's complement × Signed 2's complement*
Very useful for fixed-point 2's complement data
- Hardware is typically built in a manner broadly similar to how you would do it with paper and pencil
- The naming convention is somewhat unfortunate:

multipl
x *multiplier*

Multipliers

- Example: 4-bit unsigned *multiplicand* “ a ” times 4-bit *multiplier* “ b ”
- b could be signed or unsigned
- $p_{xy} = a_x \times b_y$
 $= a_x \text{ AND } b_y$

		a_3	a_2	a_1	a_0		
	×	b_3	b_2	b_1	b_0		
		p_{30}	p_{20}	p_{10}	p_{00}	← b_0	
		p_{31}	p_{21}	p_{11}	p_{01}	0	← b_1
	p_{32}	p_{22}	p_{12}	p_{02}	0	0	← b_2
p_{33}	p_{23}	p_{13}	p_{03}	0	0	0	← b_3

Multipliers


- Example: 4-bit signed 2's complement *multiplicand* "a" times 4-bit *multiplier* "b"
- b could be signed or unsigned
- s = partial product sign extension bits

- $p_{xy} = a_x \times b_y$
 $= a_x \text{ AND } b_y$

			a_3	a_2	a_1	a_0	
		×	b_3	b_2	b_1	b_0	
s	s	s	p_{30}	p_{20}	p_{10}	p_{00}	$\leftarrow b_0$
s	s	p_{31}	p_{21}	p_{11}	p_{01}	0	$\leftarrow b_1$
s	p_{32}	p_{22}	p_{12}	p_{02}	0	0	$\leftarrow b_2$
p_{33}	p_{23}	p_{13}	p_{03}	0	0	0	$\leftarrow b_3$

3 Main Steps in Every Multiplier

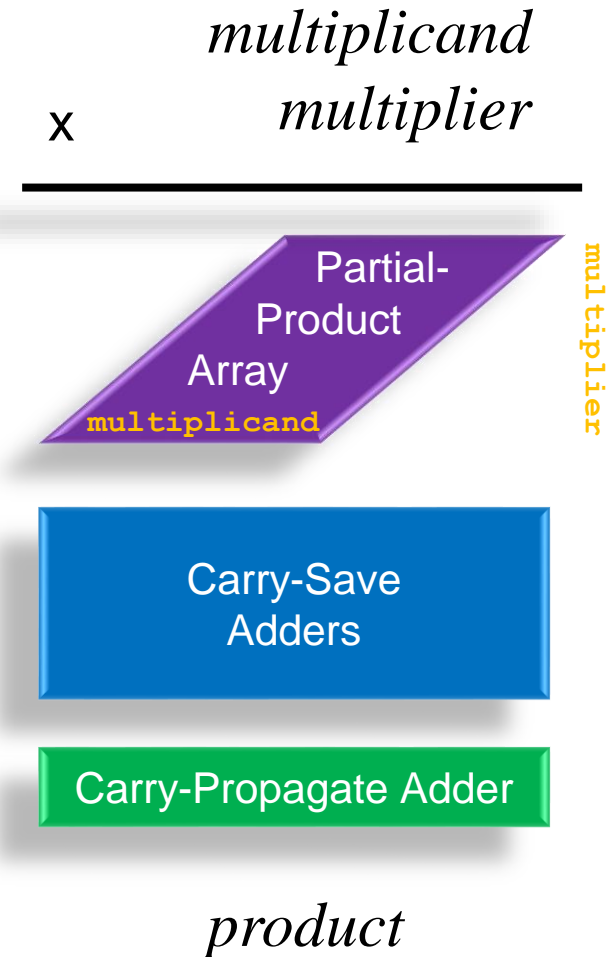
- 1) Generation of partial products
- 2) Reduction or “compression” of the partial product array (normally using carry-save addition) so that the product is composed of two words
 - Linear array addition
 - Tree addition (Wallace tree)
- 3) Final adder: Carry-propagate adder (CPA)
 - Converts the product in carry-save form into a single word form
 - Any style of CPA is fine though we probably favor faster ones



Straight-forward Partial Product Generation

- This is the simplest method to generate partial products
- Hardware looks at one bit of the *multiplier* (Y_i) at a time
- Partial products are copies of the *multiplicand* AND'd by bits of the *multiplier*
- Number of bits in the *multiplier*
= Number of partial products
= Number of terms/words/rows that must be added

Y_i	Partial product
0	0
1	$+x$ (= <i>multiplicand</i>)

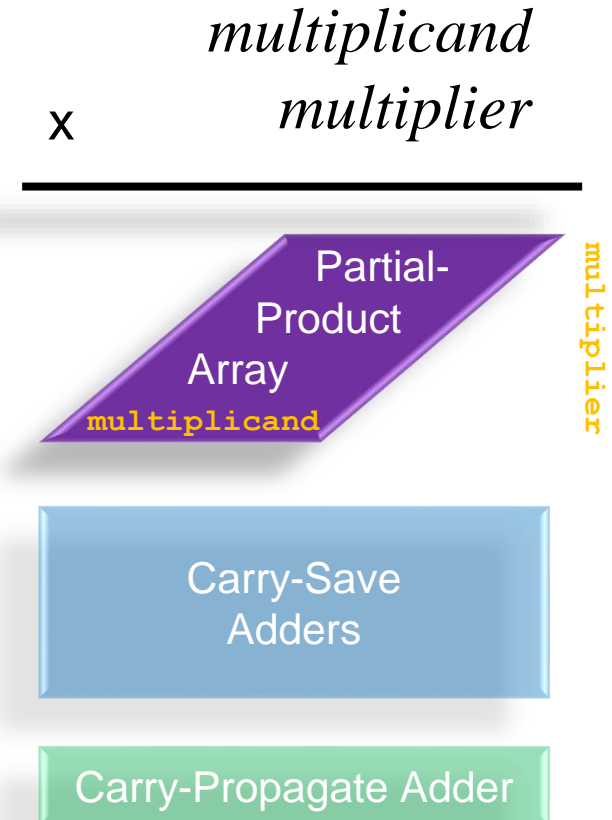

Straight-forward Partial Product Generation

- There are only two possible partial product results
- Two reasonable hardware solutions are:
 - a row of 2:1 muxes with zeros on one input
 - a row of AND gates (this should be more efficient)

+x

multiplicand

0

0

Y_i	Partial product
0	0
1	+x (= <i>multiplicand</i>)

Example unsigned 4-bit × 4-bit multiplication

- Example: 4-bit unsigned *multiplicand* “a” 1100 times 4-bit *multiplier* “b” 1010
- $1100 \times 1010 = 12 \times 10 = 120$
- $1100 \times 1010 = (12 \times 8) + (12 \times 0) + (12 \times 2) + (12 \times 0) = 120$
- $1111000 = 64 + 32 + 16 + 8 = 120$ 😊

				1	1	0	0	
			×	1	0	1	0	
				0	0	0	0	← 0
			1	1	0	0	0	← 1
		0	0	0	0	0	0	← 0
	1	1	0	0	0	0	0	← 1
	1	1	1	1	0	0	0	