

 


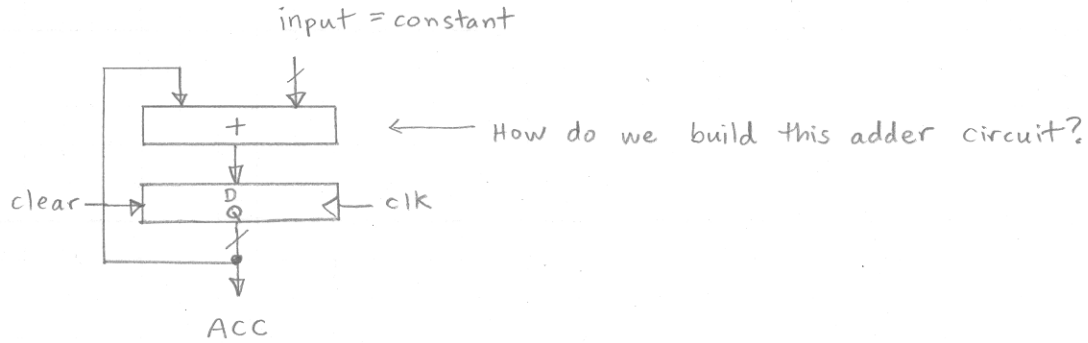Consider making a counter that can count in arbitrary increments (basically an accumulator with the same input every cycle):



 
Looking at one slice (bit slice), we need a circuit which computes a sum and a carry for two input bits:



Half Adder

A	B	S	Co
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

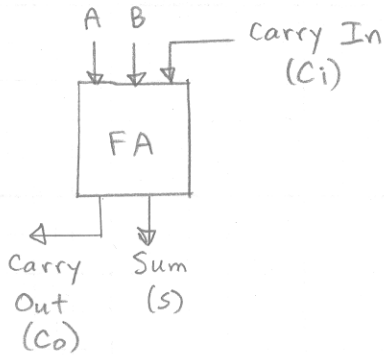
We also need to handle carry in bits for higher order bits in the word:



Full Adder

A	B	Ci	S	Co	Answer
0	0	0	0	0	0
0	0	1	1	0	1
0	1	0	1	0	1
0	1	1	0	1	2
1	0	0	1	0	1
1	0	1	0	1	2
1	1	0	0	1	2
1	1	1	1	1	3

Ex: 4-bit adder

 

Cout needed for large inputs (4-bit unsigned numbers: 0-15)

$$\begin{array}{r} \text{Ex:} \quad 1101 \\ + 1000 \\ \hline 10101 \end{array} \quad = \quad \begin{array}{r} 13_{10} \\ + 8_{10} \\ \hline 21_{10} \end{array}$$

$$\begin{array}{r} \text{Ex:} \quad 15_{10} = 1111 \\ + 0_{10} = + 0000 \\ \hline 15_{10} \quad 1111 \end{array}$$

$$\begin{array}{r} 15_{10} = 1111 \\ + 1_{10} = + 0001 \\ \hline 16_{10} \quad 10000 \end{array}$$

← carry signal "ripples" one bit at a time through the adder.

This is the slowest case (longest delay before output settles to final value). This adder structure is called a ripple-carry adder.

Delay is proportional to word size. If word bit width is N , speed is $O(N)$ or "Order N "

Faster adder structures speed up operation.