

CONTROL CIRCUITS AND COUNTERS

Control in Digital Systems


- Three primary components of digital systems
 - Datapath (does the work)
 - **Control (manager, controller)**
 - Memory (storage)

Control in Digital Systems

- Control blocks in chips
 - Typically small amount of HW
 - Typically substantial verilog code
 - Therefore:
 - We typically do not care about small circuit area
 - We typically do not care about fast circuits
 - A possible exception is in cases of “data-dependent control”. For example, if arithmetic is required to make control decisions e.g., “change states if $sum < phase$ ”
 - Verilog code can be complex
 - Many opportunities for bugs
 - May be impossible to test all states and transitions
 - Often the focus of testing by Verification Engineers


Sequential Logic

 - *Combinational circuits'* outputs are a function of the circuit's inputs and a time delay
- *Sequential circuits'* outputs are a function of the circuit's inputs, previous circuit state, and a time delay




Control with Finite State Machines

 - Of course we can design all standard finite state machines we learned in basic logic design classes
 - Moore type FSM
 - outputs depend only on the present state (**state** below)
 - Mealy type FSM
 - outputs depend on the present state and the inputs



Writing Verilog for State Machines

- Design process
 - **Think**
 - Determine all necessary registers (state, count, etc.)
 - **Think**
 - Draw state diagrams if helpful
 - Draw block diagrams if helpful
 - Draw timing diagrams
 - Pick descriptive signal names
 - **Think**

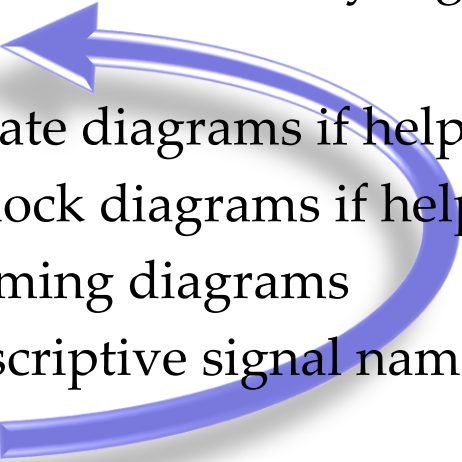 - Then...
 - Write verilog
 - Test it
- 

#1 Design Goal for Controllers: Clarity

- **Clear code** → bugs will be less likely
- It is even more important to use good signal naming conventions in control logic than with other digital circuits
 - Ex: *state_c* → *state*
- Reduce the amount of state if possible (clarity)
 - Ex: It may be better to have one global state machine instead of two separate ones
- Increase the amount of state if helpful (clarity)
 - Ex: It may be better to have two separate global state machines instead of a single global one
 - Ex: Instantiate separate counters to count independent events

I. Counters

- Typically the output is equal to the *state* of the counter
- In normal operation, the *next state* is the *present state* plus or minus a fixed number
 - Or reset to an initial state
 - Or hold the value to reduce power when idle
- Fixed simple circular counter
 - Example: $0 \rightarrow 1 \rightarrow 2 \rightarrow 3$



- This would be a good choice if you want something to happen once every four cycles, as an example


I.a. Counters—Count Up

- Count Up Counter

- Example: $0 \rightarrow 1 \rightarrow 2 \rightarrow \dots \rightarrow 23$



reset

 

```
if (count == 8'd023) begin
    ...do something...
```

- The reset hardware is simple, probably using reset-able FFs
- If the counter's ending count is programmable, detection of the finishing condition requires a more general comparator

I.a. Counters—Count Up

- Example: $0 \rightarrow 1 \rightarrow 2 \rightarrow \dots \rightarrow 23$
- When count gets to 23, hold that value to reduce power dissipation
- Fixed constants: increment = 1, stop at 23 base 10


```
reg [7:0] count; // real FF register
reg [7:0] count_c; // combinational logic

always @(count or reset) begin
    // default section is good practice
    // Try hold for default
    count_c = count; // hold

    if (count != 8'd023) begin
        count_c = count + 8'h01; // increment
    end

    if (reset == 1'b1) begin // high priority
        count_c = 8'b0000_0000;
    end
end
```
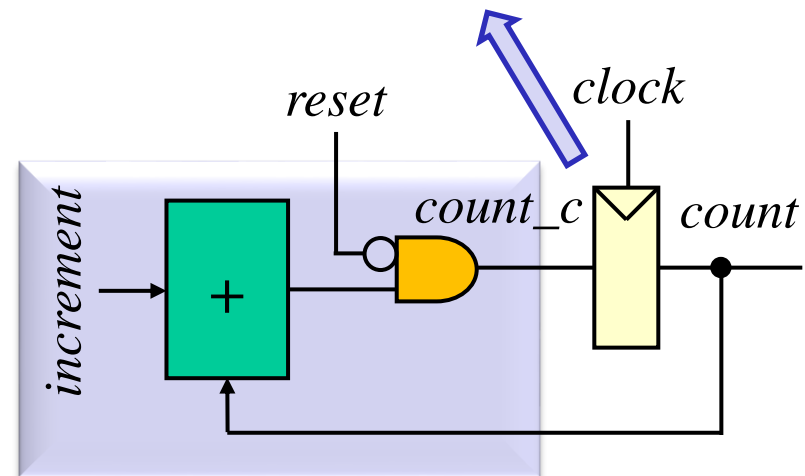
```
always @(posedge clock) begin
    count <= #1 count_c;
end
```




I.b. Counters—Count Down

- Count Down Counter

- Example: $17 \rightarrow 16 \rightarrow 15 \rightarrow \dots \rightarrow 0$



preset/reset

 

```
if (count == 8'd000) begin
    ...do something...
```

- The reset hardware is more complex especially if multiple starting values are needed
- Detection of the finishing condition is requires very simple hardware, conceptually a single NOR gate

I.b. Counters—Count Down

- Example: $17 \rightarrow 16 \rightarrow 15 \rightarrow \dots \rightarrow 0$
- When count gets to 0, hold that value to reduce power dissipation, and assert *done* output signal
- Fixed constants: increment = -1, stop at 0

```
always @(posedge clock) begin
    count <= #1 count_c;
end
```

```
reg [7:0] count; // real FF register
reg [7:0] count_c; // combinational logic
reg done; // output ==1 when done

always @(count or reset) begin
    // default section is good practice
    // Let default be decrement
    count_c = count - 8'h01; // decrement
    done = 1'b0;

    if (count == 8'h00) begin
        count_c = count; // could also be = 8'h00
        done = 1'b1;
    end

    if (reset == 1'b1) begin // highest priority
        count_c = 8'd017;
    end
end
```

I.c. One-Hot Ring Counter

- One-hot encoding
- One flip-flop for each state
- Requires circuits to initialize in a one-hot configuration
- Minimal hardware, no adders required!
- Zero-time state decode (i.e., each state is fully decoded by a FF output)

