 



Example: 2-input NAND gate w/ reg



a	b	out
0	0	1
0	1	1
1	0	1
1	1	0

// verbose example code
reg out;
always @ (a or b) begin
 out = 1'b1;
 if (a == 1'b1) begin
 if (b == 1'b1) begin
 out = 1'b0;
 end
 end
end

in order ↓

 

no ordering whatsoever

